

EE247 Administrative

- Final exam group has been changed to group 3
 - Final exam new date/time → Dec. 13th, 5pm to 8pm
- Homework #1 has been posted on course website and is due Sept 11th (next Thurs.)
 - Submissions can be on paper or via email
 - Paper submission in class or during same day office hours
 - Please show your derivations and explain your work

EE247 Lecture 3

- Active Filters
 - Active biquads
 - Sallen- Key & Tow-Thomas
 - Integrator-based filters
 - Signal flowgraph concept
 - First order integrator-based filter
 - Second order integrator-based filter & biquads
 - High order & high Q filters
 - Cascaded biquads & first order filters
 - Cascaded biquad sensitivity to component mismatch
 - Ladder type filters

Filters

2nd Order Transfer Functions (Biquads)

- Biquadratic (2nd order) transfer function:

$$H(s) = \frac{1}{1 + \frac{s}{\omega_p Q_p} + \frac{s^2}{\omega_p^2}}$$

$$|H(j\omega)| = \sqrt{\left(1 - \frac{\omega^2}{\omega_p^2}\right)^2 + \left(\frac{\omega}{\omega_p Q_p}\right)^2} \quad \longrightarrow \quad \begin{cases} |H(j\omega)|_{\omega=0} = 1 \\ |H(j\omega)|_{\omega \rightarrow \infty} = 0 \\ |H(j\omega)|_{\omega=\omega_p} = Q_p \end{cases}$$

$$\text{Biquad poles @: } s = -\frac{\omega_p}{2Q_p} \left(1 \pm j\sqrt{1-4Q_p^2} \right)$$

Note: for $Q_p \leq \frac{1}{2}$ poles are real, complex otherwise

s-Plane

$Q_p > \frac{1}{2} \rightarrow$ Complex conjugate poles:

$$s = -\frac{\omega_p}{2Q_p} \left(1 \pm j\sqrt{4Q_p^2 - 1} \right)$$

$$\arccos \frac{1}{2Q_p}$$

radius = ω_p


$$\text{real part} = -\frac{\omega_p}{2Q_p}$$

poles

Implementation of Biquads

- Passive RC: only *real poles* → can't implement *complex conjugate poles*
- Terminated LC
 - Low power, since it is passive
 - Only fundamental noise sources → load and source resistance
 - As previously analyzed, not feasible in the monolithic form for $f < \text{a few } 100\text{s of MHz}$
- Active Biquads
 - Many topologies can be found in filter textbooks!
 - Widely used topologies:
 - Single-opamp biquad: *Sallen-Key*
 - Multi-opamp biquad: *Tow-Thomas*
 - Integrator based biquads

Active Biquad Sallen-Key Low-Pass Filter

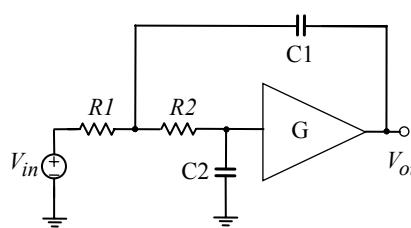

$$H(s) = \frac{G}{1 + \frac{s}{\omega_P Q_P} + \frac{s^2}{\omega_P^2}}$$
$$\omega_P = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$
$$Q_P = \frac{\omega_P}{\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-G}{R_2 C_2}}$$

- Single gain element
- Can be implemented both in discrete & monolithic form
- “Parasitic sensitive”
- Versions for LPF, HPF, BP, ...
 - Advantage: Only one opamp used to obtain 2poles
 - Disadvantage: Sensitive to parasitic – all pole no zeros

Addition of Imaginary Axis Zeros

- Sharpen transition band
- Can “notch out” interference
- High-pass filter (HPF)
- Band-reject filter

$$H(s) = K \frac{1 + \left(\frac{s}{\omega_Z}\right)^2}{1 + \frac{s}{\omega_P Q_P} + \left(\frac{s}{\omega_P}\right)^2}$$



$$\begin{aligned}|H(j\omega)|_{\omega \rightarrow 0} &= K \\ |H(j\omega)|_{\omega \rightarrow \infty} &= K \left(\frac{\omega_P}{\omega_Z}\right)^2\end{aligned}$$

Note: Always represent transfer functions as a product of a gain term, poles, and zeros (pairs if complex). Then all coefficients have a physical meaning, and readily identifiable units.

Imaginary Zeros

- Zeros substantially sharpen transition band
- At the expense of reduced stop-band attenuation at high frequency
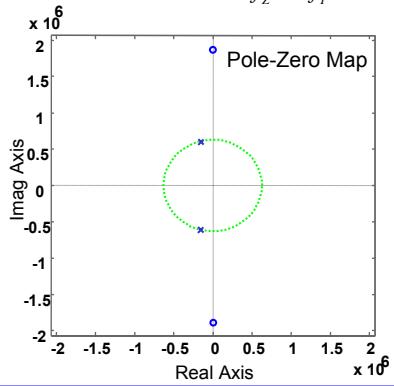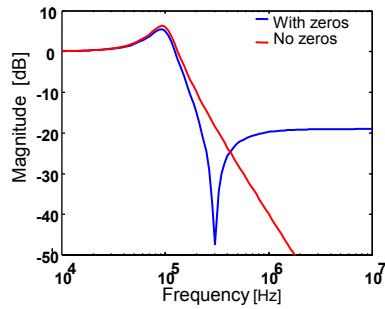
$$\begin{aligned}f_p &= 100\text{kHz} \\ Q_p &= 2 \\ f_z &= 3f_p\end{aligned}$$





Moving the Zeros


$$f_P = 100\text{kHz}$$

$$Q_P = 2$$

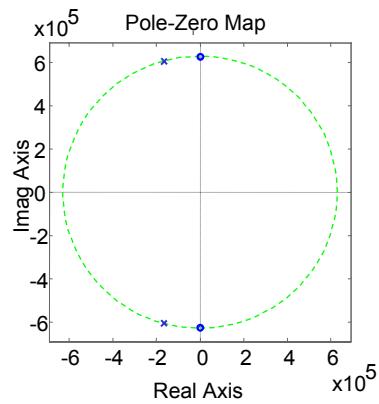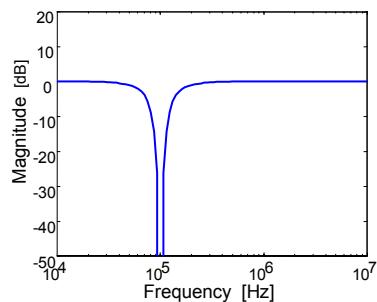$f_Z = f_P$ \rightarrow Band-reject filter



Tow-Thomas Active Biquad

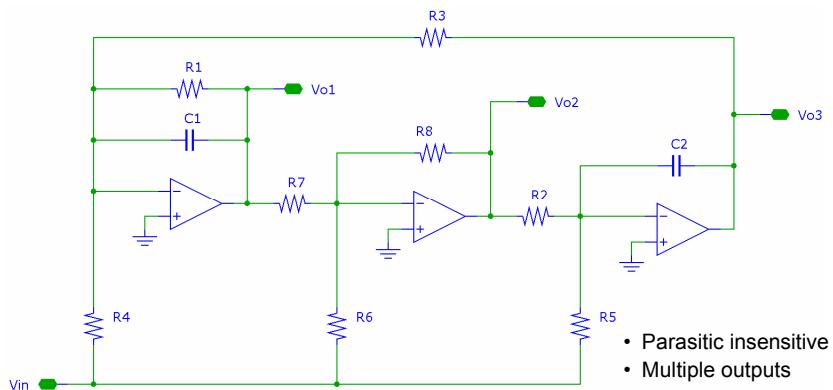

Ref: P. E. Fleischer and J. Tow, "Design Formulas for biquad active filters using three operational amplifiers," Proc. IEEE, vol. 61, pp. 662-3, May 1973.

Frequency Response

$$\frac{V_{o1}}{V_{in}} = -k_2 \frac{(b_2 a_1 - b_1)s + (b_2 a_0 - b_0)}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o2}}{V_{in}} = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o3}}{V_{in}} = -\frac{1}{k_1 \sqrt{a_0}} \frac{(b_0 - b_2 a_0)s + (a_1 b_0 - a_0 b_1)}{s^2 + a_1 s + a_0}$$

- V_{o2} implements a general biquad section with arbitrary poles and zeros
- V_{o1} and V_{o3} realize the same poles but are limited to at most one finite zero

Component Values

given a_i, b_i, k_i, C_1, C_2 and R_8 for example from the desired poles / zeros

$$b_0 = \frac{R_8}{R_3 R_5 R_7 C_1 C_2} \quad R_1 = \frac{1}{a_1 C_1}$$

$$b_1 = \frac{1}{R_1 C_1} \left(\frac{R_8}{R_6} - \frac{R_1 R_8}{R_4 R_7} \right) \quad R_2 = \frac{k_1}{\sqrt{a_0} C_2} \quad \text{it follows that}$$

$$b_2 = \frac{R_8}{R_6} \quad R_3 = \frac{1}{k_1 k_2} \frac{1}{\sqrt{a_0} C_1} \quad \omega_p = \sqrt{\frac{R_8}{R_2 R_3 R_7 C_1 C_2}}$$

$$a_0 = \frac{R_8}{R_2 R_3 R_7 C_1 C_2} \quad R_4 = \frac{1}{k_2} \frac{1}{a_1 b_2 - b_1} \frac{1}{C_1} \quad Q_p = \omega_p R_1 C_1$$


$$a_1 = \frac{1}{R_1 C_1} \quad R_5 = \frac{k_1 \sqrt{a_0}}{b_0 C_2}$$

$$k_1 = \sqrt{\frac{R_2 R_3 C_2}{R_3 R_7 C_1}} \quad R_6 = \frac{R_8}{b_2}$$

$$k_2 = \frac{R_7}{R_8} \quad R_7 = k_2 R_8$$

Higher-Order Filters in the Integrated Form

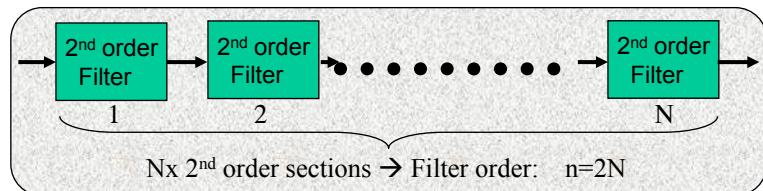- One way of building higher-order filters ($n > 2$) is via cascade of 2nd order biquads, e.g. Sallen-Key, or Tow-Thomas



Cascade of 2nd order biquads:

- ☺ Easy to implement
- ☹ Highly sensitive to component mismatch -good for low Q filters only

→ Good alternative: Integrator-based ladder type filters

Integrator Based Filters

- Main building block for this category of filters
→ Integrator
- By using **signal flowgraph** techniques
→ Conventional RLC filter topologies can be converted to integrator based type filters
- Next few pages:
 - Introduction to **signal flowgraph** techniques
 - 1st order integrator based filter
 - 2nd order integrator based filter
 - High order and high Q filters


What is a Signal Flowgraph (SFG)?

- SFG → Topological network representation consisting of nodes & branches- used to convert one form of network to a more suitable form (e.g. passive RLC filters to integrator based filters)
- Any network described by a set of linear differential equations can be expressed in SFG form
- For a given network, many different SFGs exists
- Choice of a particular SFG is based on practical considerations such as type of available components







*Ref: W.Heinlein & W. Holmes, "Active Filters for Integrated Circuits", Prentice Hall, Chap. 8, 1974.

What is a Signal Flowgraph (SFG)?

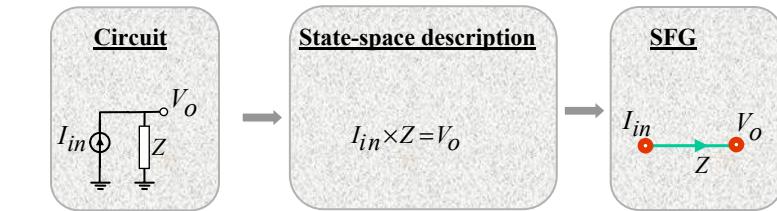- Signal flowgraph technique consist of **nodes & branches**:
 - **Nodes** represent variables (V & I in our case)
 - **Branches** represent transfer functions (we will call the transfer function *branch multiplication factor* or *BMF*)
- To convert a network to its SFG form, KCL & KVL is used to derive state space description
- Simple example:



Signal Flowgraph (SFG) Examples
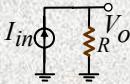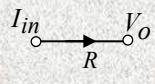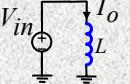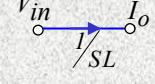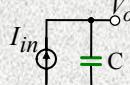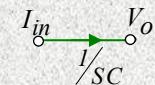
<u>Circuit</u>	<u>State-space description</u>	<u>SFG</u>
	$I_{in} \times R = V_o$	
	$V_{in} \times \frac{I}{SL} = I_o$	
	$I_{in} \times \frac{1}{SC} = V_o$	

EECS 247

Lecture 3: Filters


© 2008 H.K. Page 17

Useful Signal Flowgraph (SFG) Rules

- Two parallel branches can be replaced by a single branch with overall BMF equal to **sum** of two BMFs



- A node with only one incoming branch & one outgoing branch can be eliminated & replaced by a single branch with BMF equal to the **product** of the two BMFs

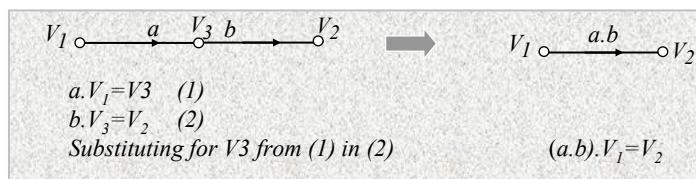

EECS 247

Lecture 3: Filters

© 2008 H.K. Page 18

Useful Signal Flowgraph (SFG) Rules

- An intermediate node can be multiplied by a factor (k). BMFs for **incoming** branches have to be **multiplied** by k and **outgoing** branches **divided** by k




$$\begin{array}{ll} a \cdot V_1 = V_3 & (1) \\ b \cdot V_3 = V_2 & (2) \end{array}$$

Multiply both sides of (1) by \mathbf{k}
 $(a \cdot \mathbf{k}) \cdot V_1 = \mathbf{k} \cdot V_3$ (1)


Divide & multiply left side of (2) by k
 $(b/k) \cdot \mathbf{k} \cdot V_3 = V_2$ (2)

Useful Signal Flowgraph (SFG) Rules

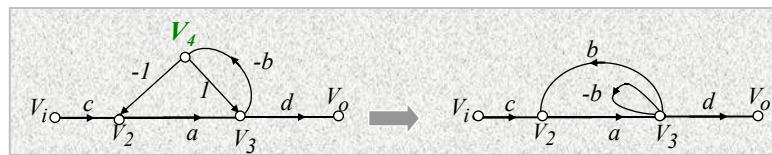- Simplifications can often be achieved by shifting or eliminating nodes
- Example: eliminating node V_4



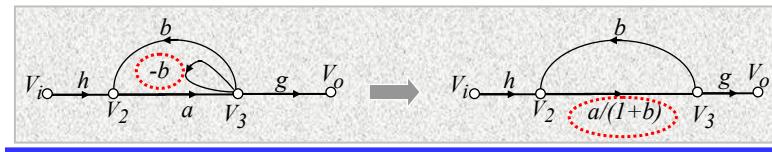
- A self-loop branch with BMF y can be eliminated by multiplying the BMF of **incoming** branches by $I/(I-y)$



Integrator Based Filters


1st Order LPF

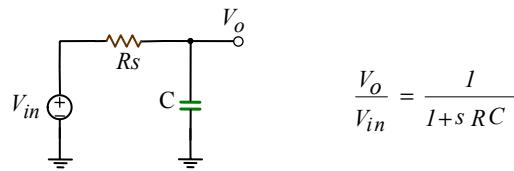- Conversion of simple lowpass RC filter to integrator-based type by using signal flowgraph techniques



What is an Integrator?

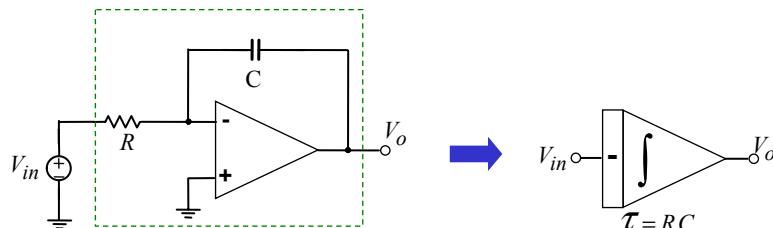Example: Single-Ended Opamp-RC Integrator



$$V_o = -V_{in} \times \frac{1}{sRC}, \quad V_o = -\frac{1}{RC} \int V_{in} dt$$


Note: Practical integrator in CMOS technology has input & output both in the form of voltage and not current → Consideration for SFG derivation

Integrator Based Filters

1st Order LPF

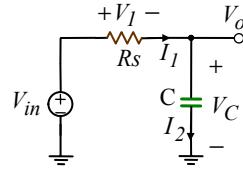1. Start from circuit prototype-

Name voltages & currents for all components



2. Use KCL & KVL to derive state space description in such a way to have BMFs in the integrator form:


- Capacitor voltage expressed as function of its current $V_{Cap} = f(I_{Cap})$
- Inductor current as a function of its voltage $I_{Ind} = f(V_{Ind})$

3. Use state space description to draw signal flowgraph (SFG) (see next page)

Integrator Based Filters

First Order LPF
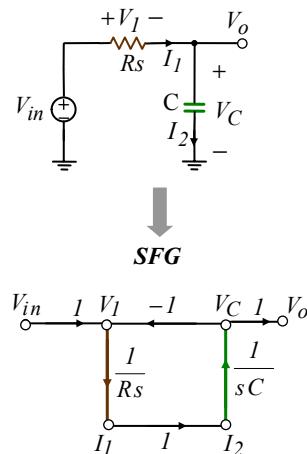
$$\begin{aligned}
 V_I &= V_{in} - V_C \\
 V_C &= I_2 \times \frac{1}{sC} \quad \text{Integrator form} \\
 V_o &= V_C \\
 I_I &= V_I \times \frac{1}{R_s} \\
 I_2 &= I_I
 \end{aligned}$$




- All voltages & currents → nodes of SFG
- Voltage nodes on top, corresponding current nodes below each voltage node

Normalize


- Since integrators are the main building blocks → require in & out signals in the form of voltage (not current)
- Convert all currents to voltages by multiplying current nodes by a scaling resistance R^*
- Corresponding BMFs should then be scaled accordingly

$$\begin{array}{c}
 V_I = V_{in} - V_o \\
 I_I = \frac{V_I}{R_s} \\
 V_o = \frac{I_2}{sC} \\
 I_2 = I_1
 \end{array}
 \rightarrow
 \begin{array}{c}
 V_I = V_{in} - V_o \\
 I_I R^* = \frac{R^*}{R_s} V_I \\
 V_o = \frac{I_2 R^*}{sC R^*} \\
 I_2 R^* = I_1 R^*
 \end{array}
 \rightarrow
 \begin{array}{c}
 V_I = V_{in} - V_o \\
 V_I = \frac{R^*}{R_s} V_I' \\
 V_o = \frac{V_2'}{sC R^*} \\
 V_2' = V_1'
 \end{array}$$

1st Order Lowpass Filter SGF Normalize

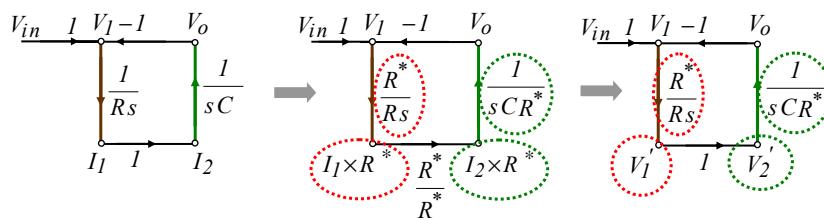

1st Order Lowpass Filter SGF Synthesis

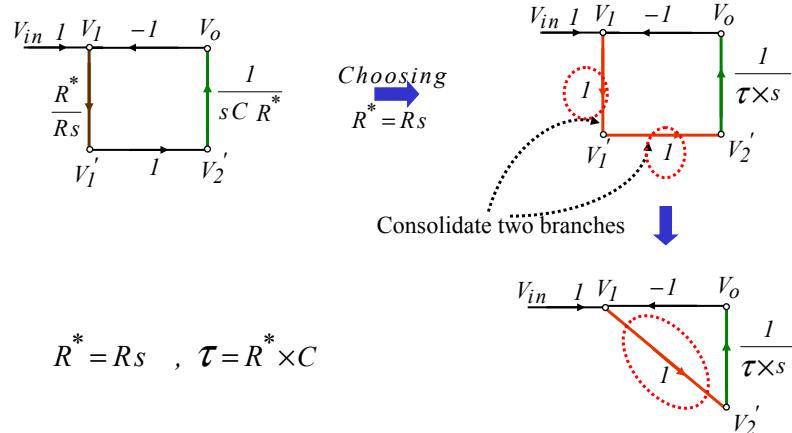


EECS 247

Lecture 3: Filters

© 2008 H.K. Page 27

First Order Integrator Based Filter

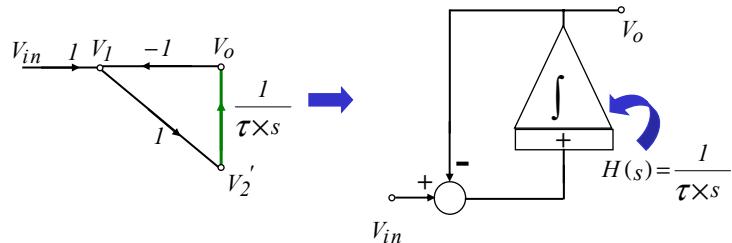


EECS 247

Lecture 3: Filters

© 2008 H.K. Page 28

1st Order Filter Built with Opamp-RC Integrator

- Single-ended Opamp-RC integrator has a sign inversion from input to output
→ Convert SFG accordingly by modifying BMF

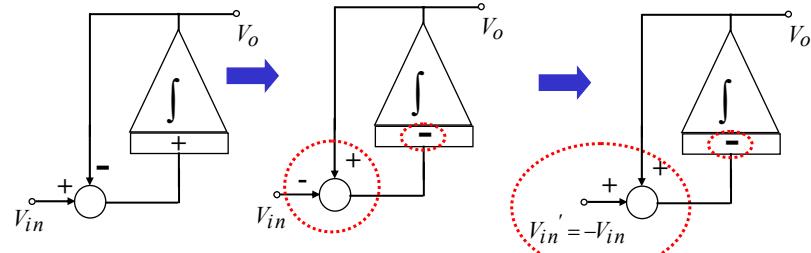


EECS 247

Lecture 3: Filters

© 2008 H.K. Page 29

1st Order Filter Built with Opamp-RC Integrator

- To avoid requiring an additional opamp to perform summation at the input node:

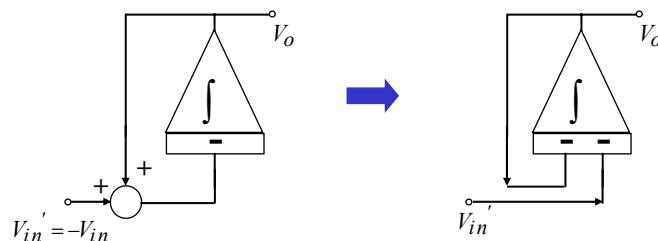


EECS 247

Lecture 3: Filters

© 2008 H.K. Page 30

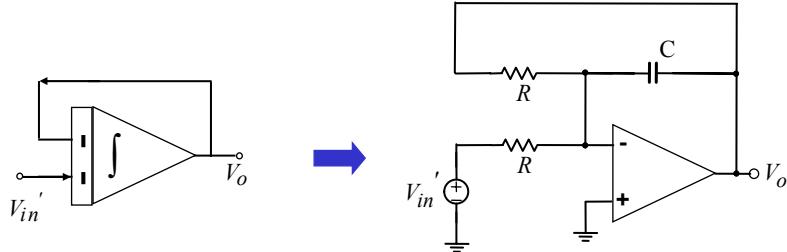1st Order Filter Built with Opamp-RC Integrator (continued)



$$\frac{V_o}{V_{in'}} = -\frac{1}{1+sRC}$$

EECS 247

Lecture 3: Filters

© 2008 H.K. Page 31

Opamp-RC 1st Order Filter Noise

Identify noise sources (here it is resistors & opamp)

Find transfer function from each noise source
to the output (opamp noise next page)

$$\overline{v_o^2} = \sum_{m=1}^k \int_0^\infty |H_m(f)|^2 S_m(f) df$$

$S_l(f) \rightarrow$ Noise spectral density of m^{th} noise source


$$|H_l(f)|^2 = |H_2(f)|^2 = \frac{1}{1 + (2\pi f RC)^2}$$

$$v_{n1}^2 = v_{n2}^2 = 4KTR\Delta f$$

$$\sqrt{\overline{v_o^2}} = \sqrt{2 \frac{kT}{C}}$$

$\alpha = 2$

Typically, α increases as filter order increases

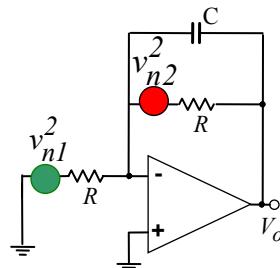


EECS 247

Lecture 3: Filters

© 2008 H.K. Page 32

Opamp-RC Filter Noise Opamp Contribution

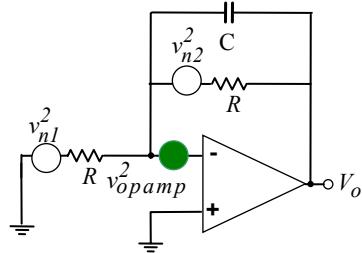- So far only the fundamental noise sources are considered
- In reality, noise associated with the opamp increases the overall noise
- For a well-designed filter opamp is designed such that noise contribution of opamp is negligible compared to other noise sources
- The bandwidth of the opamp affects the opamp noise contribution to the total noise



Integrator Based Filter 2nd Order RLC Filter

- State space description:

$$V_R = V_L = V_C = V_o$$

$$V_C = \frac{I_C}{sC}$$


Integrator form

$$I_R = \frac{V_R}{R}$$


$$I_L = \frac{V_L}{sL}$$

$$I_C = I_{in} - I_R - I_L$$

- Draw signal flowgraph (SFG)

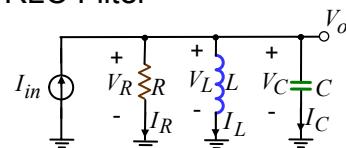


SFG

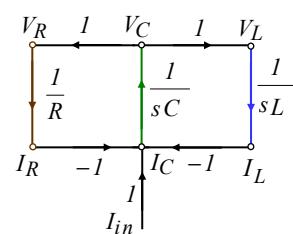


2nd Order RLC Filter SGF Normalize


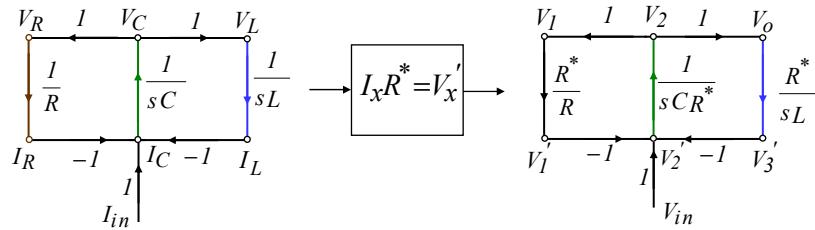
- Convert currents to voltages by multiplying all current nodes by the scaling resistance R^*



2nd Order RLC Filter SGF Synthesis

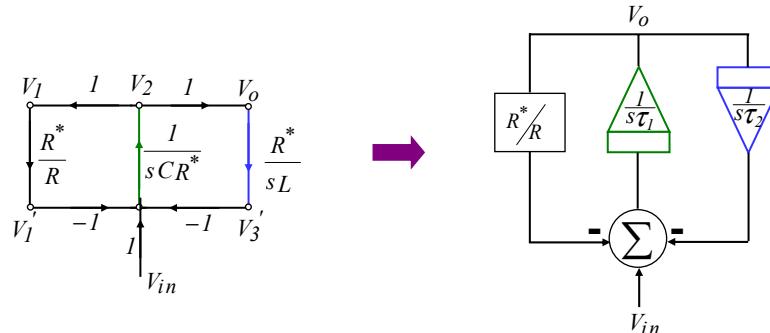
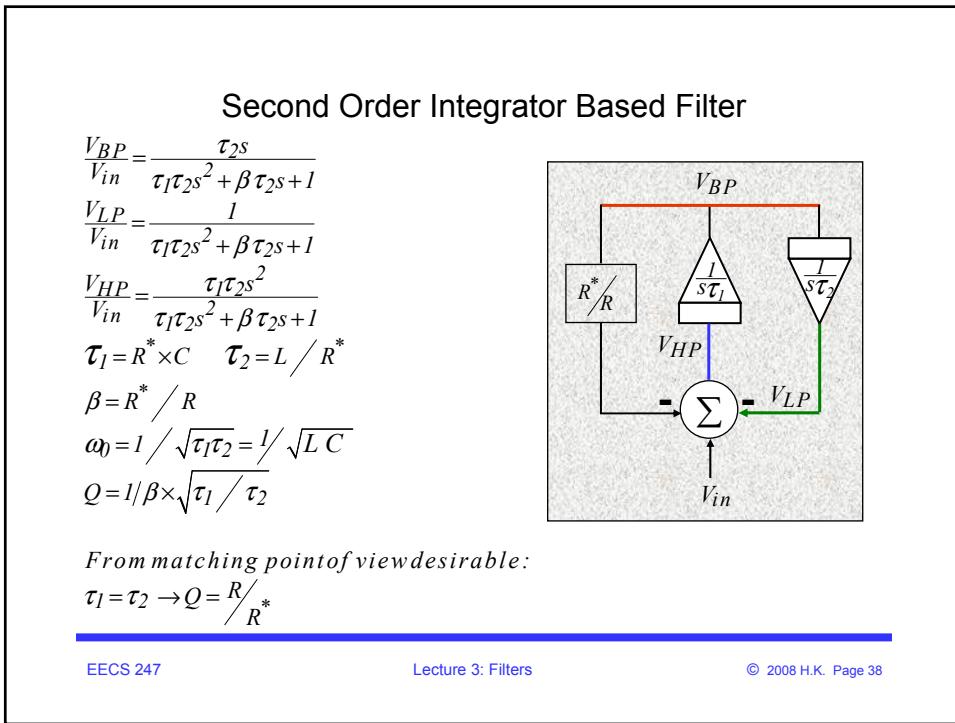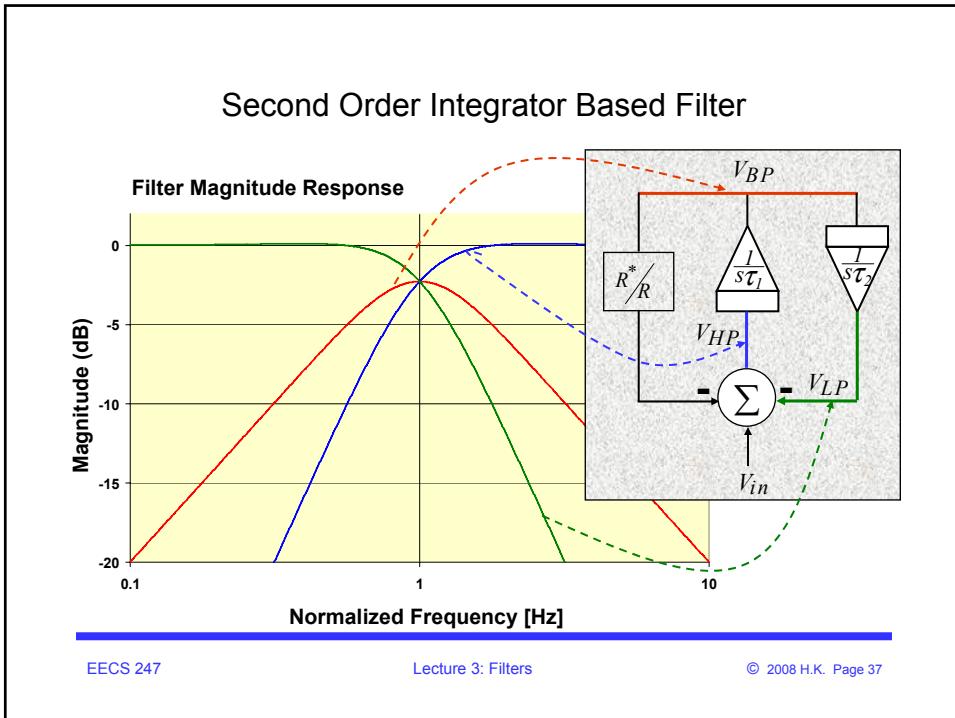
$$\tau_1 = R^* \times C \quad \tau_2 = L / R^*$$



Second Order Bandpass Filter Noise

$$\overline{v_o^2} = \sum_{m=1}^k \int_0^\infty |H_m(f)|^2 S_m(f) df$$


- Find transfer function of each noise source to the output
- Integrate contribution of all noise sources
- Here it is assumed that opamps are noise free (not usually the case!)

$$v_{n1}^2 = v_{n2}^2 = 4KTRdf$$

$$\sqrt{\overline{v_o^2}} = \sqrt{2Q \frac{kT}{C}}$$

α


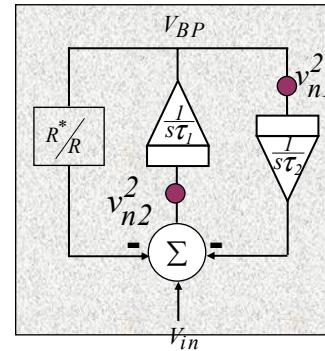
Typically, α increases as filter order increases
Note the noise power is directly proportion to Q



Second Order Integrator Based Filter Biquad

- By combining outputs can generate general biquad function:
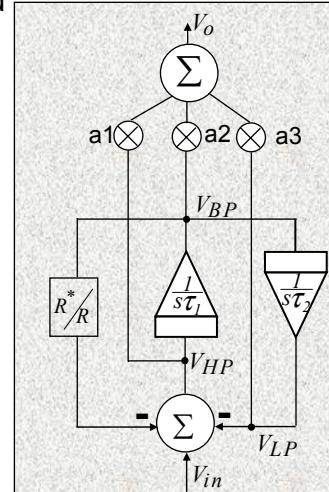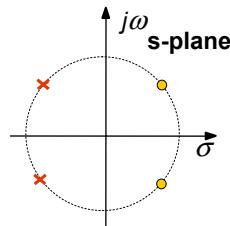
$$\frac{V_o}{V_{in}} = \frac{a_1 \tau_1 \tau_2 s^2 + a_2 \tau_2 s + a_3}{\tau_1 \tau_2 s^2 + \beta \tau_2 s + 1}$$



Summary Integrator Based Monolithic Filters

- Signal flowgraph techniques utilized to convert RLC networks to integrator based active filters
- Each reactive element (L & C) replaced by an integrator
- Fundamental noise limitation determined by integrating capacitor value:

$$-\text{ For lowpass filter: } \sqrt{v_o^2} = \sqrt{\alpha k \frac{T}{C}}$$

$$-\text{ Bandpass filter: } \sqrt{v_o^2} = \sqrt{\alpha Q \frac{k T}{C}}$$

where α is a function of filter order and topology

Higher Order Filters


- How do we build higher order filters?
 - Cascade of biquads and 1st order sections
 - Each complex conjugate pole built with a biquad and real pole with 1st order section
 - Easy to implement
 - In the case of high order high Q filters → highly sensitive to component mismatch
 - Direct conversion of high order ladder type RLC filters
 - SFG techniques used to perform exact conversion of ladder type filters to integrator based filters
 - More complicated conversion process
 - Much less sensitive to component mismatch compared to cascade of biquads

Higher Order Filters Cascade of Biquads


Example: LPF filter for CDMA cell phone baseband receiver

- LPF with
 - fpass = 650 kHz Rpass = 0.2 dB
 - fstop = 750 kHz Rstop = 45 dB
 - Assumption: Can compensate for phase distortion in the digital domain
- Matlab used to find minimum order required → 7th order Elliptic Filter
- Implementation with cascaded Biquads
Goal: Maximize dynamic range
 - Pair poles and zeros
 - In the cascade chain place lowest Q poles first and progress to higher Q poles moving towards the output node


Overall Filter Frequency Response

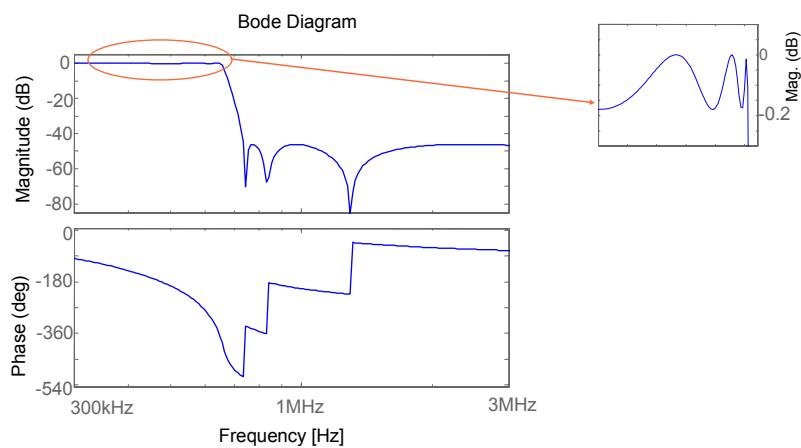

Pole-Zero Map (pzmap in Matlab)

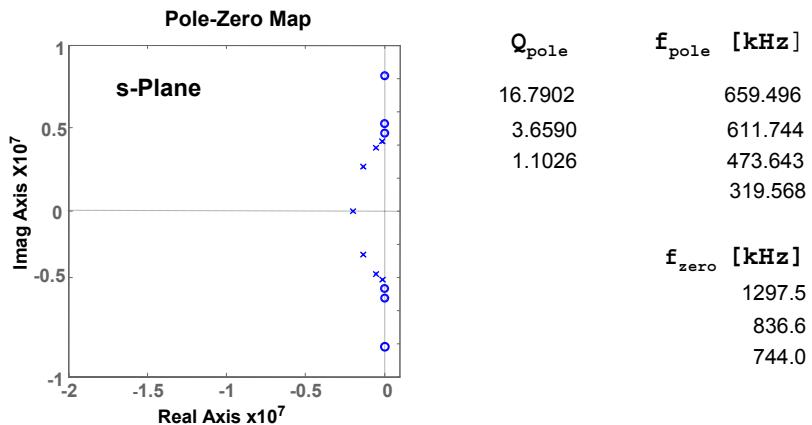


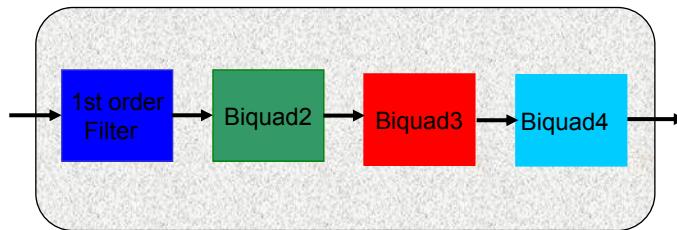CDMA Filter Built with Cascade of 1st and 2nd Order Sections




- 1st order filter implements the single real pole
- Each biquad implements a pair of complex conjugate poles and a pair of imaginary axis zeros


Biquad Response

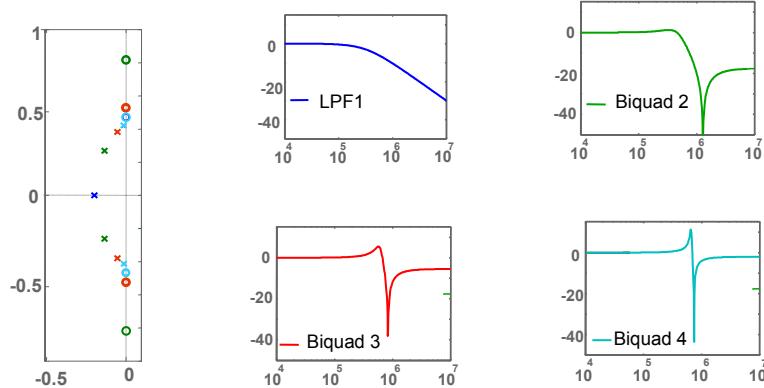

Individual Biquad Magnitude Response

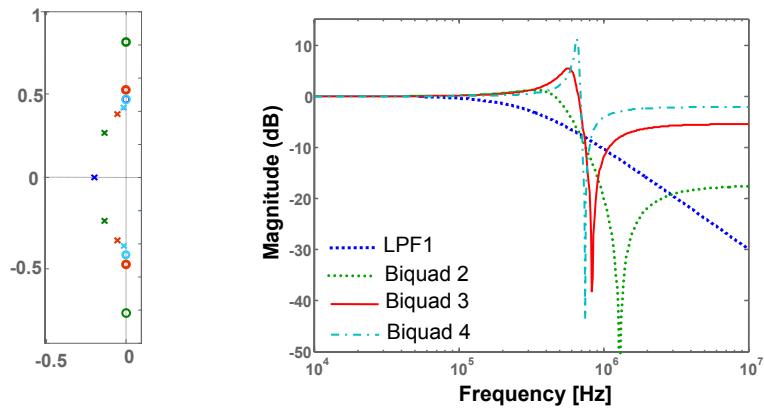

Intermediate Outputs

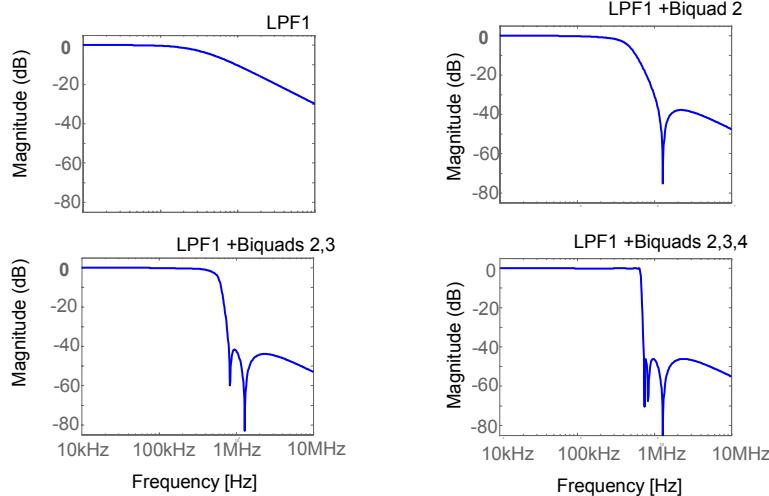

EECS 247




Lecture 3: Filters

© 2008 H.K. Page 49

Sensitivity to Relative Component Mismatch

Component variation in Biquad 4 relative to the rest
(highest Q poles):

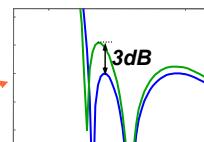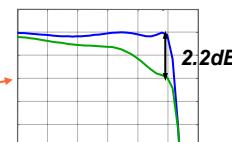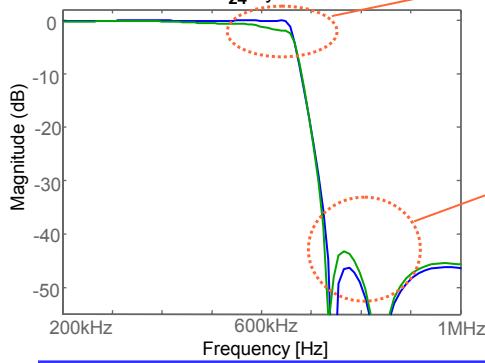- Increase Ω_{p4} by 1%
- Decrease Ω_{z4} by 1%



High Q poles \rightarrow High sensitivity
in Biquad realizations

EECS 247

Lecture 3: Filters

© 2008 H.K. Page 50


High Q & High Order Filters

- Cascade of biquads
 - Highly sensitive to component mismatch → not suitable for implementation of high Q & high order filters
 - Cascade of biquads only used in cases where required Q for all biquads <4 (e.g. filters for disk drives)
- Ladder type filters more appropriate for high Q & high order filters (next topic)
 - Will show later → Less sensitive to component mismatch

Ladder Type Filters

- For simplicity, will start with all pole (no finite zero) ladder type filters
 - Start with LC ladder type and find values for Ls & Cs
 - Convert to integrator based form – example shown
- Next will attend to high order ladder type filters incorporating zeros
 - Implement the same 7th order elliptic filter in the form of ladder RLC with zeros
 - Find level of sensitivity to component mismatch
 - Compare with cascade of biquads
 - Convert to integrator based form utilizing SFG techniques
 - Effect of integrator non-Idealities on filter frequency characteristics


LC Ladder Filters

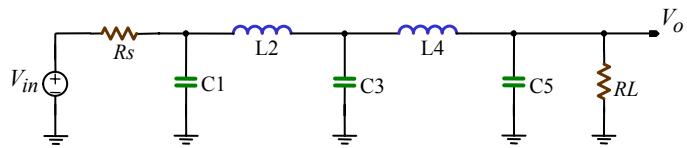

- Made of resistors, inductors, and capacitors
- Doubly terminated or singly terminated (with or w/o R_L)

Doubly terminated LC ladder filters → Lowest sensitivity to component mismatch

LC Ladder Filters

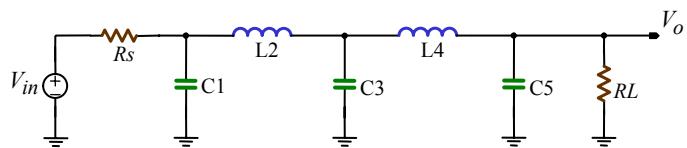

- First step in the design process → find values for L_s & C_s
 - Filter tables
 - A. Zverev, *Handbook of filter synthesis*, Wiley, 1967.
 - A. B. Williams and F. J. Taylor, *Electronic filter design*, 3rd edition, McGraw-Hill, 1995.
 - CAD tools
 - Matlab
 - Spice

LC Ladder Filter Design Example

Design a LPF with maximally flat passband:

$$f_{-3dB} = 10\text{MHz}, f_{stop} = 20\text{MHz}$$

$$Rs > 27dB @ f_{stop}$$


- Maximally flat passband → Butterworth

- Find minimum filter order
- :
- Here standard graphs from filter books are used

$$f_{stop} / f_{-3dB} = 2$$

$$Rs > 27dB$$

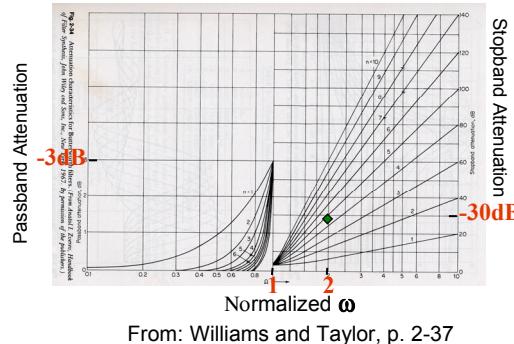Minimum Filter Order
⇒ 5th order Butterworth



From: Williams and Taylor, p. 2-37

LC Ladder Filter Design Example

NORMALIZED FILTER DESIGN TABLES

11.3

TABLE 11-2 Butterworth LC Element Values (Continued)

Find values for L & C from Table: →

Note L & C values normalized to

$$\omega_{-3dB} = 1$$

Denormalization:

Multiply all L_{Norm} , C_{Norm} by:

$$L_r = R/\omega_{-3dB}$$

$$C_r = 1/(R\omega_{-3dB})$$

R is the value of the source and termination resistor
(choose both 1Ω for now)

Then: $L = L_r \times L_{Norm}$

$$C = C_r \times C_{Norm}$$

From: Williams and Taylor, p. 11.3

LC Ladder Filter Design Example

11.3

NORMALIZED FILTER DESIGN TABLES

<i>n</i>	R_n	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.0000	0.6180	1.6180	2.0000	1.6180	0.6180	1.6180	2.0000
	0.9999	0.6178	1.6178	1.9999	1.6178	0.6178	1.6178	2.0000
	0.9999	0.6169	1.6169	2.0000	1.5443	1.7580	1.5443	1.7580
	0.9999	0.5173	0.7513	2.2845	1.3326	2.1083	1.3326	2.1083
	0.6000	0.5860	0.6094	2.5994	1.1255	2.5524	1.1255	2.5524
	0.5000	0.5860	0.4910	3.0050	0.8234	3.1531	0.8234	3.1531
	0.4000	0.8378	0.5277	3.7450	0.7274	3.9548	0.7274	3.9548
	0.3000	1.0937	0.2848	4.8833	0.5367	5.3073	0.5367	5.3073
	0.2000	1.6077	0.1861	7.1845	0.3518	7.9345	0.3518	7.9345
	0.1000	3.1522	0.0912	14.0945	0.1727	15.7108	0.1727	15.7108
6	1.0000	0.5195	1.4142	1.8919	1.4142	0.5176	1.4142	0.5176
	1.1111	0.3890	1.0403	1.3217	0.9339	1.7445	1.3347	1.7445
	1.2500	0.2445	1.1163	1.1257	2.2389	1.5498	1.6881	1.5498
	1.4286	0.2072	1.2363	0.9567	2.4991	1.3464	2.0618	1.3464
	1.6667	0.1778	1.4071	0.8863	2.3276	1.1512	1.9162	1.1512
	2.0000	0.1112	1.6542	0.5642	3.3687	0.9423	3.0998	0.9423
	2.5000	0.1108	2.0275	0.5159	4.1408	0.7450	3.9905	0.7450
	3.3333	0.0816	2.6559	0.3788	5.4325	0.5517	5.2804	0.5517
	5.0000	0.0535	5.9170	0.2484	8.0281	0.3628	7.9216	0.3628
	10.0000	0.0267	14.0945	0.1035	16.8222	0.1823	15.7108	0.1823
	Inf.	1.5529	1.7593	1.5529	1.2016	0.7579	0.2588	0.2588
7	1.0000	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450
	0.9999	0.2985	0.7111	1.4043	1.4891	2.1949	1.7260	1.2961
	0.8000	0.3215	0.6057	1.5174	1.2777	2.3338	1.5461	1.6520
	0.7000	0.3573	0.5154	1.6043	1.0917	2.1777	2.0797	2.0797
	0.6000	0.4773	0.4032	1.9886	0.7470	3.0640	1.1503	3.4771
	0.5000	0.4799	0.3536	2.2726	0.7512	3.5533	0.9513	3.0640
	0.4000	0.5899	0.2782	2.7950	0.5917	4.3799	0.7542	3.9037
	0.3000	0.7745	0.2058	3.6760	0.4373	5.7612	0.5600	5.2583
	0.2000	1.2571	0.1065	10.7004	0.1417	16.8222	0.1823	15.7108
	0.1000	2.2571	0.0665	10.7004	0.1417	16.8222	0.1823	15.7108
	Inf.	1.5576	1.7988	1.5588	1.3972	1.0550	0.6560	0.2225
<i>n</i>	$1/R_n$	L_1	C_2	L_3	C_4	L_5	C_6	L_7


From: Williams and Taylor, p. 11.3

EECS 247


Lecture 3: Filters

© 2008 H.K. Page 57

Magnitude Response Simulation

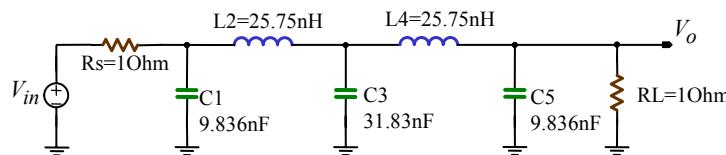

-6 dB passband attenuation
due to double termination

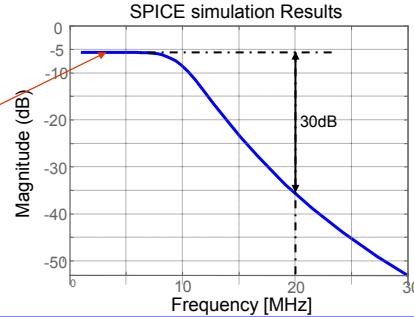

EECS 247

Lecture 3: Filters

© 2008 H.K. Page 58