

EE247 Lecture 6


- Summary last lecture
- Continuous-time filters (continued)
 - Opamp MOSFET-RC filters
 - Gm-C filters
- Frequency tuning for continuous-time filters
 - Trimming via fuses or laser
 - Automatic on-chip filter tuning
 - Continuous tuning
 - Master-slave tuning
 - Periodic off-line tuning
 - Systems where filter is followed by ADC & DSP, existing hardware can be used to periodically update filter freq. response

Summary Lecture 5

- Continuous-time filters
 - Effect of integrator non-idealities on integrated continuous-time filter behavior
 - Effect of integrator finite DC gain & non-dominant poles on filter frequency response
 - Integrator non-linearities affecting filter maximum signal handling capability (harmonic distortion and intermodulation distortion)
 - Effect of integrator component variations and mismatch on filter response & need for frequency tuning
 - Frequency tuning for continuous-time filters
 - Frequency adjustment by making provisions to have variable R or C
 - Various integrator topologies used in filters
 - Opamp MOSFET-C filters
 - Opamp MOSFET-RC filters.....to be continued today

Integrator Implementation

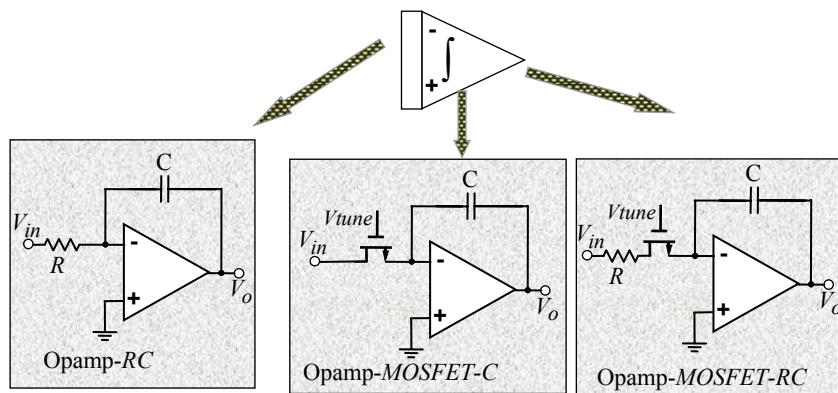Opamp-RC & Opamp-MOSFET-C & Opamp-MOSFET-RC




$$\frac{V_o}{V_{in}} = \frac{-\omega_b}{s} \quad \text{where} \quad \omega_b = \frac{1}{R_{eq}C}$$

EECS 247

Lecture 6: Filters


© 2008 H.K. Page 3

Use of MOSFETs as Variable Resistors

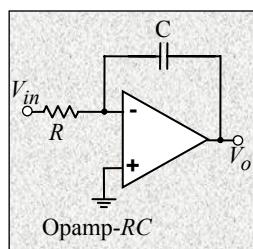


R replaced by MOSFET operating in triode mode

→ Continuously variable resistor:

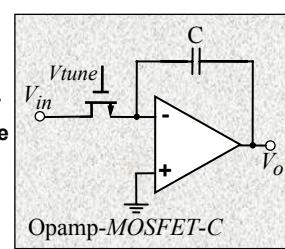

MOSFET IV characteristic:

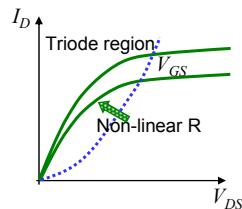

EECS 247

Lecture 6: Filters


© 2008 H.K. Page 4

Opamp MOSFET-C Integrator Single-Ended Integrator

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{gs} - V_{th}) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{gs} - V_{th}) V_i - \frac{V_i^2}{2} \right]$$
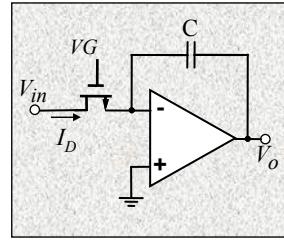
$$G = \frac{\partial I_D}{\partial V_i} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th} - V_i)$$



→ Tunable by varying V_G :

By varying V_G effective admittance is tuned
→ Tunable integrator

Problem: Single-ended MOSFET-C Integrator → Effective R non-linear
Note that the non-linearity is mainly 2nd order type

Use of MOSFETs as Resistors Differential Integrator


$$I_D = \mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_{DI} = \mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} - \frac{V_i}{4} \right) \frac{V_i}{2}$$

$$I_{D2} = -\mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} + \frac{V_i}{4} \right) \frac{V_i}{2}$$

$$I_{DI} - I_{D2} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th}) V_i$$
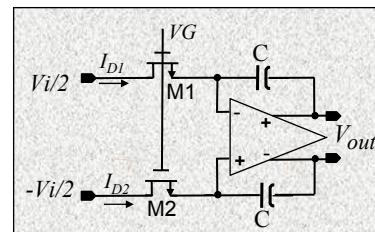
$$G = \frac{\partial (I_{DI} - I_{D2})}{\partial V_i} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th})$$




Opamp-MOSFET-C

- Non-linear term is of even order & cancelled!
- Admittance independent of V_i

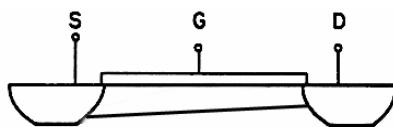
Problem: Threshold voltage dependence

Use of MOSFET as Resistor Issues

MOS xtor operating in triode region
Cross section view



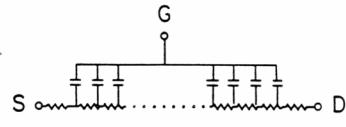
Distributed channel resistance & gate capacitance




- Distributed nature of gate capacitance & channel resistance results in infinite no. of high-frequency poles:
 - Excess phase @ the unity-gain frequency of the integrator
 - Enhanced integrator Q
 - Enhanced filter Q,
 - Peaking in the filter passband

Use of MOSFET as Resistor Issues

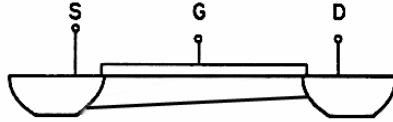MOS xtor operating in triode region
Cross section view



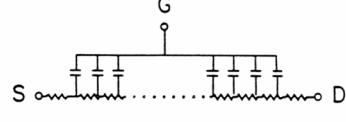
Distributed channel resistance & gate capacitance



- Tradeoffs affecting the choice of device channel length:
 - Filter performance mandates well-matched MOSFETs → long channel devices desirable
 - Excess phase increases with L^2 → Q enhancement and potential for oscillation!
 - Tradeoff between device matching and integrator Q
 - This type of filter limited to low frequencies

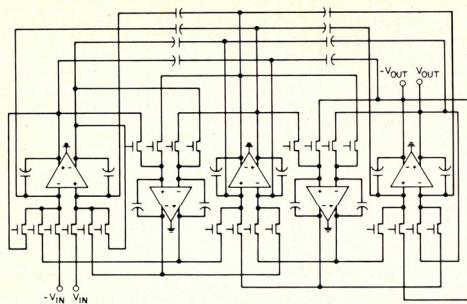Example: Opamp MOSFET-C Filter

- Suitable for low frequency applications
- Issues with linearity
- Linearity achieved ~40-50dB
- Needs tuning




5th Order Elliptic MOSFET-C LPF
with 4kHz Bandwidth

Ref: Y. Tsividis, M.Banu, and J. Khouri, "Continuous-Time MOSFET-C Filters in VLSI", *IEEE Journal of Solid State Circuits* Vol. SC-21, No.1 Feb. 1986, pp. 15-30

Improved MOSFET-C Integrator

$$\begin{aligned}
 I_D &= \mu C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds} \\
 I_{D1} &= \mu C_{ox} \frac{W}{L} \left(V_{gs1} - V_{th} - \frac{V_i}{4} \right) \frac{V_i}{2} \\
 I_{D3} &= -\mu C_{ox} \frac{W}{L} \left(V_{gs3} - V_{th} + \frac{V_i}{4} \right) \frac{V_i}{2} \\
 I_{X1} &= I_{D1} + I_{D3} \\
 &= \mu C_{ox} \frac{W}{L} \left(V_{gs1} - V_{gs3} - \frac{V_i}{2} \right) \frac{V_i}{2} \\
 I_{X2} &= \mu C_{ox} \frac{W}{L} \left(V_{gs3} - V_{gs1} - \frac{V_i}{2} \right) \frac{V_i}{2} \\
 I_{X1} - I_{X2} &= \mu C_{ox} \frac{W}{L} (V_{gs1} - V_{gs3}) V_i \\
 G &= \frac{\partial (I_{X1} - I_{X2})}{\partial V_i} = \mu C_{ox} \frac{W}{L} (V_{gs1} - V_{gs3})
 \end{aligned}$$

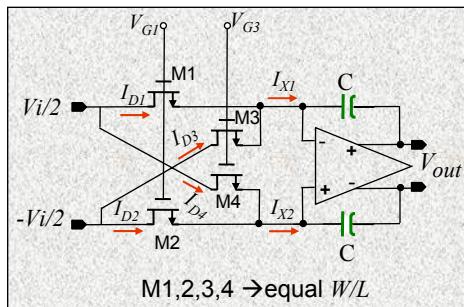


No threshold dependence

Linearity achieved in the order of 50-70dB

Ref: Z. Czarnul, "Modification of the Banu-Tsividis Continuous-Time Integrator Structure," *IEEE Transactions on Circuits and Systems*, Vol. CAS-33, No. 7, pp. 714-716, July 1986.


R-MOSFET-C Integrator

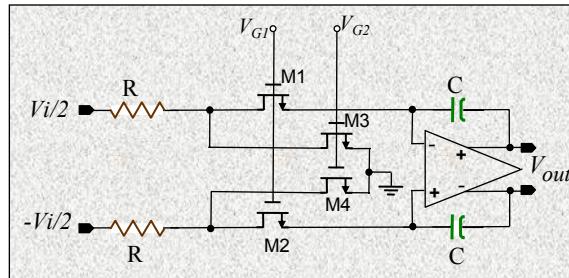

- Improvement over MOSFET-C by adding fixed resistor in series with MOSFET
- Voltage drop primarily across fixed resistor \rightarrow small MOSFET V_{ds} \rightarrow improved linearity & reduced tuning range
- Generally low frequency applications

Ref: U-K Moon, and B-S Song, "Design of a Low-Distortion 22-kHz Fifth Order Bessel Filter," *IEEE Journal of Solid State Circuits*, Vol. 28, No. 12, pp. 1254-1264, Dec. 1993.

R-MOSFET-C Lossy Integrator

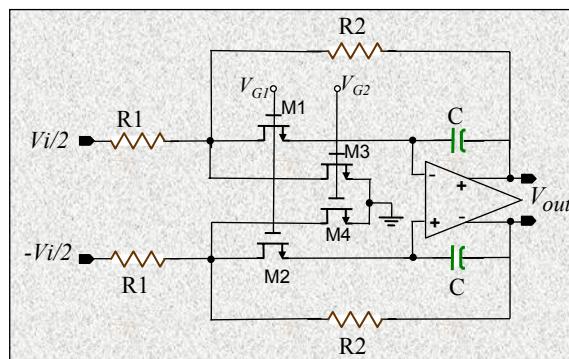


Negative feedback around the non-linear MOSFETs improves linearity but Compromises frequency response accuracy

Ref: U-K Moon, and B-S Song, "Design of a Low-Distortion 22-kHz Fifth Order Bessel Filter," *IEEE Journal of Solid State Circuits*, Vol. 28, No. 12, pp. 1254-1264, Dec. 1993.

Example:

Opamp MOSFET-RC Filter

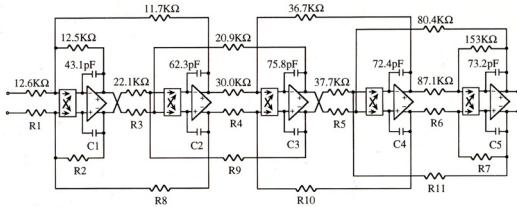


**5th Order Bessel MOSFET-RC LPF 22kHz bandwidth
THD → -90dB for 4Vp-p , 2kHz input signal**

- Suitable for low frequency, low Q applications
- Significant improvement in linearity compared to MOSFET-C
- Needs tuning

Ref: U-K Moon, and B-S Song, "Design of a Low-Distortion 22-kHz Fifth Order Bessel Filter," *IEEE Journal of Solid State Circuits*, Vol. 28, No. 12, pp. 1254-1264, Dec. 1993.


Operational Amplifiers (Opamps) versus Operational Transconductance Amplifiers (OTA)

Opamp
Voltage controlled
voltage source

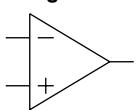


- Output in the form of voltage
- Low output impedance
- Can drive R-loads
- Good for RC filters,
OK for SC filters
- Extra buffer adds complexity,
power dissipation

OTA
Voltage controlled
current source

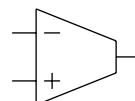

- Output in the form of current
- High output impedance
- In the context of filter design called gm-cells
- Cannot drive R-loads
- Good for SC & gm-C filters
- Typically, less complex compared to opamp → higher freq. potential
- Typically lower power

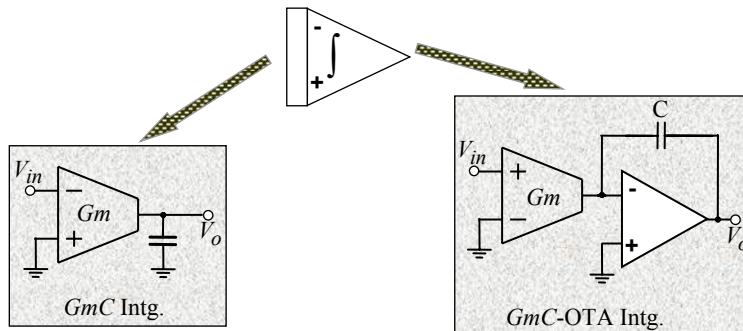
Integrator Implementation Transconductance-C & Opamp-Transconductance-C



$$\frac{V_o}{V_{in}} = \frac{-\omega_b}{s} \quad \text{where} \quad \omega_b = \frac{G_m}{C}$$


Gm-C Filters Simplest Form of CMOS Gm-C Integrator

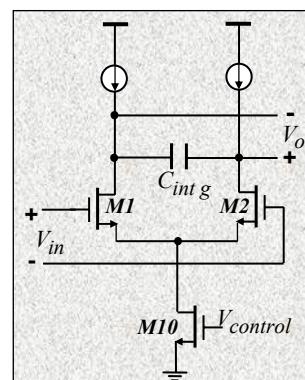- Transconductance element formed by the source-coupled pair $M1$ & $M2$
- All MOSFETs operating in saturation region
- Current in $M1$ & $M2$ can be varied by changing $V_{control}$
- Find transfer function by drawing ac half circuit



Ref: H. Khorramabadi and P.R. Gray, "High Frequency CMOS continuous-time filters," IEEE Journal of Solid-State Circuits, Vol.-SC-19, No. 6, pp.939-948, Dec. 1984.

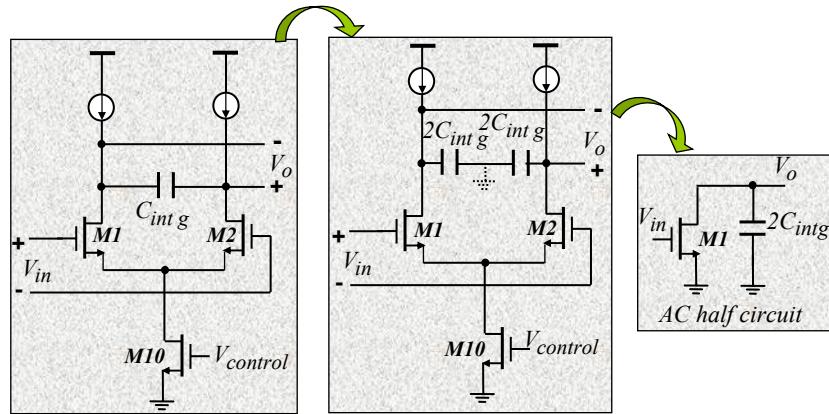Simplest Form of CMOS Gm-C Integrator AC Half Circuit



Gm-C Filters Simplest Form of CMOS Gm-C Integrator



- Use ac half circuit & small signal model to derive transfer function:

$$V_o = -g_m^{M1,2} \times V_{in} \times 2C_{intg}s$$

$$\frac{V_o}{V_{in}} = -\frac{g_m^{M1,2}}{2C_{intg}s}$$

$$\frac{V_o}{V_{in}} = \frac{-\omega_0}{s}$$
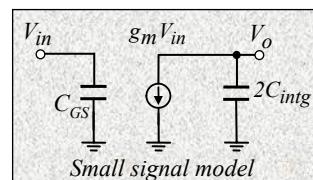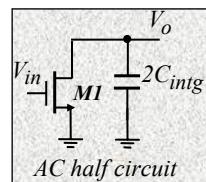
$$\rightarrow \omega_0 = \frac{g_m^{M1,2}}{2 \times C_{intg}}$$



Gm-C Filters

Simplest Form of CMOS Gm-C Integrator


- MOSFET in saturation region:

$$I_d = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{gs} - V_{th})^2$$

- Gm is given by:

$$\begin{aligned} g_m^{M1 \& M2} &= \frac{\partial I_d}{\partial V_{gs}} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th}) \\ &= 2 \frac{I_d}{(V_{gs} - V_{th})} \\ &= 2 \left(\frac{1}{2} \mu C_{ox} \frac{W}{L} I_d \right)^{1/2} \end{aligned}$$

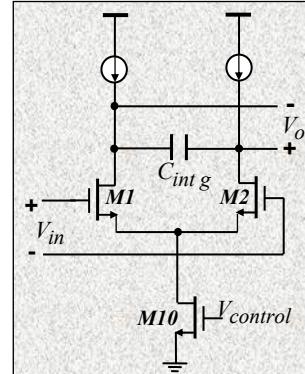
Id varied via Vcontrol
 $\rightarrow gm$ tunable via $V_{control}$




Gm-C Filters

2nd Order Gm-C Filter

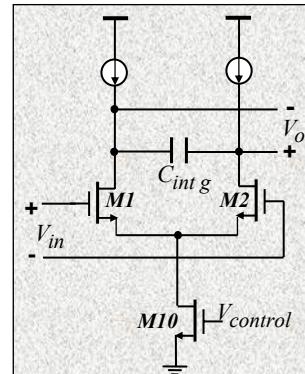- Use the Gm-cell to build a 2nd order bandpass filter



2nd Order Bandpass Filter

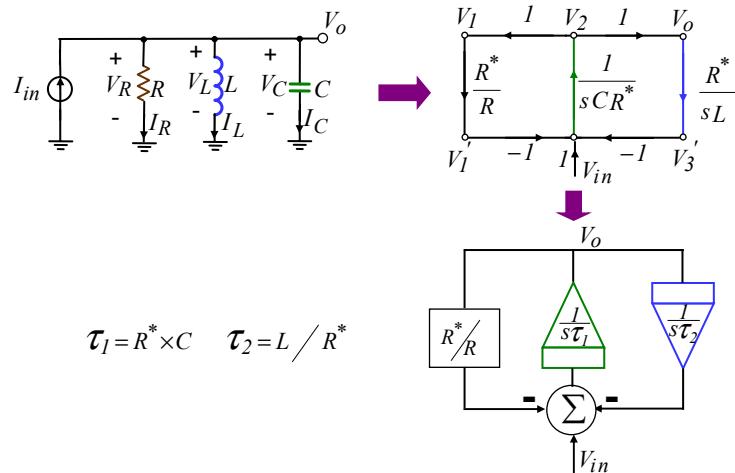

2nd Order Integrator-Based Bandpass Filter

$$\frac{V_{BP}}{V_{in}} = \frac{\tau_2 s}{\tau_1 \tau_2 s^2 + \beta \tau_2 s + 1}$$

$$\tau_1 = R^* \times C \quad \tau_2 = L / R^*$$


$$\beta = R^* / R$$

$$\omega_0 = 1 / \sqrt{\tau_1 \tau_2} = 1 / \sqrt{L C}$$

$$Q = 1 / \beta \times \sqrt{\tau_1 / \tau_2}$$

From matching point of view desirable:

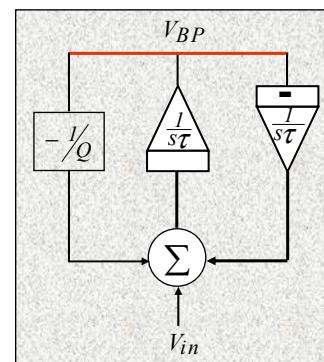
$$\tau_1 = \tau_2 = \tau = \frac{1}{\omega_0} \rightarrow Q = R / R^*$$





2nd Order Integrator-Based Bandpass Filter

First implement this part
With transfer function:


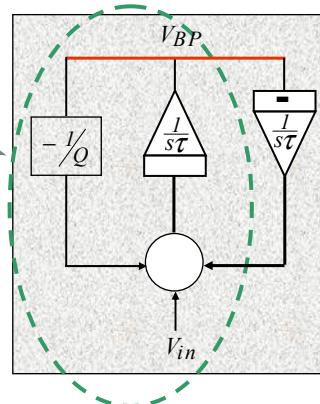
$$\frac{V_0}{V_{in}} = \frac{-1}{\frac{s}{\omega_0} + \frac{1}{Q}}$$



Terminated Gm-C Integrator

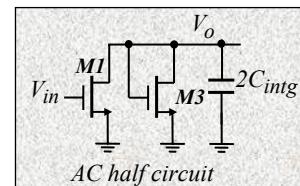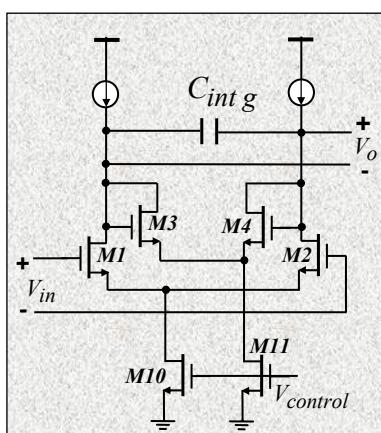



Terminated Gm-C Integrator

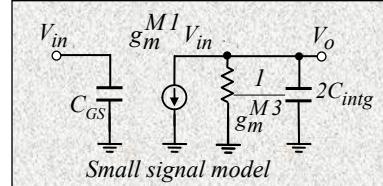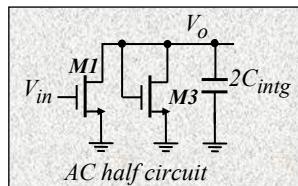

$$\frac{V_o}{V_{in}} = \frac{-1}{s \frac{2C_{intg}}{g_m^{MI}} + \frac{g_m^{M3}}{g_m^{MI}}}$$

Compare to: $\frac{V_o}{V_{in}} = \frac{-1}{\frac{s}{\omega_0} + \frac{I}{Q}}$

Terminated Gm-C Integrator

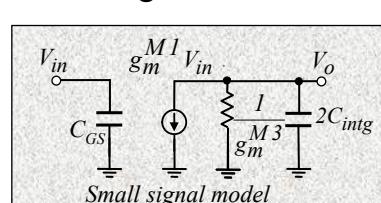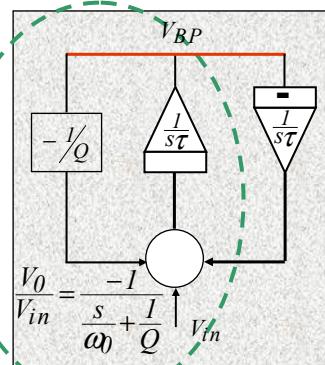

$$\frac{V_o}{V_{in}} = \frac{-1}{s \times 2C_{intg} + \frac{g_m^{M3}}{g_m^{MI}}}$$

$$\rightarrow \omega_0 = \frac{g_m^{MI}}{2C_{intg}} \quad \& \quad Q = \frac{g_m^{MI}}{g_m^{M3}}$$

Question: How to define Q accurately?


Terminated Gm-C Integrator

$$g_m^{M1} = 2 \left(\frac{1}{2} \mu C_{ox} \frac{W_{M1}}{L_{M1}} I_d^{M1} \right)^{1/2}$$

$$g_m^{M3} = 2 \left(\frac{l}{2} \mu C_{ox} \frac{W_{M3}}{L_{M3}} I_d^{M3} \right)^{1/2}$$

Let us assume equal channel lengths for $M1$, $M3$ then:
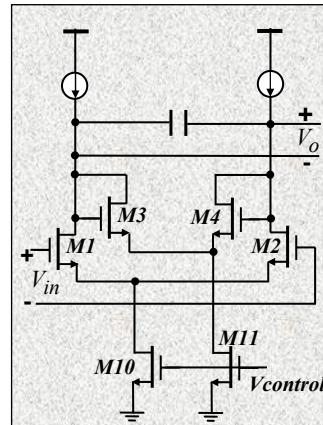
$$\frac{g_m^{M1}}{g_m^{M3}} = \left(\frac{I_d^{M1}}{I_d^{M3}} \times \frac{W_{M1}}{W_{M3}} \right)^{1/2}$$



Terminated Gm-C Integrator


Note that:

$$\frac{I_d^{M1}}{I_d^{M3}} = \frac{I_d^{M10}}{I_d^{M11}}$$



Assuming equal channel lengths for M10, M11:

$$\frac{I_d^{M10}}{I_d^{M11}} = \frac{W_{M10}}{W_{M11}}$$
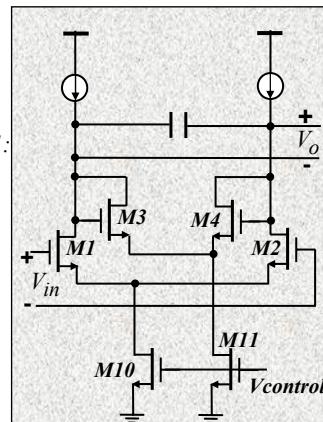
$$\rightarrow \frac{g_m^{M1}}{g_m^{M3}} = \left(\frac{W_{M10}}{W_{M11}} \times \frac{W_{M1}}{W_{M3}} \right)^{1/2}$$



2nd Order Gm-C Filter

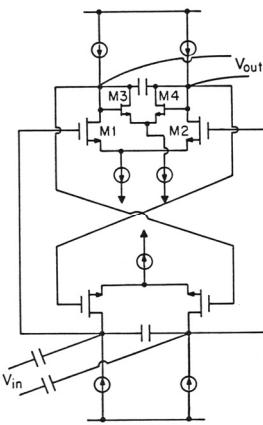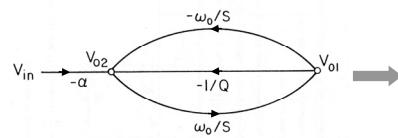

- Simple design
- Tunable
- Q function of device ratios:

$$Q = \frac{g_m^{M1,2}}{g_m^{M3,4}}$$


Integrated Continuous-Time Filter Frequency Tuning Techniques

- Component trimming
- Automatic on-chip filter tuning
 - Continuous tuning
 - Master-slave tuning
 - Periodic off-line tuning
 - Systems where filter is followed by ADC & DSP, existing hardware can be used to periodically update filter freq. response

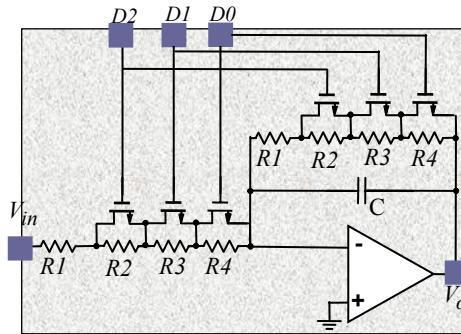Example: Tunable Opamp-RC Filter

Post manufacturing:


- Usually at wafer-sort tuning performed
- Measure -3dB frequency
 - If frequency too high decrement D to D-1
 - If frequency too low increment D to D+1
 - If frequency within 10% of the desired corner freq. stop



Not practical to require end-user to tune the filter
→ Need to fix the adjustment at the factory


Factory Trimming

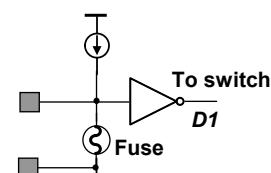- Factory component trimming
 - Build fuses on-chip
 - Based on measurements @ wafer-sort blow fuses selectively by applying high current to the fuse
 - Expensive
 - Fuse regrowth problems!
 - Does not account for temp. variations & aging
 - Laser trimming
 - Trim components or cut fuses by laser
 - Even more expensive
 - Does not account for temp. variations & aging



Fuse not blown → D1=1
Fuse blown → D1=0

Example:Tunable/Trimmable Opamp-RC Filter

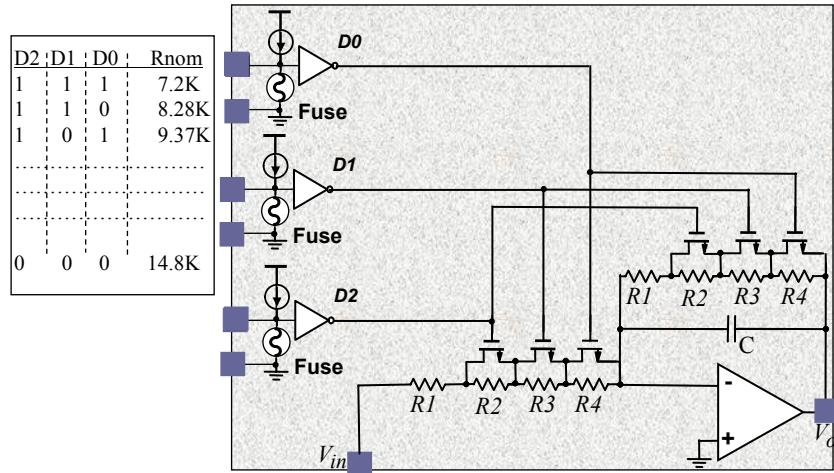

EECS 247

Lecture 6: Filters

© 2008 H.K. Page 33

Automatic Frequency Tuning

- By adding additional circuitry to the main filter circuit
 - Have the filter critical frequency automatically tuned
 - ☺Expensive trimming avoided
 - ☺Accounts for critical frequency variations due to temperature, supply voltage, and effect of aging
 - ☺Additional hardware, increased Si area & power

EECS 247

Lecture 6: Filters

© 2008 H.K. Page 34

Master-Slave Automatic Frequency Tuning


- Following facts used in this scheme:
 - Use a replica of the main filter or its main building block in the tuning circuitry
 - Tuning signal generated to tune the replica, also used to tune the main filter
 - Place the replica in close proximity of the main filter to ensure good matching
 - The replica is called the *master* and the main filter is named the *slave*
 - In the literature, this scheme is called *master-slave* tuning!

Master-Slave Frequency Tuning 1-Reference Filter (VCF)

- Use a biquad built with replica of main filter integrator for master filter (VCF)
- Utilize the fact that @ the frequency f_o , the lowpass (or highpass) outputs are 90 degree out of phase wrt to input

$$\frac{V_{LP}}{V_{in}} = \frac{I}{\frac{s^2}{\omega_b^2} + \frac{s}{Q\omega_b} + I} \quad @ \omega = \omega_b \quad \phi = -90^\circ$$

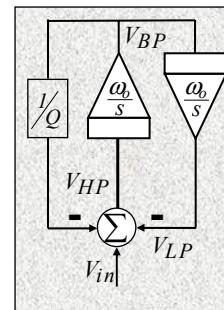
- Apply a sinusoid at the desired f_o^{desired}
- Compare the phase of LP output versus input
- Based on the phase difference:
 - Increase or decrease filter critical freq.



Master-Slave Frequency Tuning 1-Reference Filter (VCF)



$$\begin{aligned}
 V_{ref} &= A \sin(\omega t) \\
 V_{LP} &= A \sin(\omega t + \phi) \\
 V_{ref} \times V_{LP} &= A^2 \sin(\omega t) \sin(\omega t + \phi) \\
 V_{ref} \times V_{LP} &= \underbrace{\frac{A^2}{2} \cos \phi}_{\text{Filter Out}} - \underbrace{\frac{A^2}{2} \cos(2\omega t + \phi)}_{\text{Phase Comparator}}
 \end{aligned}$$

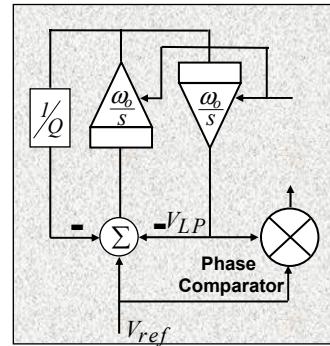Note that this term is=0 only when the incoming signal is at exactly the filter -3dB frequency



Master-Slave Frequency Tuning 1-Reference Filter (VCF)
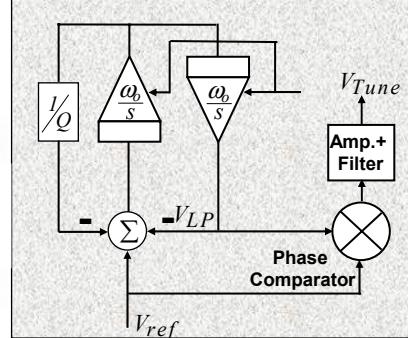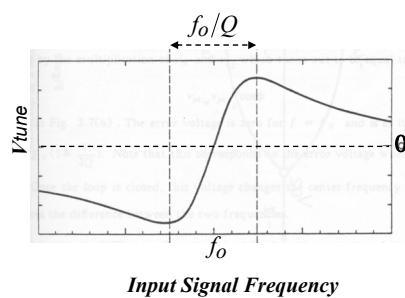
$$V_{tune} \approx -K \times V_{ref}^{rms} \times V_{LP}^{rms} \times \cos \phi$$




Master-Slave Frequency Tuning 1-Reference Filter (VCF)


- By closing the loop, feedback tends to drive the error voltage to zero.

→ Locks f_o to f_o^{desired} , the critical frequency of the filter to the accurate reference frequency

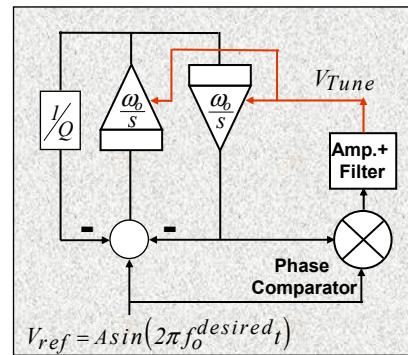- Typically the reference frequency is provided by a crystal oscillator with accuracies in the order of few ppm



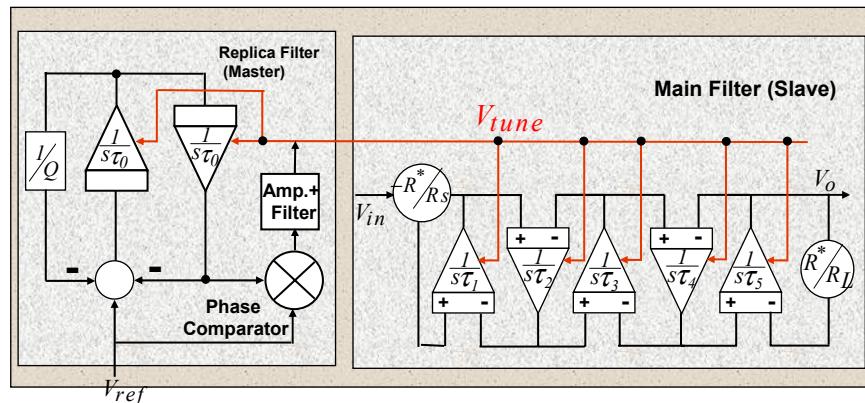Master-Slave Frequency Tuning 1-Reference Filter (VCF)



Ref: H. Khorramabadi and P.R. Gray, "High Frequency CMOS continuous-time filters," IEEE Journal of Solid-State Circuits, Vol.-SC-19, No. 6, pp.939-948, Dec. 1984.

Master-Slave Frequency Tuning


1- Reference Filter (VCF)

- Issues to be aware of:
 - Input reference tuning signal needs to be sinusoid → Disadvantage since clocks are usually available as square waveform
 - Reference signal feed-through to the output of the filter can limit filter dynamic range (reported levels of about $100\mu\text{VRms}$)
 - Ref. signal feed-through is a function of:
 - Reference signal frequency with respect to filter passband
 - Filter topology
 - Care in the layout
 - Fully differential topologies beneficial

Master-Slave Frequency Tuning

2- Reference Voltage-Controlled-Oscillator (VCO)

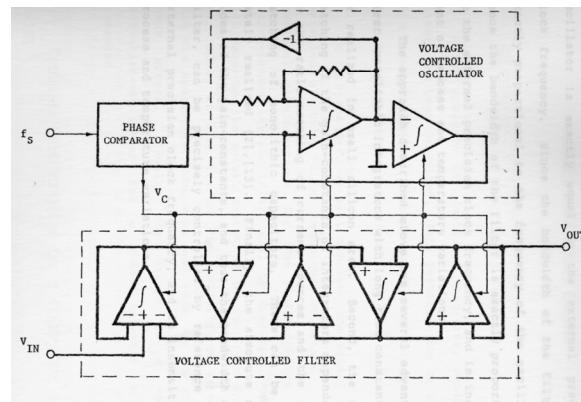- Instead of VCF a voltage-controlled-oscillator (VCO) is used
- VCO made of replica integrator used in main filter
- Tuning circuit operates exactly as a conventional phase-locked loop (PLL)
- Tuning signal used to tune main filter



Ref: K.S. Tan and P.R. Gray, "Fully integrated analog filters using bipolar FET technology," IEEE, J. Solid-State Circuits, vol. SC-13, no.6, pp. 814-821, December 1978..


Master-Slave Frequency Tuning

2- Reference Voltage-Controlled-Oscillator (VCO)

- Issues to be aware of:
 - Design of stable & repeatable oscillator challenging
 - VCO operation should be limited to the linear region of the integrator or else the operation loses accuracy (e.g. large signal transconductance versus small signal in a gm-C filter)
 - Limiting the VCO signal range to the linear region not a trivial design issue
 - In the case of VCF based tuning ckt, there was only ref. signal feedthrough. In this case, there is also the feedthrough of the VCO signal!!
 - Advantage over VCF based tuning → Reference input signal square wave (not sin.)


Master-Slave Frequency Tuning

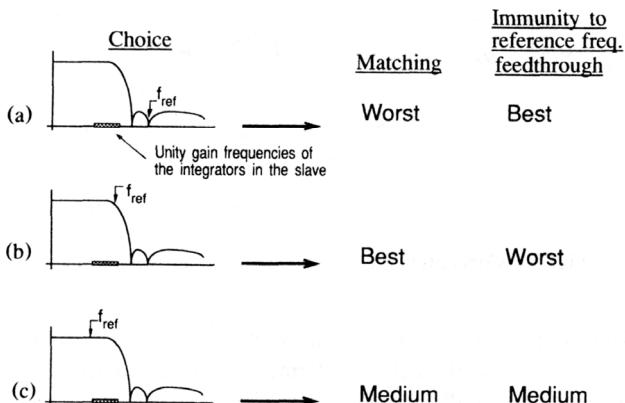Choice of Ref. Frequency wrt Feedthrough Immunity



Ref: V. Gopinathan, et. al, "Design Considerations for High-Frequency Continuous-Time Filters and Implementation of an Antialiasing Filter for Digital Video," *IEEE JSSC*, Vol. SC-25, no. 6 pp. 1368-1378, Dec. 1990.

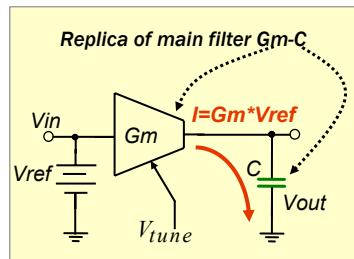Master-Slave Frequency Tuning 3-Reference Integrator Locked to Reference Frequency





- Replica of main filter integrator e.g. Gm-C building block used
- Utilizes the fact that a DC voltage source connected to the input of the Gm cell generates a constant current at the output proportional to the transconductance and the voltage reference

$$I = Gm \cdot V_{ref}$$

Reference Integrator Locked to Reference Frequency

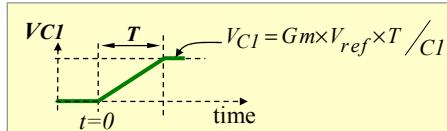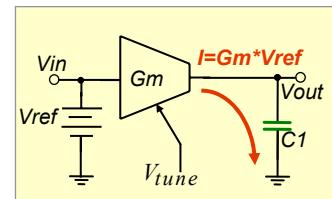- Consider the following sequence:
 - Integrating capacitor is fully discharged @ $t = 0$
 - At $t=0$ the capacitor is connected to the output of the Gm cell then:





$$\begin{aligned} Q_{C1} &= V_{C1} \times C_1 = Gm \times V_{ref} \times T \\ &\rightarrow V_{C1} = Gm \times V_{ref} \times T / C_1 \end{aligned}$$

Reference Integrator Locked to Reference Frequency

Since at the end of the period T:

$$V_{CI} \approx Gm \times V_{ref} \times T / C_I$$

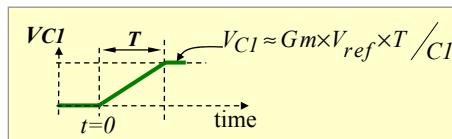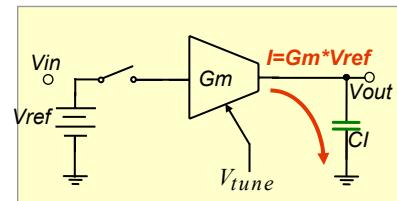
If V_{CI} is forced to be equal to V_{ref} then:




How do we manage to force $V_{CI} = V_{ref}$?

→ Use feedback!!

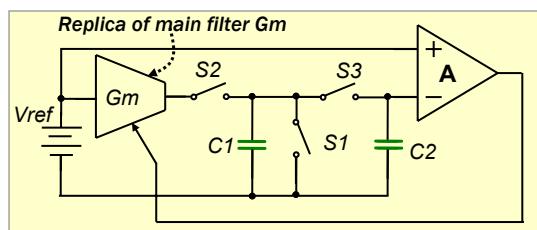Reference Integrator Locked to Reference Frequency





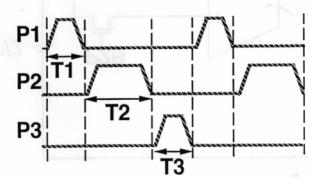- Three clock phase operation
- To analyze → study one phase at a time





Ref: A. Durham, J. Hughes, and W. Redman-White, "Circuit Architectures for High Linearity Monolithic Continuous-Time Filtering," *IEEE Transactions on Circuits and Systems*, pp. 651-657, Sept. 1992.

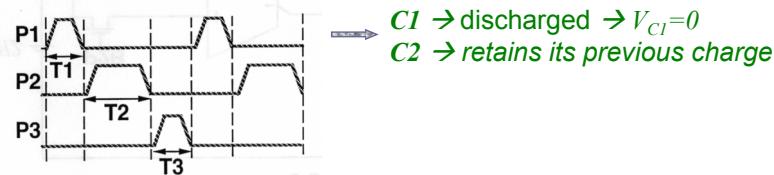
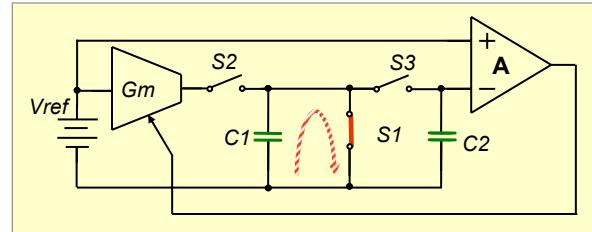
Reference Integrator Locked to Reference Frequency
 P1 high \rightarrow S1 closed



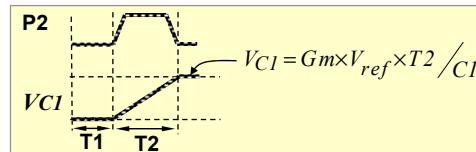
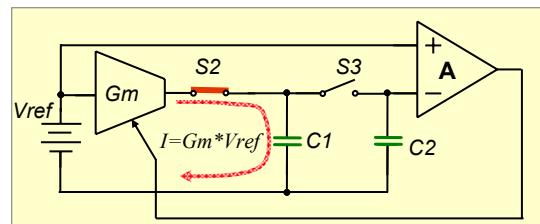
Reference Integrator Locked to Reference Frequency
 P2 high \rightarrow S2 closed



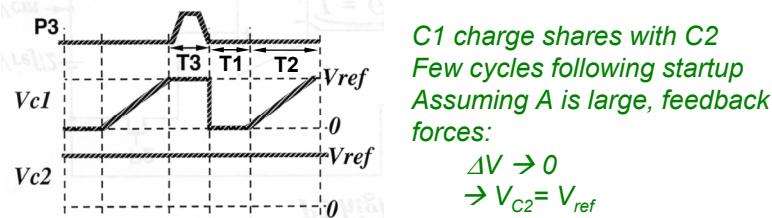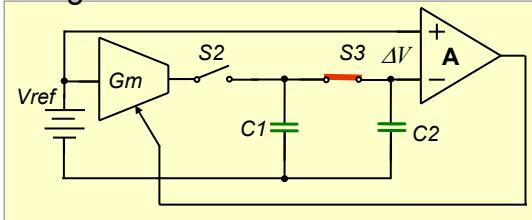Reference Integrator Locked to Reference Frequency
 P3 high \rightarrow S3 closed




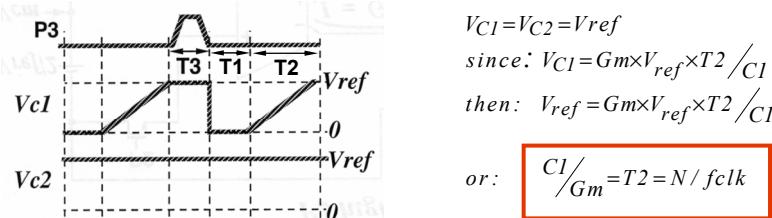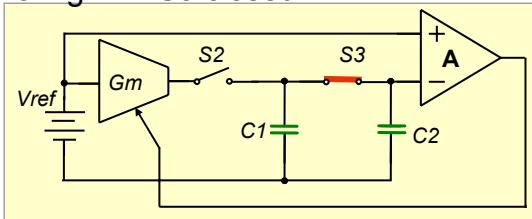Reference Integrator Locked to Reference Frequency
 P3 high \rightarrow S3 closed



Summary

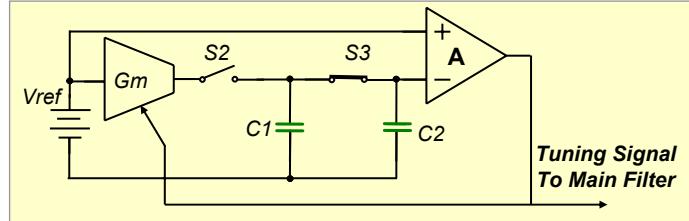Replica Integrator Locked to Reference Frequency



Feedback forces Gm to assume a value so that :

- Integrator time constant locked to an accurate frequency
- Tuning signal used to adjust the time constant of the main filter integrators


$$\tau_{intg} = \frac{C_1}{G_m} = N/f_{clk}$$

or

$$\omega_0^{intg} = \frac{G_m}{C_1} = f_{clk}/N$$

Issues

1- Loop Stability

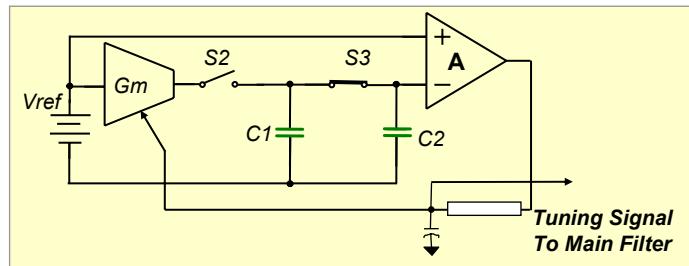


- Note: Need to pay attention to loop stability
 - ✓ C1 chosen to be smaller than C2 – tradeoff between stability and speed of lock acquisition
 - ✓ Lowpass filter at the output of amplifier (A) helps stabilize the loop

Issues

2- GM-Cell DC Offset Induced Error

Problems to be aware of:

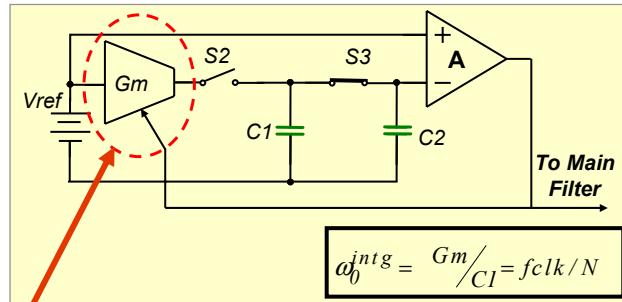

→ Tuning error due to master integrator DC offset

Issues

Gm Cell DC Offset


What is DC offset?

Simple example:

For the differential pair shown here, mismatch in input device or load characteristics would cause DC offset:

→ $V_o = 0$ requires a non-zero input voltage

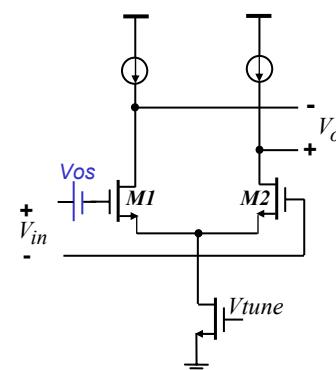Offset could be modeled as a small DC voltage source at the input for which with shorted inputs → $V_o = 0$




Example: Differential Pair

Simple Gm-Cell DC Offset

Mismatch associated with M1 & M2
 → DC offset

$$V_{os} = (V_{th1} - V_{th2}) - \frac{I}{2} V_{ovl,2} \frac{\Delta(W/L)_{M1,2}}{(W/L)_{M1,2}}$$

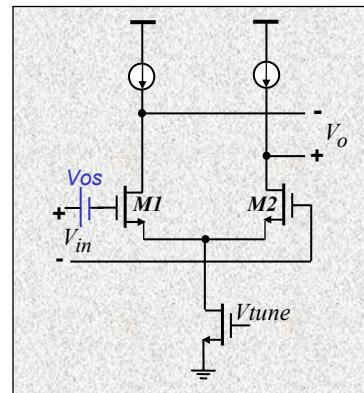Assuming offset due to load device mismatch is negligible




Ref: Gray, Hurst, Lewis, Meyer, *Analysis & Design of Analog Integrated Circuits*, Wiley 2001, page 335

EECS 247

Lecture 6: Filters

© 2008 H.K. Page 57

Gm-Cell Offset Induced Error

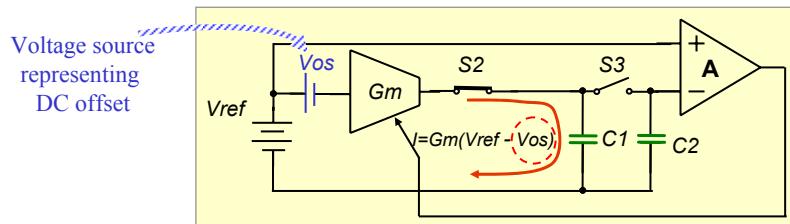

•Effect of Gm-cell DC offset:

$$V_{C1} = V_{C2} = V_{ref}$$

$$\text{Ideal: } V_{C1} = Gm \times V_{ref} \times T2 / C_1$$

$$\text{with offset: } V_{C1} = Gm \times (V_{ref} - V_{os}) \times T2 / C_1$$


$$\text{or: } C_1 / Gm = T2 \left(1 - \frac{V_{os}}{V_{ref}} \right)$$

EECS 247

Lecture 6: Filters

© 2008 H.K. Page 58

Gm-Cell Offset Induced Error

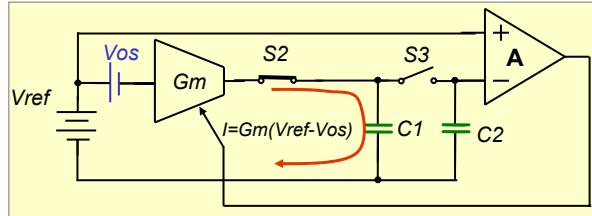

- Example:



$$C_1/G_m = T_2 \left(1 - \frac{V_{os}}{V_{ref}} \right) \quad f_{critical} \propto G_m/C_1$$

$$\text{for } \frac{V_{os}}{V_{ref}} = 1/10$$



10% error in tuning!

Gm-Cell Offset Induced Error Solution

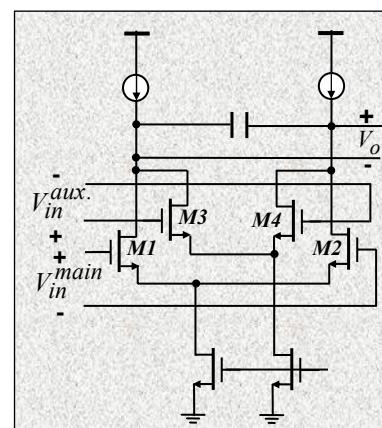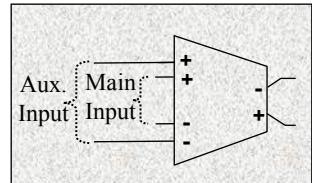- Assume differential integrator
- Add a pair of auxiliary inputs to the input stage for offset cancellation purposes



Simple Gm-Cell AC Small Signal Model

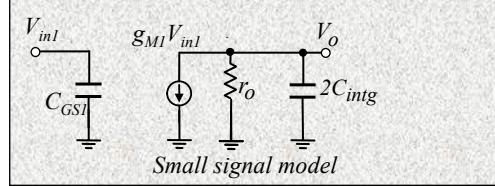
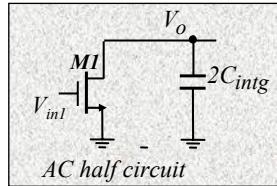


$$V_o = \left(g_m^{MI} V_{in1} \right) \left(r_o \parallel \frac{1}{s \times 2C_{intg}} \right) \quad r_o \text{ is parallel combination of } r_o \text{ of M1 & load}$$

$$V_o = \frac{-g_m^{MI} r_o}{1 + s \times 2C_{intg} r_o} V_{in1} \quad \& \quad g_m^{MI} r_o = aI \rightarrow \text{Integrator finite DC gain}$$

$$V_o = \frac{-aI}{1 + aI \times s \times 2C_{intg}} V_{in1} \quad \text{Note: } aI \rightarrow \infty, \quad V_o = \frac{-g_m^{MI}}{s \times 2C_{intg}} V_{in1}$$

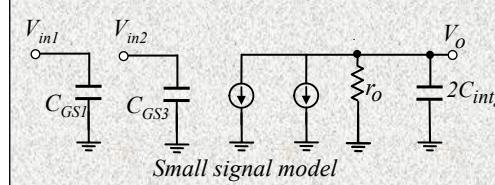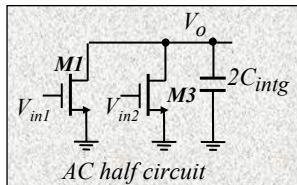Simple Gm-Cell + Auxiliary Inputs AC Small Signal Model




$$V_o = \left(g_m^{MI} V_{in1} + g_m^{M3} V_{in2} \right) \left(r_o \parallel \frac{1}{s \times 2C_{intg}} \right) \quad r_o \text{ parallel combination of } r_o \text{ of M1, M3, & current source}$$


$$V_o = \frac{-g_m^{MI} r_o}{1 + s \times 2C_{intg} r_o} V_{in1} - \frac{g_m^{M3} r_o}{1 + s \times 2C_{intg} r_o} V_{in2}$$

$$V_o = \frac{-aI}{1 + aI \times s \times 2C_{intg}} V_{in1} - \frac{a^3}{1 + a^3 \times s \times 2C_{intg}} V_{in2}$$


Gm-Cell DC Model

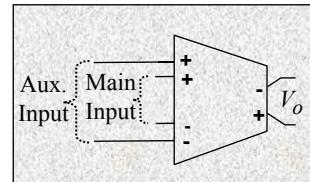

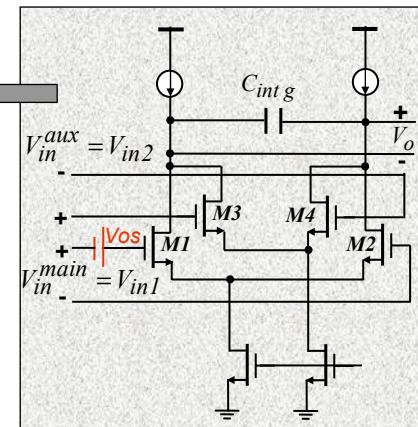
$$V_o = a1(V_{in1} + V_{os}) + a3 V_{in2}$$



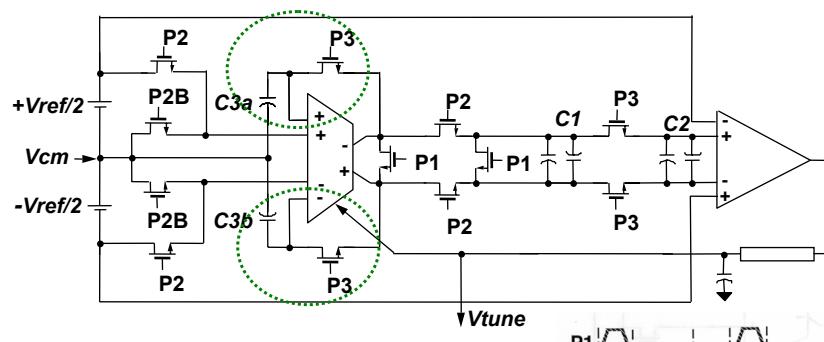
Reference Integrator Locked to Reference Frequency Offset Cancellation Incorporated



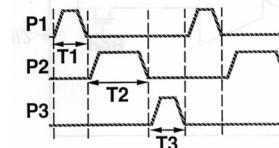Gm-cell → two sets of input pairs
 Aux. input pair + C3a,b → Offset cancellation
 Same clock timing



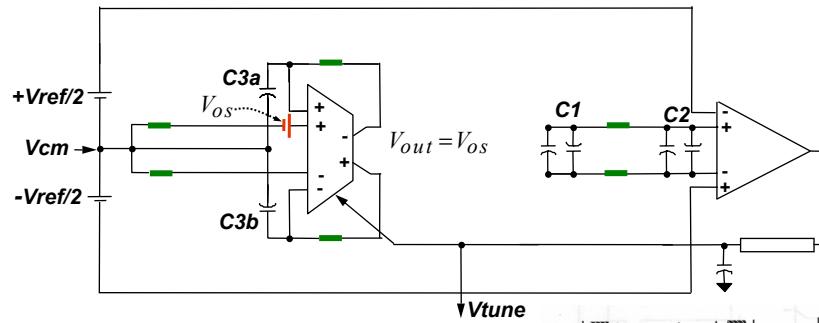Reference Integrator Locked to Reference Frequency P3 High (Update & Store offset)



Gm-cell \rightarrow Unity gain configuration via aux. inputs
Main inputs shorted
 $C1, C2 \rightarrow$ Charge sharing

Reference Integrator During Offset Cancellation Phase

$$V_o = a1(V_{in1} + V_{os}) + a3 V_{in2}$$

$$V_{in2} = -V_o$$


$$V_o = a1 \times V_{os} - a3 \times V_o$$

$$\rightarrow V_o = \frac{a1}{1 + a3} \times V_{os}$$


Assuming $a1 = a3 \gg 1$

$$V_o = V_{os} \quad \& \quad V_{in2} = -V_{os}$$

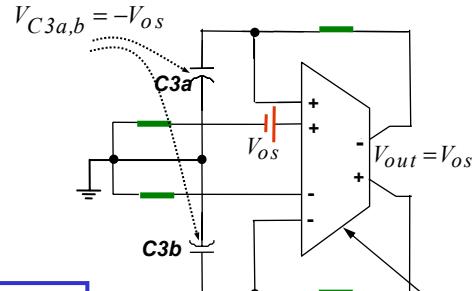$C3a,b \rightarrow$ Store main Gm-cell offset




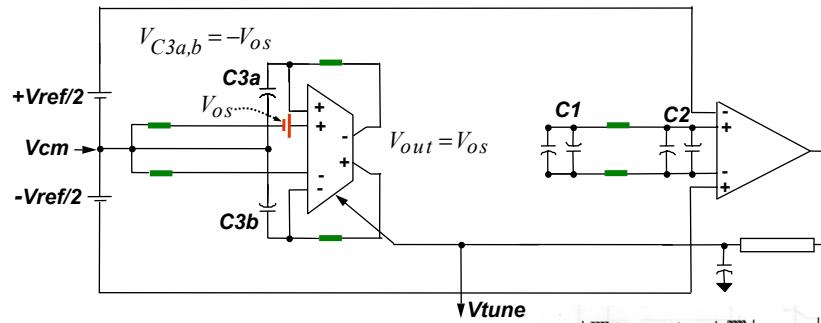Reference Integrator Locked to Reference Frequency P3 High (Update & Store offset)




Gm-cell → Unity gain configuration via aux. inputs
Main input shorted
 $C3a,b \rightarrow$ Store Gm-cell offset
 $C1, C2 \rightarrow$ Charge sharing

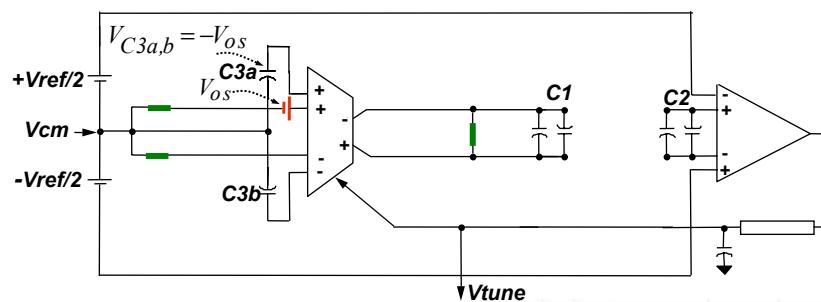Reference Integrator Locked to Reference Frequency P1 High (Reset)




Gm-cell → Reset.
 $C1 \rightarrow$ Discharge
 $C2 \rightarrow$ Hold Charge
 $C3a,b \rightarrow$ Hold Charge
→ Offset previously stored on $C3a,b$ cancels gm-cell offset

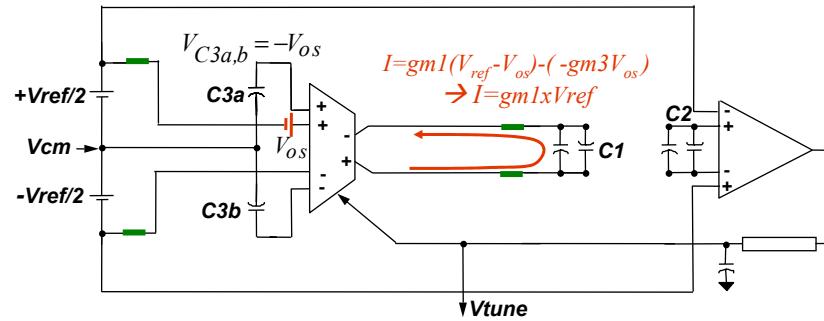Reference Integrator Locked to Reference Frequency P2 High (Charge)



Gm-cell → Charging C1
 $C_{3a,b}$ → Store/hold Gm-cell offset
 C_2 → Hold charge

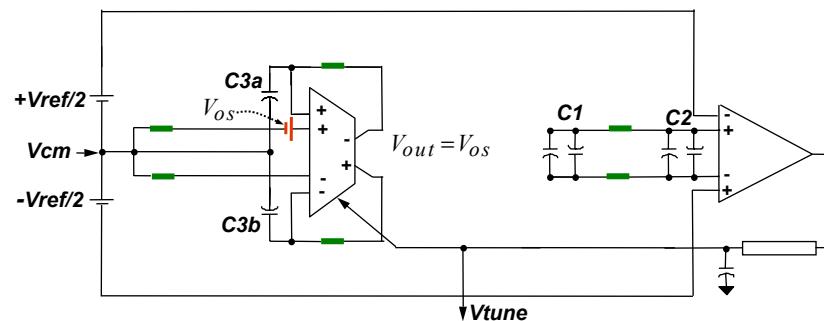Summary Reference Integrator Locked to Reference Frequency



Key point: Tuning error due to Gm-cell offset cancelled
 *Note: Same offset compensation technique can be used in many other applications

Summary


Reference Integrator Locked to Reference Frequency

Tuning error due to gm-cell offset voltage resolved

Advantage over previous schemes:

→ f_{clk} can be chosen to be at much higher frequencies compared to filter bandwidth ($N > I$)

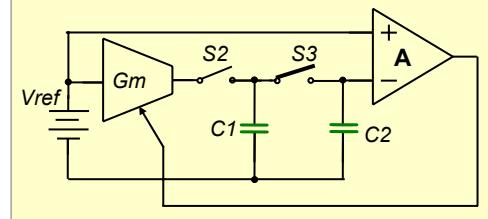→ Feedthrough of clock falls out of band and thus attenuated by filter



Feedback forces Gm to vary so that :

$$\tau_{intg} = \frac{C_1}{G_m} = N / f_{clk}$$

or

$$\omega_0^{intg} = \frac{G_m}{C_1} = f_{clk} / N$$