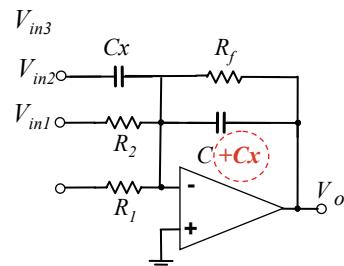


## EE247 Lecture 9

- Continuous-time filters (continued)
  - Various Gm-C filter implementations
  - Performance comparison of various continuous-time filter topologies
- Switched-capacitor filters
  - Emulating a resistor by using a switched capacitor
  - Tradeoffs in choosing sampling rate
  - Effect of sample and hold
  - Switched-capacitor network electronic noise
  - Switched-capacitor integrators
    - DDI integrators
    - LDI integrators


## Correction to Lecture 4 Slide # 48 Transmission Zero Generation Opamp-RC Integrator

$$V_o = -\frac{I}{s(C+C_x)} \left[ \frac{V_{in1}}{R_1} + \frac{V_{in2}}{R_2} + \frac{V_o}{R_f} \right] - V_{in3} \times \frac{C_x}{C+C_x}$$


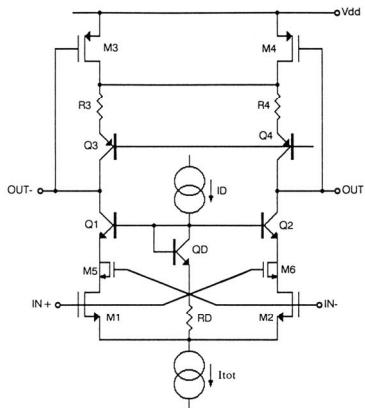
## BiCMOS Gm-C Integrator


- M1,2 → triode mode
- Q1,2 → hold  $V_{ds}$  of M1,2 constant
- Current source ID used to tune filter critical frequency by varying  $V_{ds}$  of M1,2 and thus controlling  $gm$  of M1,2
- M3, M4 operate in triode mode and added to provide common-mode feedback
- Needs higher supply voltage compared to the previous design since quite a few devices are stacked vertically



**Ref:** R. Alini, A. Baschirotto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.

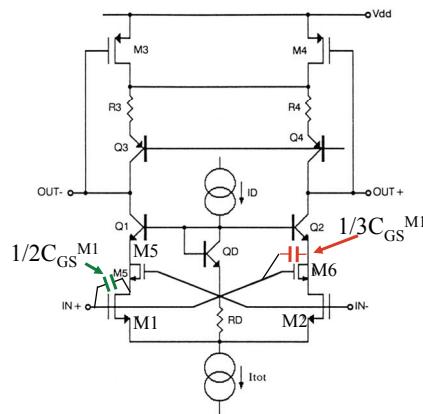
## BiCMOS Gm-C Integrator

- M5 & M6 configured as capacitors- added to compensate for RHP zero due to  $C_{gd}$  of M1,2 (moves it to LHP) size of M5,6 →  $1/3$  of M1,2



**Ref:** R. Alini, A. Baschirotto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.
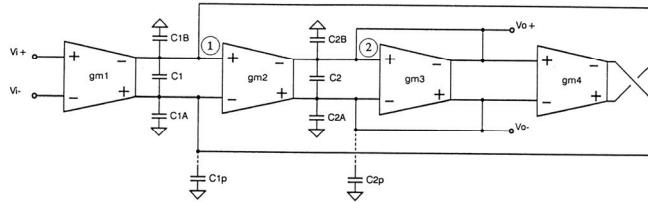
## BiCMOS Gm-C Filter For Disk-Drive Application



- Using the integrators shown in the previous page
- Biquad filter for disk drives
- $gm_1 = gm_2 = gm_4 = 2gm_3$
- $Q=2$
- Tunable from 8MHz to 32MHz

**Ref:** R. Alini, A. Baschirrotto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.

## Summary Continuous-Time Filters



- Opamp RC filters
  - Good linearity → High dynamic range (**60-90dB**)
  - Only discrete tuning possible
  - Medium usable signal bandwidth (**<10MHz**)
- Opamp MOSFET-C
  - Linearity compromised (typical dynamic range **40-60dB**)
  - Continuous tuning possible
  - Low usable signal bandwidth (**<5MHz**)
- Opamp MOSFET-RC
  - Improved linearity compared to Opamp MOSFET-C (D.R. **50-90dB**)
  - Continuous tuning possible
  - Low usable signal bandwidth (**<5MHz**)
- Gm-C
  - Highest frequency performance -at least an order of magnitude higher compared to other integrator-based active filters (**<100MHz**)
  - Dynamic range not as high as Opamp RC but better than Opamp MOSFET-C (**40-70dB**)

## Switched-Capacitor Filters

- SC filters are sampled-data type circuits operating with continuous signal amplitude & quantized time
- Emulating resistor via switched-capacitor network
- 1<sup>st</sup> order switched-capacitor filter
- Switch-capacitor filter considerations:
  - Issue of aliasing and how to prevent aliasing
  - Tradeoffs in choice of sampling rate
  - Effect of sample and hold
  - Switched-capacitor filter electronic noise
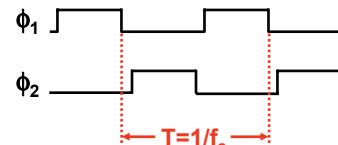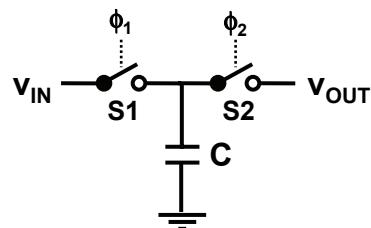
## Switched-Capacitor Resistor


- Capacitor C is the “switched capacitor”
- Non-overlapping clocks  $\phi_1$  and  $\phi_2$  control switches S1 and S2, respectively
- $V_{IN}$  is sampled at the falling edge of  $\phi_1$ 
  - Sampling frequency  $f_s$
- Next,  $\phi_2$  rises and the voltage across C is transferred to  $V_{OUT}$
- Why does this behave as a resistor?



## Switched-Capacitor Resistors

- Charge transferred from  $v_{IN}$  to  $v_{OUT}$  during each clock cycle is:

$$Q = C(v_{IN} - v_{OUT})$$

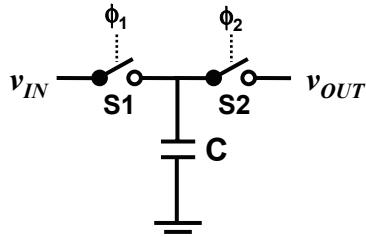


- Average current flowing from  $v_{IN}$  to  $v_{OUT}$  is:

$$i = Q/t = Q \cdot f_s$$

Substituting for  $Q$ :

$$i = f_s C(v_{IN} - v_{OUT})$$

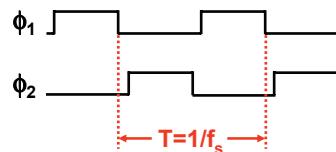

## Switched-Capacitor Resistors

$$i = f_s C(v_{IN} - v_{OUT})$$



With the current through the switched-capacitor resistor proportional to the voltage across it, the equivalent "switched capacitor resistance" is:

$$R_{eq} = \frac{v_{IN} - v_{OUT}}{i} = \frac{1}{f_s C}$$

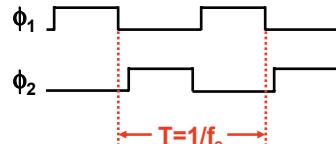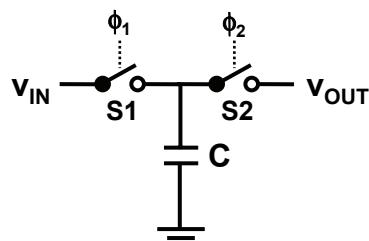Example:

$$\begin{aligned} f_s &= 100\text{kHz}, C = 0.1\text{pF} \\ \rightarrow R_{eq} &= 100\text{Mega}\Omega \end{aligned}$$

Note: Can build large time-constant in small area





# Switched-Capacitor Filter


- Let's build a "switched- capacitor" filter ...
- Start with a simple RC LPF
- Replace the physical resistor by an equivalent switched-capacitor resistor
- 3-dB bandwidth:

$$\omega_{-3dB} = \frac{1}{R_{eq}C_2} = f_s \times \frac{C_1}{C_2}$$
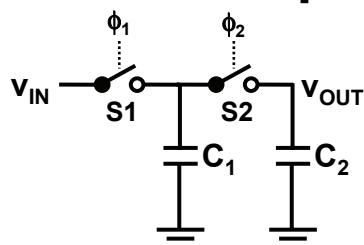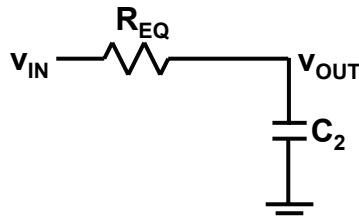
$$f_{-3dB} = \frac{1}{2\pi} f_s \times \frac{C_1}{C_2}$$



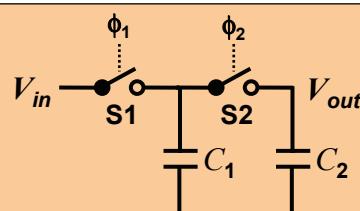
## Switched-Capacitor Filter Advantage versus Continuous-Time Filter



$$f_{-3dB} = \frac{1}{2\pi} f_s \times \frac{C_1}{C_2}$$

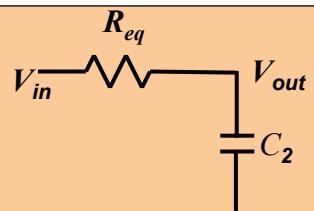- Corner freq. proportional to:  
System clock (accurate to few ppm)  
C ratio accurate  $\rightarrow < 0.1\%$




$$f_{-3dB} = \frac{1}{2\pi} \times \frac{1}{R_{eq}C_2}$$

- Corner freq. proportional to:  
Absolute value of Rs & Cs  
Poor accuracy  $\rightarrow 20$  to  $50\%$

**Main advantage of SC filters  $\rightarrow$  inherent corner frequency accuracy**
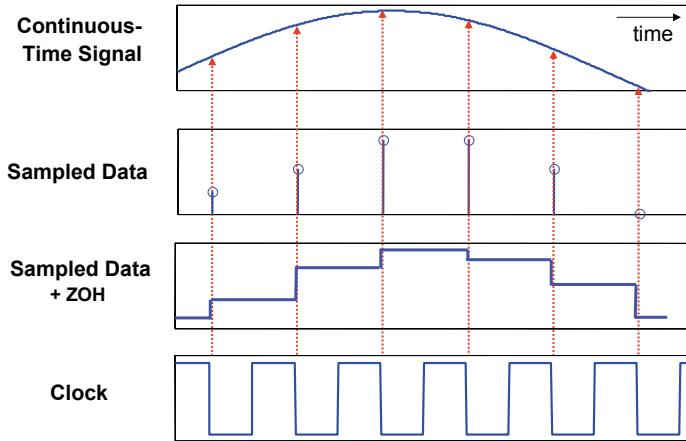
## Typical Sampling Process

$\text{Continuous-Time(CT)} \Rightarrow \text{Sampled Data (SD)}$



EECS 247 Lecture 9

Switched-Capacitor Filters


© 2008 H. K. Page 13

## Uniform Sampling

### Nomenclature:

Continuous time signal	$x_c(t)$
Sampling interval	$T$
Sampling frequency	$f_s = 1/T$
Sampled signal	$x_d(kT) = x/k$

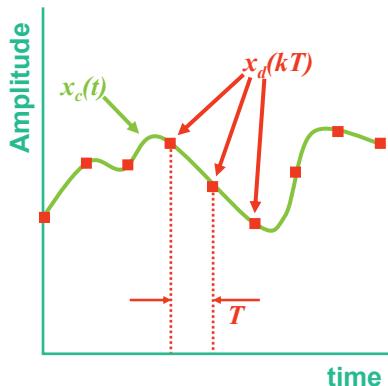- Problem: Multiple continuous time signals can yield exactly the same discrete time signal
- Let's look at samples taken at  $1\mu\text{s}$  intervals of several sinusoidal waveforms ...




Note: Samples are the waveform values at  $kT$  instances and undefined in between

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 14

## Sampling Sine Waves

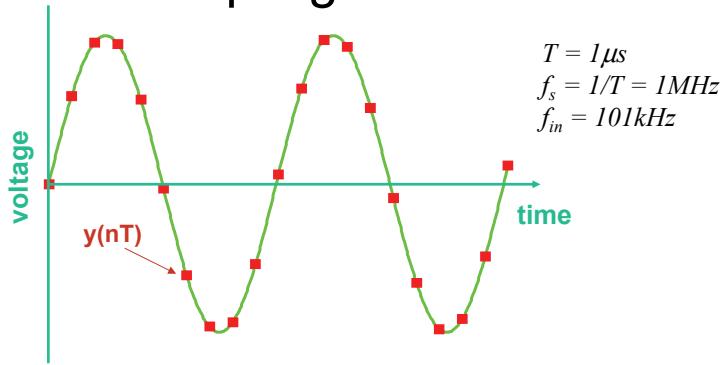


$$v(t) = \cos(2\pi f_{in} t)$$

Sampled-data domain  $\rightarrow t \rightarrow n \cdot T$  or  $t \rightarrow n/f_s$

$$v(n) = \cos\left(2\pi \frac{f_{in}}{f_s} \cdot n\right) = \cos\left(2\pi \frac{101kHz}{1MHz} \cdot n\right)$$


## Sampling Sine Waves Aliasing

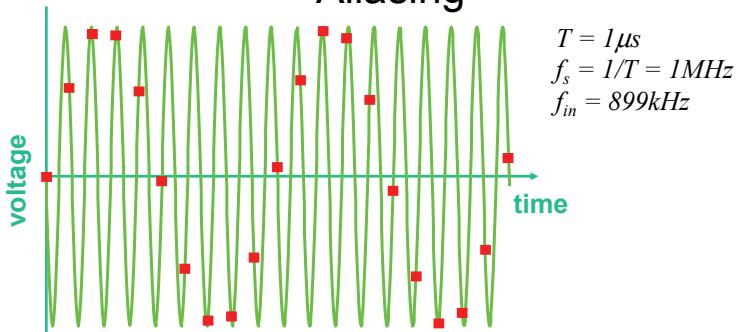

$$v(n) = \cos\left(2\pi \frac{899kHz}{1MHz} \cdot n\right) = \cos\left(2\pi \frac{(1000kHz - 101kHz)}{1MHz} \cdot n\right) = \cos\left(2\pi - \frac{101kHz}{1MHz} \cdot n\right)$$

$= \cos\left(2\pi \frac{101kHz}{1MHz} \cdot n\right)$

## Sampling Sine Waves Aliasing

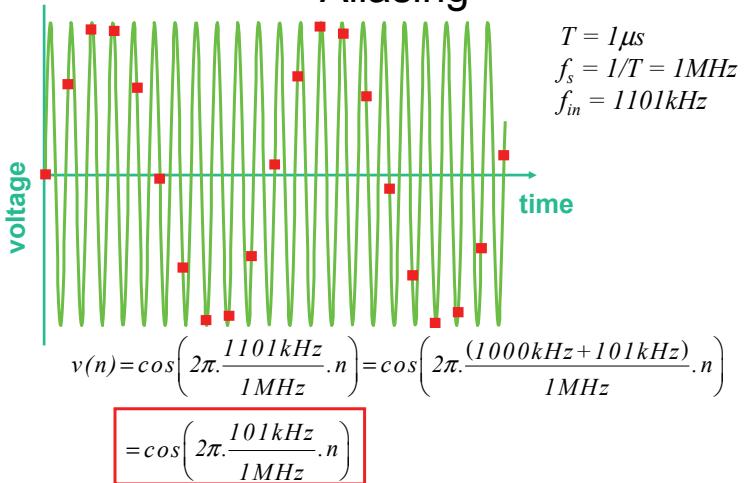

## Sampling Sine Waves

### Problem:

Identical samples for:

$$v(t) = \cos [2\pi f_{in} t]$$

$$v(t) = \cos [2\pi(n \cdot f_s + f_{in})t]$$


$$v(t) = \cos [2\pi(n \cdot f_s - f_{in})t]$$

\* (n-integer)


→ Multiple continuous time signals can yield exactly the same discrete time signal

## Sampling Sine Waves Frequency Spectrum

Signal scenario  
before sampling

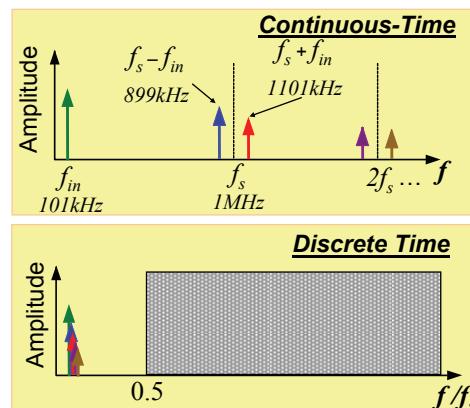


Signal scenario  
after sampling

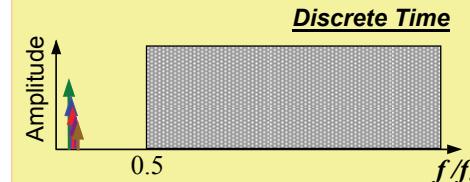

Key point: Signals @  $n f_s \pm f_{max\_signal}$  fold back into band of interest → Aliasing

## Sampling Sine Waves Frequency Spectrum

Signal scenario  
before sampling

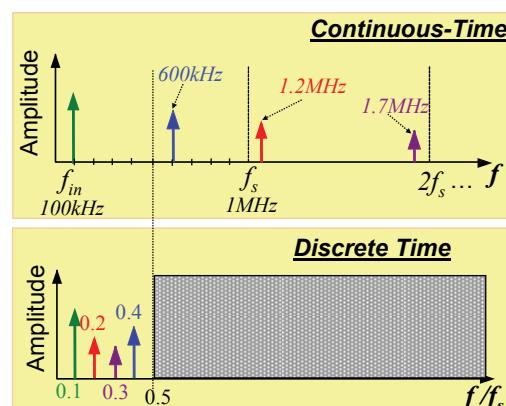

Signal scenario  
after sampling



Key point: Signals @  $n f_s \pm f_{max\_signal}$  fold back into band of interest → Aliasing

# Aliasing

- Multiple continuous time signals can produce identical series of samples
- The folding back of signals from  $nf_s \pm f_{sig}$  (n integer) down to  $f_{fin}$  is called aliasing
  - Sampling theorem:  $f_s > 2f_{max\_Signal}$
- If aliasing occurs, no signal processing operation downstream of the sampling process can recover the original continuous time signal

## How to Avoid Aliasing?

- Must obey sampling theorem:


$$f_{max\text{-}Signal} < f_s / 2$$

\*Note:

Minimum sampling rate of  $f_s = 2f_{max\text{-}Signal}$  is called Nyquist rate

- Two possibilities:
  1. Sample fast enough to cover all spectral components, including "parasitic" ones outside band of interest
  2. Limit  $f_{max\text{-}Signal}$  through filtering → attenuate out-of-band components prior to sampling



## How to Avoid Aliasing? 1-Sample Fast

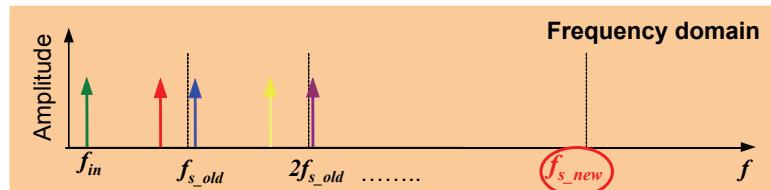

Push sampling frequency to  $\times 2$  of the highest frequency signal to cover all unwanted signals as well as wanted signals



→ In vast majority of cases not practical
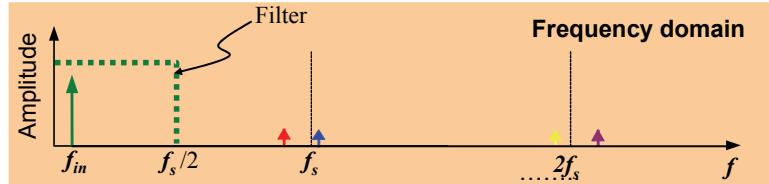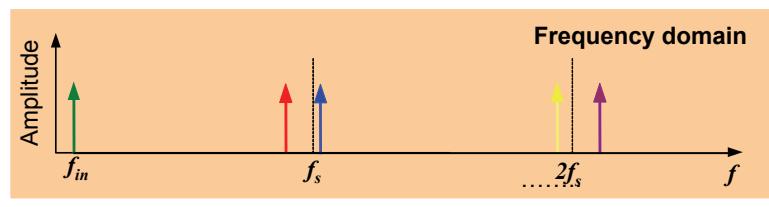
## How to Avoid Aliasing? 2-Filter Out-of-Band Signal Prior to Sampling



Pre-filter signal to eliminate/attenuate signals above  $f_s/2$ - then sample


## Anti-Aliasing Filter Considerations

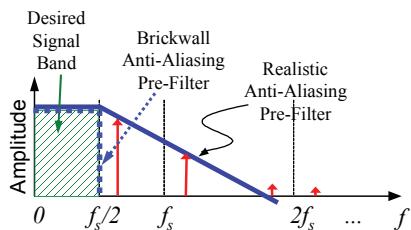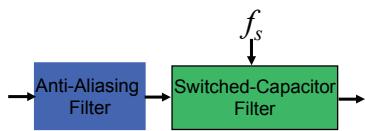

Case1-  $B = f_{sig\ max} = f_s/2$


- Non-practical since an extremely high order anti-aliasing filter (close to an ideal brickwall filter) is required
- Practical anti-aliasing filter → Non-zero filter "transition band"
- In order to make this work, we need to sample much faster than 2x the signal bandwidth  
→ "Oversampling"

## Practical Anti-Aliasing Filter

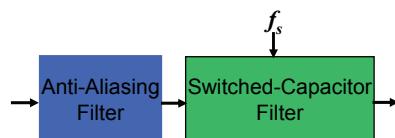


Case2 -  $B = f_{max\_Signal} \ll f_s/2$

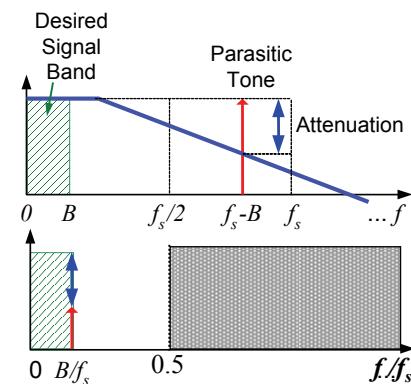- More practical anti-aliasing filter
- Preferable to have an anti-aliasing filter with:
  - The lowest order possible
  - No frequency tuning required (if frequency tuning is required then why use switched-capacitor filter, just use the prefilter!?)


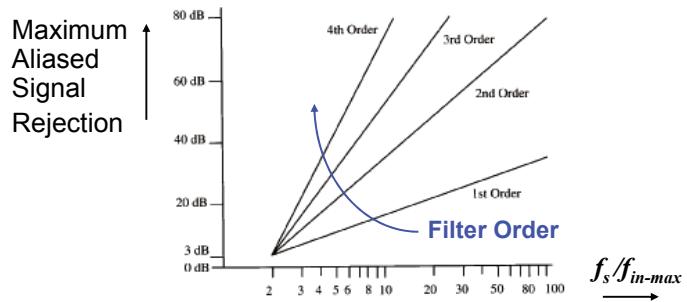
## Tradeoff Oversampling Ratio versus Anti-Aliasing Filter Order




\* Assumption → anti-aliasing filter is Butterworth type (not a necessary requirement)

→ Tradeoff: Sampling frequency versus anti-aliasing filter order

Ref: R. v. d. Plassche, *CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters*, 2nd ed., Kluwer publishing, 2003, p.41


## Effect of Sample & Hold

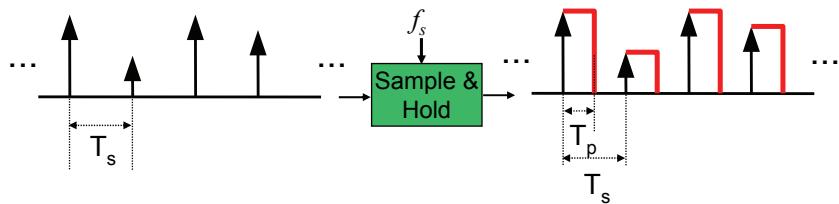

- Using the Fourier transform of a rectangular impulse:

$$|H(f)| = \frac{T_p}{T_s} \frac{\sin(\pi f T_p)}{\pi f T_p} \rightarrow \frac{\sin x}{x} \text{ shape}$$
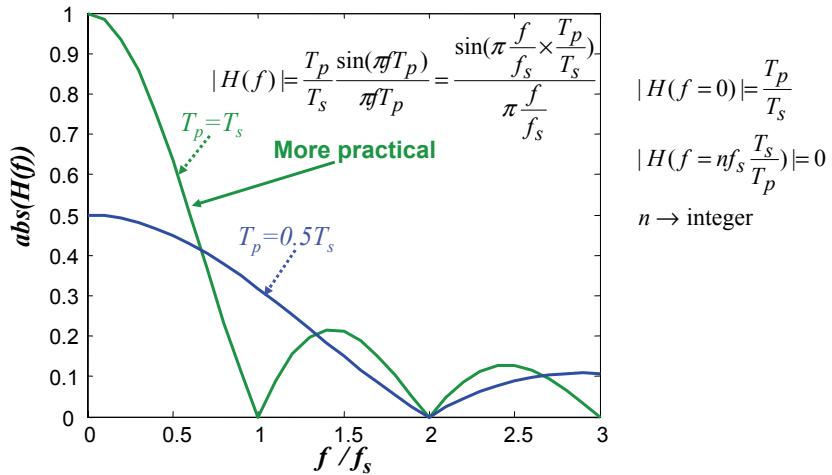
## Effect of Sample & Hold on Frequency Response




EECS 247 Lecture 9


Switched-Capacitor Filters

© 2008 H. K. Page 29
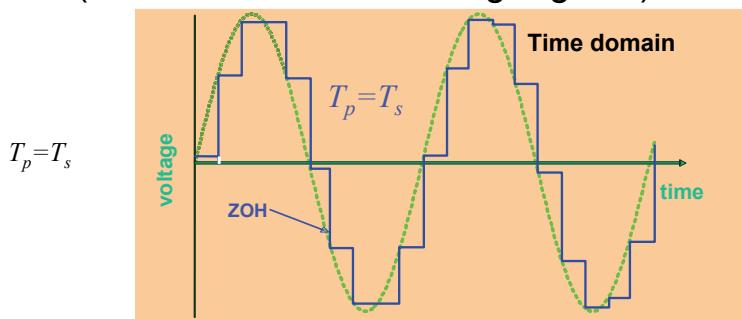
## Sample & Hold Effect (Reconstruction of Analog Signals)



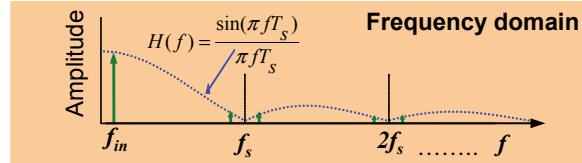Magnitude droop due to  $\sin x/x$  effect



EECS 247 Lecture 9


Switched-Capacitor Filters

© 2008 H. K. Page 30


## Sample & Hold Effect (Reconstruction of Analog Signals)

Magnitude droop  
due to  $\sin x/x$   
effect:

Case 1)  $f_{sig} = f_s/4$

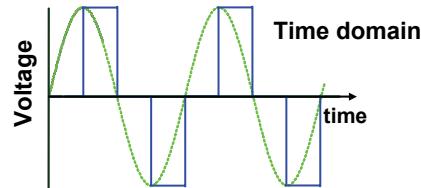

Droop = -1dB

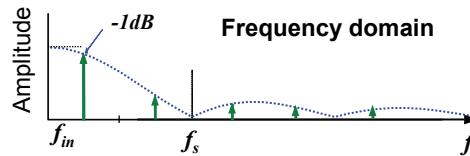



## Sample & Hold Effect (Reconstruction of Analog Signals)

Magnitude droop due to  
 $\sin x/x$  effect:


Case 2)  
 $f_{sig} = f_s/32$

Droop = -0.0035dB

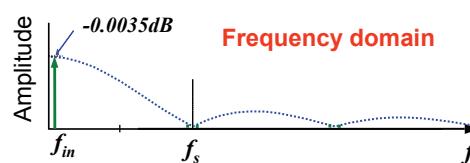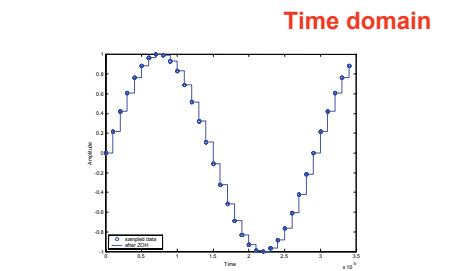- Insignificant droop  
→ High oversampling ratio desirable



## Sampling Process Including S/H

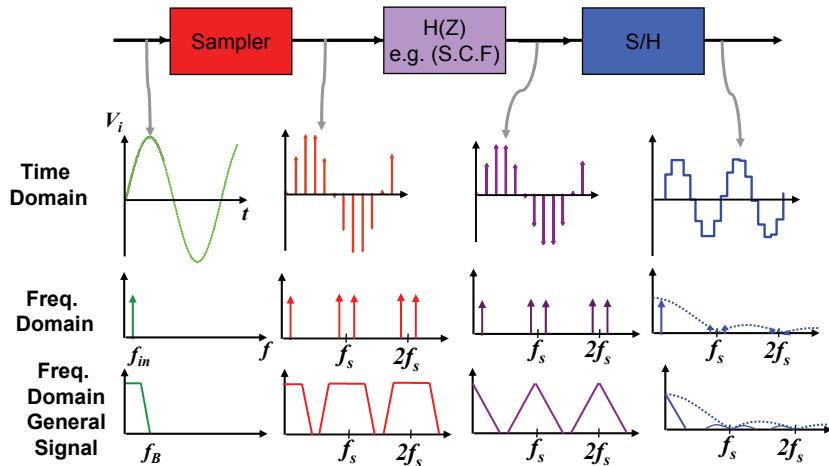

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 33



## 1<sup>st</sup> Order Filter S.C. versus C.T. Transient Analysis

1<sup>st</sup> Order RC versus SC LPF

$$f_s = 1\text{MHz}$$

$$f_{-3dB} = 50\text{kHz}$$

$$f_{in} = 3.6\text{kHz}$$

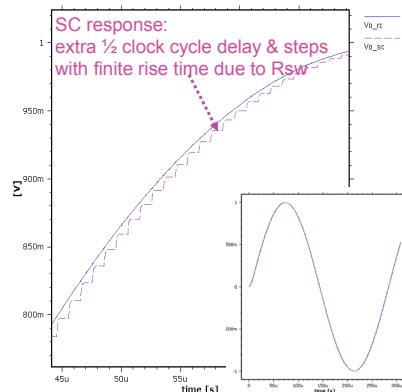
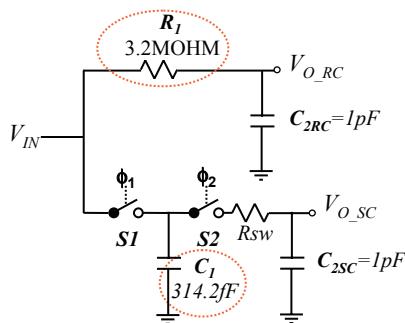


EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 34
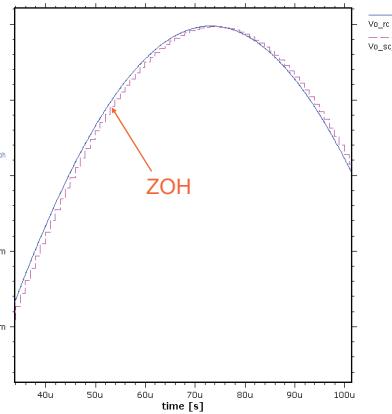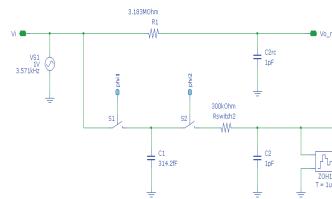
## 1<sup>st</sup> Order Filter Transient Analysis



- ZOH: Emulates an ideal S/H → pick signal after settling (usually at end of clock phase)
- Adds delay and  $\sin(x)/x$  shaping
- When in doubt, use a ZOH in periodic ac simulations

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 35


## Periodic AC Analysis

### 1st Order RC / SC LPF

$f_s = 1\text{MHz}$   
 $f_c = 50\text{kHz}$   
 $f_x = 3.571\text{kHz}$

Periodic AC Analysis PAC1  
log sweep from 1 to 31M (1001 steps)

Netlist  
ahnd\_include "zoh.def"

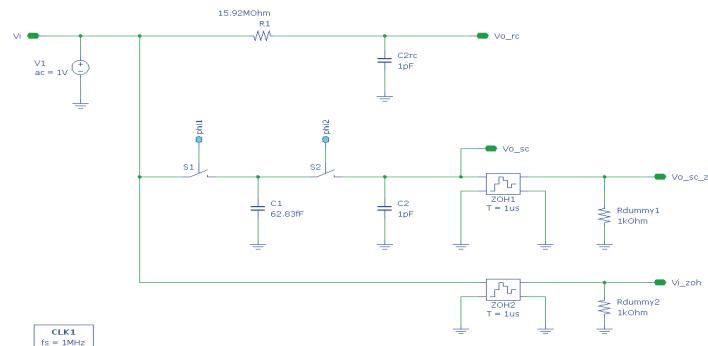


EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 36
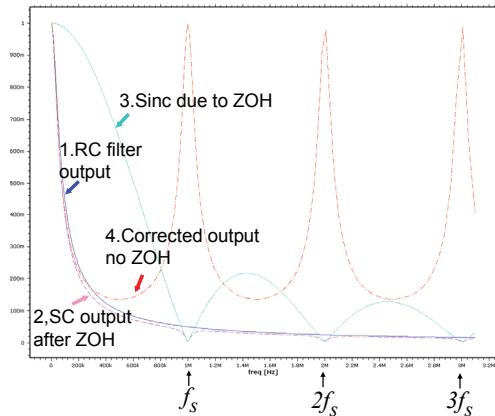
## 1<sup>st</sup> Order Filter Magnitude Response



1. RC filter output
2. SC output after ZOH
3. Output after single ZOH
4. Output w/o effect of ZOH
  - (2) over (3)
  - Repeats filter shape around  $nf_s$
  - Identical to RC for  $f \ll f_s/2$

## Periodic AC Analysis

- SPICE frequency analysis
  - ac linear, **time-invariant** circuits
  - pac linear, **time-variant** circuits
- SpectreRF statements
 

```
V1 ( Vi 0 ) vsource type=dc dc=0 mag=1 pacmag=1
PSS1 pss period=lu errpreset=conservative
PAC1 pac start=1 stop=1M lin=1001
```
- Output
  - Divide results by  $\text{sinc}(f/f_s)$  to correct for ZOH distortion

## Spectre Circuit File

```
rc_pac
simulator lang=spectre
ahdl_include "zoh.def"

S1 ( Vi c1 phil 0 ) relay ropen=100G rclosed=1 vt1=-500m vt2=500m
S2 ( c1 Vo_sc phi2 0 ) relay ropen=100G rclosed=1 vt1=-500m vt2=500m
C1 ( c1 0 ) capacitor c=314.159f
C2 ( Vo_sc 0 ) capacitor c=1p
R1 ( Vi Vo_rc ) resistor r=3.1831M
C2rc ( Vo_rc 0 ) capacitor c=1p
CLK1_Vphil ( phil 0 ) vsource type=pulse val0=-1 val1=1 period=1u
width=450n delay=50n rise=10n fall=10n
CLK1_Vphi2 ( phi2 0 ) vsource type=pulse val0=-1 val1=1 period=1u
width=450n delay=550n rise=10n fall=10n
V1 ( Vi 0 ) vsource type=dc dc=0 mag=1 pacmag=1
PSS1 pss period=1 errpreset=conservative
PAC1 pac start=1 stop=3.1M log=1001
ZOH1 ( Vo_sc_zoh 0 Vo_sc 0 ) zoh period=1u delay=500n aperture=1n tc=10p
ZOH2 ( Vi_zoh 0 Vi 0 ) zoh period=1u delay=0 aperture=1n tc=10p
```

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 39

## ZOH Circuit File


```
// Copy from the SpectreRF Primer
module zoh (Pout, Nout, Pin, Nin) (period,
delay, aperture, tc)
node [V,I] Pin, Nin, Pout, Nout;
parameter real period=1 from (0:inf);
parameter real delay=0 from [0:inf];
parameter real aperture=1/100 from (0:inf);
parameter real tc=1/500 from (0:inf);
{
integer n; real start, stop;
node [V,I] hold;
analog {
// determine the point when aperture begins
n = ($time() - delay + aperture) / period
+ 0.5;
start = n*period + delay - aperture;
$break_point(start);
// determine the time when aperture ends
n = ($time() - delay) / period + 0.5;
stop = n*period + delay;
$break_point(stop);
}
// Implement switch with effective series
// resistance of 1 Ohm
if ( ($time() > start) && ($time() <= stop))
I(hold) <- V(hold) - V(Pin, Nin);
else
I(hold) <- 1.0e-12 * (V(hold) - V(Pin, Nin));
// Implement capacitor with an effective
// capacitance of tc
I(hold) <- tc * dot(V(hold));
// Buffer output
V(Pout, Nout) <- V(hold);
// Control time step tightly during
// aperture and loosely otherwise
if (( $time() >= start) && ($time() <= stop))
$bound_step(tc);
else
$bound_step(period/5);
}
```

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 40

## First Order S.C. Filter

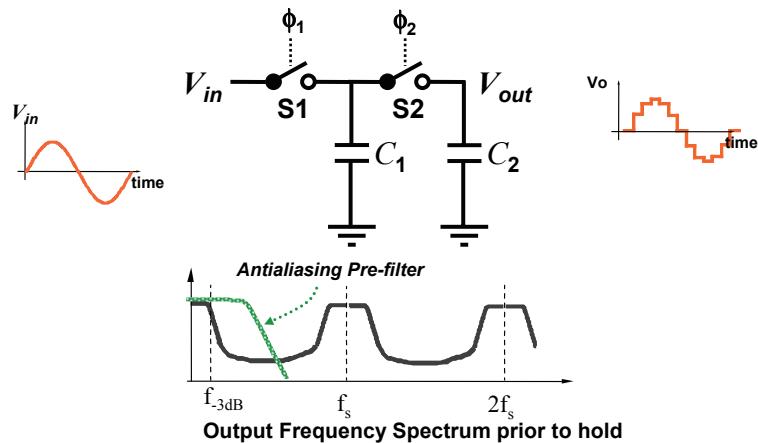


Switched-Capacitor Filters → problem with aliasing

## Sampled-Data Systems (Filters) Anti-aliasing Requirements

- Frequency response repeats at  $f_s, 2f_s, 3f_s, \dots$
- High frequency signals close to  $f_s, 2f_s, \dots$  folds back into passband (aliasing)
- Most cases must pre-filter input to a sampled-data systems (filter) to attenuate signal at:  
 $f > f_s/2$  (Nyquist  $\rightarrow f_{max} < f_s/2$ )
- Usually, anti-aliasing filter  $\rightarrow$  included on-chip as continuous-time filter with relaxed specs. (no tuning)

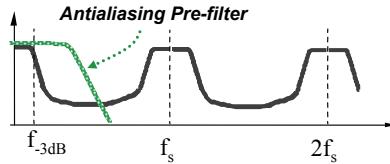
## Example : Anti-Aliasing Filter Requirements



- Voice-band CODEC S.C. filter  $f_{-3dB} = 4\text{kHz}$  &  $f_s = 256\text{kHz}$
- Anti-aliasing filter requirements:
  - Need at least 40dB attenuation of all out-of-band signals which can alias inband
  - Incur no phase-error from 0 to 4kHz
  - Gain error due to anti-aliasing filter  $\rightarrow 0$  to 4kHz  $< 0.05\text{dB}$
  - Allow  $\pm 30\%$  variation for anti-aliasing filter corner frequency (no tuning)

**Need to find minimum required filter order**
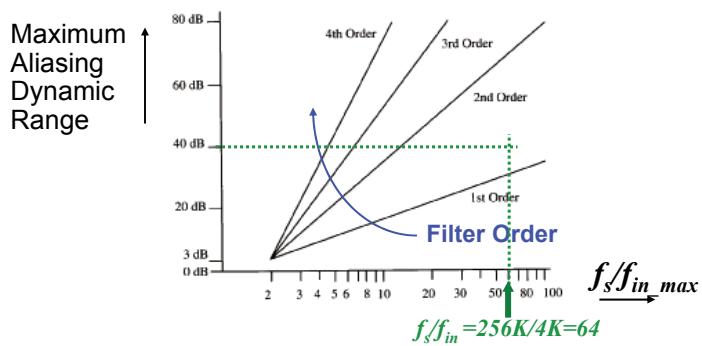
## Oversampling Ratio versus Anti-Aliasing Filter Order




\* Assumption  $\rightarrow$  anti-aliasing filter is Butterworth type

$\rightarrow$  2<sup>nd</sup> order Butterworth

$\rightarrow$  Need to find minimum corner frequency for mag. droop  $< 0.05\text{dB}$

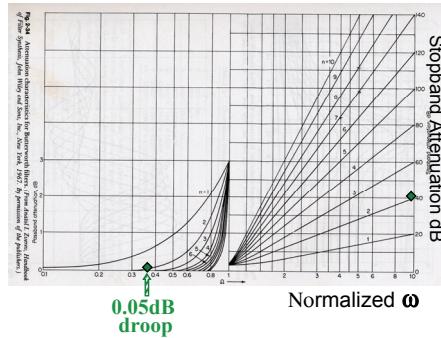
## Example : Anti-Aliasing Filter Specifications

- Normalized frequency for 0.05dB droop: need perform passband simulation  $\rightarrow 0.34 \rightarrow 4\text{kHz}/0.34=12\text{kHz}$
- Set anti-aliasing filter corner frequency for minimum corner frequency 12kHz  $\rightarrow$  Find nominal corner frequency:  $12\text{kHz}/0.7=17.1\text{kHz}$
- Check if attenuation requirement is satisfied for widest filter bandwidth  $\rightarrow 17.1 \times 1.3 = 22.28\text{kHz}$
- Find  $(f_s f_{sig})/f_{-3dB}^{\max}$   $\rightarrow 252/22.2=11.35 \rightarrow$  make sure enough attenuation
- Check phase-error within 4kHz bandwidth for min. filter bandwidth via simulation



From: Williams and Taylor, p. 2-37

## Example : Anti-Aliasing Filter

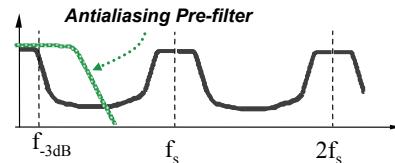


- Voice-band S.C. filter  $f_{-3dB}=4\text{kHz}$  &  $f_s=256\text{kHz}$
  - Anti-aliasing filter requirements:
    - Need 40dB attenuation at clock freq.
    - Incur no phase-error from 0 to 4kHz
    - Gain error 0 to 4kHz  $< 0.05\text{dB}$
    - Allow  $\pm 30\%$  variation for anti-aliasing corner frequency (no tuning)
- $\rightarrow$  2-pole Butterworth LPF with nominal corner freq. of 17kHz & no tuning (min.=12kHz & max.=22kHz corner frequency )

## Summary

- Sampling theorem  $\rightarrow f_s > 2f_{max\_Signal}$
- Signals at frequencies  $nf_S \pm f_{sig}$  fold back down to desired signal band,  $f_{sig}$ 
  - This is called aliasing & usually mandates use of anti-aliasing pre-filters
- Oversampling helps reduce required order for anti-aliasing filter
- S/H function shapes the frequency response with  $\sin x/x$  shape
  - Need to pay attention to droop in passband due to  $\sin x/x$
- If the above requirements are not met, CT signals can NOT be recovered from sampled-data networks without loss of information
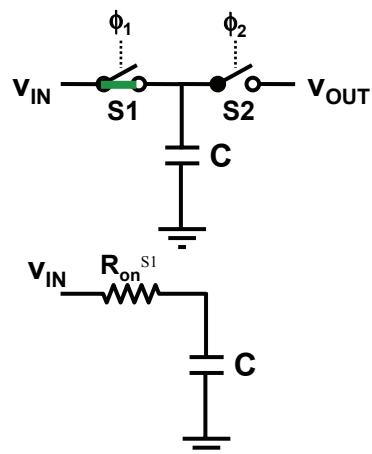
## Switched-Capacitor Network Noise

- During  $\phi_1$  high: Resistance of switch S1 ( $R_{on}^{S1}$ ) produces a noise voltage on C with variance  $kT/C$  (lecture 1- first order filter noise)



- The corresponding noise charge is:



$$Q^2 = C^2 V^2 = C^2 \cdot kT/C = kTC$$

- $\phi_1$  low: S1 open → This charge is sampled

# Switched-Capacitor Noise

- During  $\phi_2$  high: Resistance of switch S2 contributes to an uncorrelated noise charge on C at the end of  $\phi_2$ : with variance  $kT/C$
- Mean-squared noise charge transferred from  $v_{IN}$  to  $v_{OUT}$  per sample period is:

$$Q^2 = 2kTC$$

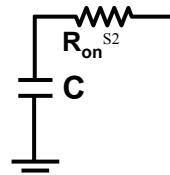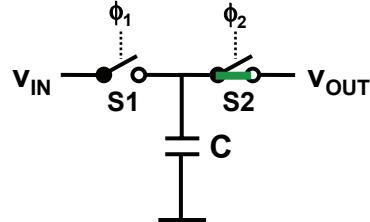

# Switched-Capacitor Noise

- The mean-squared noise current due to S1 and S2's  $kT/C$  noise is :

$$\text{Since } i = \frac{Q}{t} \text{ then } \bar{i^2} = (Qf_s)^2 = 2k_B T C f_s^2$$

- This noise is approximately white and distributed between 0 and  $f_s/2$  (noise spectra  $\rightarrow$  single sided by convention)
- The spectral density of the noise is found:

$$\frac{\bar{i^2}}{\Delta f} = \frac{2k_B T C f_s^2}{f_s/2} = 4k_B T C f_s$$


$$\text{Since } R_{EQ} = \frac{1}{f_s C} \text{ then:}$$

$$\boxed{\frac{\bar{i^2}}{\Delta f} = \frac{4k_B T}{R_{EQ}}}$$

**→S.C. resistor noise = a physical resistor noise with same value!**

## Periodic Noise Analysis SpectreRF

### Sampling Noise from SC S/H

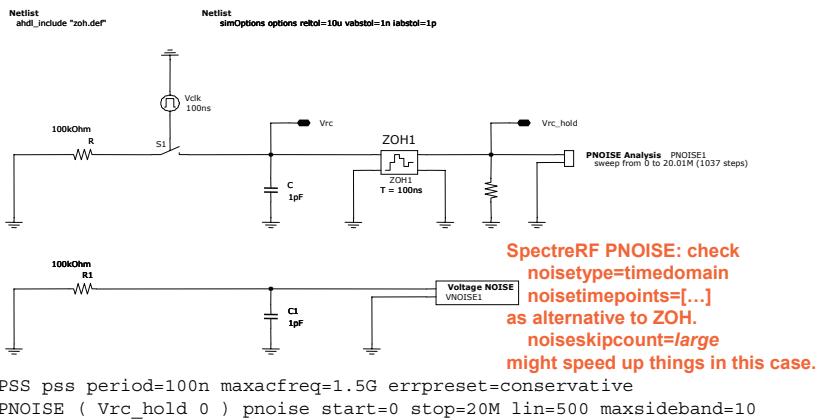


EECS 247 Lecture 9


Switched-Capacitor Filters

© 2008 H. K. Page 51

## Sampled Noise Spectrum

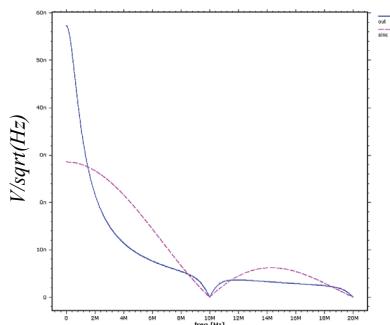

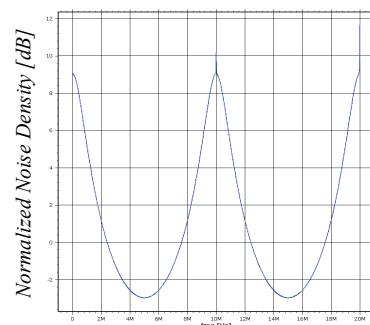Spectral density of sampled noise including  $\sin x/x$  effect




Noise spectral density with  $\sin x/x$  effect taken out

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 52


# Total Noise

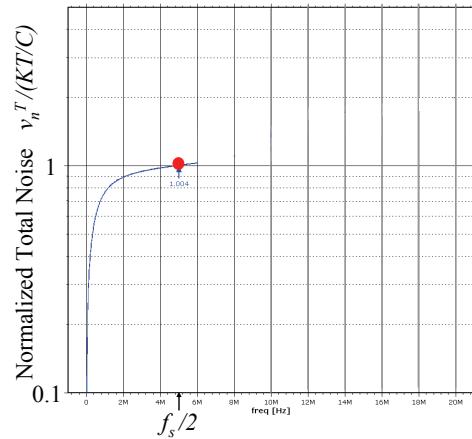

Sampled simulated noise  
in  $0 \dots f_s/2$ :  $62.2\mu\text{V}$  rms


(expect  $64\mu\text{V}$  for  $1\text{pF}$ )

## Switched-Capacitor Integrator

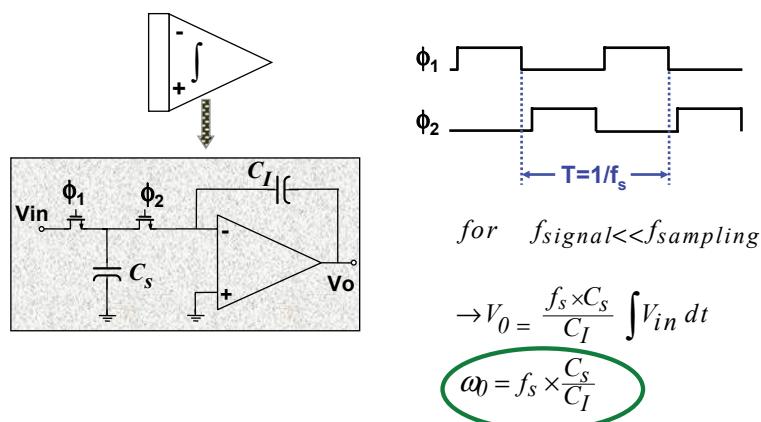

Main advantage: No tuning needed  
→ Critical frequency function of ratio of capacitors & clock freq.

## Switched-Capacitor Integrator

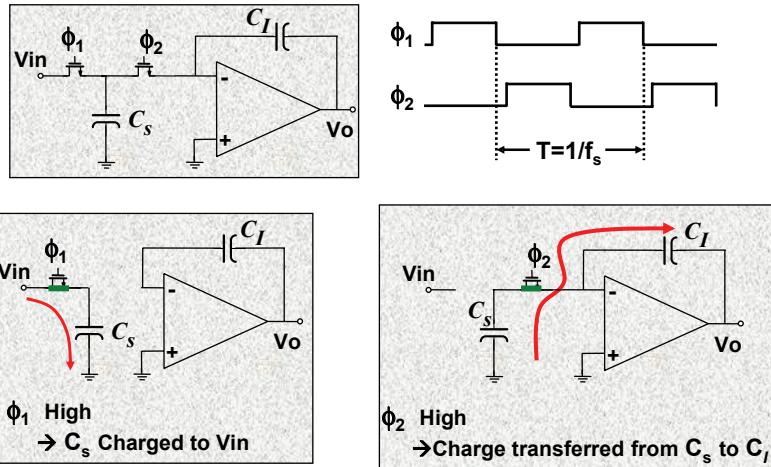

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 55

## Continuous-Time versus Discrete Time Analysis Approach

### Continuous-Time

- Write differential equation
- Laplace transform ( $F(s)$ )
- Let  $s=j\omega \rightarrow F(j\omega)$
- Plot  $|F(j\omega)|$ ,  $\text{phase}(F(j\omega))$

### Discrete-Time

- Write difference equation  $\rightarrow$  relates output sequence to input sequence
  - Use delay operator  $z^{-1}$  to transform the recursive realization to algebraic equations in  $z$  domain
  - Set  $z = e^{j\omega T}$
  - Plot mag./phase versus frequency
- $$V_o(z) = z^{-I} V_i(z) \dots \dots$$

EECS 247 Lecture 9

Switched-Capacitor Filters

© 2008 H. K. Page 56

## Discrete Time Design Flow

- Transforming the recursive realization to algebraic equation in  $z$  domain:
  - Use delay operator  $z$  :

$$\begin{aligned} nT_s &\dots \rightarrow I \\ [(n-1)T_s] &\dots \rightarrow z^{-1} \\ [(n-1/2)T_s] &\dots \rightarrow z^{-1/2} \\ [(n+1)T_s] &\dots \rightarrow z^{+1} \\ [(n+1/2)T_s] &\dots \rightarrow z^{+1/2} \end{aligned}$$

\* Note:  $z = e^{j\omega T_s} = \cos(\omega T_s) + j \sin(\omega T_s)$

### Switched-Capacitor Integrator Output Sampled on $\phi_1$

