

EE247

Lecture 4


- Active ladder type filters
 - For simplicity, will start with all pole ladder type filters
 - Convert to integrator based form- example shown
 - Then will attend to high order ladder type filters incorporating zeros
 - Implement the same 7th order elliptic filter in the form of ladder RLC with zeros
 - Find level of sensitivity to component mismatch
 - Compare with cascade of biquads
 - Convert to integrator based form utilizing SFG techniques
 - Effect of integrator non-Idealities on filter frequency characteristics

Summary Lecture 3

- Active Filters
 - Active biquads
 - Integrator-based filters
 - Signal flowgraph concept
 - First order integrator-based filter
 - Second order integrator-based filter & biquads
 - High order & high Q filters
 - Cascaded biquads & first order filters
 - Cascaded biquad sensitivity to component mismatch
 - Ladder type filters

RLC Ladder Filters


Example: 5th Order Lowpass Filter

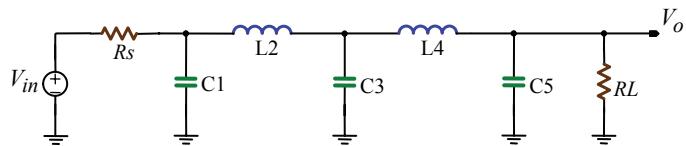

- Made of resistors, inductors, and capacitors
- Doubly terminated or singly terminated (with or w/o R_L)

Doubly terminated LC ladder filters → Lowest sensitivity to component mismatch

LC Ladder Filters

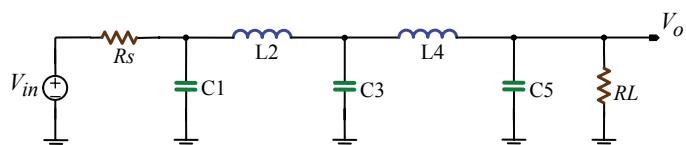

- First step in the design process is to find values for Ls and Cs based on specifications:
 - Filter graphs & tables found in:
 - A. Zverev, *Handbook of filter synthesis*, Wiley, 1967.
 - A. B. Williams and F. J. Taylor, *Electronic filter design*, 3rd edition, McGraw-Hill, 1995.
 - CAD tools
 - Matlab,
 - Agilent ADS (includes Filter package → does the job of the tables)
 - Spice

LC Ladder Filter Design Example

Design a LPF with maximally flat passband:

$$f_{-3dB} = 10\text{MHz}, f_{stop} = 20\text{MHz}$$

$$Rs > 27dB @ f_{stop}$$


- Maximally flat passband → Butterworth

- Find minimum filter order
- :
- Here standard graphs from filter books are used

$$f_{stop} / f_{-3dB} = 2$$

$$Rs > 27dB$$

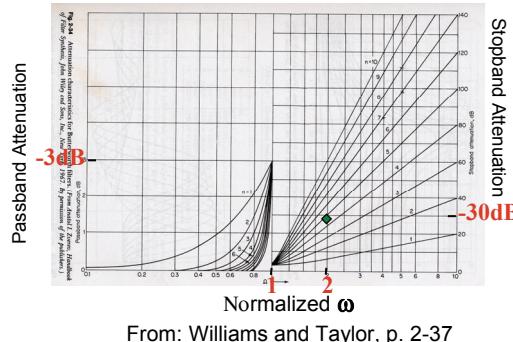Minimum Filter Order
⇒ 5th order Butterworth



LC Ladder Filter Design Example

Find values for L & C from Table: →

Note L & C values normalized to

$$\omega_{-3dB} = 1$$

Denormalization:

Multiply all L_{Norm} , C_{Norm} by:

$$L_r = R/\omega_{-3dB}$$

$$C_r = 1/(R\omega_{-3dB})$$

R is the value of the source and termination resistor
(choose both 1Ω for now)

Then: $L = L_r \times L_{Norm}$

$$C = C_r \times C_{Norm}$$

NORMALIZED FILTER DESIGN TABLES

11.3

TABLE 11-2 Butterworth LC Element Values (Continued)

n	R_n	C_1	L_2	C_2	L_4	C_4	L_8	C_8
5	1.0000	0.6180	1.6180	2.0000	1.6180	0.6180		
0.9000	0.4416	1.0265	1.9095	1.7562	1.5887			
0.8000	0.3667	0.8513	2.0925	1.3443	2.1087			
0.7000	0.3173	0.7513	2.2848	1.3399	2.1083			
0.6000	0.3860	0.6094	2.5998	1.1255	2.5524			
0.5000	0.6857	0.4955	3.0510	0.9237	3.1331			
0.4000	0.8374	0.3877	3.7350	0.7274	3.9648			
0.3000	0.9397	0.2967	4.6453	0.5367	4.7975			
0.2000	1.6077	0.1861	7.1849	0.3518	7.9345			
0.1000	3.1522	0.0912	14.0945	0.1727	15.7105			
Inf.	1.5451	1.6944	1.3820	0.8944	0.3090			
6	1.0000	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176	
1.1100	0.4245	1.1163	1.1357	2.3369	1.7443	1.6881		
1.2200	0.3445	1.1163	1.1357	2.3369	1.7443	1.6881		
1.4286	0.2072	1.2363	0.9567	2.4991	1.3464	2.0618		
1.6667	0.1732	1.4071	0.8011	2.8380	1.1431	2.5092		
2.0000	0.1412	1.6831	0.6546	3.3754	0.8343	3.9958		
2.5000	0.1125	2.0542	0.5149	4.1408	0.6745	4.9995		
3.3333	0.0816	2.6559	0.3788	5.4325	0.5517	5.2804		
5.0000	0.0535	3.9170	0.2486	8.0201	0.3628	7.9216		
10.0000	0.0263	7.7053	0.1232	15.7855	0.1788	15.7375		
Inf.	1.5529	1.7593	1.5329	1.2016	0.7579	1.5388		
7	1.0000	0.4985	1.8043	2.0912	1.8043	0.4985	0.4985	
0.9000	0.3985	0.7111	1.0493	1.4991	0.7149	1.7268	1.2961	
0.8000	0.3215	0.6057	1.5174	1.2777	2.3338	1.5461	1.6520	
0.7000	0.3571	0.5154	1.6883	1.0910	2.6177	1.3494	2.0277	
0.6000	0.4073	0.4354	1.9284	0.8770	3.0050	1.1505	2.4771	
0.5000	0.4756	0.3626	2.1731	0.7313	3.4043	1.3640	2.6640	
0.4000	0.5899	0.2782	2.7930	0.5917	4.3799	0.7542	3.9037	
0.3000	0.7745	0.2052	3.6700	0.4373	5.7619	0.5606	5.2583	
0.2000	1.1448	0.1356	5.4267	0.2871	8.5263	0.5362	9.0779	
0.1000	2.0576	0.0726	10.0417	0.1482	15.7822	0.2821	15.7340	
Inf.	1.5576	1.7988	1.6598	1.3972	1.0550	0.6560	0.2225	
n	$1/R_n$	L_1	C_2	L_3	C_4	L_5	C_6	L_8

From: Williams and Taylor, p. 11.3

LC Ladder Filter Design Example

NORMALIZED FILTER DESIGN TABLES

11.3

<i>n</i>	R_n	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.0000	0.6180	1.6180	2.0000	1.6180	0.6180	1.6180	2.0000
	0.9999	0.6178	1.6178	2.0000	1.6178	0.6178	1.6178	2.0000
	0.9999	0.6169	1.6169	2.0000	1.6169	0.6169	1.6169	2.0000
	0.9999	0.6159	1.6159	2.0000	1.6159	0.6159	1.6159	2.0000
	0.9999	0.5173	0.7513	2.2845	1.3326	2.1083		
	0.6000	0.5860	0.6094	2.5995	1.1255	2.5524		
	0.5000	0.5860	0.4910	3.0050	0.8720	3.1341		
	0.4000	0.8378	0.8377	3.7545	0.7274	3.6248		
	0.3000	1.0937	0.2848	4.8835	0.5367	5.3073		
	0.2000	1.6077	0.1861	7.1845	0.3518	7.9345		
	0.1000	3.1522	0.0912	14.0945	0.1727	15.7108		
	1.0000	0.6180	1.6180	2.0000	1.6180	0.6180	1.6180	2.0000
6	1.0000	0.5195	1.4142	1.9319	1.9319	1.4142	0.5176	
	1.1111	0.3890	1.0403	1.3217	2.0539	1.7445	1.3347	
	1.2500	0.2445	1.1163	1.1257	2.2389	1.5498	1.6881	
	1.4286	0.2072	1.2363	0.9567	2.4991	1.3464	2.0618	
	1.6667	0.1778	1.4071	0.8842	2.3676	1.1311	1.9162	
	2.0000	0.1112	1.4674	0.6542	2.3687	0.9423	3.0998	
	2.5000	0.1108	2.0275	0.5139	4.1408	0.7450	3.9305	
	3.3333	0.0816	2.6559	0.3788	5.4325	0.5517	5.2804	
	5.0000	0.0535	3.9170	0.2484	8.0281	0.3628	7.9216	
	10.0000	0.0268	7.9049	0.1335	16.8222	0.1823	15.7480	
	Inf.	1.5529	1.7593	1.5529	1.2016	0.7579	0.2585	
<i>n</i>	$1/R_n$	L_1	C_2	L_3	C_4	L_5	C_6	L_7

From: Williams and Taylor, p. 11.3

Find values for L & C from Table:

Normalized values:

$$C_{1\text{Norm}} = C_{5\text{Norm}} = 0.618$$

$$C_{3\text{Norm}} = 2.0$$

$$L_{2\text{Norm}} = L_{4\text{Norm}} = 1.618$$

Denormalization:

$$\text{Since } \omega_{-3dB} = 2\pi \times 10\text{MHz}$$

$$L_r = R/\omega_{-3dB} = 15.9 \text{ nH}$$

$$C_r = 1/(R\omega_{-3dB}) = 15.9 \text{ nF}$$

$$R = 1$$

$$\Rightarrow C_1 = C_5 = 9.836 \text{ nF}, C_3 = 31.83 \text{ nF}$$


$$\Rightarrow L_2 = L_4 = 25.75 \text{ nH}$$

EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 7

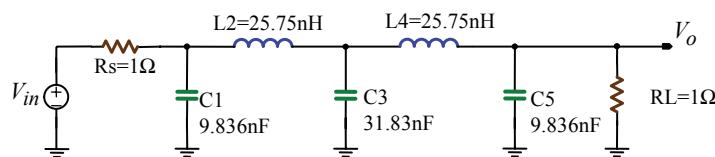Last Lecture: Example: 5th Order Butterworth Filter




Specifications:

$$f_{-3dB} = 10\text{MHz}$$

$$f_{stop} = 20\text{MHz}$$

$$R_s > 27\text{dB}$$

Used filter tables to obtain
 L_s & C_s

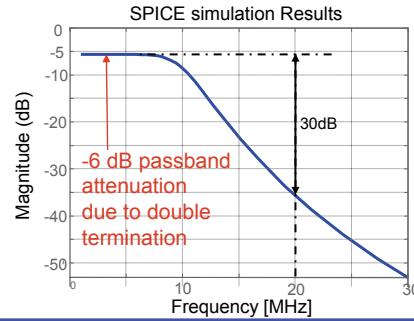


EECS 247

Lecture 4: Active Filters


© 2009 H.K. Page 8

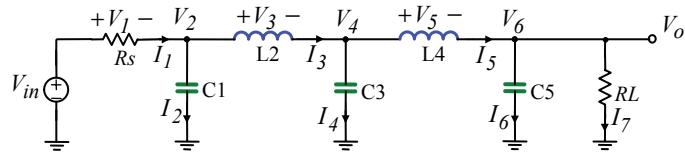Low-Pass RLC Ladder Filter Conversion to Integrator Based Active Filter



- To convert RLC ladder prototype to integrator based filer:
 - ❑ Use Signal Flowgraph technique
 - ✓ Name currents and voltages for all components
 - ✓ Use KCL & KVL to derive equations
 - ✓ Make sure reactive elements expressed as 1/s term
→ $V(C) = f(I)$ & $I(L) = f(V)$
 - ✓ Use state-space description to derive the SFG
 - ✓ Modify & simplify the SFG for implementation with integrators e.g. convert all current nodes to voltage

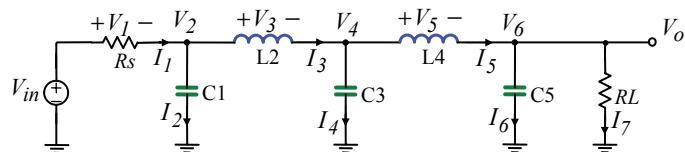Low-Pass RLC Ladder Filter Conversion to Integrator Based Active Filter



- Use KCL & KVL to derive equations:

$$V_1 = V_{in} - V_2 \quad , \quad V_2 = \frac{I_2}{sC_1} \quad , \quad V_3 = V_2 - V_4$$


$$V_4 = \frac{I_4}{sC_3} \quad , \quad V_5 = V_4 - V_6 \quad , \quad V_6 = \frac{I_6}{sC_5} \quad , \quad V_o = V_6$$

$$I_1 = \frac{V_1}{R_s} \quad , \quad I_2 = I_1 - I_3 \quad , \quad I_3 = \frac{V_3}{sL_2}$$

$$I_4 = I_3 - I_5 \quad , \quad I_5 = \frac{V_5}{sL_4} \quad , \quad I_6 = I_5 - I_7 \quad , \quad I_7 = \frac{V_6}{R_L}$$

Low-Pass RLC Ladder Filter Signal Flowgraph

$$\begin{aligned}
 V_I &= V_{in} - V_2 \quad , \quad V_2 = \frac{I_2}{sC_1} \quad , \quad V_3 = V_2 - V_4 \\
 V_4 &= \frac{I_4}{sC_3} \quad , \quad V_5 = V_4 - V_6 \quad , \quad V_6 = \frac{I_6}{sC_5} \quad V_o = V_6 \\
 I_1 &= \frac{V_I}{R_s} \quad , \quad I_2 = I_1 - I_3 \quad , \quad I_3 = \frac{V_3}{sL_2} \\
 I_4 &= I_3 - I_5 \quad , \quad I_5 = \frac{V_5}{sL_4} \quad , \quad I_6 = I_5 - I_7 \quad , \quad I_7 = \frac{V_6}{R_L}
 \end{aligned}$$

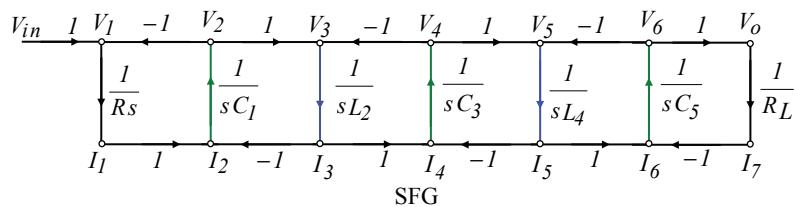


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 11

Low-Pass RLC Ladder Filter Normalize

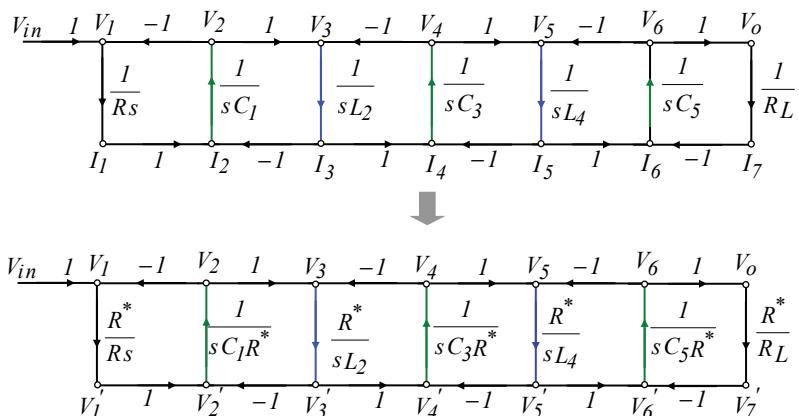


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 12

Low-Pass RLC Ladder Filter Synthesize

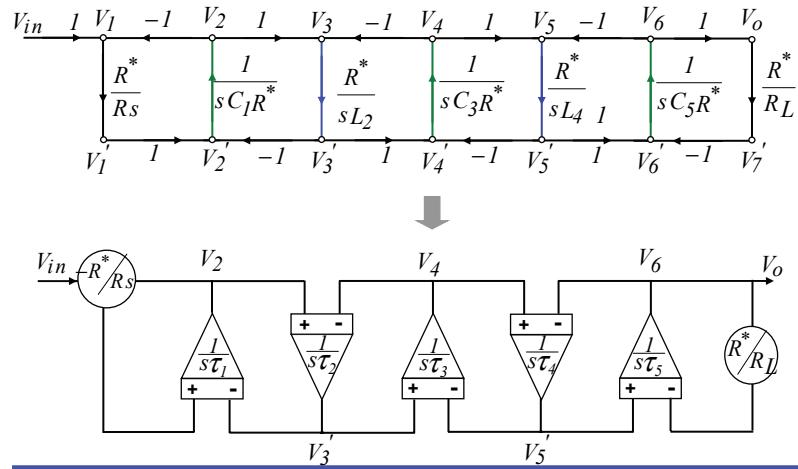


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 13

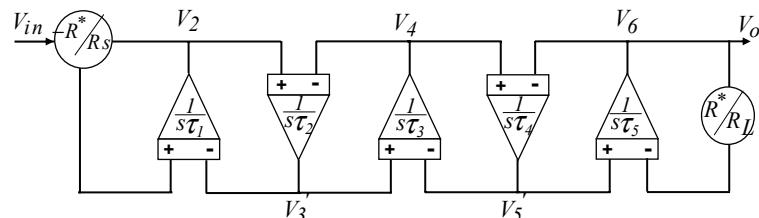Low-Pass RLC Ladder Filter Integrator Based Implementation



$$\tau_1 = C_1 R^*, \quad \tau_2 = \frac{L_2}{R^*} = C_2 R^*, \quad \tau_3 = C_3 R^*, \quad \tau_4 = \frac{L_4}{R^*} = C_4 R^*, \quad \tau_5 = C_5 R^*$$

Main building block: Integrator
Let us start to build the filter with RC& Opamp type integrator


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 14


Opamp-RC Integrator

Single-Ended

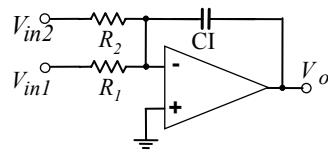

$$V_o = -V_{in1} \times \frac{1}{sR_1CI} - V_{in2} \times \frac{1}{sR_2CI}$$

Differential

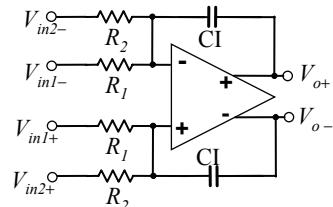


$$V_{o+} - V_{o-} = (V_{in1+} - V_{in1-}) \times \frac{1}{sR_1CI} + (V_{in2+} - V_{in2-}) \times \frac{1}{sR_2CI}$$

Note: Implementation with single-ended integrator requires extra circuitry for sign inversion whereas in differential case both signal polarities are available


Differential Integrator Based LP Ladder Filter

Synthesize

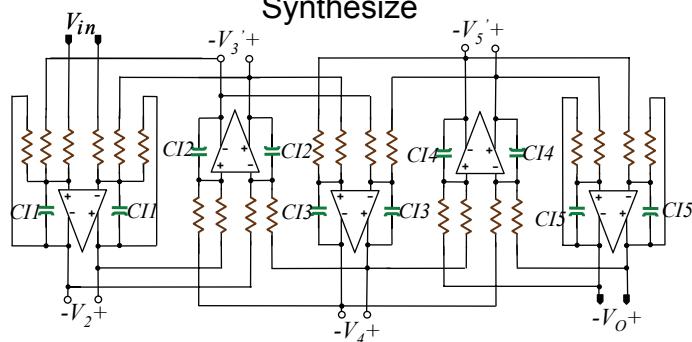

- First iteration:
 - ❑ All resistors are chosen=1Ω
 - ❑ Values for $\tau_x = R_x C I_x$ found from RLC analysis
 - ❑ Capacitors: $CII = CI5 = 9.836nF$, $CII = CI4 = 25.45nF$, $CII = CI3 = 31.83nF$

Simulated Magnitude Response

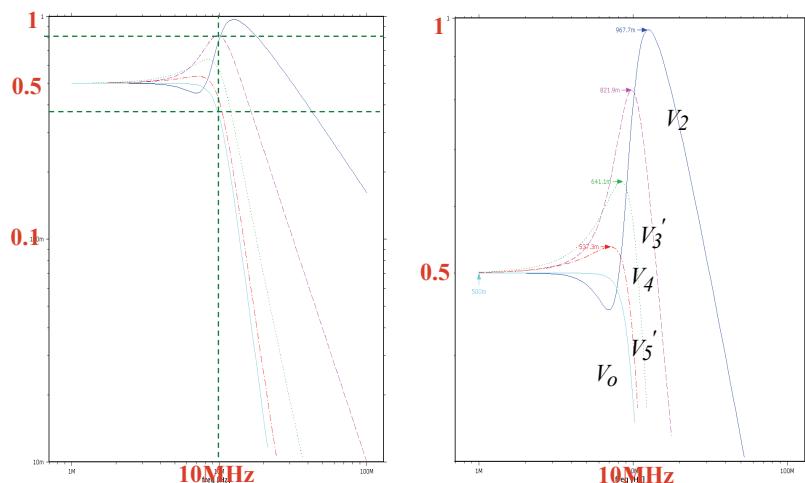

EECS 247


Lecture 4: Active Filters

© 2009 H.K. Page 17

Scale Node Voltages

Scale V_o by factor “s”

To maximize dynamic range
→ scale node voltages

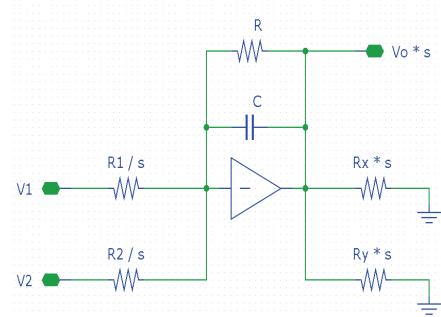


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 18

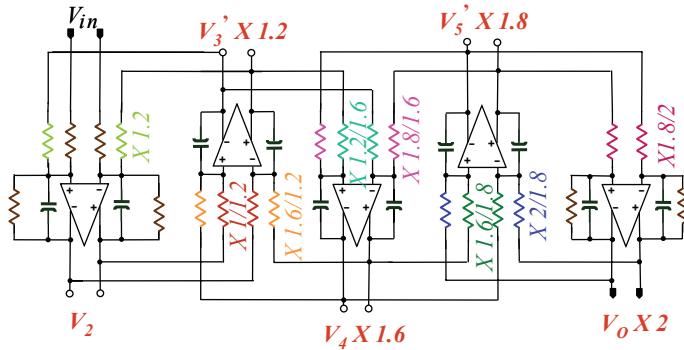
Differential Integrator Based LP Ladder Filter Node Scaling




- Second iteration:
 - ❑ Nodes scaled, note output node x2
 - ❑ Resistor values scaled according to scaling of nodes
 - ❑ Capacitors the same : $C1=C5=9.836nF$, $C2=C4=25.45nF$, $C3=31.83nF$

Maximizing Signal Handling by Node Voltage Scaling


Before Node Scaling

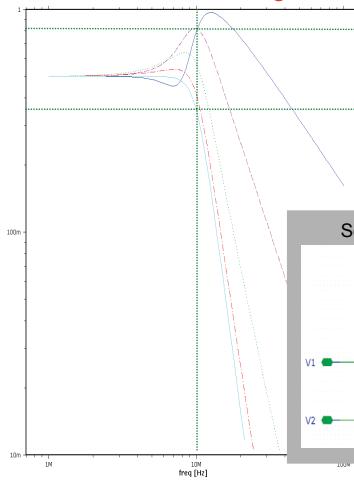


After Node Scaling

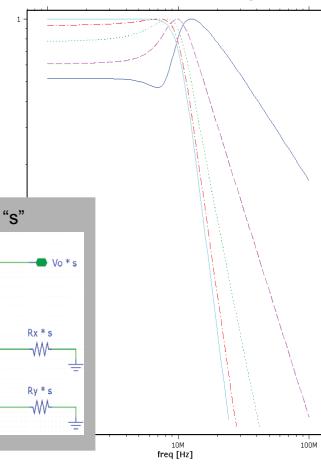

Scale V_o by factor "s"

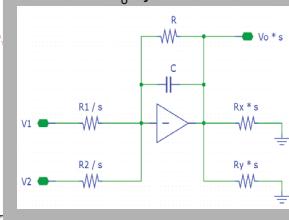

Filter Noise

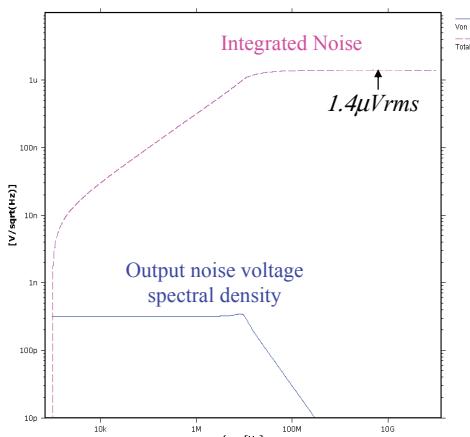

Total noise @ the output:
1.4 $\mu\text{V rms}$
(noiseless opamps)


That's excellent, but:

- Capacitors too large for integration
→ Unrealistically large Si area
- Resistors too small
→ high power dissipation

Typical applications allow higher noise, assuming tolerable noise in the order of 140 $\mu\text{V rms}$...


Scale to Meet Noise Target

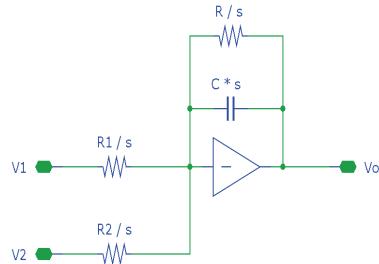Scale capacitors and resistors to meet noise objective




$$s = 10^{-4} \rightarrow (V_{n1}/V_{n2})^2$$

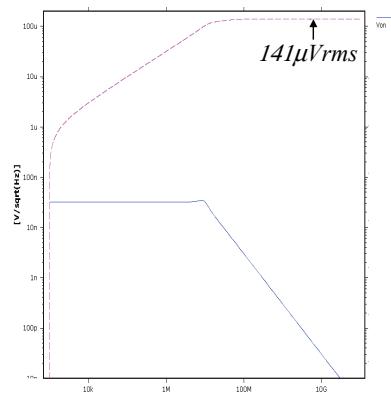Noise after scaling: 141 $\mu\text{V rms}$ (assuming noiseless opamps)





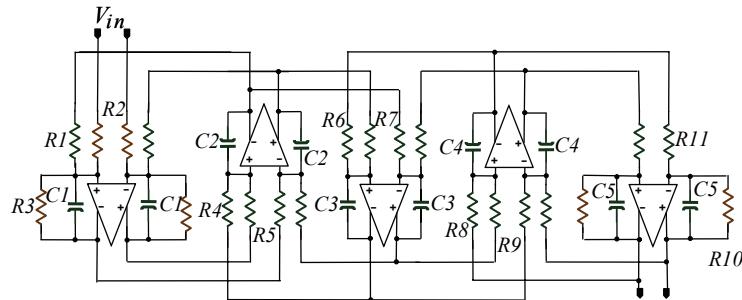Differential Integrator Based LP Ladder Filter Final Design



- Final iteration:
 - Based on scaled nodes and noise considerations
 - Capacitors: $C_1 = C_5 = 0.9836\text{pF}$, $C_2 = C_4 = 2.545\text{pF}$, $C_3 = 3.183\text{pF}$
 - Resistors: $R_1 = 11.77K$, $R_2 = 9.677K$, $R_3 = 10K$, $R_4 = 12.82K$, $R_5 = 8.493K$,
 $R_6 = 11.93K$, $R_7 = 7.8K$, $R_8 = 10.75K$, $R_9 = 8.381K$, $R_{11} = 10K$, $R_{10} = 9.306K$

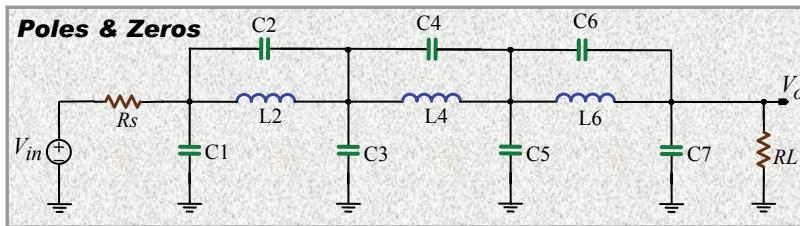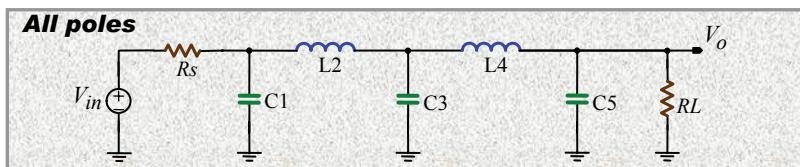
RLC Ladder Filters Including Transmission Zeros



RLC Ladder Filter Design Example

- Design a baseband filter for CDMA IS95 cellular phone receive path with the following specs.
 - Filter frequency mask shown on the next page
 - Allow enough margin for manufacturing variations
 - Assume overall tolerable pass-band magnitude variation of 1.8dB
 - Assume the -3dB frequency can vary by +/-8% due to manufacturing tolerances & circuit inaccuracies
 - Assume any phase impairment can be compensated in the digital domain
- * Note this is the same example as for cascade of biquad while the specifications are given closer to a real product case

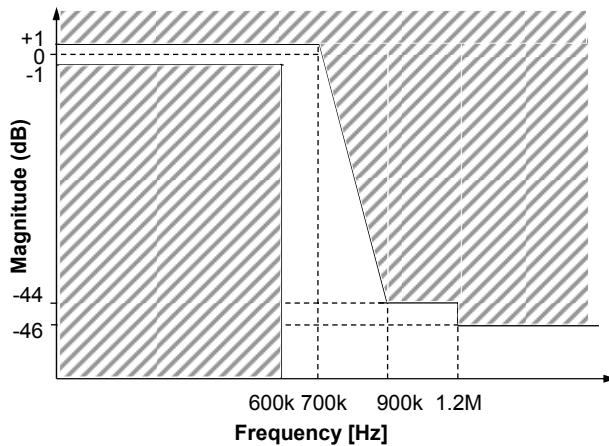RLC Ladder Filter Design Example CDMA IS95 Receive Filter Frequency Mask




RLC Ladder Filter Design

Example: CDMA IS95 Receive Filter

- Since phase impairment can be corrected for, use filter type with max. roll-off slope/pole
→ Filter type → Elliptic
- Design filter freq. response to fall well within the freq. mask
 - Allow margin for component variations & mismatches
- For the passband ripple, allow enough margin for ripple change due to component & temperature variations
 - Design nominal passband ripple of 0.2dB
- For stopband rejection add a few dB margin $44+5=49$ dB
- Final design specifications:
 - $f_{pass} = 650 \text{ kHz}$ $R_{pass} = 0.2 \text{ dB}$
 - $f_{stop} = 750 \text{ kHz}$ $R_{stop} = 49 \text{ dB}$
- Use Matlab or ADS or filter tables to decide the min. order for the filter (same as cascaded biquad example)
 - 7th Order Elliptic

RLC Low-Pass Ladder Filter Design

Example: CDMA IS95 Receive Filter

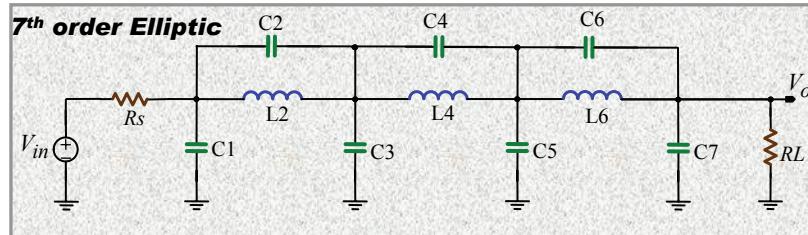

- Use filter tables & charts to determine LC values

RLC Ladder Filter Design Example: CDMA IS95 Receive Filter


- Specifications
 - $f_{pass} = 650 \text{ kHz}$ $R_{pass} = 0.2 \text{ dB}$
 - $f_{stop} = 750 \text{ kHz}$ $R_{stop} = 49 \text{ dB}$
 - Use filter tables to determine LC values
 - Table from: A. Zverev, *Handbook of filter synthesis*, Wiley, 1967
 - Elliptic filters tabulated wrt “reflection coefficient ρ ”

$$R_{pass} = -10 \times \log(1 - \rho^2)$$

- Since $R_{pass} = 0.2 dB \rightarrow \rho = 20\%$
 - Use table accordingly

RLC Ladder Filter Design Example: CDMA IS95 Receive Filter

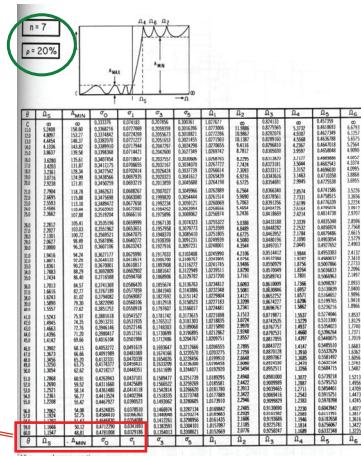- Table from Zverev book page #281 & 282:
 - Since our spec. is $A_{min}=44dB$ add 5dB margin & design for $A_{min}=49dB$



59.0	1.1666	50.12	0.4712290	0
60.0	1.1547	48.81	0.4781008	0
θ	Ω_S	A_{MIN}	σ_o	

- Table from Zverev page #281 & 282:

- Normalized component values:

$$C1=1.17677$$

$$C2=0.19393$$

$$L2=1.19467$$

$$C3=1.51134$$

$$C4=1.01098$$

$$L4=0.72398$$

$$C5=1.27776$$


$$C6=0.71211$$

$$L6=0.80165$$

$$C7=0.83597$$


θ	C_1	C_2	L_2	C_3	C_4	L_4	C_5	C_6	L_6	C_7
0	1.335	0.00000	1.389	2.240	0.00000	1.515	2.240	0.00000	1.389	1.315
1.0	1.30644	0.09503	1.38116	2.21490	0.02330	1.48669	2.20558	0.01537	1.36926	1.31941
2.0	1.28062	0.08753	1.38027	2.19750	0.03770	1.47767	2.19558	0.02049	1.35826	1.31485
3.0	1.28982	0.08704	1.38104	2.20943	0.03764	1.47534	2.19192	0.02795	1.38161	1.31923
4.0	1.28744	0.08681	1.37982	2.19959	0.03792	1.46807	2.18424	0.02667	1.35731	1.30975
5.0	1.28490	0.08674	1.37943	2.19959	0.03792	1.46807	2.18424	0.02667	1.35731	1.30975
6.0	1.32577	0.01072	1.37712	2.18863	0.04973	1.45484	2.16721	0.04999	1.34775	1.30000
7.0	1.32457	0.02113	1.37564	2.17999	0.05627	1.44798	2.15786	0.05959	1.34249	1.29774
8.0	1.32400	0.01862	1.37406	2.17773	0.06323	1.43886	2.14796	0.04551	1.33891	1.29321
9.0	1.32194	0.01750	1.37231	2.17509	0.06323	1.43886	2.14796	0.04551	1.33891	1.29321
10.0	1.32051	0.01689	1.37061	2.17509	0.07848	1.42107	2.13749	0.05527	1.32478	1.28336
11.0	1.31900	0.01866	1.36871	2.14852	0.08677	1.41149	2.11493	0.06113	1.31823	1.27803
12.0	1.31784	0.02050	1.36740	2.13964	0.08677	1.40140	2.10283	0.06732	1.31137	1.27244
13.0	1.31574	0.02250	1.36523	2.10766	0.11443	1.38093	2.07699	0.08071	1.29668	1.26458
14.0	1.31398	0.02457	1.36505	2.10597	0.12461	1.38674	2.06327	0.08792	1.28882	1.25405
15.0	1.31215	0.02674	1.36505	2.10597	0.12461	1.38674	2.06327	0.08792	1.28882	1.25405
16.0	1.31027	0.03067	1.36490	2.10597	0.12461	1.38674	2.06327	0.08792	1.28882	1.25405
17.0	1.30822	0.03138	1.36440	2.08919	0.14648	1.34473	2.04247	0.10443	1.27806	1.24748
18.0	1.30612	0.03386	1.35281	2.07790	0.15820	1.33207	2.01890	0.11174	1.26338	1.23322
19.0	1.30493	0.03545	1.35017	2.06800	0.16890	1.31898	2.00395	0.12044	1.25427	1.22527
20.0	1.30387	0.03614	1.34843	2.05813	0.18325	1.30563	1.98952	0.13041	1.24541	1.20394
21.0	1.29930	0.04196	1.34439	2.04165	0.19663	1.29156	1.96980	0.13905	1.23407	1.20988
22.0	1.29684	0.04488	1.34136	2.02878	0.21059	1.27772	1.95241	0.14899	1.22485	1.20154
23.0	1.29444	0.04780	1.33904	2.01817	0.24036	1.24230	1.91669	0.15938	1.21440	1.19291
24.0	1.29144	0.05099	1.33404	2.00187	0.25621	1.23173	1.89717	0.18146	1.19250	1.17479
25.0	1.28888	0.05438	1.33156	1.98782	0.25621	1.23173	1.89717	0.18146	1.19250	1.17479
26.0	1.28603	0.05780	1.32860	1.97738	0.27274	1.21576	1.87776	0.19323	1.18106	1.16529
27.0	1.28399	0.06131	1.32620	1.96785	0.29557	1.19876	1.85796	0.20323	1.16928	1.15549
28.0	1.28201	0.06504	1.32662	1.94336	0.30794	1.18263	1.83747	0.21832	1.15710	1.14569
29.0	1.27983	0.06887	1.31671	1.92777	0.32668	1.16545	1.81659	0.23168	1.14471	1.13499
30.0	1.27935	0.07041	1.31620	1.91719	0.34645	1.14795	1.79524	0.24560	1.13197	1.12428
31.0	1.27704	0.07696	1.31269	1.89542	0.36660	1.13193	1.77424	0.26177	1.11938	1.11348
32.0	1.27662	0.08123	1.30416	1.87867	0.38787	1.11174	1.75113	0.27529	1.10532	1.10192
33.0	1.27627	0.08566	1.29961	1.86154	0.41006	1.09308	1.73837	0.29110	1.09151	1.09020
34.0	1.27592	0.08843	1.29807	1.84432	0.43243	1.07443	1.72650	0.30729	1.08170	1.08079
35.0	1.27529	0.09504	1.29007	1.82814	0.45146	1.05467	1.68151	0.32484	1.06285	1.06296
36.0	1.27125	0.09999	1.28532	1.80786	0.48277	1.04393	1.65741	0.34285	1.04799	1.05331
37.0	1.27074	0.10153	1.28200	1.79870	0.50926	1.04184	1.63787	0.36167	1.02378	1.04032
38.0	1.27001	0.10313	1.27962	1.78957	0.53675	1.03703	1.61796	0.38049	1.01727	1.02079
39.0	1.26932	0.10504	1.27662	1.78036	0.56424	1.03213	1.60252	0.40196	1.01311	1.01327
40.0	1.26862	0.10704	1.27384	1.77179	0.59173	1.02723	1.58752	0.42356	0.98503	0.99952
41.0	1.26714	0.10904	1.27126	1.76326	0.61924	1.02233	1.57252	0.44616	0.96839	0.98475
42.0	1.26662	0.11213	1.26813	1.75467	0.64671	1.01743	1.55752	0.46846	0.95207	0.97027
43.0	1.26627	0.11523	1.26556	1.74608	0.67418	1.01253	1.54252	0.49036	0.93640	0.95470
44.0	1.26592	0.11833	1.26307	1.73750	0.70165	1.00763	1.52752	0.51226	0.91626	0.93907
45.0	1.26559	0.12143	1.26057	1.72882	0.72912	1.00273	1.51252	0.53416	0.89627	0.92222
46.0	1.26529	0.12454	1.25807	1.72024	0.75659	0.99783	1.49752	0.55596	0.87602	0.90554
47.0	1.26499	0.12764	1.25556	1.71166	0.78406	0.99293	1.48252	0.57786	0.85574	0.88654
48.0	1.26464	0.13074	1.25304	1.70308	0.81153	0.98703	1.46752	0.59976	0.83507	0.86861
49.0	1.26430	0.13384	1.25052	1.69450	0.83891	0.98113	1.45252	0.62167	0.81443	0.85072
50.0	1.26392	0.13694	1.24797	1.68592	0.86639	0.97523	1.43752	0.64356	0.79379	0.83272
51.0	1.26362	0.13997	1.24544	1.67734	0.89387	0.96933	1.42252	0.66546	0.77279	0.81471
52.0	1.26332	0.14307	1.24291	1.66874	0.92135	0.96343	1.40752	0.68736	0.75179	0.79674
53.0	1.26302	0.14614	1.23934	1.65992	0.94878	0.95753	1.39252	0.70926	0.73076	0.77874
54.0	1.26271	0.14921	1.23581	1.65130	0.97625	0.95163	1.37752	0.73115	0.70973	0.76074
55.0	1.26240	0.15228	1.23228	1.64268	1.00372	0.94572	1.36252	0.75305	0.68871	0.74272
56.0	1.26209	0.16141	1.22834	1.63302	0.81628	0.89020	1.34365	0.57779	0.87962	0.80654
57.0	1.26160	0.16902	1.21810	1.58118	0.86054	0.97570	1.36518	0.60854	0.86072	0.88611
58.0	1.26119	0.17696	1.21058	1.55884	0.90754	0.77208	1.33637	0.64106	0.84143	0.87222
59.0	1.26084	0.18342	1.20305	1.53614	0.94494	0.82298	1.31708	0.67299	0.82299	0.85397
60.0	1.11767	0.19393	1.19467	1.51134	1.01098	0.72398	1.27756	0.71211	0.81035	0.83957

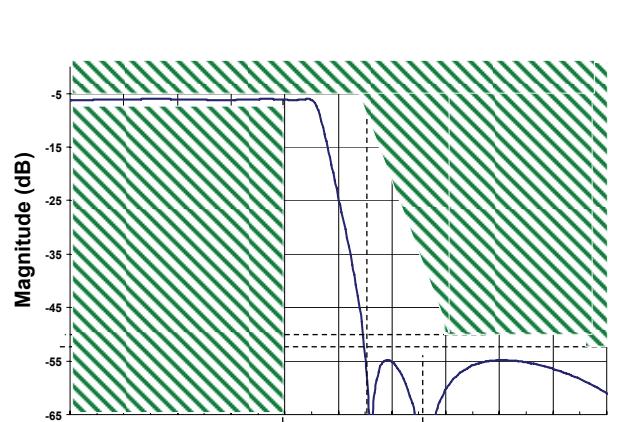- Component values denormalized
- Frequency response simulated
- Frequency mask superimposed
- Frequency response well within spec.



Frequency Response Passband Detail

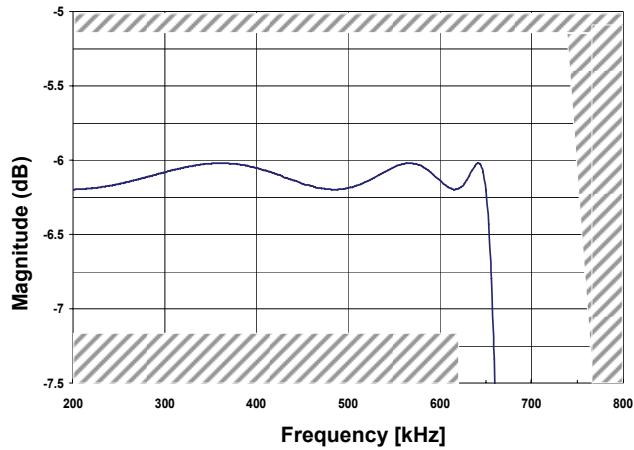- Passband well within spec.
- Make sure enough margin is allowed for variations due to process & temperature




RLC Ladder Filter Sensitivity

- The design has the same specifications as the previous example implemented with cascaded biquads
- To compare the sensitivity of RLC ladder versus cascaded-biquads:
 - Changed all L_s & C_s one by one by 2% in order to change the pole/zeros by 1% (similar test as for cascaded biquad)
 - Found frequency response → most sensitive to L_4 variations
 - Note that by varying L_4 both poles & zeros are varied


RCL Ladder Filter Sensitivity

Component mismatch in RLC filter:

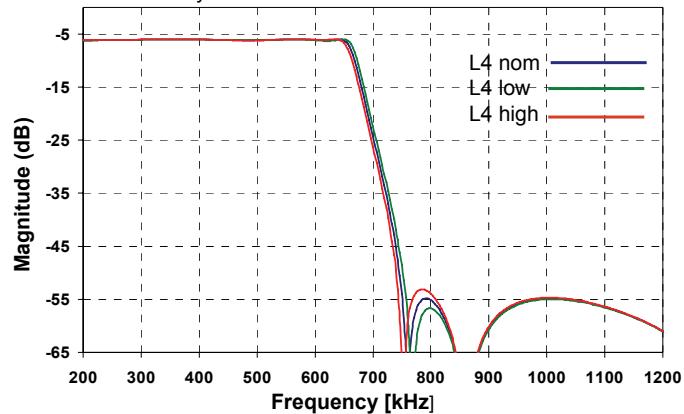- Increase L4 from its nominal value by 2%
- Decrease L4 by 2%




RCL Ladder Filter Sensitivity

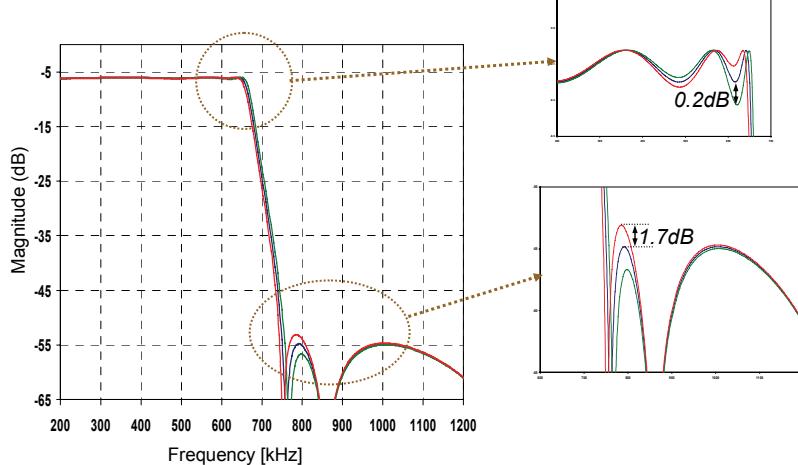

Sensitivity of Cascade of Biquads

Component mismatch in Biquad 4 (highest Q pole):

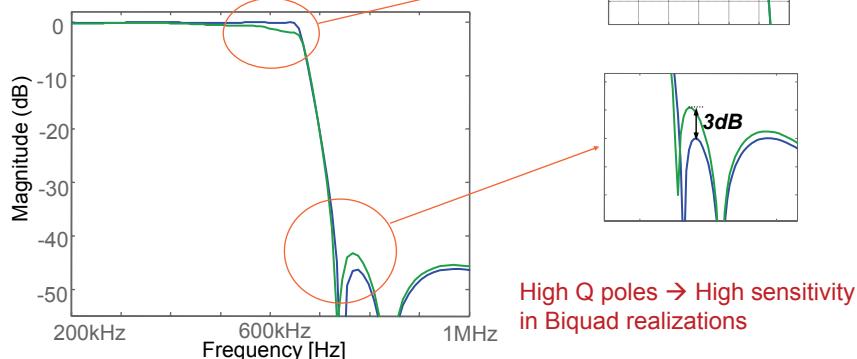- Increase ω_{p4} by 1%
- Decrease ω_{z4} by 1%



Sensitivity Comparison for Cascaded-Biquads versus RLC Ladder


- 7th Order elliptic filter
 - 1% change in pole & zero pair

	<u>Cascaded Biquad</u>	<u>RLC Ladder</u>
Passband deviation	2.2dB (29%)	0.2dB (2%)
Stopband deviation	3dB (40%)	1.7dB (21%)

Doubly terminated LC ladder filters \Rightarrow Significantly lower sensitivity compared to cascaded-biquads particularly within the passband

RLC Ladder Filter Design

Example: CDMA IS95 Receive Filter

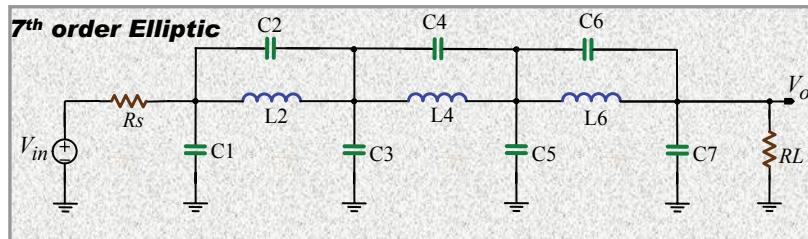


- Previously learned to design integrator based ladder filters without transmission zeros
→ Question:
 - How do we implement the transmission zeros in the integrator-based version?
 - Preferred method → no extra power dissipation → no extra active elements

Integrator Based Ladder Filters

How Do to Implement Transmission zeros?

- Use KCL & KVL to derive :

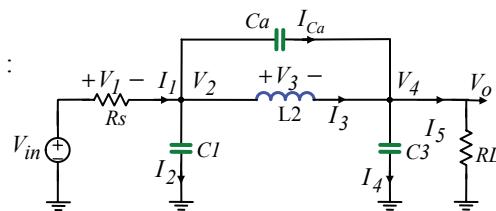


$$I_2 = I_1 - I_3 - I_{C_a}, \quad I_{C_a} = (V_2 - V_4)sC_a, \quad V_2 = \frac{I_2}{sC_I}$$

$$\text{Substituting for } I_2 \rightarrow V_2 = \frac{I_1 - I_3 - I_{C_a}}{sC_I}$$

$$\text{Substituting for } I_{C_a} \text{ and rearranging :} \quad V_2 = \frac{I_1 - I_3}{s(C_I + C_a)} + V_4 \times \frac{C_a}{C_I + C_a}$$

Integrator Based Ladder Filters

How Do to Implement Transmission zeros?

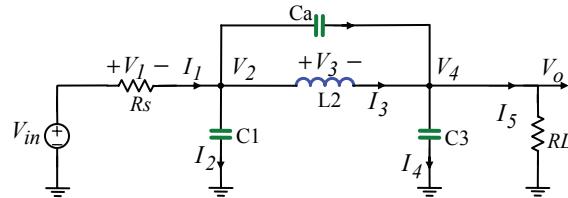

- Use KCL & KVL to derive :

$$V_2 = \frac{I_1 - I_3}{s(C_1 + C_a)} + V_4 \times \frac{C_a}{C_1 + C_a}$$


*Frequency independent constants
Can be substituted by:*

$$V_4 = \frac{I_3 - I_5}{s(C_3 + C_a)} + V_2 \times \frac{C_a}{C_3 + C_a}$$

Voltage-Controlled Voltage Source

Integrator Based Ladder Filters



Transmission zeros

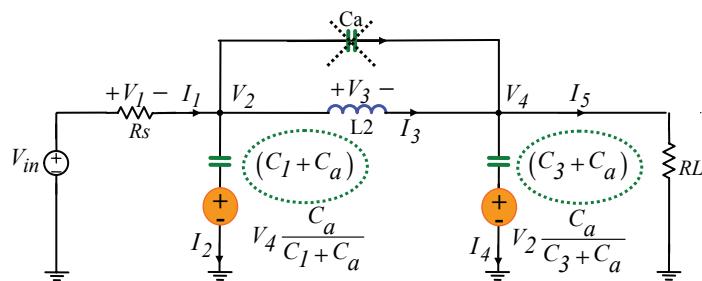



- Replace *shunt capacitors* with *voltage controlled voltage sources*:

$$\left. \begin{aligned} V_2 &= \frac{I_1 - I_3}{s(C_1 + C_a)} + V_4 \frac{C_a}{C_1 + C_a} \\ V_4 &= \frac{I_3 - I_5}{s(C_3 + C_a)} + V_2 \frac{C_a}{C_3 + C_a} \end{aligned} \right\} \text{Exact same expressions as with } C_a \text{ present}$$

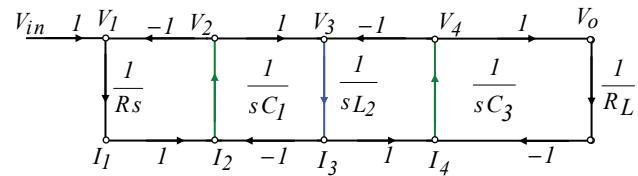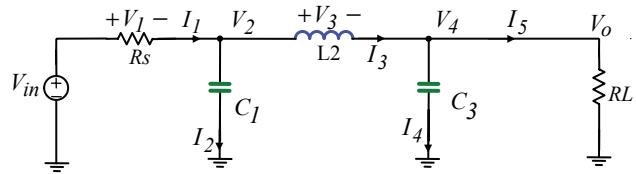3rd Order Lowpass Filter All Poles & No Zeros



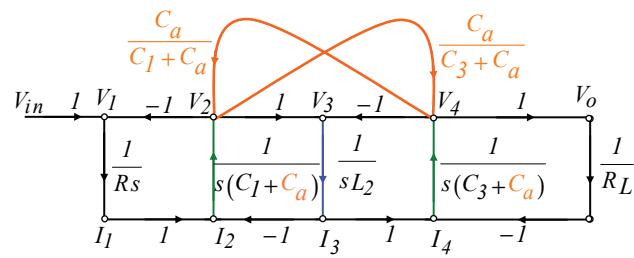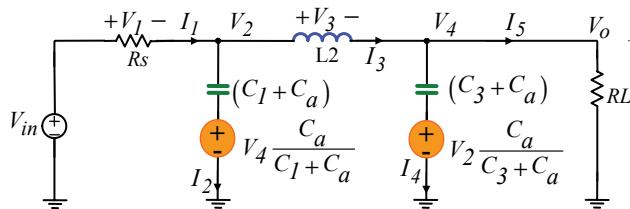
Implementation of Zeros in Active Ladder Filters Without Use of Active Elements



Integrator Based Ladder Filters

Higher Order Transmission zeros

Convert zero generating Cs in C loops to voltage-controlled voltage sources


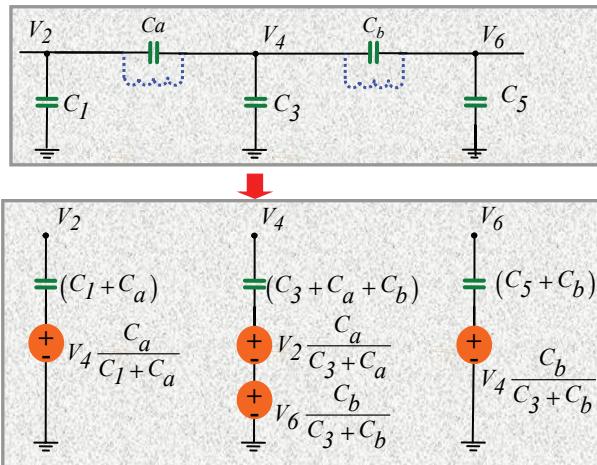


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 45

Higher Order Transmission zeros

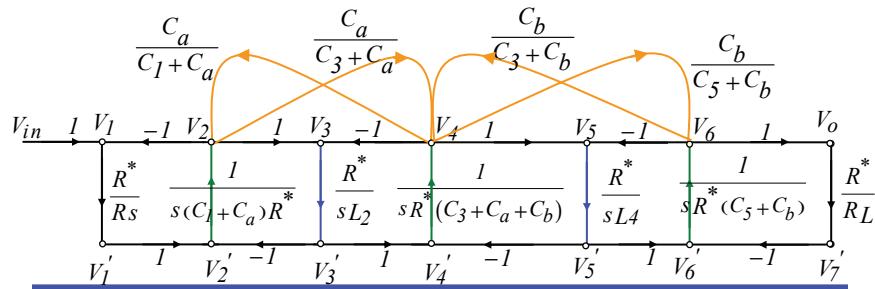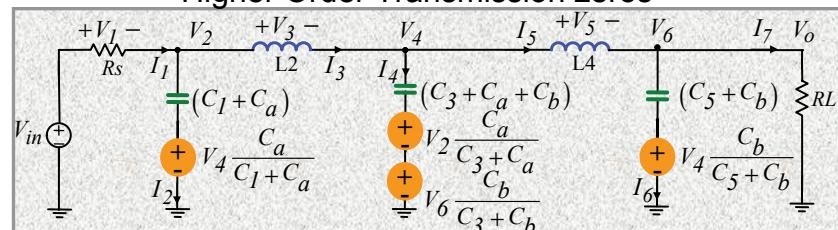


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 46

Example: 5th Order Chebyshev II Filter

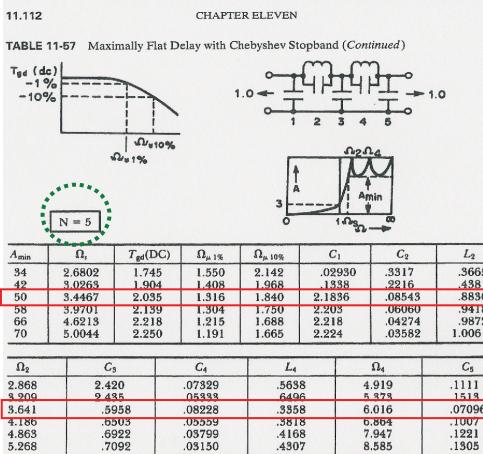

- 5th order Chebyshev II

- Table from: Williams & Taylor book, p. 11.112


- 50dB stopband attenuation

- $f_{-3\text{dB}} = 10\text{MHz}$


Transmission Zero Generation Opamp-RC Integrator

$$V_o = -\frac{I}{s(C+C_x)} \left[\frac{V_{in1}}{R_1} + \frac{V_{in2}}{R_2} + \frac{V_o}{R_f} \right]$$


$$-V_{in3} \times \frac{C_x}{C+C_x}$$

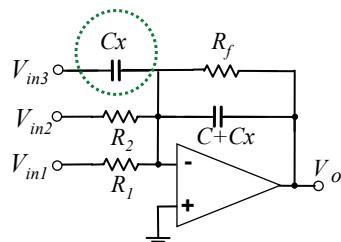

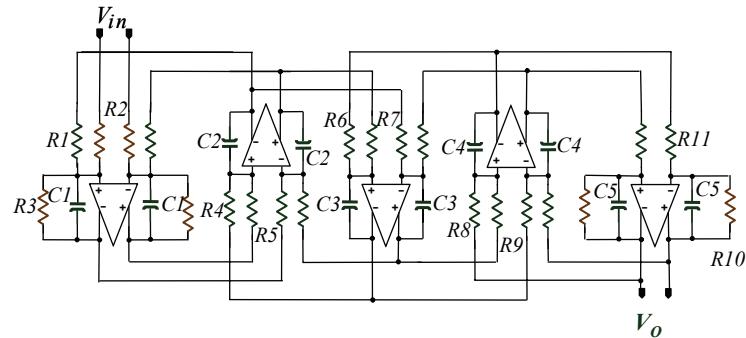Differential Integrator Based LP Ladder Filter Final Design 5th Order All-Pole



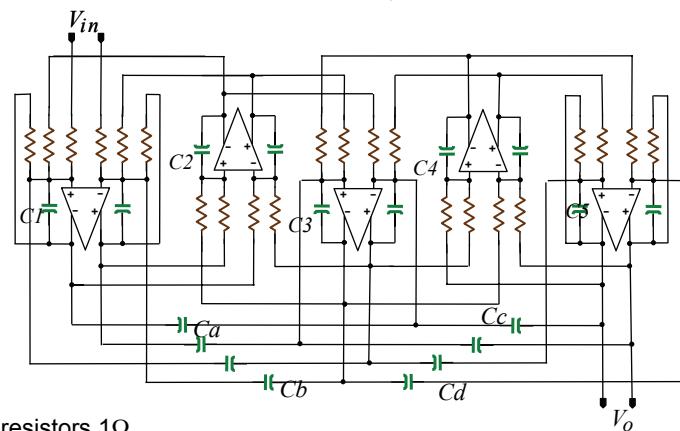Differential 5th Order Chebychev Lowpass Filter




❑ All resistors 1Ω


❑ Capacitors: $C1=36.11nF$, $C2=14.05nF$, $C3=12.15nF$, $C4=5.344nF$, $C5=2.439nF$

❑ Coupling capacitors: $Ca=1.36nF$, $Cb=1.36nF$, $Cc=1.31nF$, $Cd=1.31nF$

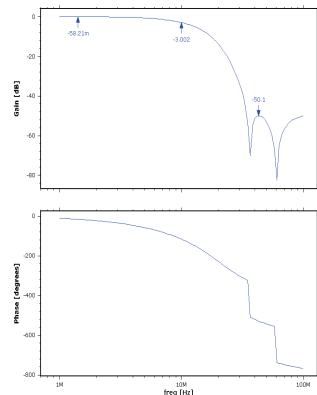5th Order Chebyshev II Filter Simulated Frequency Response



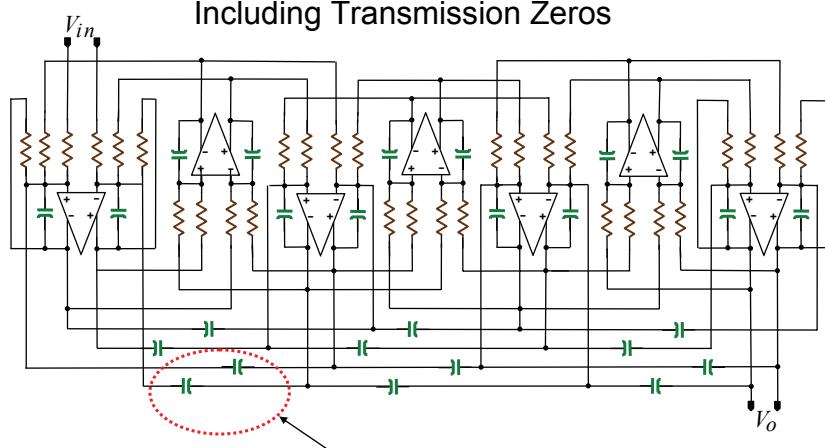7th Order Differential Lowpass Filter Including Transmission Zeros



*Transmission zeros implemented with
pair of coupling capacitors*

Effect of Integrator Non-Idealities on Filter Frequency Characteristics


- In the passive filter design (RLC filters) section:
 - Reactive element (L & C) non-idealities → expressed in the form of Quality Factor (Q)
 - Filter impairments due to component non-idealities explained in terms of component Q
- In the context of active filter design (integrator-based filters)
 - Integrator non-idealities → Translates to the form of Quality Factor (Q)
 - Filter impairments due to integrator non-idealities explained in terms of integrator Q

Effect of Integrator Non-Idealities on Filter Performance

- Ideal integrator characteristics
- Real integrator characteristics:
 - Effect of opamp finite DC gain
 - Effect of integrator non-dominant poles

Effect of Integrator Non-Idealities on Filter Performance

Ideal Integrator

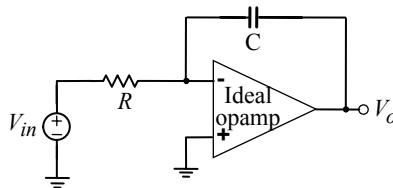

Ideal Integrator:


DC gain = ∞

Single pole @ DC

→ no non-dominant poles

$$H(s) = \frac{-\omega_0}{s}$$

$$\omega_0 = 1/RC$$

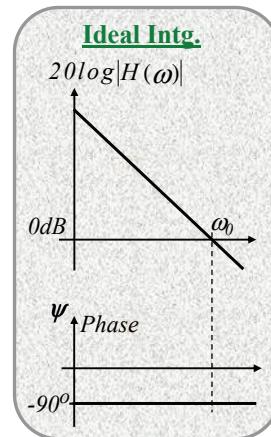

Ideal Integrator Quality Factor


Ideal intg. transfer function: $H(s) = \frac{-\omega_0}{s} = \frac{-\omega_0}{j\omega} = -\frac{j}{\frac{\omega}{\omega_0}}$

Since component Q is defined as::
$$\begin{cases} H(j\omega) = \frac{1}{R(\omega) + jX(\omega)} \\ Q = \frac{X(\omega)}{R(\omega)} \end{cases}$$


Then:

$Q_{ideal}^{intg.} = \infty$

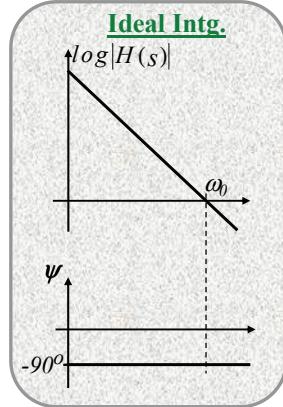Real Integrator Opamp Related Non-Idealities



$$H(s) = \frac{-\omega_b}{s}$$

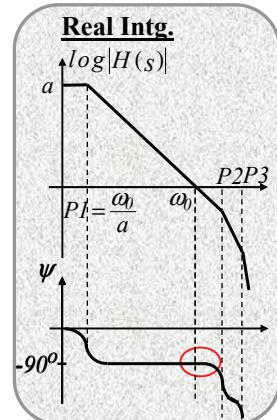



$$H(s) \approx \frac{-a}{(1+s\frac{a}{\omega_b})(1+\frac{s}{p_2})(1+\frac{s}{p_3})\dots}$$

EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 57

Effect of Integrator Finite DC Gain on Q

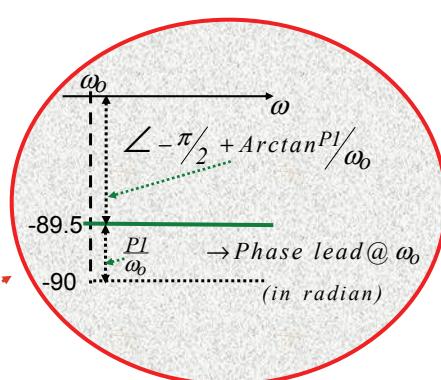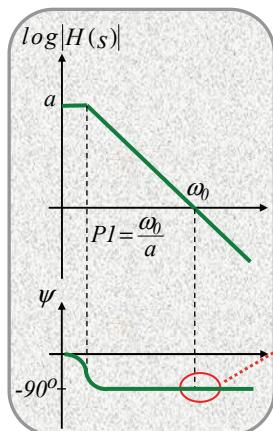

Example: $a=100 \rightarrow P1/\omega_0 = 1/100$
 \rightarrow phase error $\equiv +0.5\text{degree}$


EECS 247

Lecture 4: Active Filters

© 2009 H.K. Page 58

Effect of Integrator Finite DC Gain on Q


Example: Lowpass Filter

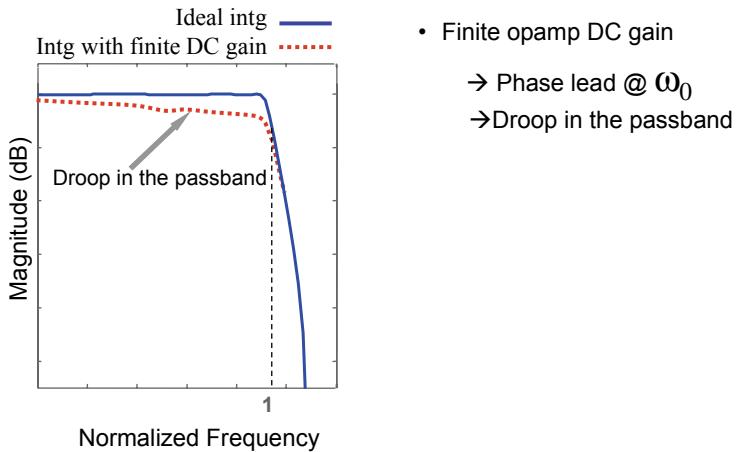

Effect of Integrator Finite DC Gain on Q


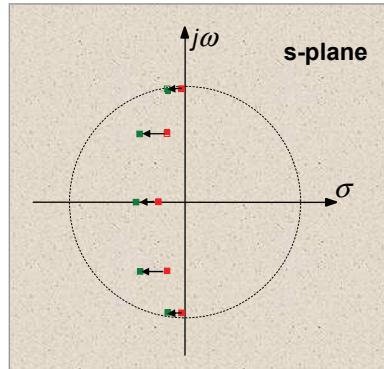
Example: Lowpass Filter

- Effect of opamp finite DC gain on filter singularities
- Pushes the ideal poles away from the $j\omega$ axis
- Results in Q reduction of the poles and thus droop in the passband




- Opamp with finite DC gain
- Ideal opamps & ideal filter pole locations

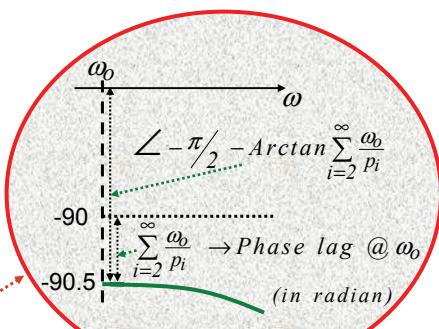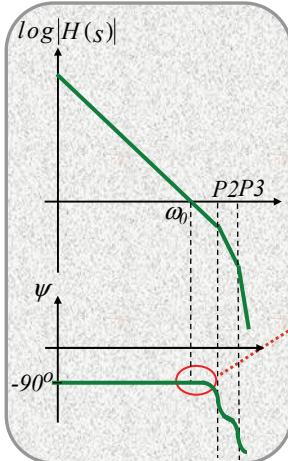Effect of Integrator Opamp Related Non-Dominant Poles



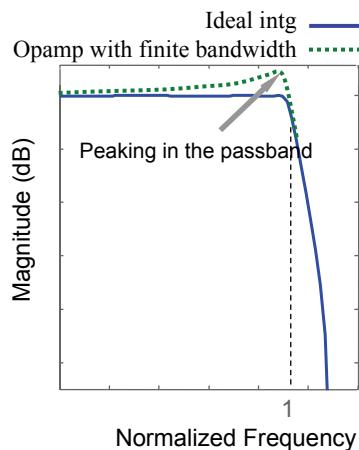Example: $\omega_0/P_2 = 1/100$
 \rightarrow phase error ≈ -0.5 degree

Effect of Integrator Non-Dominant Poles Example: Lowpass Filter




- Additional poles due to opamp poles:
- Phase lag @ ω_0
- Peaking in the passband
- In extreme cases could result in oscillation!


Effect of Integrator Non-Dominant Poles

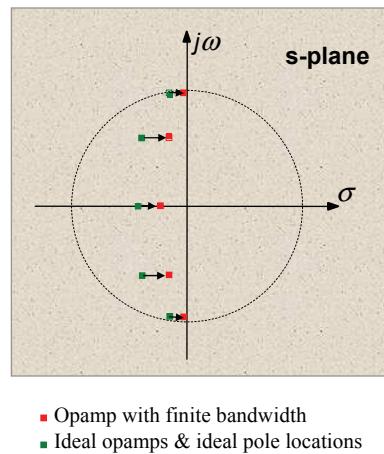Example: Lowpass Filter

- Effect of opamp finite bandwidth on filter singularities
- Pushes the ideal poles towards $j\omega$ axis
- Results in Q enhancement of the poles and thus peaking in the passband



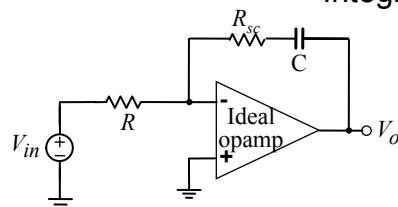Effect of Integrating Capacitor Series Resistance on Integrator Q




Finite R_{sc} adds LHP zero @ $\frac{I}{R_{sc}C}$


$$H(s) = \frac{-\omega_0(l + R_{sc}Cs)}{s}$$

$$\rightarrow Q_{intg} \approx \frac{R}{R_{sc}}$$

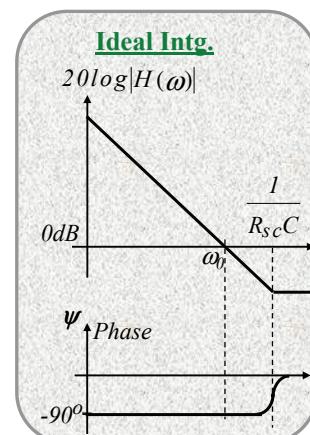Typically, opamp non-idealites dominate Q_{intg}



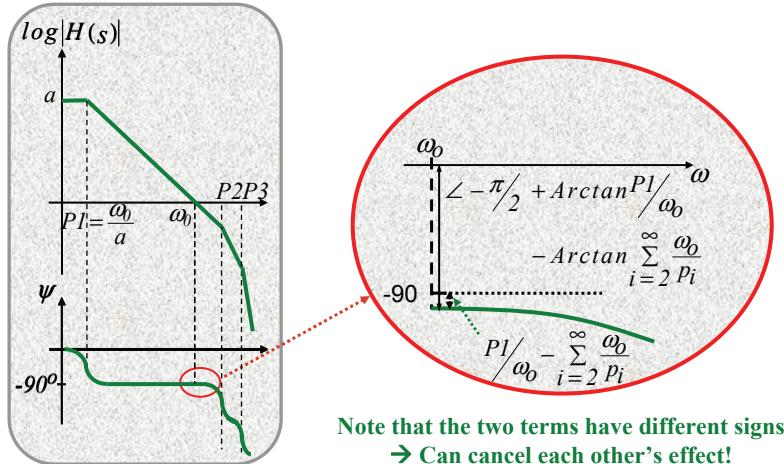Effect of Integrator Non-Dominant Poles & Finite DC Gain on Q



Integrator Quality Factor

Real intg. transfer function: $H(s) \approx \frac{-a}{(1+s\frac{a}{\omega_0})(1+\frac{s}{p_2})(1+\frac{s}{p_3})\dots}$

Based on the definition of Q and assuming that:


$$\frac{\omega_0}{p_{2,3,\dots}} \ll 1 \quad \& \quad a \gg 1$$

It can be shown that in the vicinity of unity-gain-frequency:


$$Q_{real}^{intg.} \approx \frac{1}{\frac{1}{a} - \omega_0 - \sum_{i=2}^{\infty} \frac{1}{p_i}}$$

Phase lead @ ω_0 *Phase lag @ ω_0*

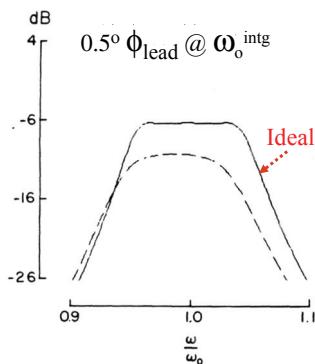Example:
Effect of Integrator Finite Q on Bandpass Filter Behavior




Integrator DC gain=100

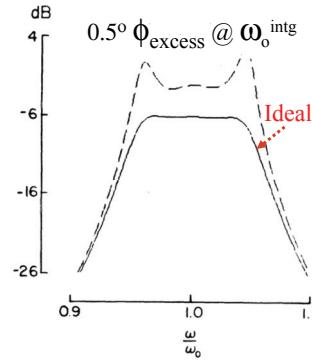

Integrator $P2 @ 100. \omega_0$

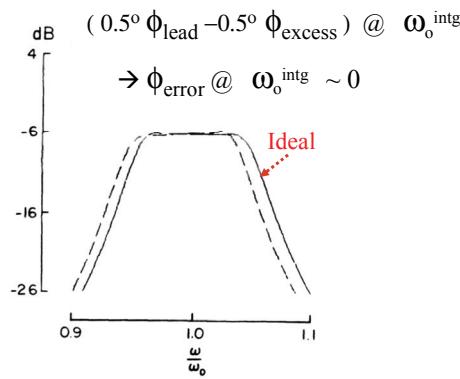Example:
Effect of Integrator Q on Filter Behavior



Integrator DC gain=100 & $P2 @ 100. \omega_0$

Summary

Effect of Integrator Non-Idealities on Q

$$Q_{ideal}^{intg.} = \infty$$

$$Q_{real}^{intg.} \approx \frac{1}{\frac{1}{a} - \omega_b \sum_{i=2}^{\infty} \frac{1}{p_i}}$$

- Amplifier finite DC gain reduces the overall Q in the same manner as series/parallel resistance associated with passive elements
- Amplifier poles located above integrator unity-gain frequency enhance the Q!
 - If non-dominant poles close to unity-gain freq. → Oscillation
- Depending on the location of unity-gain-frequency, the two terms can cancel each other out!
- Overall quality factor of the integrator has to be much higher compared to the filter's highest pole Q