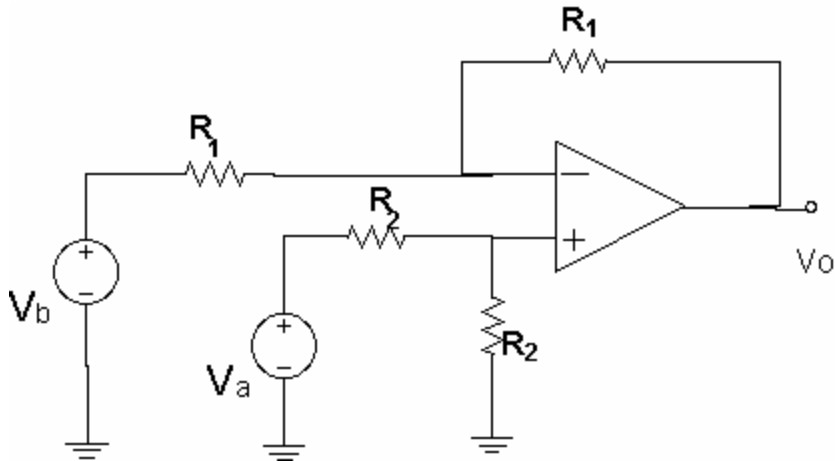


Op-Amp Practice Problems

Solutions

Problem 1:



Problem 2:

$R_f = 2.24 \text{ K}$ saturates the amplifier at $V_O = 18 \text{ V}$; impossible to saturate amplifier at $V_O = -9 \text{ V}$ (would require negative R_f)

Problem 3:

If using ideal op-amp, $R_T = 0$ (leave gain as A and take limit towards infinity)

If using op-amp non-ideal (realistic) equivalent circuit, very complicated.

$$R_T = 20 / (20 \cdot R_i \cdot A + 2 \cdot R_i \cdot R_o + 23 \cdot R_i + 40 \cdot R_o + 260) \cdot R_i \cdot (2 \cdot R_o + 13)$$