


**Homework Assignment #7**

Due at 11:00 AM in 240 Cory on Friday, 10/24/03


\* Be sure to put your name and **Discussion Section number** on your paper; **otherwise 5 pts will be deducted from your score!**

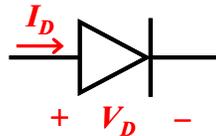**Problem 1: pn-Junction Diode  $I$ - $V$  characteristic**

The  $I$ - $V$  characteristic of a pn-junction diode is given by the equation  $I_D = I_S (e^{qV_D/kT} - 1)$  where the **diode saturation current  $I_S$  is proportional to  $n_i^2$** .



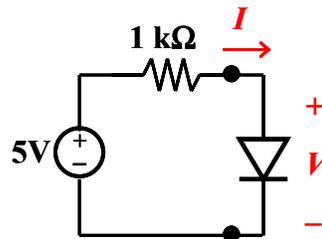
Suppose a diode is to be used in the following circuit, maintained at  $T = 300\text{K}$ :



- Solve for  $I$  and  $V$  using the load line analysis method, assuming a Si diode with  $I_S = 10^{-15}$  A.
- Now solve for  $I$  and  $V$  using the large-signal model of the diode, with  $V_{Don} = 0.7\text{V}$ . Compare these values of  $I$  and  $V$  against the ones which you obtained in part (a).
- Suppose the silicon diode is replaced with an AlGaAs light-emitting diode. (See Slide 11 of Lecture 20.) How would you expect  $I$  and  $V$  to change, qualitatively? Explain.  
(Hint: Recall that the energy of the emitted photons  $E = h\nu = hc/\lambda$  corresponds to the energy given up by a conduction electron when it recombines with a hole, and therefore corresponds to the energy required to generate an electron-hole pair. Recall from Slide 2 of Lecture 18 that the energy required to generate an electron-hole pair in Si is 1.1 eV, which corresponds to wavelength  $\lambda \cong 1\mu\text{m}$ .)

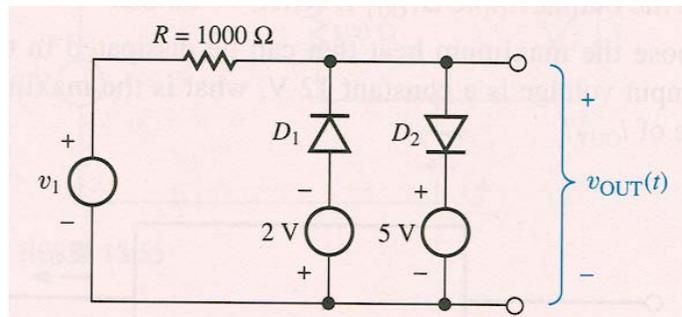**Problem 2: Diode Circuit**

The circuit shown below is known as a “clipper”, and can be used to protect the circuit that it is connected to it from excess voltages. Assume the diodes are perfect rectifiers and the input voltage  $v_1(t) = 10 \sin(2\pi t)$ . Sketch the output voltage  $v_{OUT}(t)$ .



### **Problem 3: MOSFET Fundamentals**

- a) Explain qualitatively (without using any equations) how a conductive path is formed between the n-type source and drain regions of an n-channel enhancement-mode MOSFET (with a p-type body), by applying a suitable voltage on the gate electrode. How does the resistance between the source and drain change with increasing gate voltage?
- b) How does the resistance between the source and drain change with drain voltage increasing from 0 V up to the gate voltage, for a long n-channel MOSFET? (Again, explain qualitatively without resorting to any equations.) Assume that the source and the body are each biased at 0 Volts.
- c) How does your answer to part (b) change if the channel length is very short (so that velocity saturation effects are evident)?

### **Problem 4: MOSFET $I$ - $V$ characteristics**

A long-channel n-channel enhancement-mode MOSFET has threshold voltage  $V_T = 0.5$  V, process transconductance parameter  $k_n' = 0.2$  mA/V<sup>2</sup>, channel length  $L = 1$   $\mu$ m and channel width  $W = 10$   $\mu$ m.

- a) Sketch the drain current vs. gate voltage ( $I_{DS}$  vs.  $V_{GS}$ ) characteristic for  $0 \leq V_{GS} \leq 5$  V,  $V_{DS} = 0.5$  V.
- b) Sketch the drain current vs. drain voltage ( $I_{DS}$  vs.  $V_{DS}$ ) characteristics for  $0 \leq V_{DS} \leq 5$  V, for  $V_{GS} = 0$  V, 1 V, 2 V, 3 V, 4 V, and 5 V.
- c) For each set of voltages below, state the region of operation and compute the drain current:
  - i)  $V_{GS} = 1$  V and  $V_{DS} = 5$  V
  - ii)  $V_{GS} = 1$  V and  $V_{DS} = 0.5$  V
  - iii)  $V_{GS} = 0$  V and  $V_{DS} = 5$  V