


{ 240 Fall 05 - HW #8 Solutions - BART

Note Title


11/1/2005

(10.8) $i_D = I_S e^{V_D/nV_T} \Rightarrow \frac{i_{D1}}{i_{D2}} = \frac{e^{V_{D1}/nV_T}}{e^{V_{D2}/nV_T}} = e^{(V_{D1} - V_{D2})/nV_T} \Rightarrow \boxed{n = 1.336}$

$I_S = 31.5 \mu A$

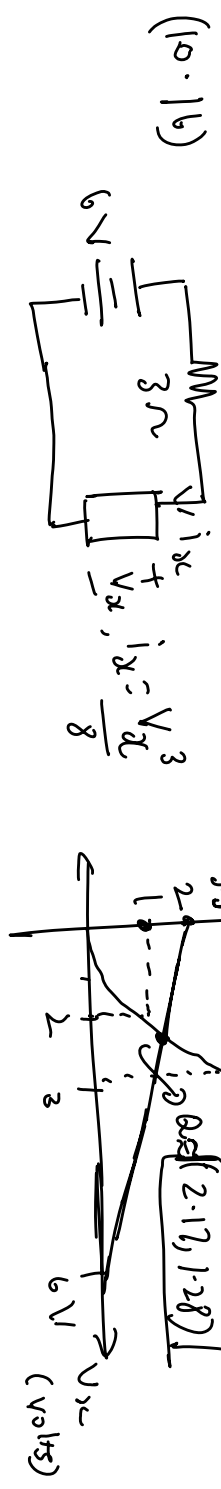

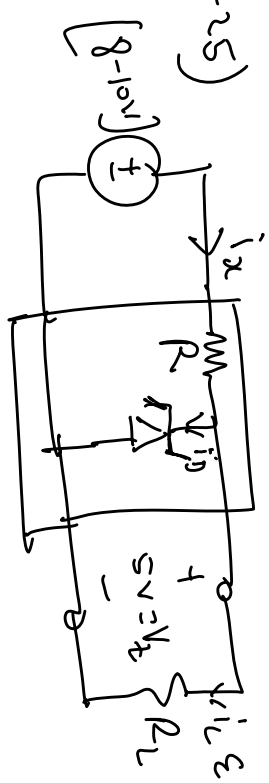(10.25) $i_x \in [0 \text{ mA}, 100 \text{ mA}]$ Key: $i_x = i_D$ til



Now, choose $V_2 = 5V$, we want R such that $i_D > 0$ for all i_c .
 Now, as V_{in} increases, i_x will increase \Rightarrow worst CASE: $V_{in} = 8V, i_c = 100 \text{ mA}$

$i_x = \frac{V_{in} - V_2}{R} \Rightarrow R = \frac{3}{i_x}$

Suppose $R = 1k, i_x = 3 \text{ mA} \Rightarrow i_D = -97 \text{ mA}$ X

$\therefore R = 1N, i_x = 3A \Rightarrow$ way too big, although will work.

Idea 2: $i_D = 0 \Rightarrow i_x = 100 \text{ mA} \Rightarrow \boxed{R = 30 \Omega}$

$$R = 30 \Omega, V_T = 5 V$$

Worst case power:

$$V_n = 10 V$$

$$P_{gen} = V_{gen} I_{gen}$$

$$P_{30\Omega} = I^2 R = 0.83 mW$$

$$= (-5)(-66 mA)$$

$$P_{total} = 0.32 mW$$

(10.33) Have to make an educated guess about diode states:

(a) D_1 on, D_2 off. $V = 10 V, I = 0 A$

(b) D_1 on, D_2 off. $V = 6 V, I = 6 mA$

(c) D_1 on, D_2 on. $V = 30 V, I = 33.6 mA$

(10.61) This circuit is explained in lecture 25:

