



EE 40 – Introduction to Microelectronic Circuits

Fall 2005,

Dept. EECS, 509 Cory

UC Berkeley

Course Web Site

Prof. A. R. Neureuther

neureuth@eecs.berkeley.edu, 642-4590

Office Hours: M1, W 3, F10

[http://www inst.eecs.berkeley.edu/~ee40/](http://www.inst.eecs.berkeley.edu/~ee40/)

Problem Set # 9


Due: 5 PM Tuesday, Nov. 8th, 2005 in 240 Cory

9.1 Phasors, Transfer Functions and Frequency Response

Use the values $C1 = 1\mu\text{F}$, $R1 = 100\text{k}\Omega$, $C2 = 1\mu\text{F}$, $R2 = 100\Omega$, $C3 = 1\text{nF}$, $R3 = 100\Omega$.

Use $a = b = 100$.

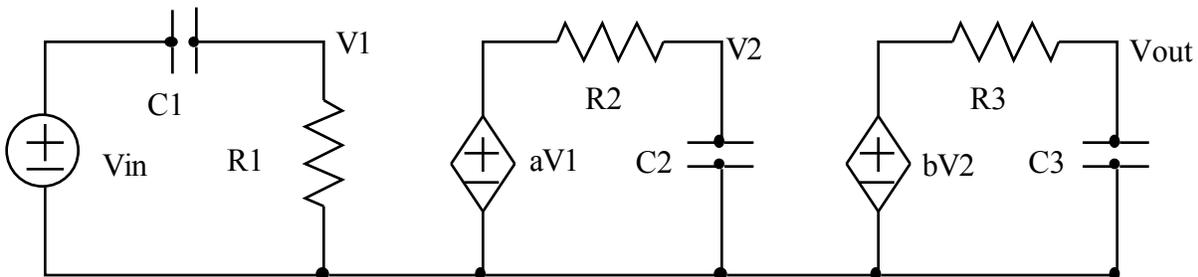Given the following circuit, work through the following:



- Derive a complex algebraic solution for V_{out}/V_{in} . Write this transfer function in fully factored form (both the numerator and the denominator should be written as a product of complex factors of the form either $j\omega A$ or $(1+j\omega B)$).
- On the calculator you will use at the exam, calculate the complex value V_{out}/V_{in} at a frequency of $\omega = 10^5$ rad/s. Write this in both $A + jB$ and $Me^{j(\text{phase})}$ form.
- Find the limit as frequency goes to 0, and to infinity, of the magnitude and phase of the transfer function. Also, determine any break frequencies of zeros and poles of your transfer function.
- Provide a magnitude Bode plot and a phase Bode plot of the transfer function. Be sure to choose your range on the frequency axis to capture all important behaviors of your transfer function.


9.2 Cascade Op-amps

Suppose you are designing a circuit that, given two inputs $V1$ and $V2$, is supposed to perform the following task: over each second, you want to take the time-varying difference $V1 - V2$ and make sure that the integral of this difference over each second of observation is not greater than $5V \cdot s$ (assume the circuit you design simply reports the integral value to some greater control circuit).

You have at your disposal: ideal op-amps, resistors, capacitors. Assume you can use a switching discharge circuit (just use a switch symbol in your drawings) for any capacitors so that they automatically discharge completely at the end of every second. Construct your circuit.

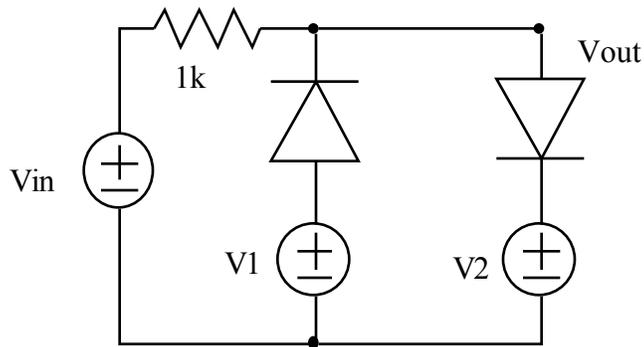9.3 Analyzing Diode Circuits

Suppose the following circuit. Assume $R = 1\text{k}\Omega$, $V_1 = -2\text{V}$, $V_2 = 3\text{V}$. Assume you are using the ideal diode model.



- For an input $V_{in} = -3\text{V}$, determine V_{out} and the current through the resistor (with direction).
- For an input of $V_{in} = 4\text{V}$, determine V_{out} and the current through the resistor (with direction).
- Given an input sinusoid $V_{in1} = 5\cos(2\pi t)$, plot the output of the circuit over the interval from 0 to 5 seconds.
- What does the circuit do?

9.4 Diode Logic Gates

Use the circuit from slide 20 of lecture 24 (Diodes in TTL). Use the large signal model for diodes, assume V_{in} goes into both the A and B terminals. Assume V_{out} is taken at terminal F. Let $R_1 = 5\text{k}\Omega$ and $R_2 = 1\text{k}\Omega$, and use a value of $\beta = 30$.

- Plot the input current I_1 as identified in the circuit versus V_{in} .
- Plot V_{out} versus V_{in} .
- Assume the output of this circuit feeds the inputs of N identical gates. Find the maximum value of N where this circuit could still have an output $V_{out} = 1\text{V}$ for some input.
- Show how to add a diode and a voltage source to the output so that the output cannot go above 5V or below 0.2V .