


EE 40

Homework 5

Due Tuesday, April 15, 2003 at start of class (3:30 PM)

40 Total Points Possible

Problem 1: 8 Points Possible

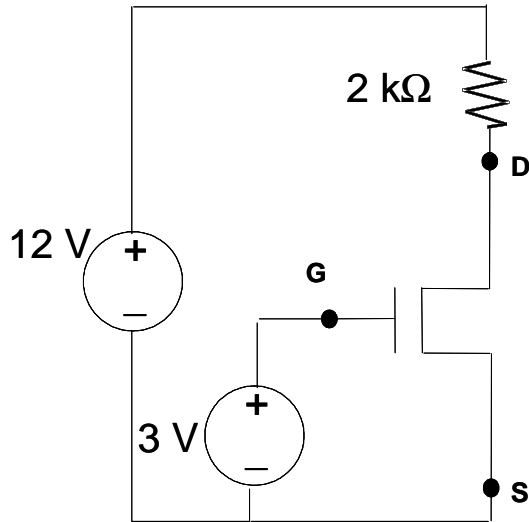


For the NMOS transistor circuit at left, let

$$V_{TH(N)} = 1 \text{ V},$$
$$W/L \mu_N C_{OX} = 1 \text{ mA/V}^2,$$
$$\lambda = 0 \text{ V}^{-1}.$$

Find V_{DS} and I_D for the transistor.

Problem 2: 8 Points Possible

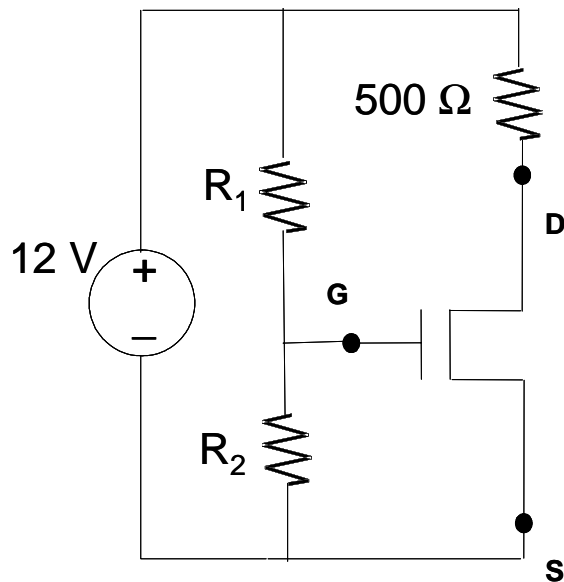


For the NMOS transistor circuit at left, let

$$V_{TH(N)} = 1 \text{ V},$$
$$W/L \mu_N C_{OX} = 1 \text{ mA/V}^2,$$
$$\lambda = 0 \text{ V}^{-1}.$$

Find values for R_1 and R_2 so that the circuit will supply a constant 8 mA to the resistor when the transistor is in saturation mode.

Problem 3: 8 Points Possible

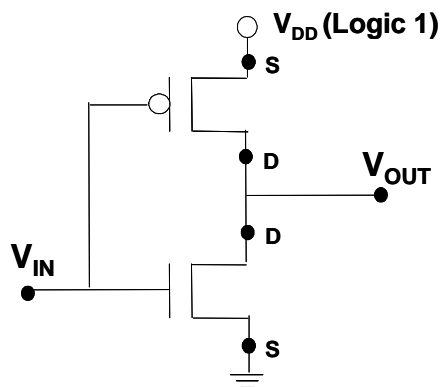


Consider the unloaded CMOS inverter at right with

$$\begin{aligned} V_{DD} &= 5 \text{ V} \\ V_{TH(N)} &= -V_{TH(P)} = 1 \text{ V} \\ C_{OX} &= 5 \text{ fF}/\mu\text{m}^2 && \text{for both transistors} \\ L &= 2.5 \mu\text{m} && \text{for both transistors} \\ \lambda &= 0 && \text{for both transistors} \\ \mu_N &= 50000 \text{ mm}^2 / (\text{V s}) \\ \mu_P &= 25000 \text{ mm}^2 / (\text{V s}) \end{aligned}$$

Find a width W_N for the NMOS transistor channel and width W_P for the PMOS transistor channel that together will make $V_M = 2 \text{ V}$.

Problem 4: 8 Points Possible

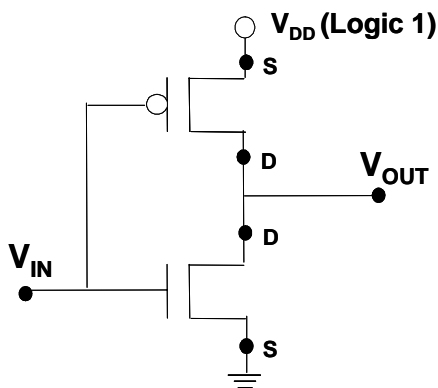


Consider the unloaded CMOS inverter at right with

$$\begin{aligned} V_{DD} &= 5 \text{ V}, \\ W/L \mu C_{OX} &= 1 \text{ mA}, \\ V_{TH(N)} &= -V_{TH(P)} = 1 \text{ V}, \\ \lambda &= 0. \end{aligned}$$

Find $V_{DS(N)}$, $I_{D(N)}$, $V_{DS(P)}$, and $I_{D(P)}$ corresponding to $V_{IN} = 3.5 \text{ V}$.

Problem 5: 8 Points Possible

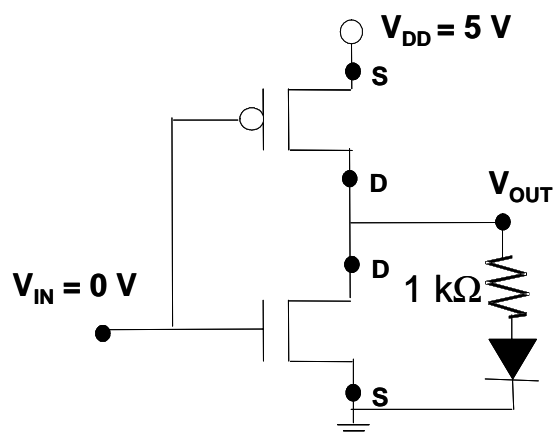

Consider the CMOS inverter at right with

$$\begin{aligned} W/L \mu C_{OX} &= 1 \text{ mA}, \\ V_{TH(N)} &= -V_{TH(P)} = 1 \text{ V}, \\ \lambda &= 0 \end{aligned}$$

and diode (large-signal model) with $V_F = 0.7 \text{ V}$.

Find the power absorbed by the transistor, resistor, and diode.