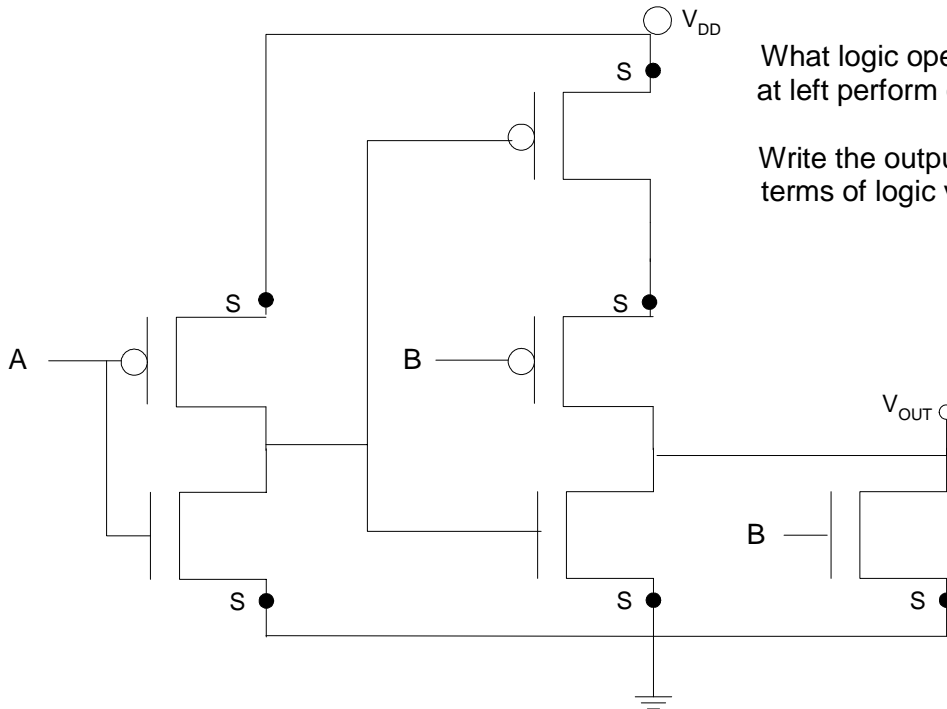


Homework #6


Due Tuesday, April 22, 2003, 3:30 PM

40 Total Points Possible

Problem 1: 10 Points Possible

What logic operation does the CMOS circuit at left perform on the binary inputs A and B?

Write the output as a Boolean function in terms of logic voltages A and B.

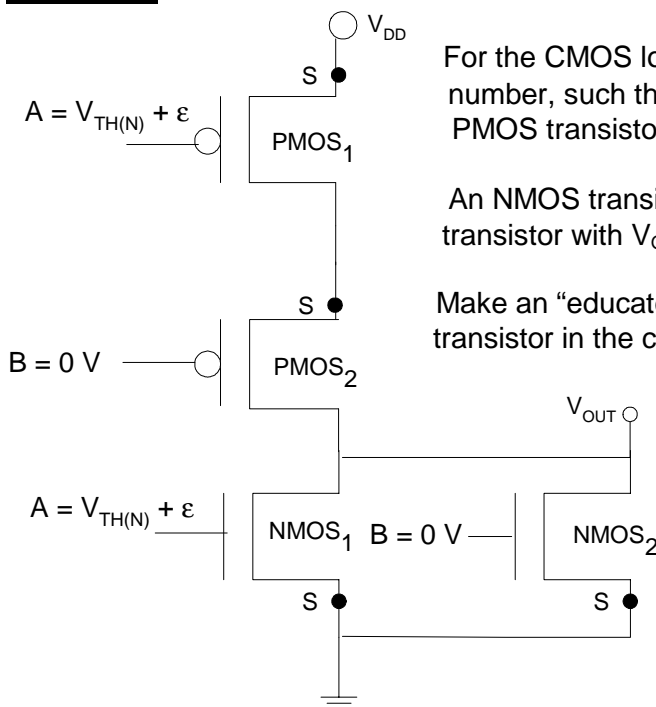
Problem 2: 8 Points Possible

For the CMOS logic circuit at left, assume that ϵ is a small positive number, such that an NMOS transistor with $V_{GS(N)} = V_{TH(N)} + \epsilon$ (or PMOS transistor with $V_{GS(P)} = V_{TH(P)} - \epsilon$) would be “barely” turned on.

An NMOS transistor with $V_{GS(N)} = V_{DD} - (V_{TH(N)} + \epsilon)$ (or PMOS transistor with $V_{GS(P)} = -V_{DD} - (V_{TH(P)} - \epsilon)$) would be “fully” turned on.

Make an “educated guess” for the mode of operation of each transistor in the circuit at left. Assume $V_{TH(N)} \approx -V_{TH(P)}$.

Problem 3: 12 Points Possible

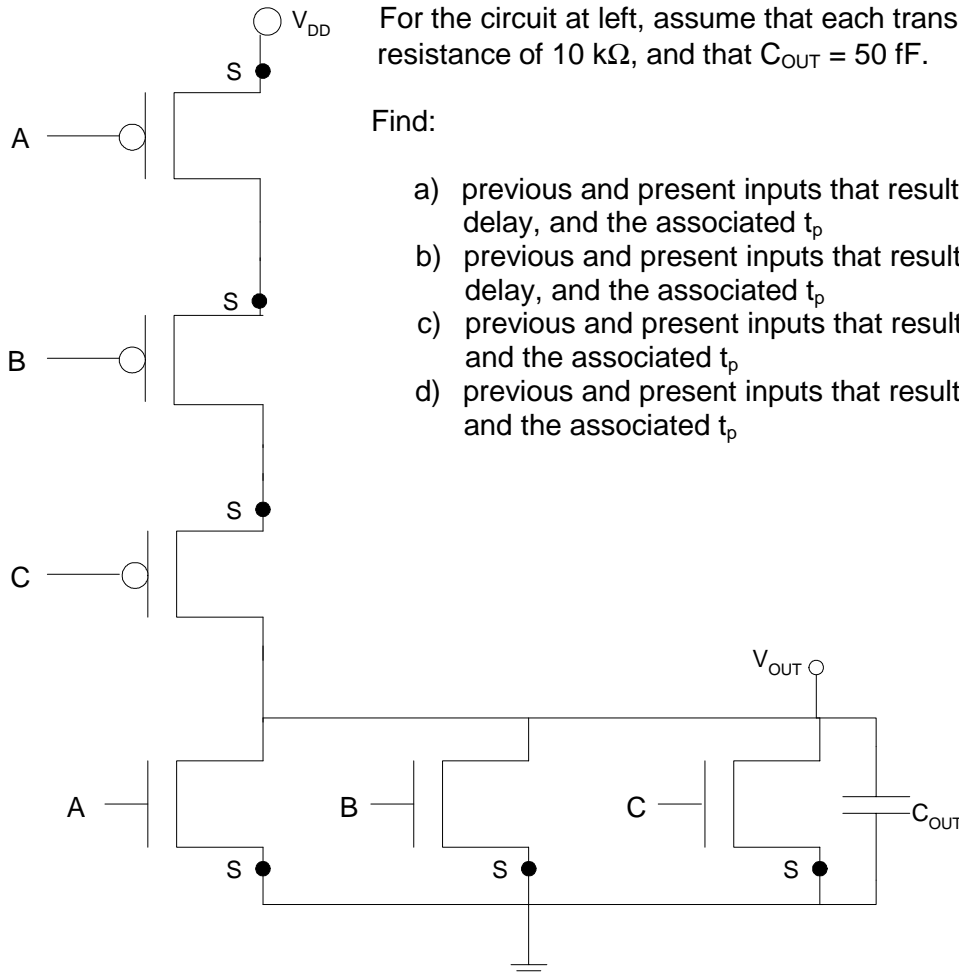

For the circuit at left, assume that each transistor has a pull-up/pull-down resistance of $10\text{ k}\Omega$, and that $C_{\text{OUT}} = 50\text{ fF}$.


Find:

- previous and present inputs that result in the shortest pull-down delay, and the associated t_p
- previous and present inputs that result in the longest pull-down delay, and the associated t_p
- previous and present inputs that result in the shortest pull-up delay, and the associated t_p
- previous and present inputs that result in the longest pull-up delay, and the associated t_p

 Problem 4: 10 Points Possible

Consider the logic circuit below. Each logic gate is constructed using the appropriate CMOS circuit given in lecture. With

$V_{\text{DD}} = 5\text{ V}$
 $V_{\text{TH(N)}} = -V_{\text{TH(P)}} = 1\text{ V}$
 $C_{\text{OX}} = 5\text{ fF}/\mu\text{m}^2$ for both transistors
 $L = 1\text{ }\mu\text{m}$ for both transistors
 $W = 2\text{ }\mu\text{m}$ for both transistors
 $\lambda = 0$ for both transistors
 $\mu_{\text{N}} = 50000\text{ mm}^2 / (\text{V s})$
 $\mu_{\text{P}} = 25000\text{ mm}^2 / (\text{V s})$



- Find the low-to-high and high-to-low propagation delays t_p for the inverter in the circuit as shown. Take into account the pull-up and pull-down resistances of the transistors (which you must calculate here), as well as the gate capacitances of the attached gates (calculate also).
- Suppose I require that the maximum propagation delay through the inverter is 2 ns . Determine the maximum fan-out: the maximum number of NAND or NOR gates that can be attached to the inverter output if the propagation delay through the inverter is to be 2 ns maximum.