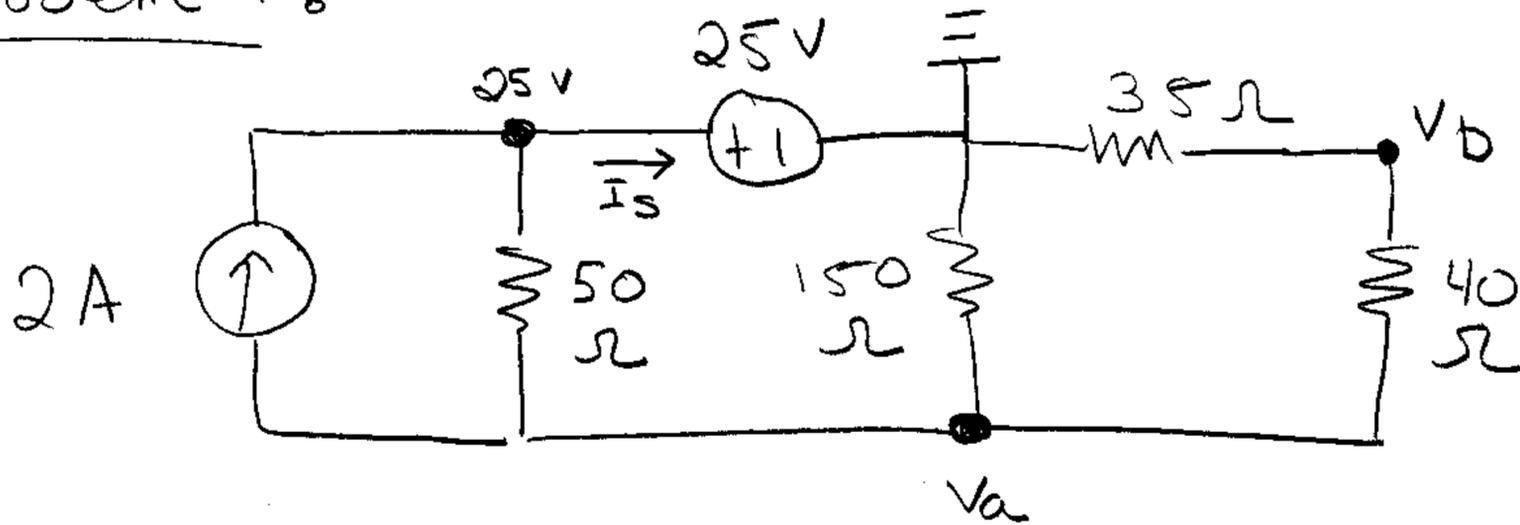


EE 40
 Homework #3
 Solutions

Problem 1°



I chose ground & identified unknown node voltages V_a & V_b .

$$\textcircled{a} V_a: \quad 2A + \frac{V_a - 25V}{50\Omega} + \frac{V_a}{150\Omega} + \frac{V_a - V_b}{40\Omega} = 0$$

$$\textcircled{b} V_b: \quad \frac{V_b}{35\Omega} + \frac{V_b - V_a}{40\Omega} = 0$$

$$V_a = -37.5V \quad V_b = -17.5V$$


Current through 25V source is I_s

$$I_s = 2 + \frac{V_a - 25}{50} = 750 \text{ mA}$$

$$P = I_s \cdot 25V = 18.75 \text{ W}$$

Problem 2:

2

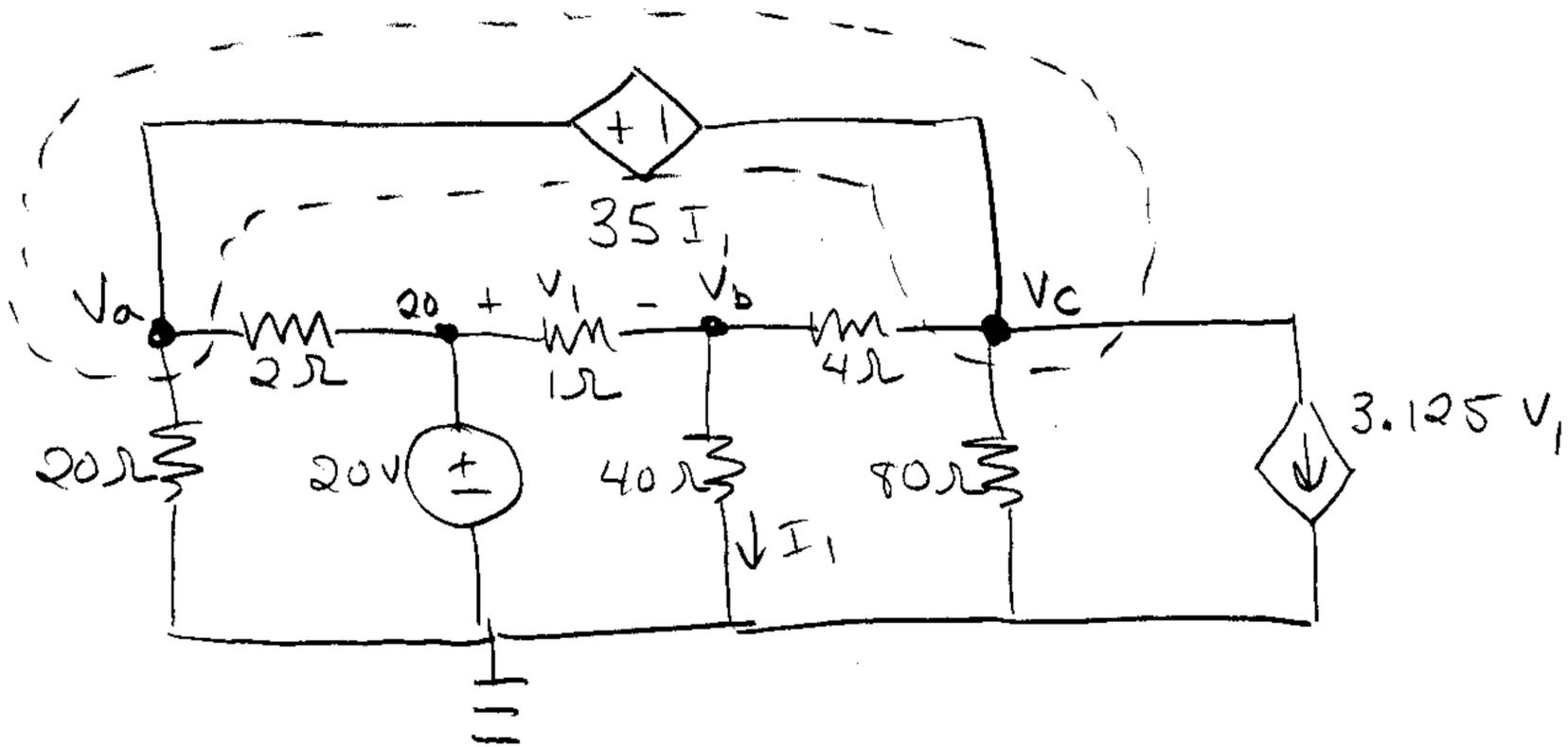

Supernode $V_a + V_c$ as shown since $\diamond +1$ has neither terminal at ground.

KCL @ supernode:

$$\frac{V_a}{20\Omega} + \frac{V_a - 20V}{2\Omega} + \frac{V_c - V_b}{4\Omega} + \frac{V_c}{80\Omega} + 3.125V_1 = 0$$

Voltage relationship given by $\diamond +1$:

$$V_a - V_c = 35I_1$$

KCL @ V_b :

$$\frac{V_b - 20V}{1\Omega} + \frac{V_b}{40\Omega} + \frac{V_b - V_c}{4\Omega} = 0$$

Controlling parameters:

$$I_1 = \frac{V_b}{40\Omega}$$

$$V_1 = 20V - V_b$$

$$V_a = -20.25 \text{ V} \quad V_b = 10 \text{ V} \quad V_c = -29 \text{ V}$$


③

$$P = (V_c)(3.125 \text{ V}) = (V_c)(3.125(20 - V_b))$$

$$= -906.25 \text{ W}$$

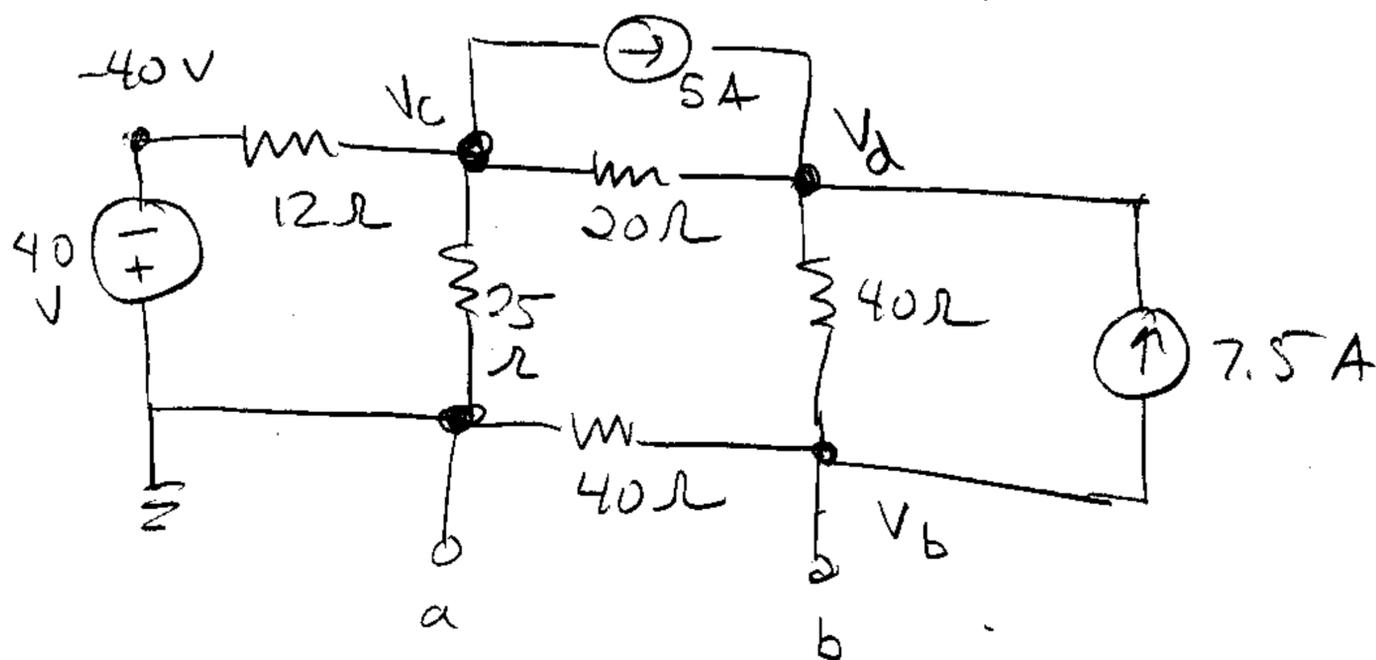Problem 3:

Method #1: Finding V_T & I_N directly via nodal analysis




$$\text{KCL @ } V_b: \frac{V_b}{40\Omega} + \frac{V_b - V_d}{40\Omega} + 7.5 \text{ A} = 0$$

$$\text{KCL @ } V_c: \frac{V_c - 40}{12\Omega} + \frac{V_c}{25\Omega} + \frac{V_c - V_d}{20\Omega} + 5 \text{ A} = 0$$

$$\text{KCL @ } V_d: \frac{V_d - V_c}{20\Omega} + \frac{V_d - V_b}{40\Omega} = 5 \text{ A} + 7.5 \text{ A}$$

$$V_b = -84 \text{ V} \quad V_c = -10 \text{ V} \quad V_d = 132 \text{ V}$$

$$V_{ab} = V_T = 84 \text{ V}$$

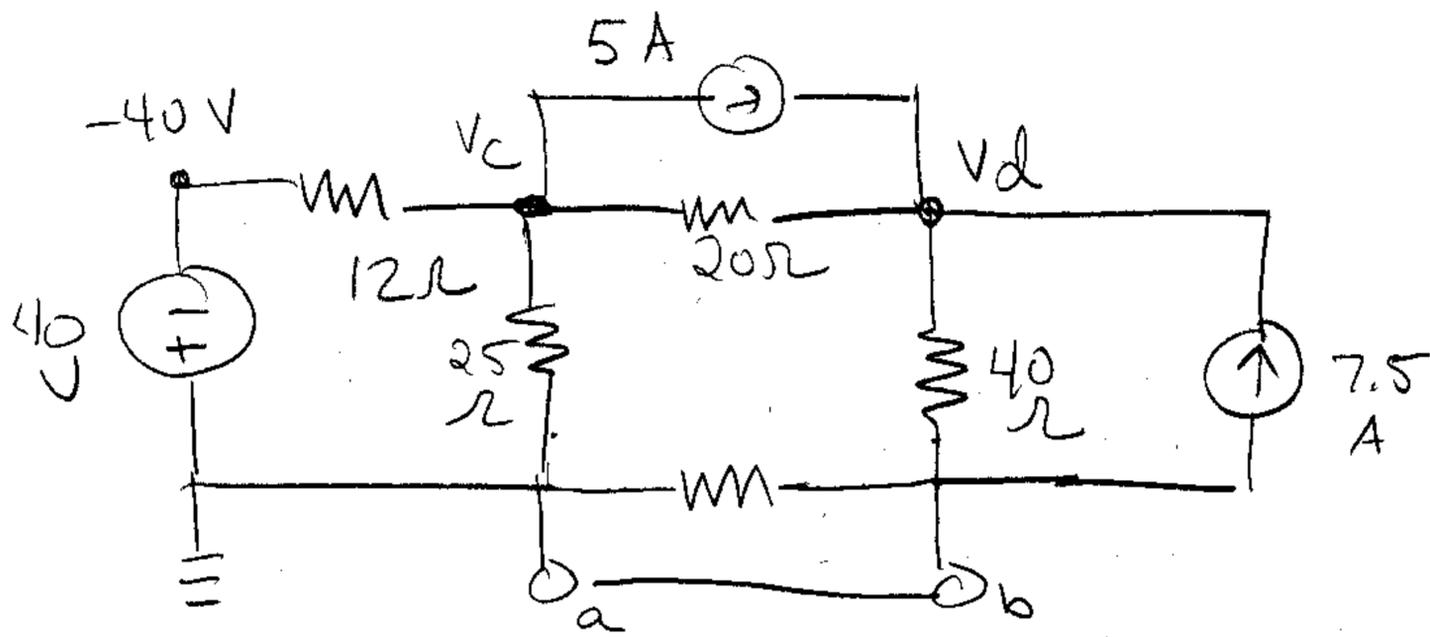

KCL @ V_c : $\frac{V_c - 40}{12\Omega} + 5A + \frac{V_c}{25\Omega} + \frac{V_c - V_d}{20\Omega} = 0$

KCL @ V_d : $\frac{V_d - V_c}{20\Omega} + \frac{V_d}{40\Omega} = 5A + 7.5A$


$V_c = 0V$ $V_d = 166 \frac{2}{3} V$

$I_N + 7.5A = \frac{V_d}{40}$ $I_N = -3 \frac{1}{3} A$

$R_T = R_N = -\frac{V_T}{I_N} = 25.2\Omega$





Method 2: Alternative R_T calculation:






Turn off independent sources

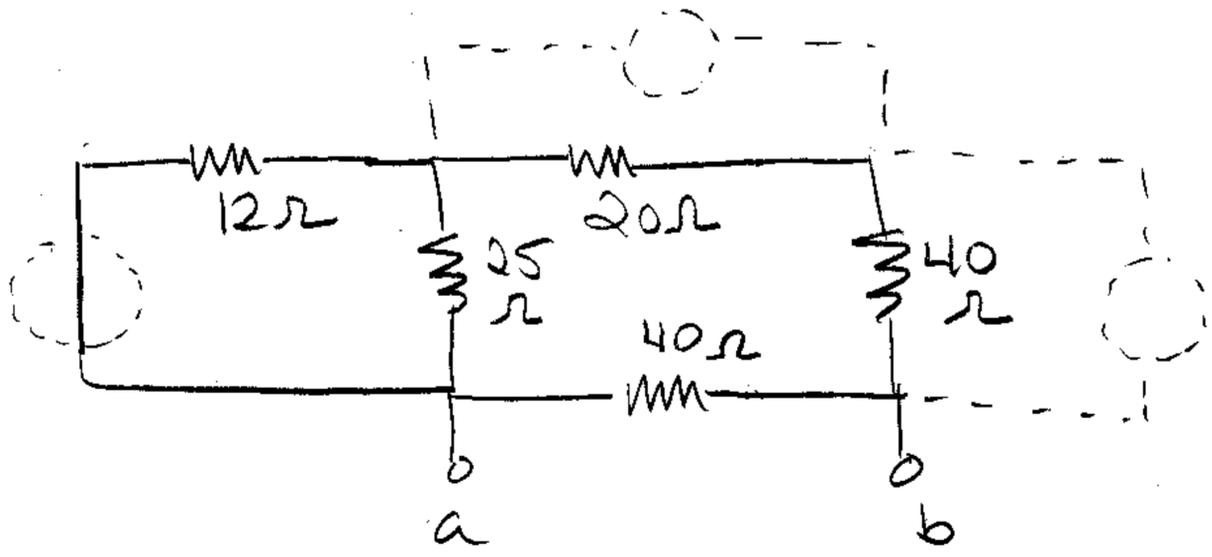


$R_{eq} = R_T = 25.2\Omega$

Method 3° Source Transformations

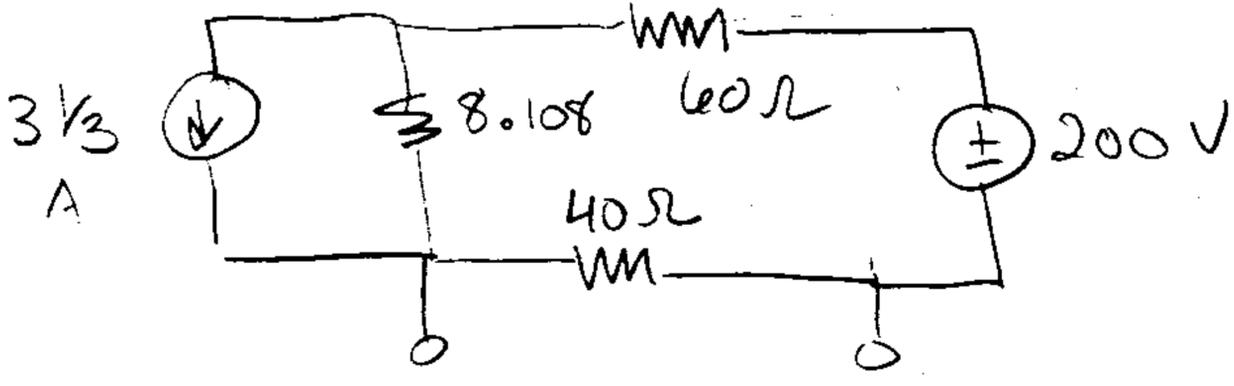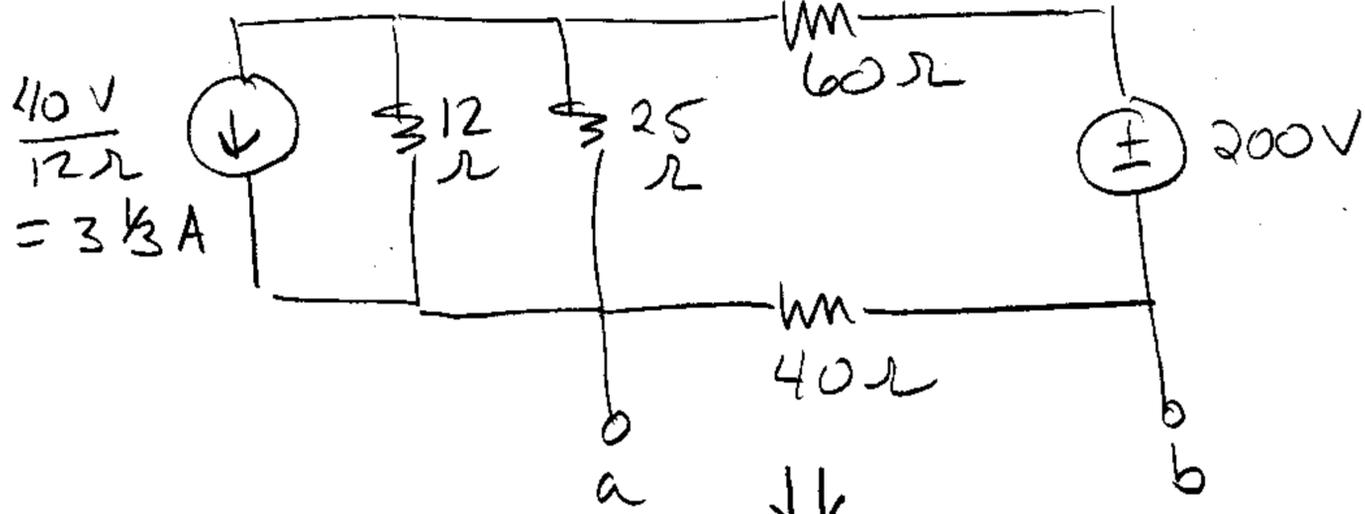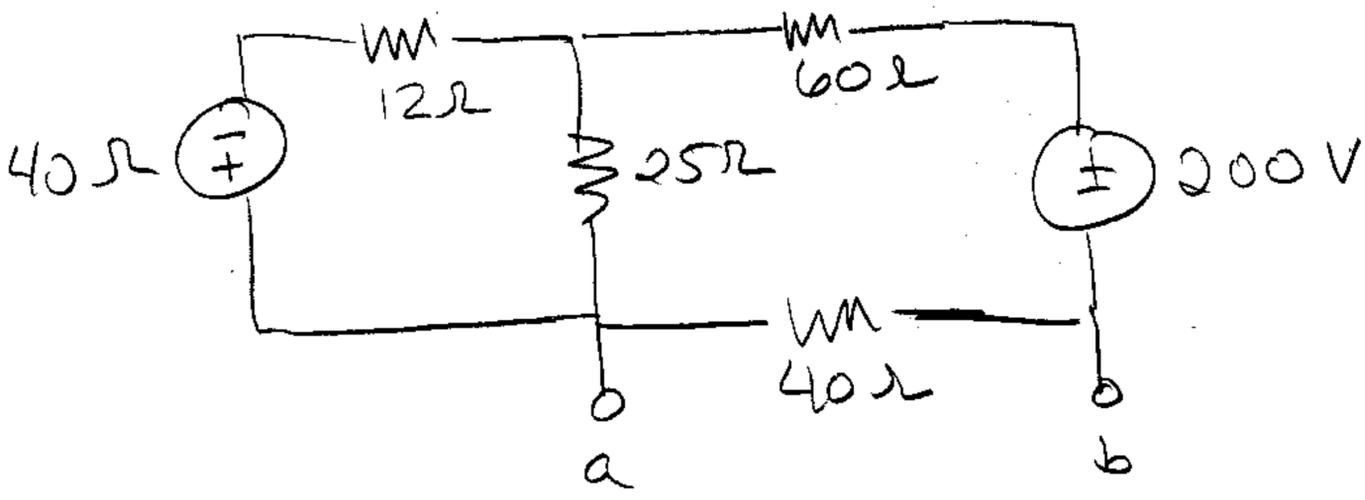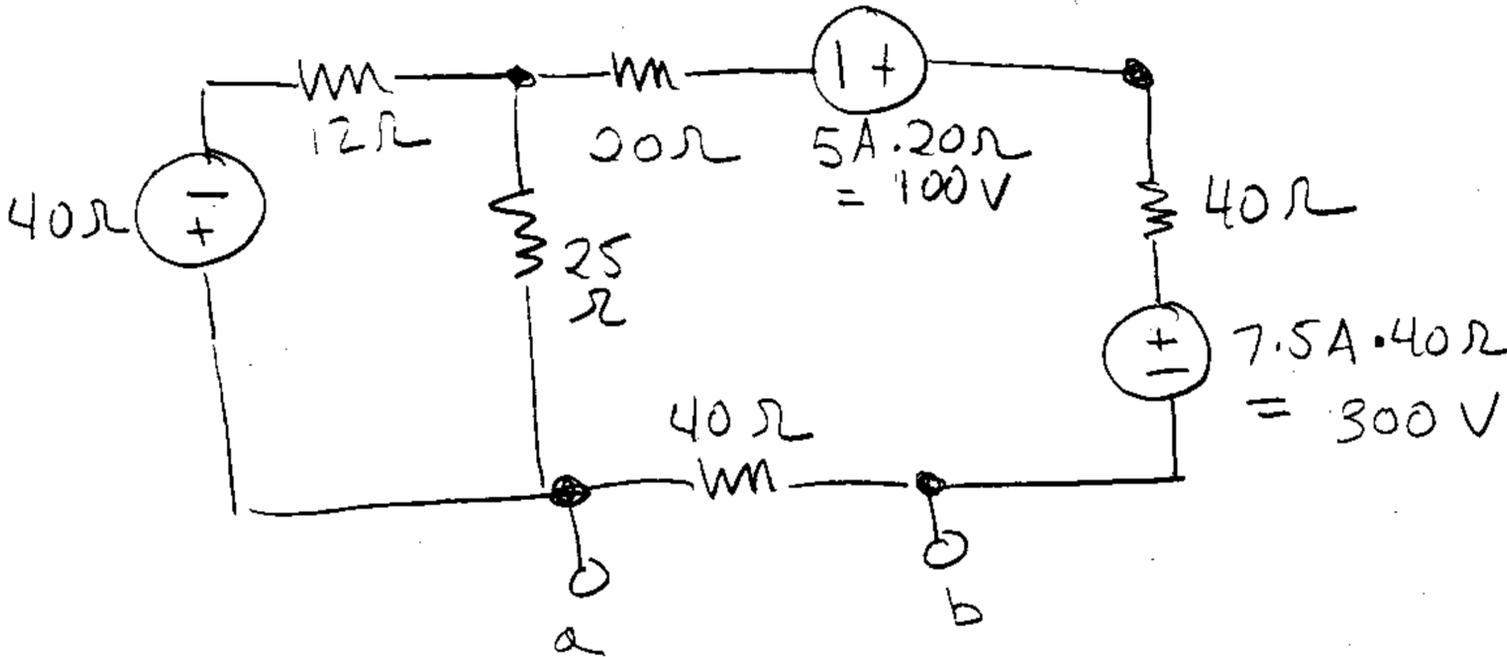

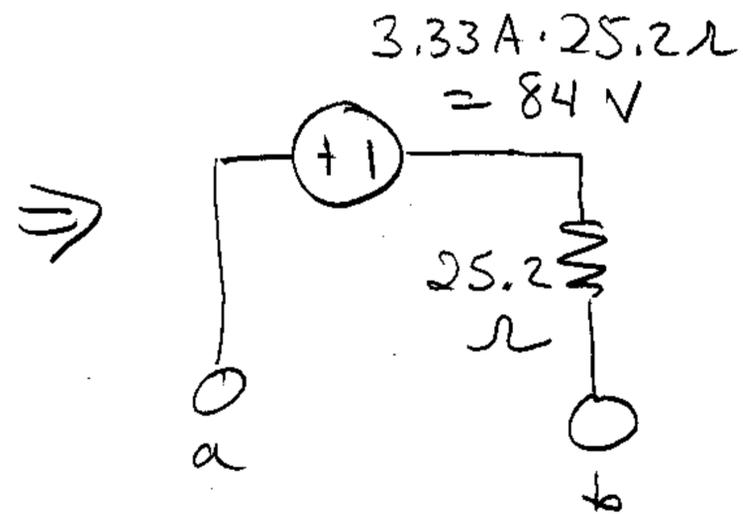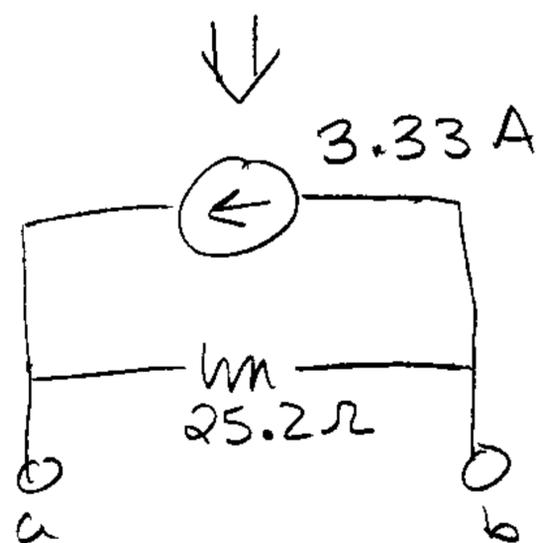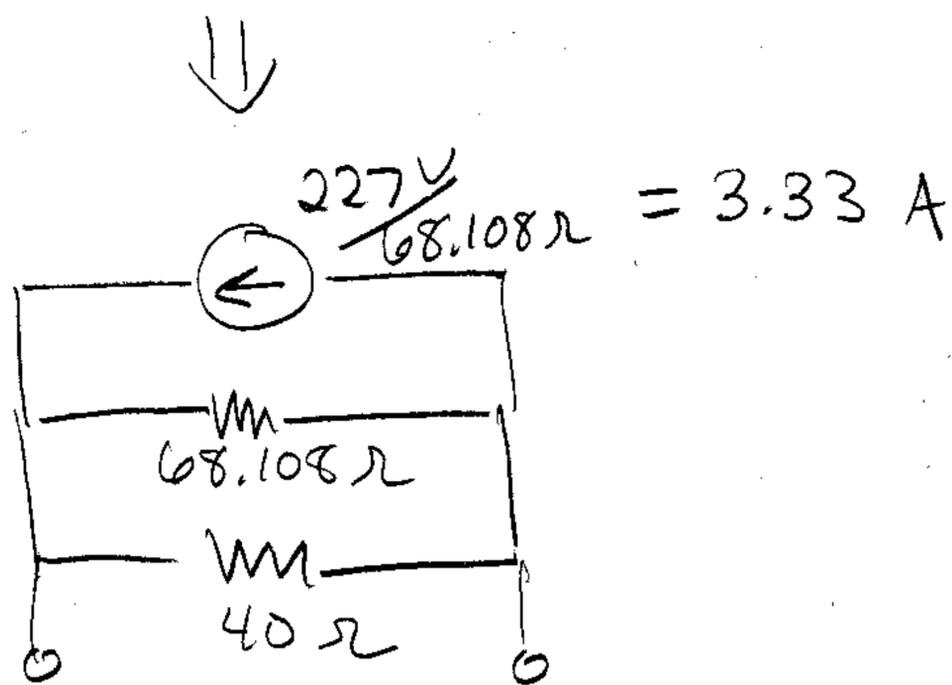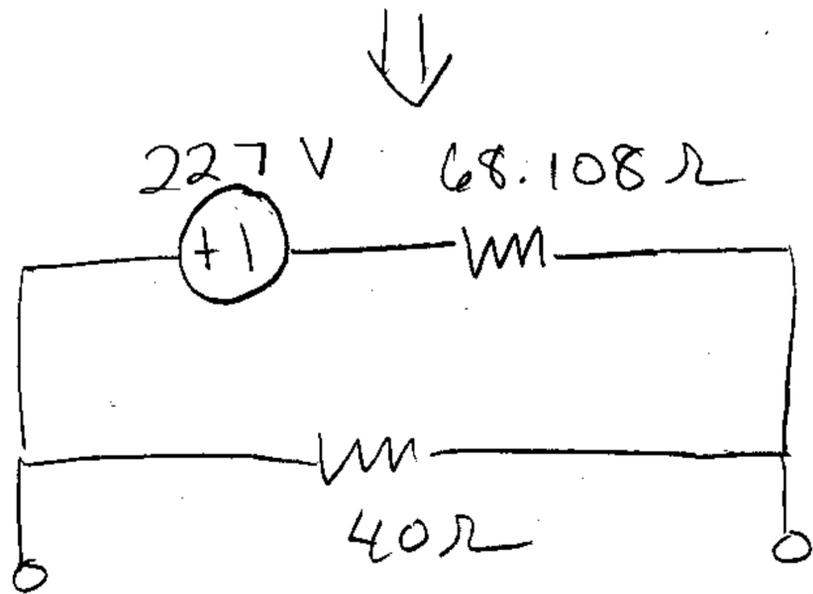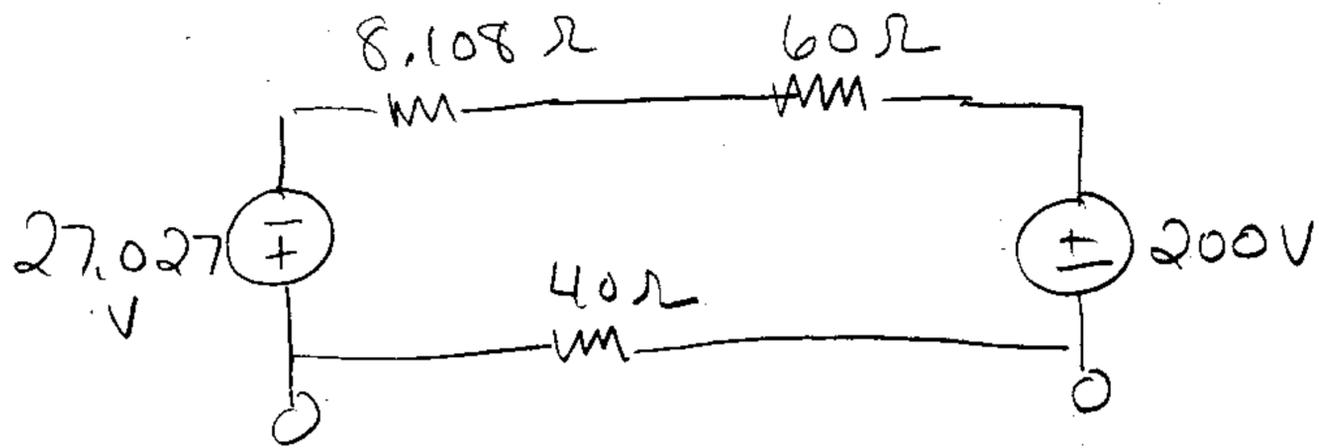

Problem 4°

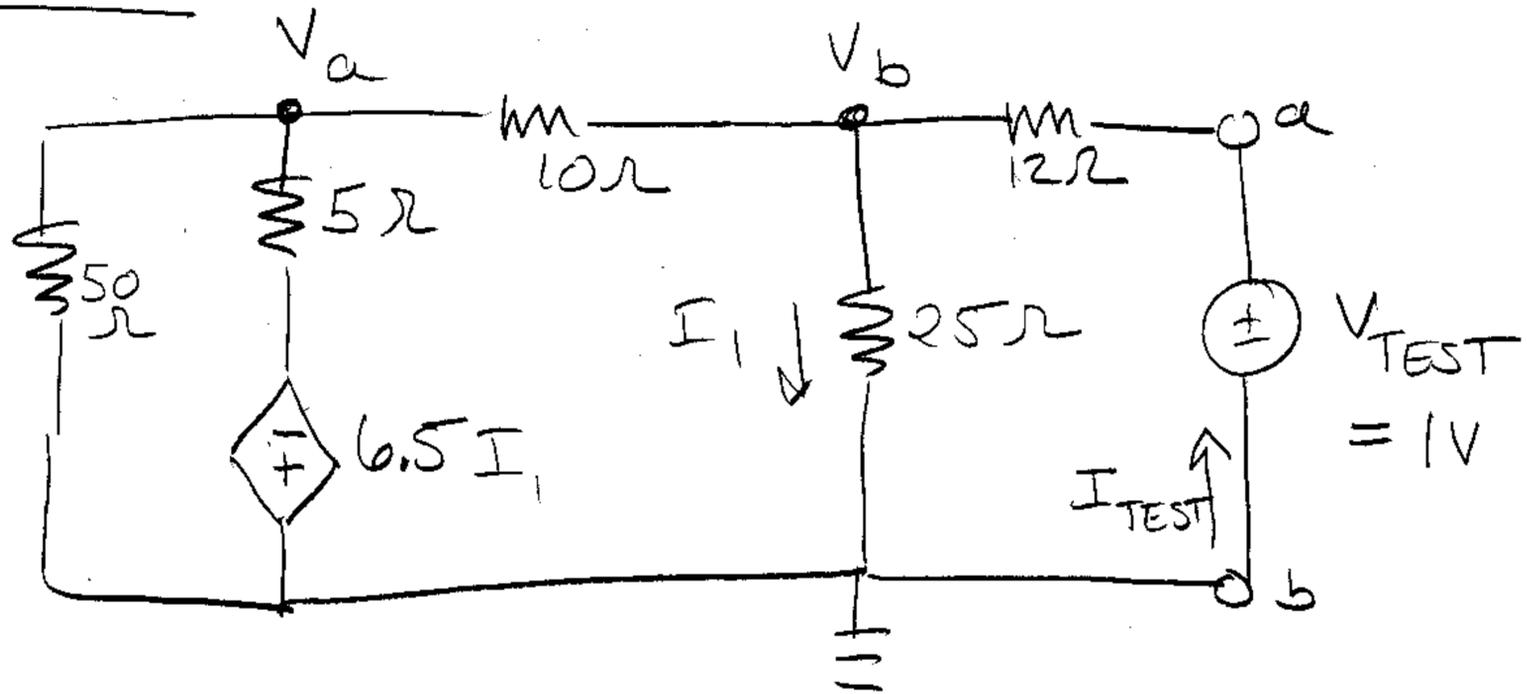

Nodal analysis:

KCL @ V_a : $\frac{V_a}{50\Omega} + \frac{V_a - 6.5I_1}{5\Omega} + \frac{V_a - V_b}{10\Omega} = 0$

$I_1 = V_b / 25$

KCL @ V_b : $\frac{V_b - V_a}{10\Omega} + \frac{V_b}{25\Omega} + \frac{V_b - 1V}{12\Omega} = 0$

$V_a = 60\text{ mV}$ $V_b = 400\text{ mV}$

$I_{TEST} = \frac{V_{TEST} - V_b}{12\Omega} = 50\text{ mA}$

$R_T = R_N = \frac{V_{TEST}}{I_{TEST}} = \frac{1\text{ V}}{50\text{ mA}} = 20\Omega$

$V_T = 0\text{ V}$ $I_N = 0\text{ A}$

Problem 5° No, I cannot find the Thevenin equivalent. This measurement gives me only 1 point on the I-V line. (If there were no independent sources, then the origin would be a 2nd point.)