


EE 40
Homework #4
Solutions

Problem 1:

Inverting amplifier has relationship


$$V_o(t) = -\frac{R_F}{R_1} V_s(t) = \frac{-150 \text{ k}\Omega}{7.5 \text{ k}\Omega} V_s(t) = -20 V_s(t)$$

Rails limit $V_o(t)$ to the interval -5 V to 5 V

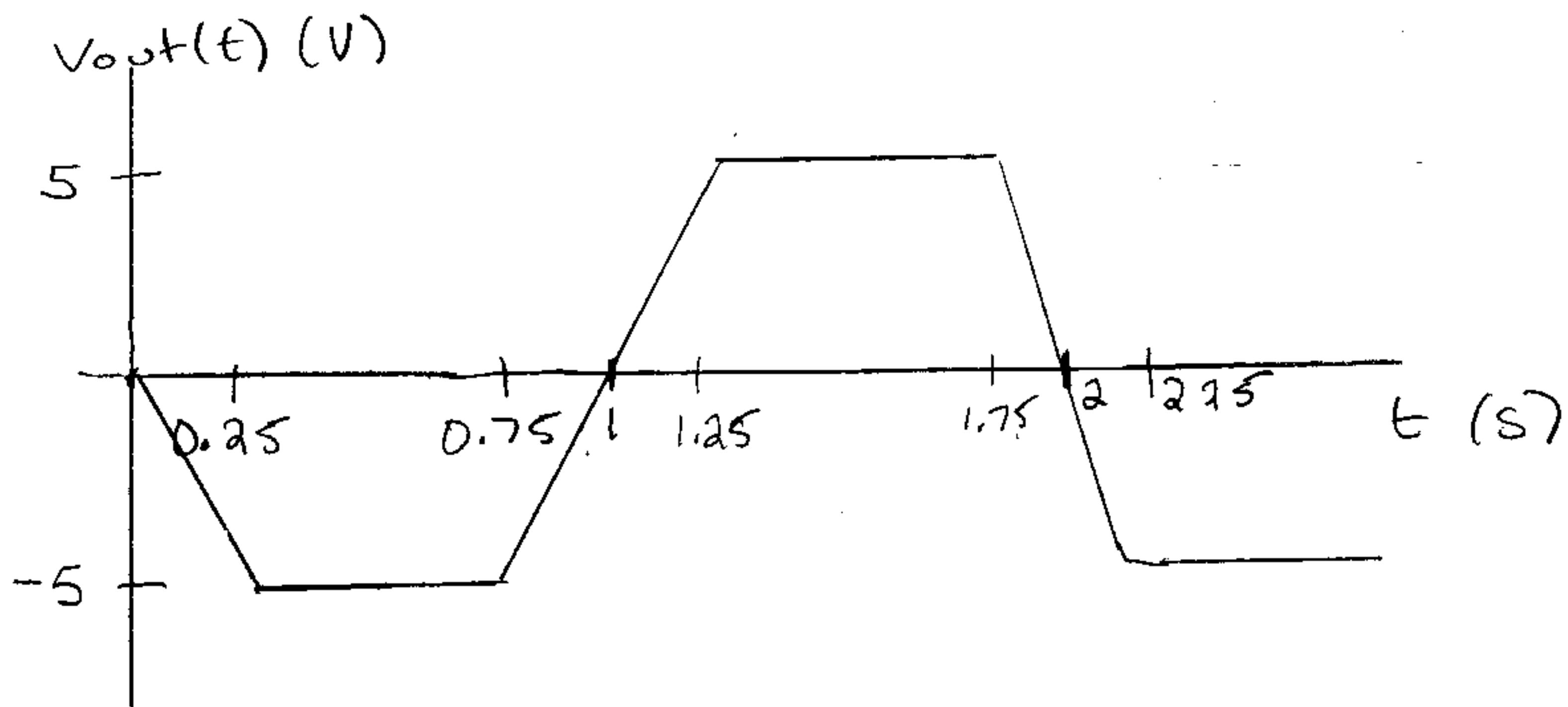

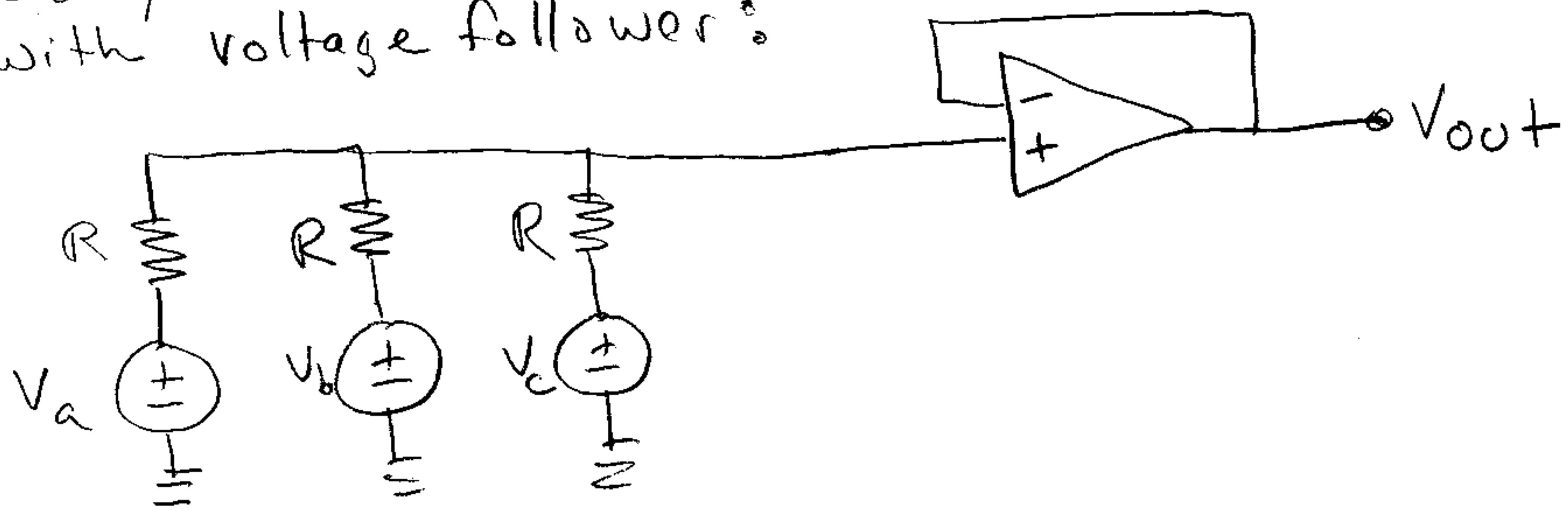
Problem 2:

Easy solution combines Exam 1 Review answer
with voltage follower:




2

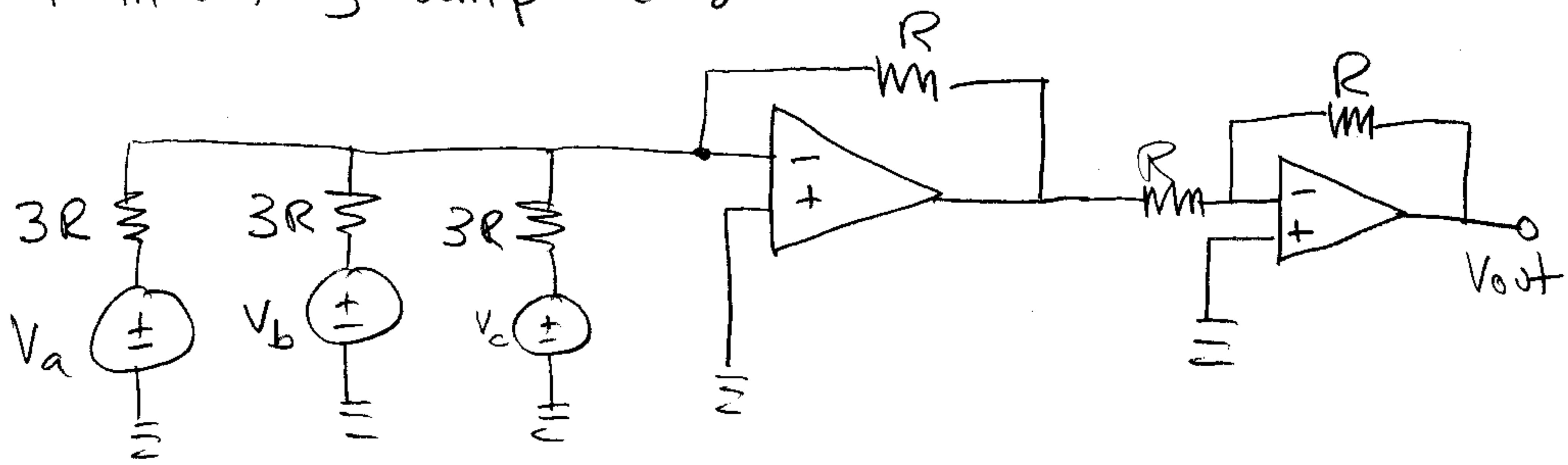
Other solutions involve inverting-summing + inverting amplifier:



Or even the summing amplifier:

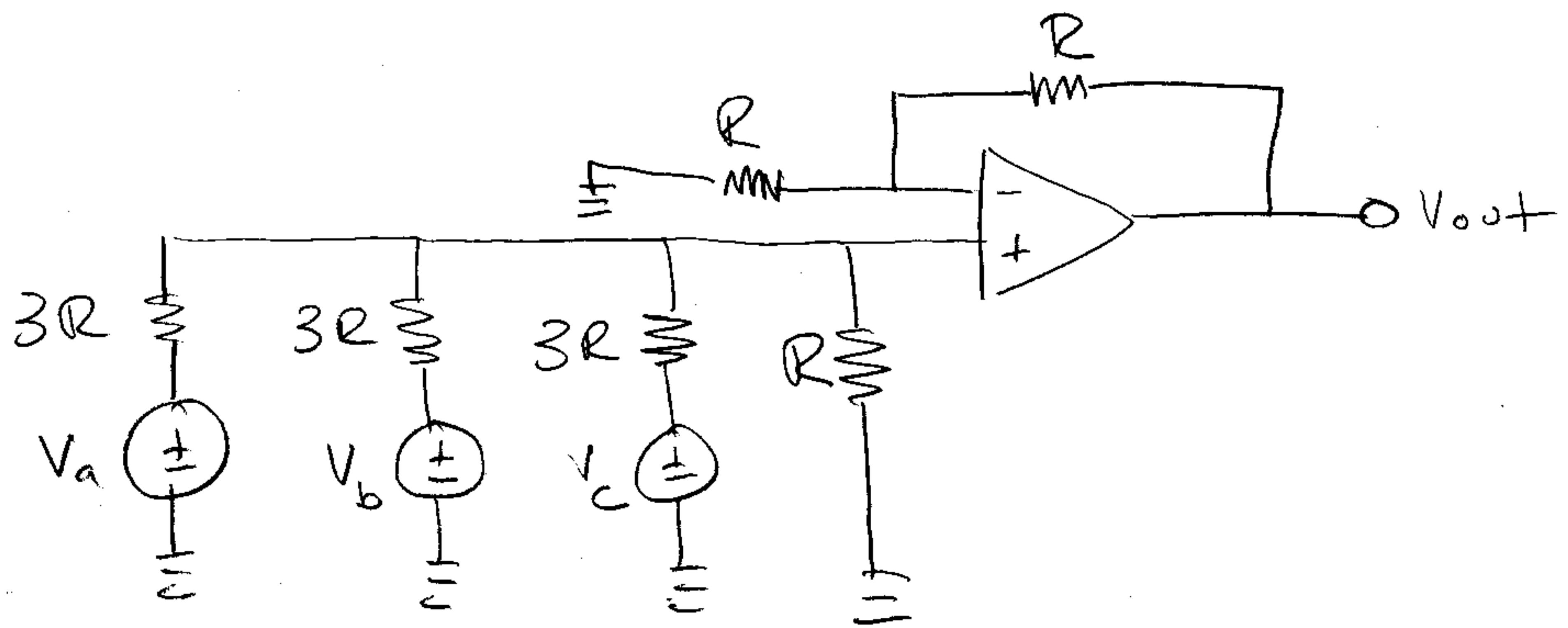

Problem 3°

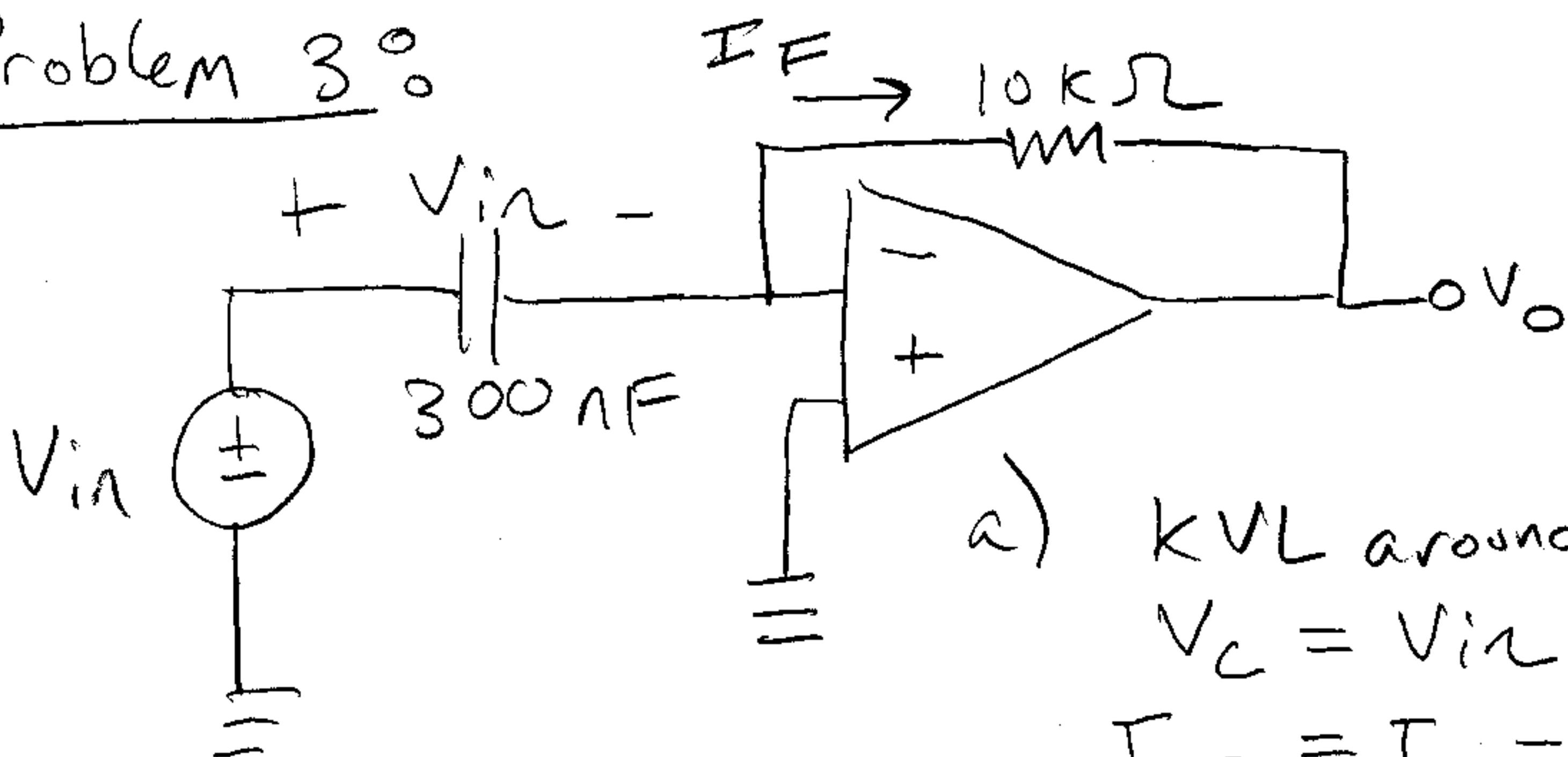

a) KVL around input loop:

$$V_C = V_{in}$$

$$I_F = I_C = C \frac{dV_C}{dE} = C \frac{dV_{in}}{dt}$$

KVL around output loop: $V_o + R I_F = 0$

③



$$V_o = -R F_F = -RC \frac{dV_{in}}{dt} = -3 \times 10^{-3} \frac{dV_{in}}{dt}$$

b)

With $V_{in}(t) = \sin(120\pi t) + 10^6 \sin(10^6 \cdot 120\pi t)$,

$$\frac{dV_{in}}{dt} = 120\pi \cos(120\pi t) + 10^6 \cdot 120\pi \cos(10^6 \cdot 120\pi t)$$
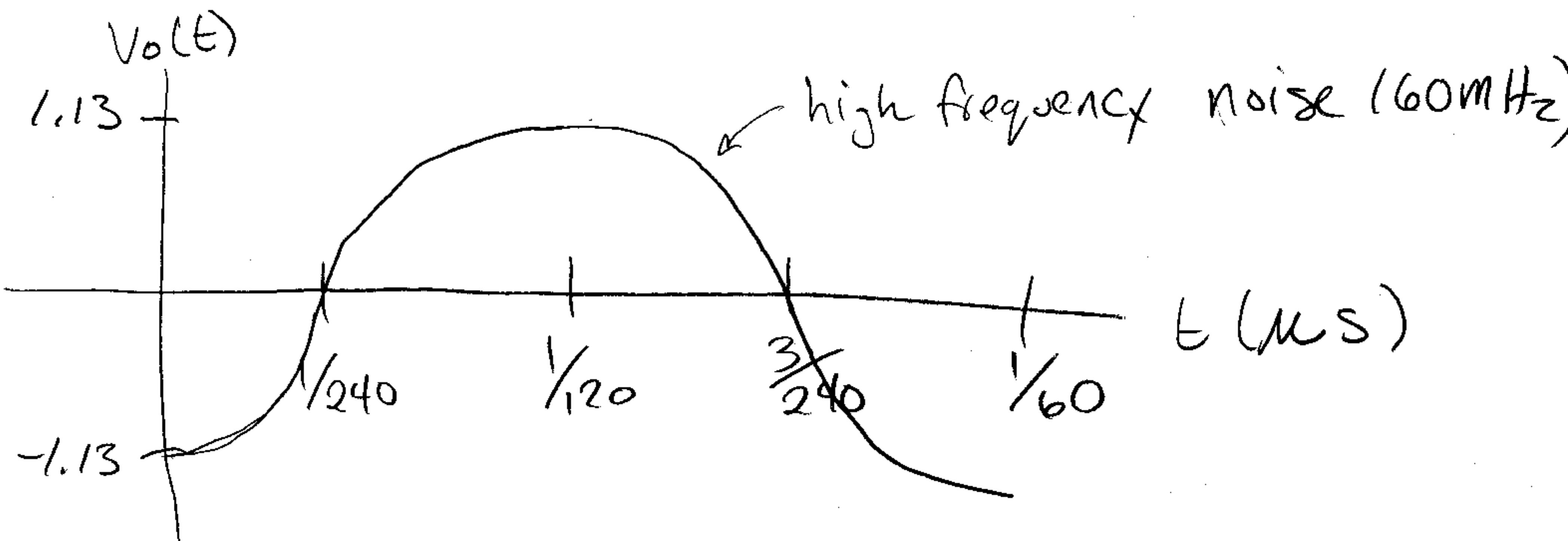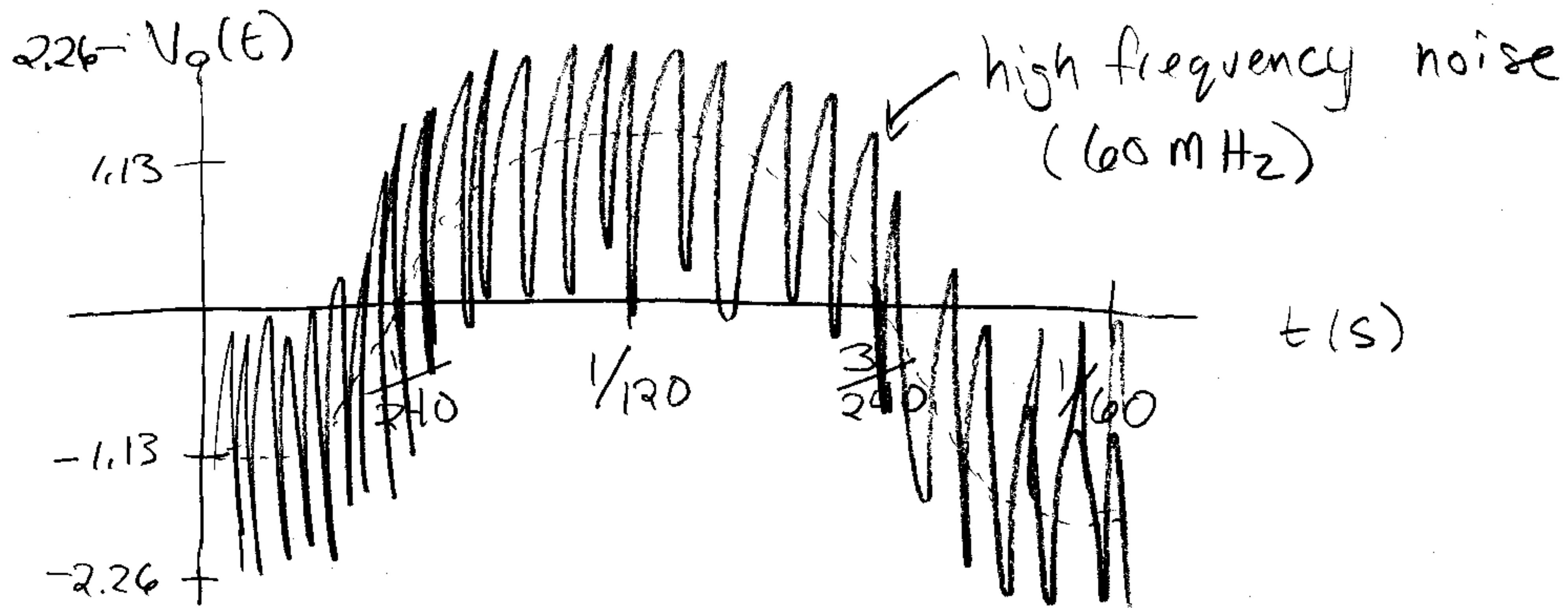
$$V_o(t) = -360\pi \cdot 10^{-3} (\cos(120\pi t) + \cos(10^6 \cdot 120\pi t))$$



4

Problem 4:

The non-inverting amplifier has

$$V_o = \left(1 + \frac{R_F}{R_i}\right) V_{in} = \left(1 + \frac{\alpha \cdot 5000 \Omega}{1000 \Omega}\right) (1V)$$

$$= 1 + 5\alpha \quad \checkmark$$

V_o must be between 5V and -5V.

$$1 + 5\alpha \leq 5$$


$$\alpha \leq 4/5$$

$$1 + 5\alpha \geq -5 \quad \alpha \geq -6/5$$

Problem 5:

a) $\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC = S_1$


b)

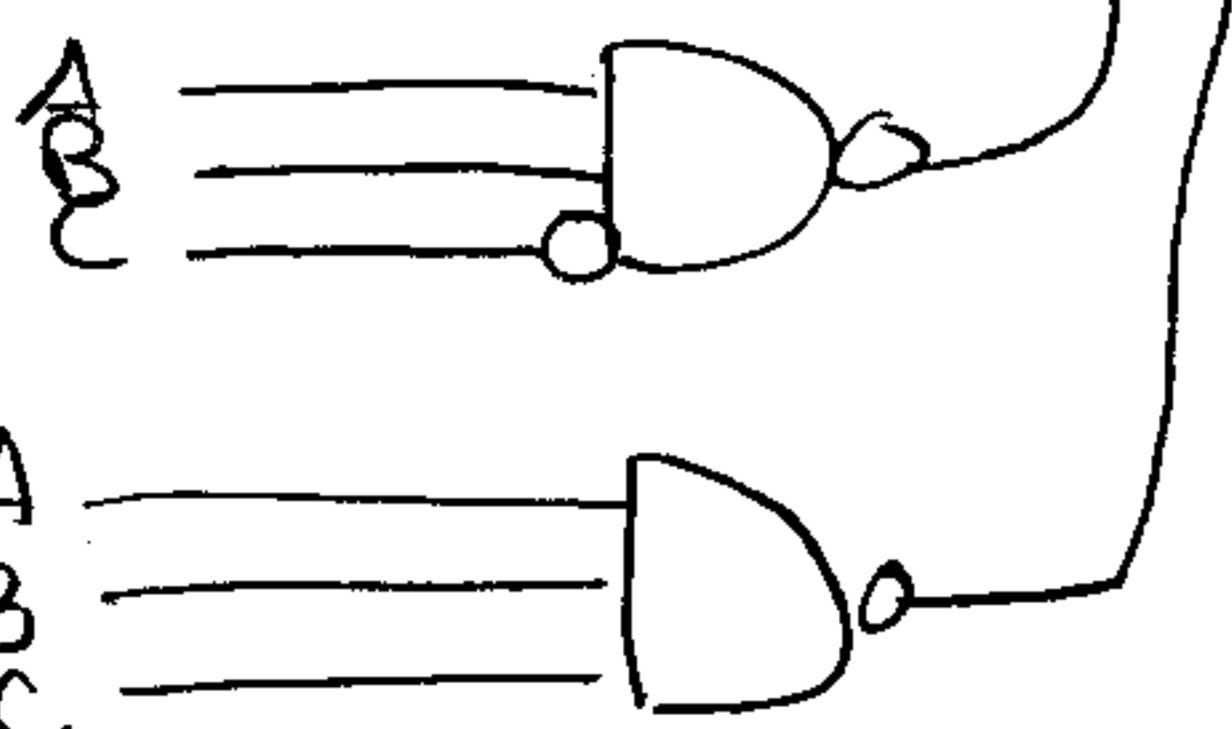

c) Using Karnaugh map technique
(see lecture!)


$$S_1 = AB + BC + AC$$

I can't think of a simpler expression.

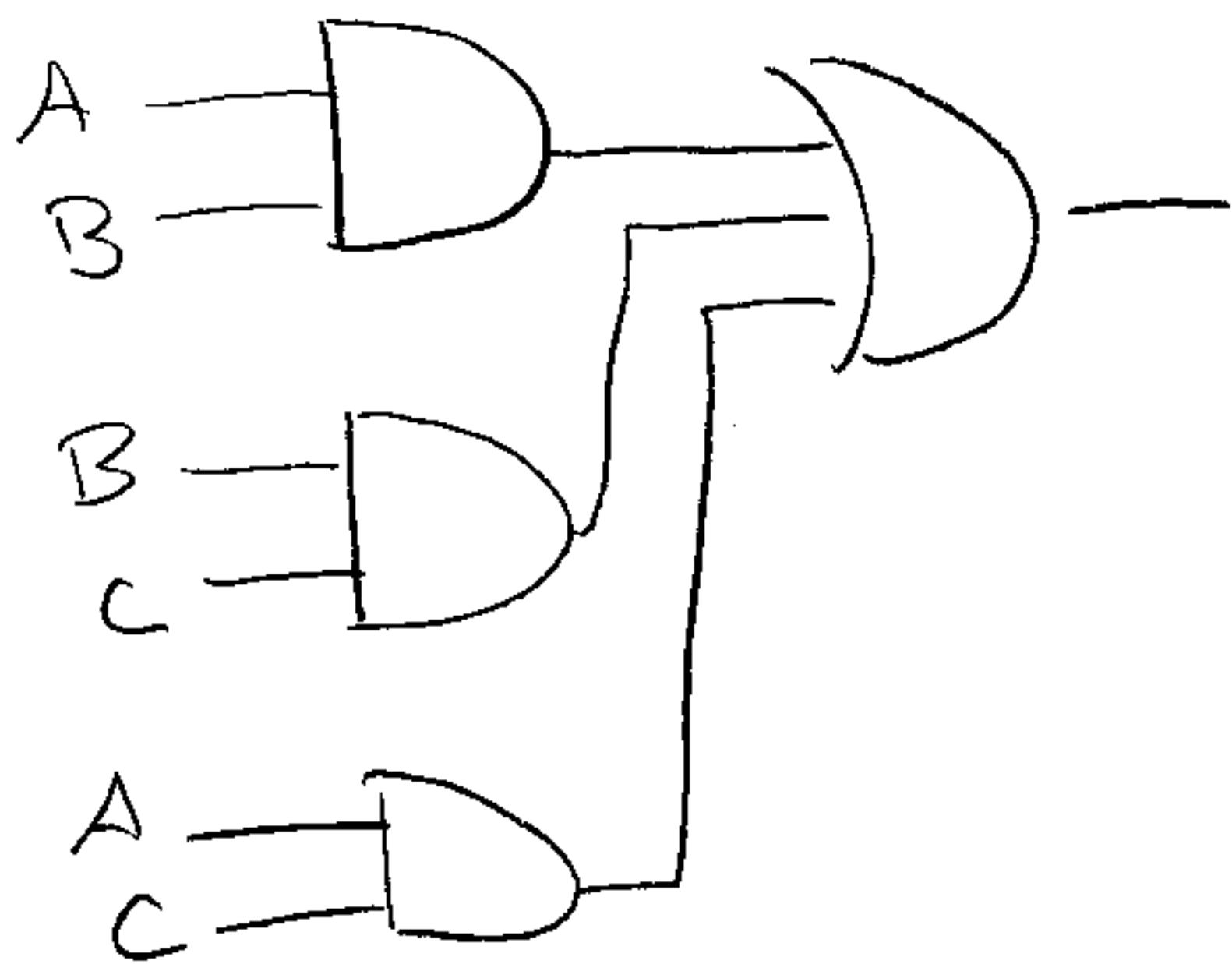

or NAND-NAND version
of the same

Problem 6:

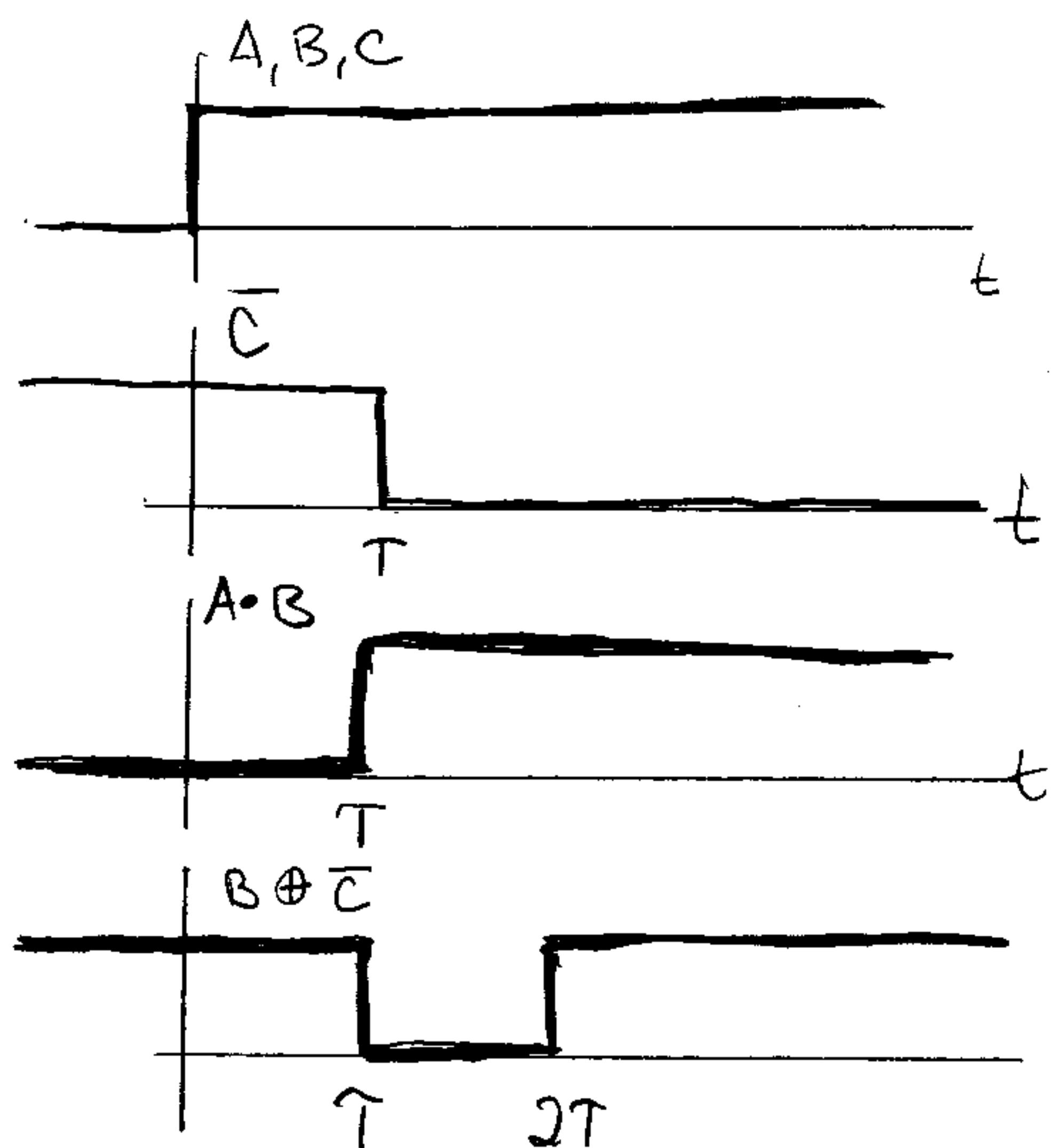

$$F = (A \cdot B) \cdot (B \oplus \bar{C})$$

