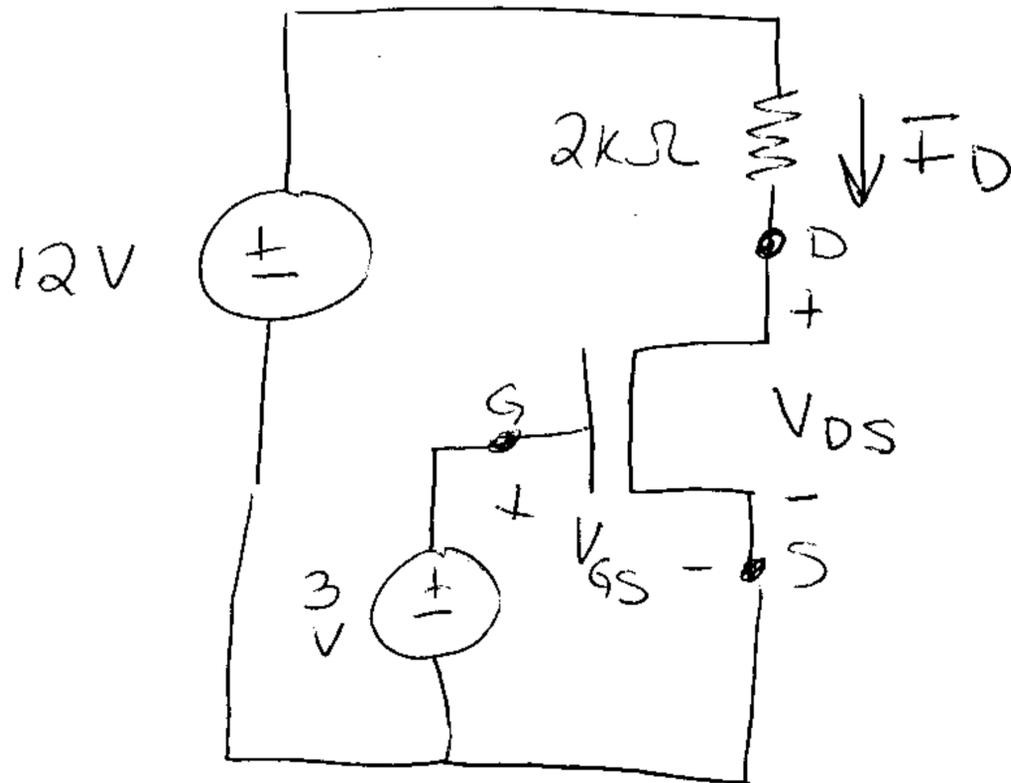


EE 40
Homework 5
Solutions

Problem 1:



$V_{GS} = 3V \Rightarrow$ transistor is not cutoff ($V_{GS} > V_{THN} = 1V$)

Assume saturation (since it is easiest).

$$\begin{aligned} I_D = I_{DSAT} &= \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{THN})^2 \\ &= \frac{1}{2} (1 \text{ mA/V}^2) (3V - 1V)^2 \\ &= 2 \text{ mA} \end{aligned}$$


$$\begin{aligned} V_{DS} &= 12V - 2k\Omega I_D \quad (\text{KVL around outside loop}) \\ &= 12V - 2k\Omega \cdot 2 \text{ mA} = 8V \end{aligned}$$

Check that these answers are valid for saturation:

Saturation requires $V_{DS} \geq V_{GS} - V_{THN}$

Indeed $8V \geq 3V - 1V$ So answers are correct.

Problem 2:

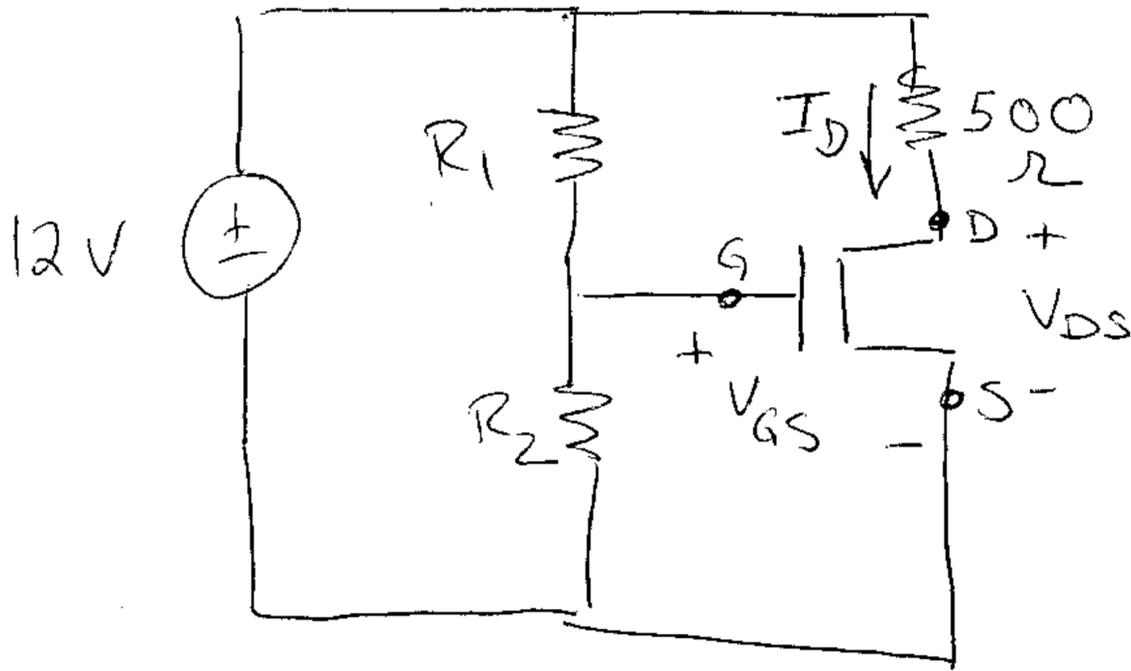

Since no current goes into gate, R_1 & R_2 have same current.

$$V_{GS} = \frac{R_2}{R_1 + R_2} \cdot 12V$$

by voltage division.

Saturation current should be 8mA:

$$8mA = I_{D_{SAT}} = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \cdot 1mA/V^2 (V_{GS} - 1V)^2$$


$$(V_{GS} - 1V)^2 = 16V^2 \Rightarrow V_{GS} = 5V$$

$$5V = V_{GS} = \frac{R_2}{R_1 + R_2} \cdot 12V \Rightarrow \frac{R_2}{R_1 + R_2} = \frac{5}{12}$$

Many solutions possible;

for example, $R_2 = 5k\Omega$, $R_1 = 7k\Omega$.

Problem 3:

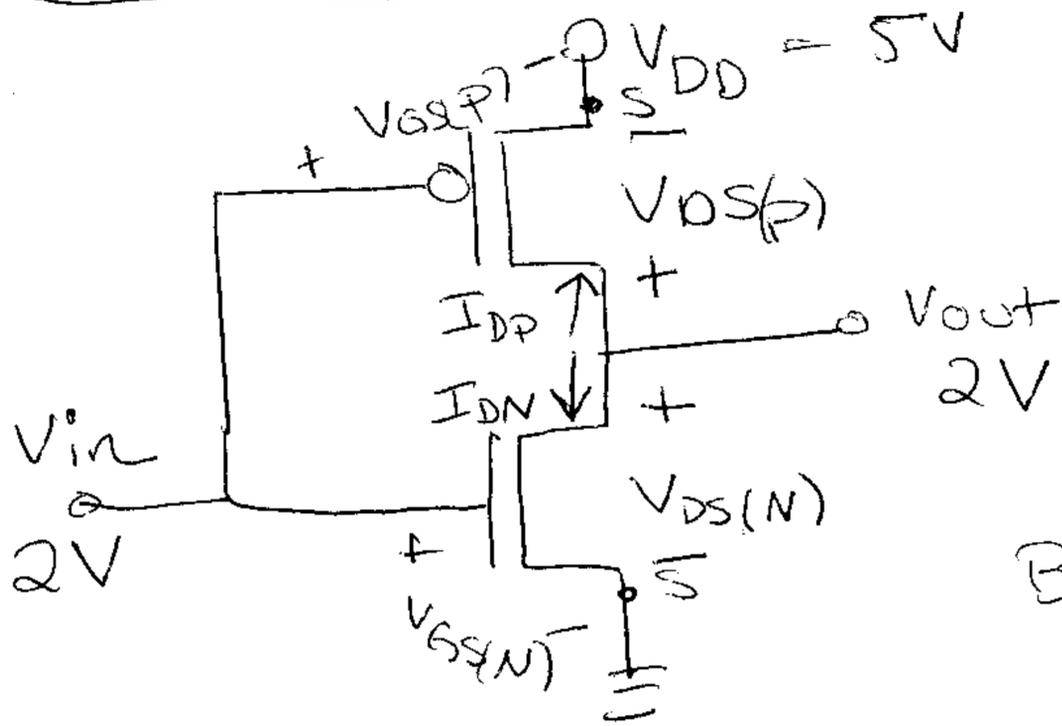

When $V_{in} = V_{out} = 2V$,

$$V_{GSP} = V_{DSP} = -3V$$

$$V_{GSN} = V_{DSN} = 2V$$

Both transistors in saturation.

$$I_{D(N)} = I_{DSAT(N)}$$

$$I_{D(P)} = I_{DSAT(P)}$$

By KCL, $I_{D(P)} + I_{D(N)} = 0 \Rightarrow I_{DN} = -I_{DP}$

$$I_{DSAT(N)} = \frac{1}{2} \frac{W_N}{L_N} \mu_n C_{ox} (V_{GSN} - V_{THN})^2$$

$$= \frac{1}{2} \cdot \frac{1}{2.5 \mu m} \cdot W_N \cdot \frac{50000 \text{ mm}^2}{V_s} \cdot \frac{5 \text{ fF}}{\mu m^2} (2V - 1V)^2$$

$$= 50 W_N$$

$$I_{DSAT(P)} = -\frac{1}{2} \frac{W_P}{L_P} \mu_p C_{ox} (V_{GSP} - V_{THP})^2$$

$$= -\frac{1}{2} \cdot \frac{1}{2.5 \mu m} \cdot W_P \cdot \frac{25000 \text{ mm}^2}{V_s} \cdot \frac{5 \text{ fF}}{\mu m^2} (-3V - -1V)^2$$

$$= -100 W_P$$


$$I_{D(N)} = -I_{D(P)} \Rightarrow I_{DSAT(N)} = -I_{DSAT(P)} \Rightarrow 50 W_N = 100 W_P$$

$\frac{W_N}{W_P} = 2$

Possible answers: $W_N = 2 \mu m$
 $W_P = 1 \mu m$

Problem 4:

(4)

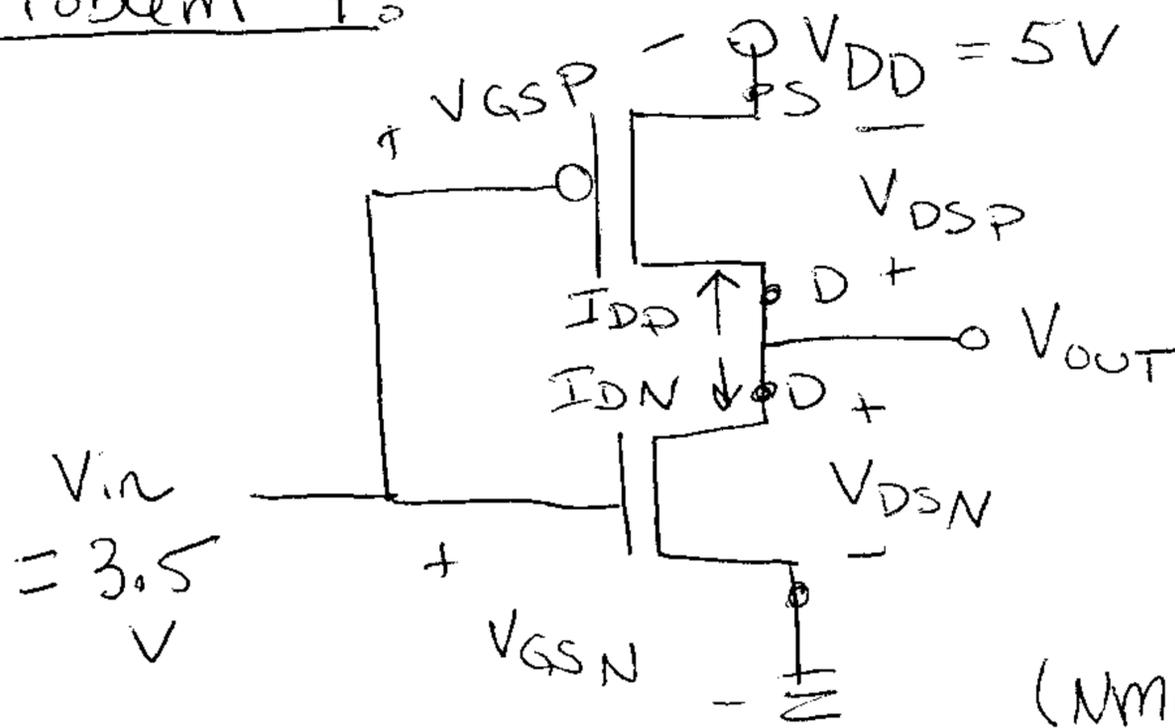

$V_{GS(N)} = 3.5\text{ V}$
 $V_{GS(P)} = -1.5\text{ V}$

$V_{in} = 3.5\text{ V}$

Looks like "Region D" (NMOS fully on, PMOS barely on)

Assume PMOS saturation, NMOS triode

$$I_{DP} = I_{DSATP} = -\frac{1}{2} \frac{W}{L} \mu_p C_{ox} (V_{GSP} - V_{THP})^2$$

$$= -\frac{1}{2} \cdot 1\text{ mA/V}^2 \cdot (-1.5\text{ V} - -1\text{ V})^2$$

$I_{DP} = -125\text{ }\mu\text{A}$

$$I_{DN} = \frac{W}{L} \mu_n C_{ox} (V_{GSN} - V_{THN} - \frac{V_{DSN}}{2}) V_{DSN}$$

$$= 1\text{ mA/V}^2 (3.5\text{ V} - 1\text{ V} - \frac{V_{DSN}}{2}) V_{DSN}$$

By KCL, $I_{DN} = -I_{DP}$


$-I_{DP} = 125\text{ }\mu\text{A} = I_{DN} = 1\text{ mA/V}^2 (2.5\text{ V} - \frac{V_{DSN}}{2}) V_{DSN}$

Solutions: $V_{DSN} = \{0.05\text{ V}, 4.95\text{ V}\}$

4.95 V impossible for triode; $4.95\text{ V} \nless V_{GSN} - V_{THN} = 2.5\text{ V}$

$V_{DSN} = 0.05\text{ V}$ $V_{DSP} = V_{DSN} - V_{DD} = -4.95\text{ V}$

Problem 5

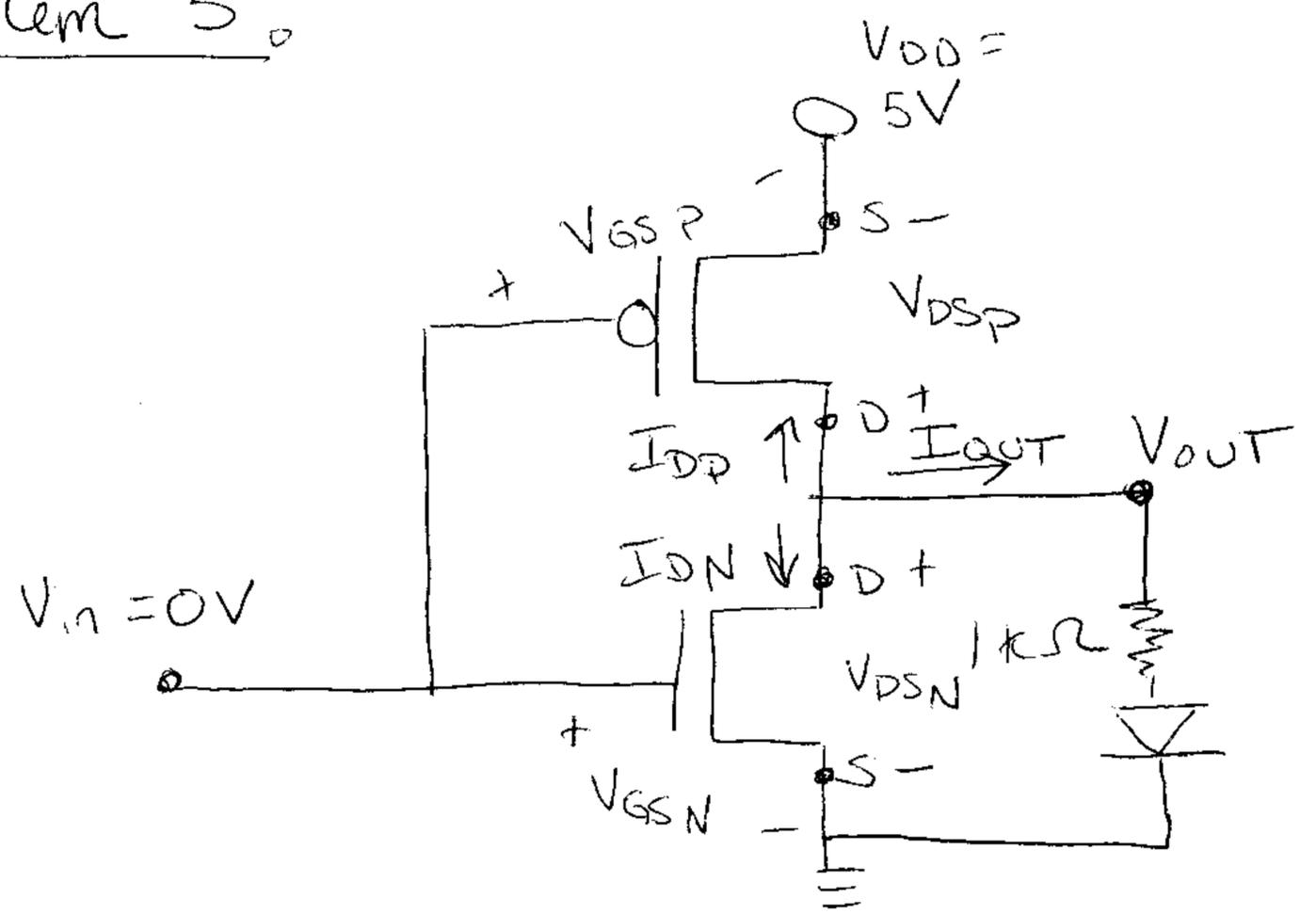

NMOS cutoff! $V_{GSN} = 0V < V_{THN}$
 PMOS "fully on" $V_{GSP} = -5V$

PMOS triode happens to be the right guess, but it's hard to guess this.

First I will show that PMOS triode is correct. Then I will show why PMOS saturation is wrong.

PMOS triode (Also guess diode forward biased)

$$I_{DP} = -\frac{W}{L} \mu_p C_{ox} (V_{GSP} - V_{THP} - \frac{V_{DSP}}{2}) V_{DSP}$$

$$= -1mA/V^2 (-5V - -1V - \frac{V_{DSP}}{2}) V_{DSP}$$

$$I_{DP} + I_{DN} + I_{OUT} = 0 \quad \text{by KCL}$$

$$I_{DP} = -I_{OUT} \quad \text{①}$$

$$I_{OUT} = \frac{V_{DSN} - 0.7}{1K} \quad \text{②}$$

6

$$V_{DSN} = V_{DD} + V_{DSP} = 5V + V_{DSP}$$

(3)

Plug equations (1), (2) and (3) into I_{Dp} triode eqn

$$\frac{5V + V_{DSP} - 0.7V}{1k\Omega} = -1mA/\sqrt{2} \left(-4V - \frac{V_{DSP}}{2} \right) V_{DSP}$$

Solutions: $V_{DSP} = \{ -9.05V, -0.95V \}$

$$V_{DSP} = -9.05V < V_{GSp} - V_{THp} = -4V$$

so this is impossible for triode mode.

$V_{DSP} = -0.95V$ is possible for triode mode.

$$I_{Dp} = -I_{out} = -\frac{5V + V_{DSP} - 0.7V}{1k\Omega} = -3.35 \text{ mA}$$

Power absorbed by PMOS transistor:

$$P_{Pmos} = I_{Dp} V_{DSP} = (-3.35 \text{ mA})(0.95V) = 3.18 \text{ mW}$$

Power absorbed by NMOS transistor:

$$P_{Nmos} = I_{DN} V_{PSN} = 0 \text{ W} \quad (I_{DN} = 0A \text{ since NMOS cutoff})$$

Power absorbed by resistor:

$$P_R = I^2 R = (3.35 \text{ mA})^2 \cdot 1k\Omega = 11.2 \text{ mW}$$

Power absorbed by diode:

$$P_D = VI = 0.7V \cdot 3.35 \text{ mA} = 2.34 \text{ mW}$$

Now to show PMOS saturation is wrong:

If PMOS saturation,

$$I_{Dp} = -\frac{1}{2} \frac{W}{L} \mu_p C_{ox} (V_{GSp} - V_{THp})^2$$

$$= -\frac{1}{2} 1mA / \sqrt{2} (5V - -1V)^2 = 8mA$$

Thus current must flow in the branch with the resistor + diode (since NMOS cutoff $\Rightarrow I_{DN} = 0A$).

So diode is forward biased. (Voltage 0.7V.)

Resistor voltage is $8mA \cdot 1k\Omega = 8V$.

$$V_{DSp} = 8V + 0.7V - 5V = 3.7V$$

Which is impossible for saturation;

V_{DSp} must be less than $V_{GSp} - V_{THp} = -4V$.