

## **Lecture 15**

### **Diode Circuits**

Today we will analyze a variety of diode circuits that are used for different purposes.

#### **Different Model, Different Result**

We will compare the results obtained using up to 3 different diode models: ideal model, large-signal model, and small-signal model.

- ❖ If we skip analysis using a particular model due to time constraints, do the analysis at home for practice!

#### **What Happens When Diode Direction is Reversed?**

Each circuit behaves somewhat differently when the diode's polarity is reversed.

- ❖ Practice these analyses for each circuit, reversing the directions of the diodes.




#### **Model Parameters**

For the analyses to follow, we will assume  $V_F = 0.7 \text{ V}$  and  $R_D = 20 \Omega$ .

**Circuit 1: Half-Wave Rectifier**

Let  $V_s(t) = \sin(t)$ ,  $R = 20 \Omega$ .




Sketch  $V_{out}(t)$  for the ideal diode model, large-signal model, and small-signal model.

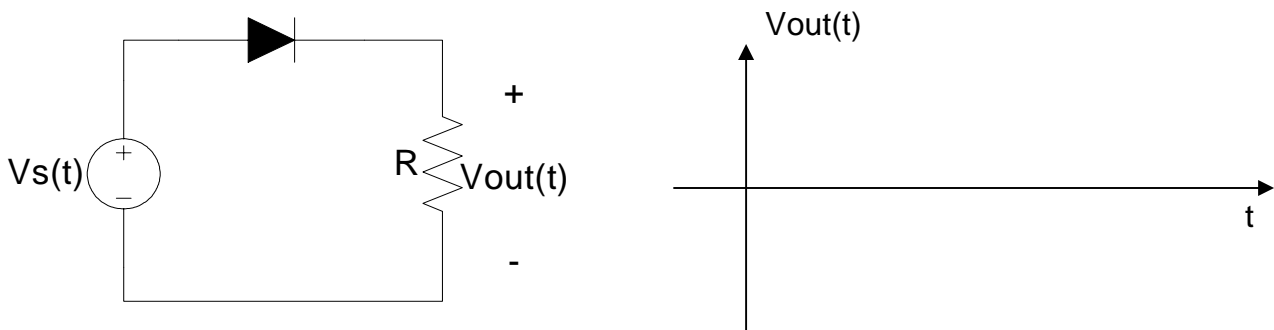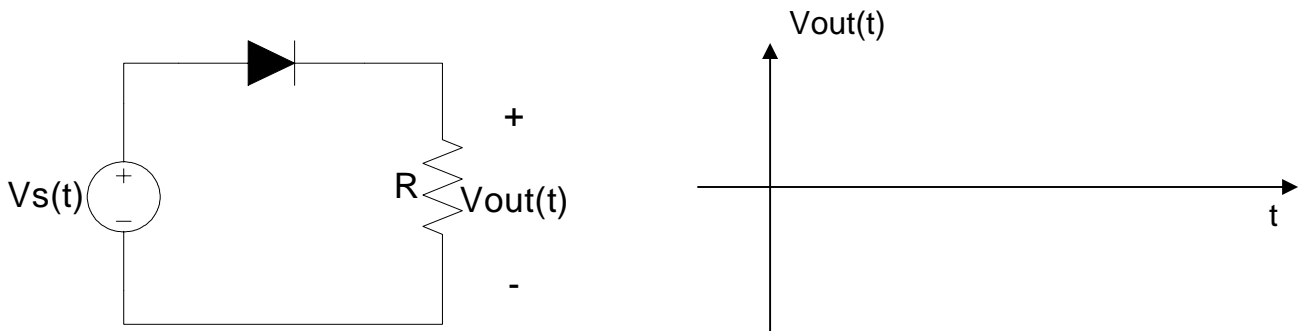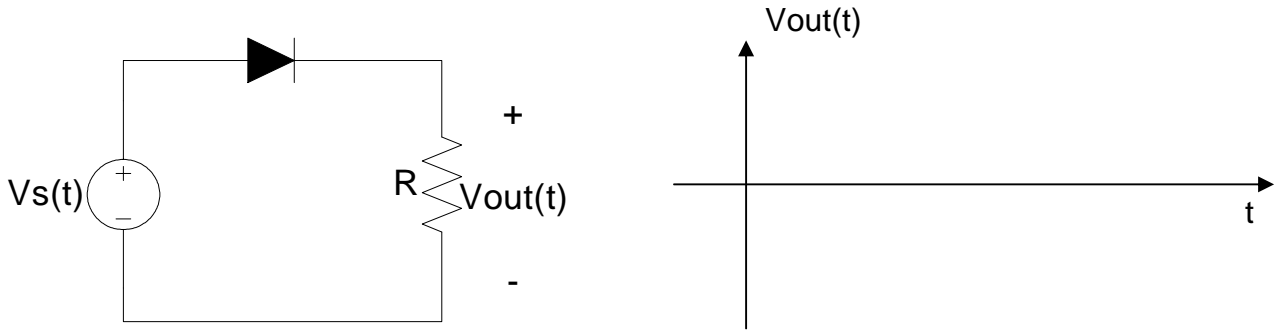

**Circuit 2: Clipper**

Let  $V_s(t) = \sin(t)$ ,  $R = 20 \Omega$ .







Sketch  $V_{out}(t)$  for the ideal diode model, large-signal model, and small-signal model.

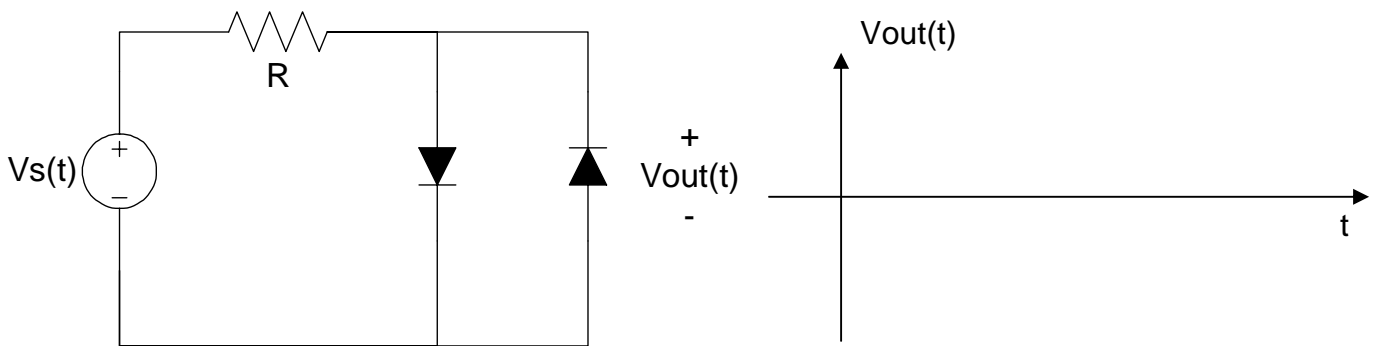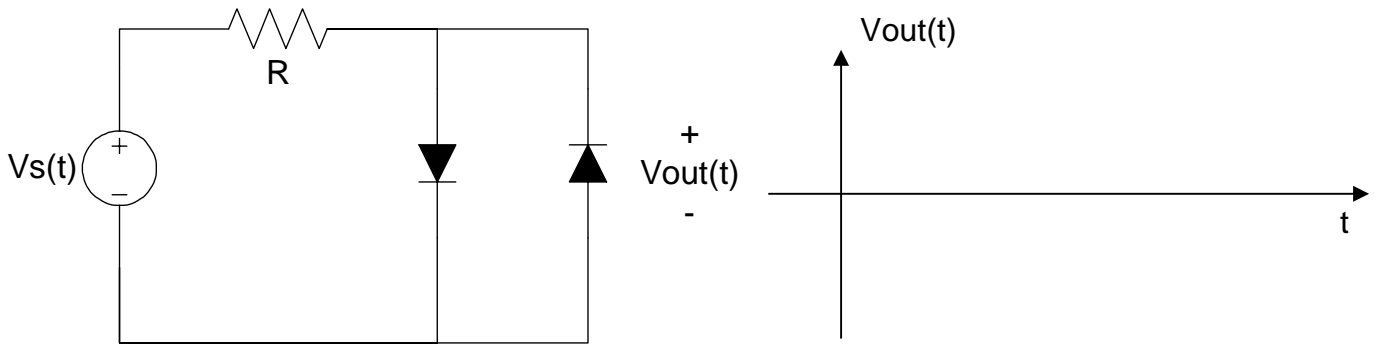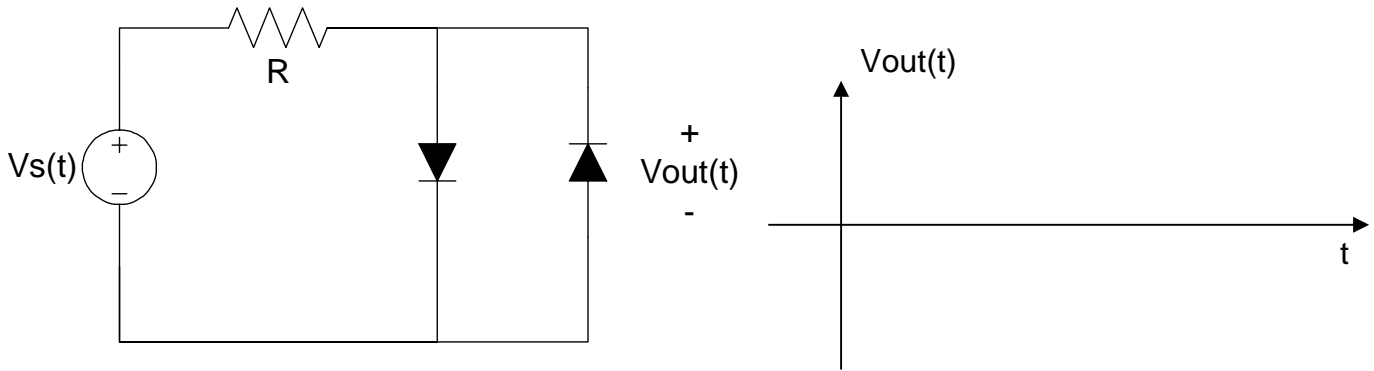

**Circuit 3: Full-Wave Rectifier**

Let  $V_s(t) = 2 \sin(t)$ ,  $R = 20 \Omega$ .



Sketch  $V_{out}(t)$  for the ideal diode model, large-signal model, and small-signal model.

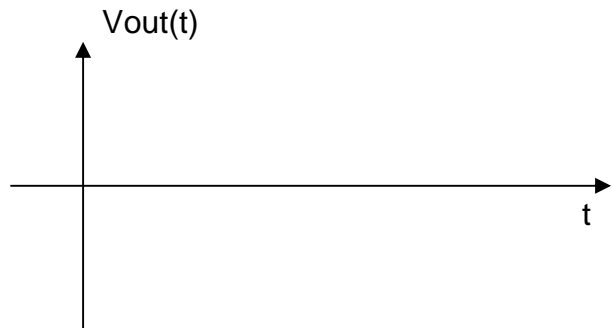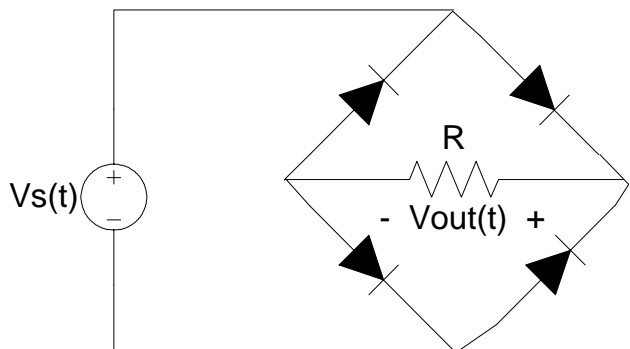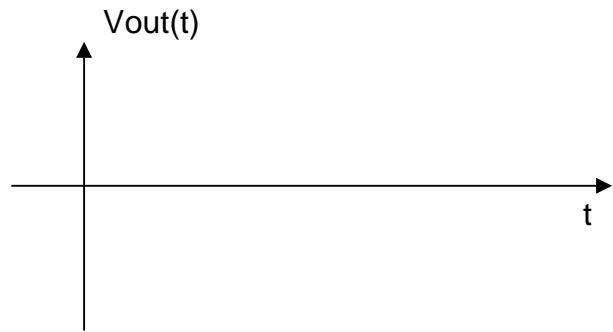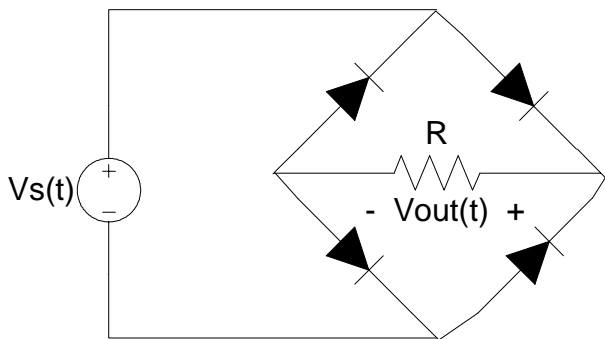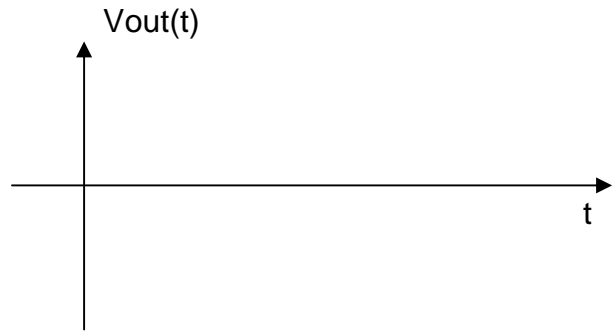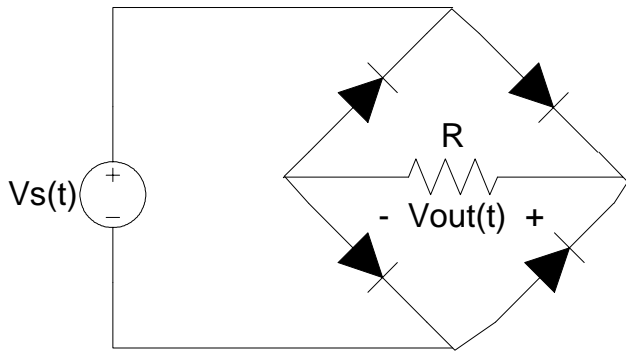

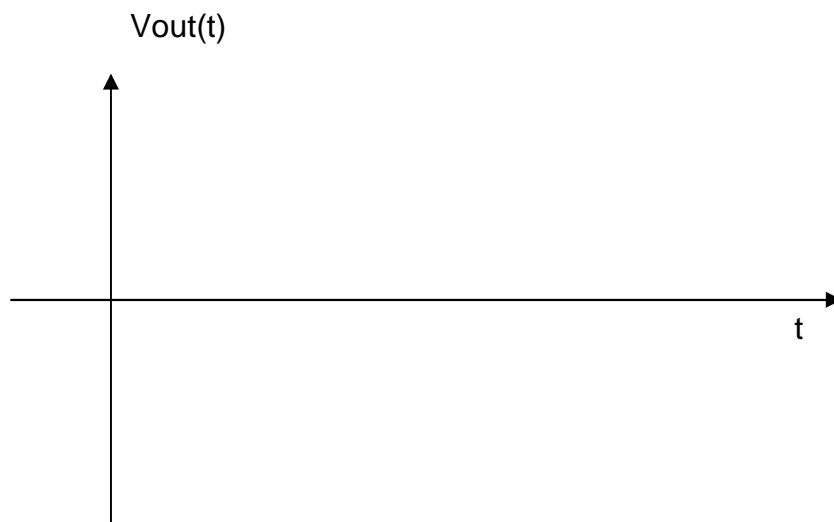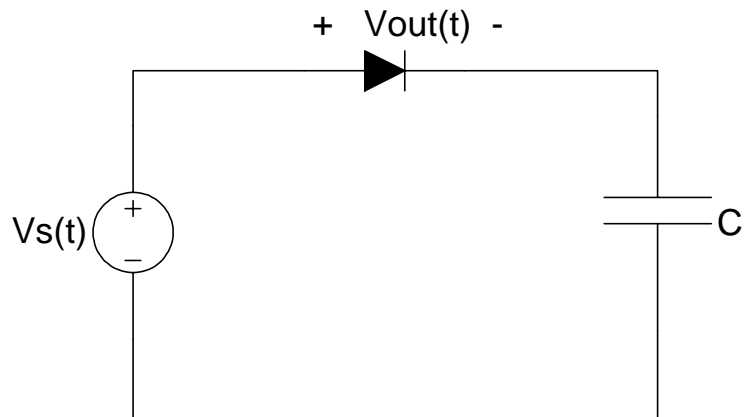**Circuit 4: Clamper (DC Restorer)**

Let  $V_s(t)$  be a square wave with amplitude 1 V, period 1 s, duty cycle 50%, and DC offset 0 V.  
Let  $C = 500 \mu\text{F}$ .

Sketch  $V_{out}(t)$  for the small-signal diode model.





- ❖ What happens if the ideal or large signal diode model is used to analyze this circuit?

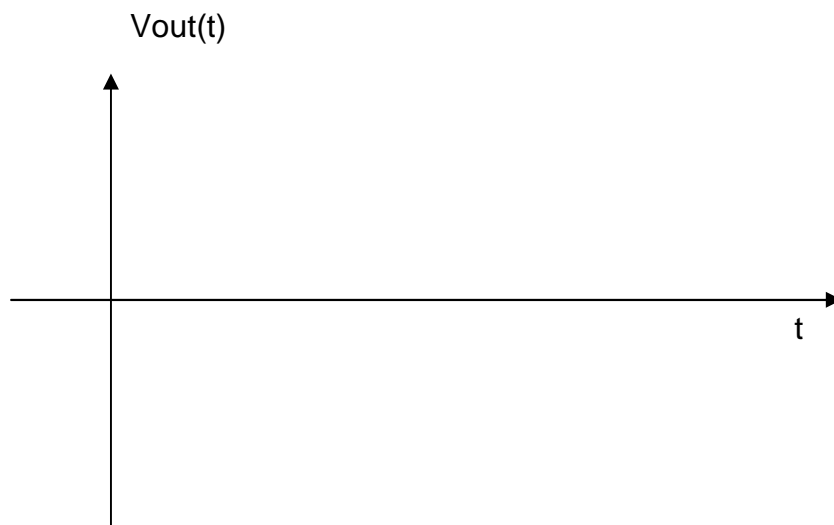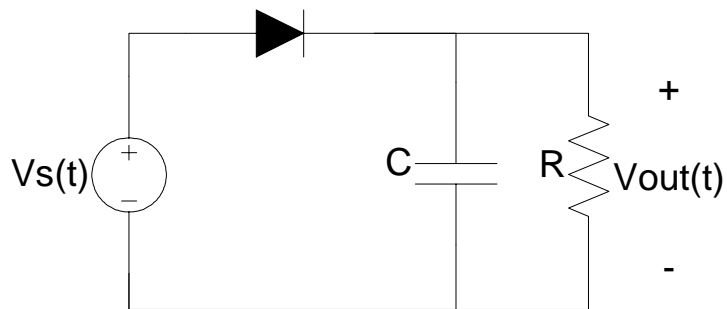**Circuit 5: Half-Wave Rectifier with Filter Capacitor (Peak or Envelope Detector)**

Let  $V_s(t)$  be a square wave with amplitude 1 V, period 1 s, duty cycle 50%, and DC offset 0 V.  
Let  $C = 500 \mu\text{F}$  and  $R = 10 \text{ k}\Omega$ .

Sketch  $V_{out}(t)$  for the small-signal diode model.



- ❖ What happens if the ideal or large signal diode model is used to analyze this circuit?
- ❖ What values should  $R$  and  $C$  take to make the circuit function as a peak detector ( $V_{out}(t)$  is highest voltage achieved by  $V_s(t)$  up until that time  $t$ )?
- ❖ What values should  $R$  and  $C$  take to make the circuit function as an envelope detector ( $V_{out}(t)$  approximately connects the peaks of  $V_s(t)$ )?