

Name: _____
Student ID: _____
Name: _____
Student ID: _____
Section: _____
Date: _____

UNIVERSITY OF CALIFORNIA, BERKELEY
EE40: Introduction to Microelectronic Circuits

Diodes Report

Half Wave Rectifier

- 2a) Measure V_T when the input is Frequency = 1KHz, $V_{pp} = 5V$, Offset = 0.
- 2b) What happens when you lower V_{pp} ?
- 2c) What happens if you use a negative offset?
- 2d) What happens to the output if you make the input $V_{pp} = 0.5V$ and you increase the offset = 0.5V.
- 2e) What happens if you lower the frequency of the function generator?
- 2f) What happens as you vary the resistance on the rheostat?
- 2g) Do different color LED's have different threshold voltages?
- 3) Replace the LED with a 1N914 diode and measure the new threshold voltage.
Is it different?

Diode Logic

- 2) $R_s =$
3) OR Gate

A (V)	B (V)	C (V)
0	0	
0	5	
5	0	
5	5	

- 4) AND Gate

A (V)	B (V)	C (V)
0	0	
0	5	
5	0	
5	5	

- 5) Chained

A _{OR} (V)	B _{OR} (V)	B _{AND} (V)	C (V)
0	0	0	
0	0	5	
0	5	0	
0	5	5	
5	0	0	
5	0	5	
5	5	0	
5	5	5	

- 6) Does it still perform normally? Why or why not?