
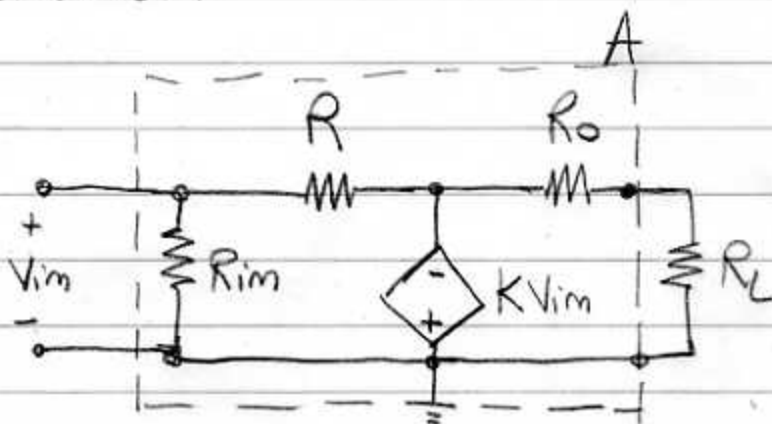


1) Consider the following circuit

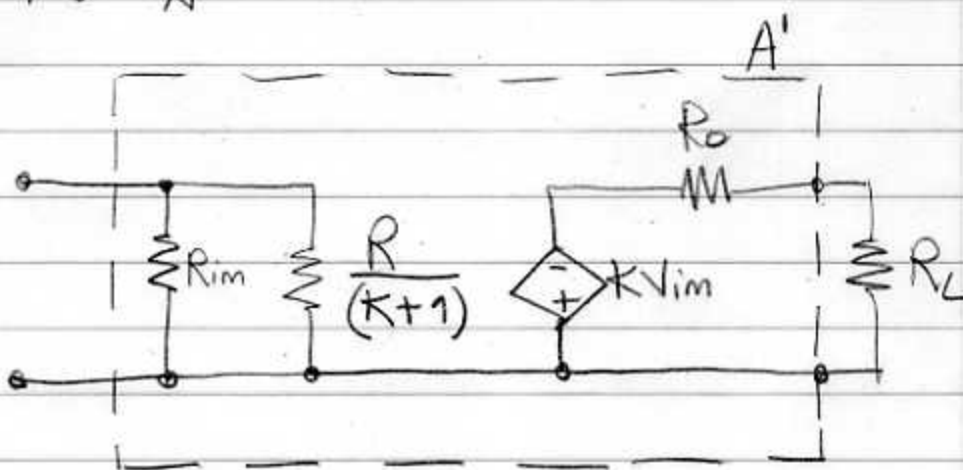


Prove that  $A$  is equivalent, from the point of view of  $V_{in}$ , to  $A'$



(This is known as Miller effect. John M. Miller, 1918)


1)

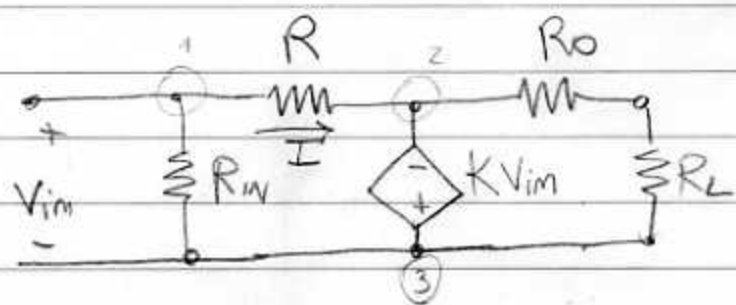

$$I = \frac{(V_{im} + K V_{im})}{R} = \frac{V_{im} (1 + K)}{R}$$

$$\frac{V_{im}}{I} = \frac{R}{K + 1}$$

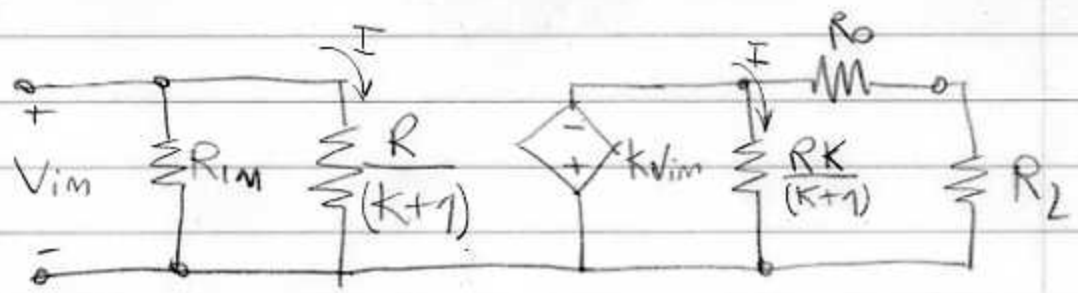
We want to add two elements, one between node 1 and 3 and the other between 2 and 3 in order to have the same currents.



↑ the Miller theorem

2)

PLANAR CIRCUITS

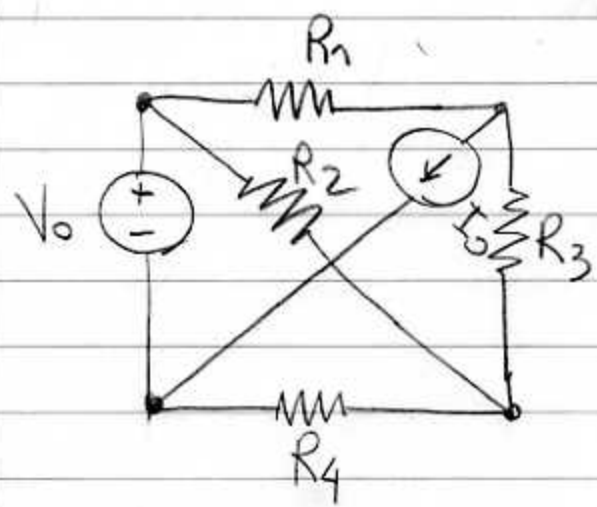



$R_1 = R_2 = 1 \Omega$   
 $R_3 = R_4 = 2 \Omega$   
 $I_0 = 2 A$   
 $V_0 = 1 V$

Solve the circuit using mesh current analysis


- 2.1) How many nodes do you have?
- 2.2) How many branches?
- 2.3) How many branches are going to be in the Tree?
- 2.4) How many branches are going to be in the cotree?
- 2.5) How many equations will you have?

After solving the circuit, try to understand what is happening, how currents are flowing!


2)

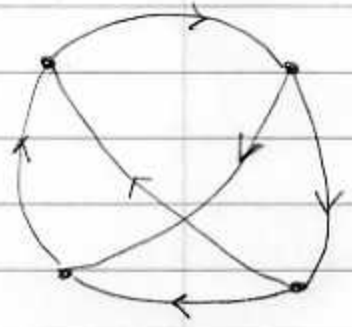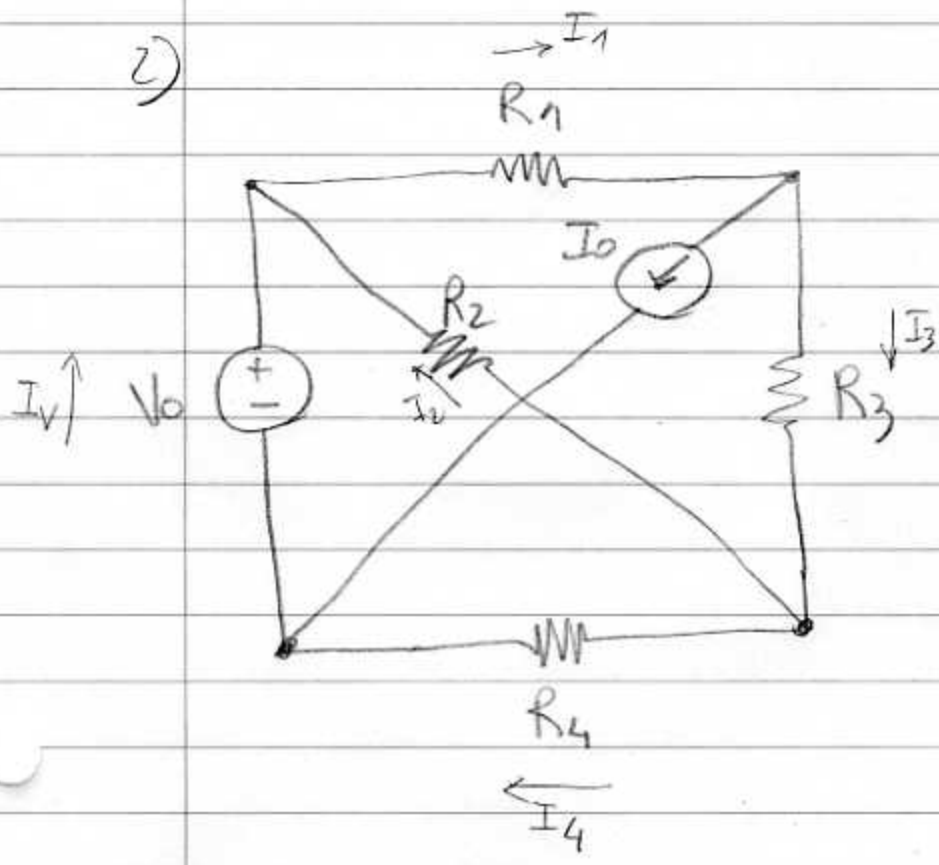

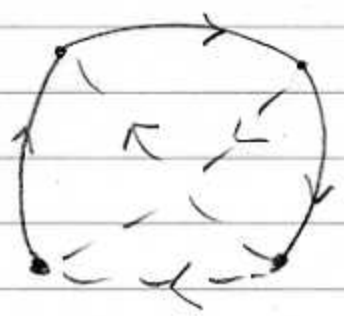A smart choice is to have the current source in the cotree because it is going to fix a value for the loop-current.



— tree  
--- co-tree

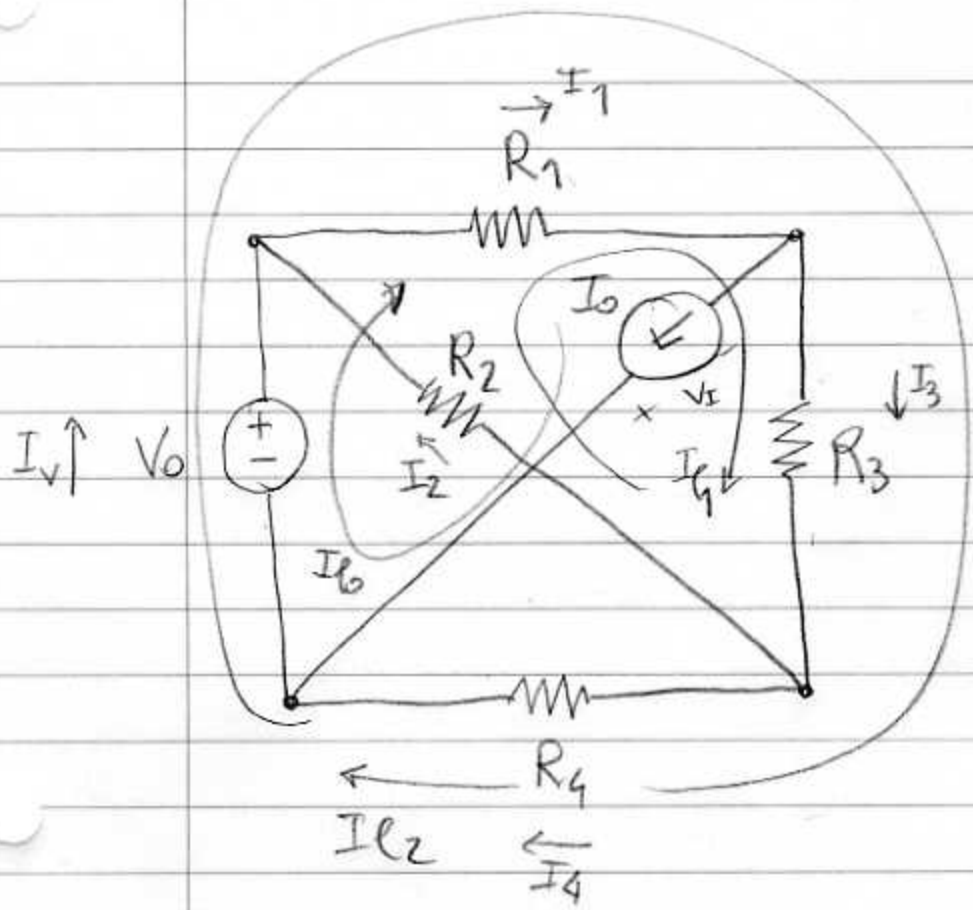

- 2.1) 4 (N)
- 2.2) 6 (R)
- 2.3)  $4 - 1 = 3$  (N-1)
- 2.4)  $6 - 3 = 3$  (R - (N-1))
- 2.5) 3

$$\left\{ \begin{array}{l} -V_0 + R_1 I_{e_0} + R_1 I_{e_2} + R_1 I_{e_1} - V_I = 0 \\ I_{e_1} (R_1 + R_2 + R_3) + I_{e_2} (R_1 + R_3) + I_{e_0} R_1 = 0 \\ -V_0 + I_{e_2} (R_1 + R_3 + R_4) + I_{e_0} R_1 + I_{e_1} R_3 = 0 \\ I_{e_0} = I_0 \end{array} \right.$$

$$\begin{cases} -V_0 + R_1 I_0 + R_1 I_{e1} + R_1 I_{e2} - V_I = 0 \\ I_0 R_1 + I_{e1} (R_1 + R_2 + R_3) + I_{e2} (R_1 + R_3) = 0 \\ -V_0 + I_0 R_1 + I_{e1} (R_1 + R_3) + I_{e2} (R_1 + R_3 + R_4) = 0 \end{cases}$$

$$\begin{cases} I_{e1} + I_{e2} - V_I = -1 \\ 4I_{e1} + 3I_{e2} = -2 \\ 3I_{e1} + 5I_{e2} = -1 \end{cases}$$

$$\begin{bmatrix} 4 & 3 \\ 3 & 5 \end{bmatrix} \begin{bmatrix} I_{e1} \\ I_{e2} \end{bmatrix} = \begin{bmatrix} -2 \\ 1 \end{bmatrix}$$

$$I_{e1} = \frac{-1 - 5I_{e2}}{3} = -\frac{1}{3} - \frac{5}{3}I_{e2}$$

$$-\frac{4}{3} - \frac{20}{3}I_{e2} + 3I_{e2} = -2 \Rightarrow -\frac{4}{3} - \frac{11}{3}I_{e2} = -2$$

$$\Rightarrow I_{e2} = \frac{2}{3} \cdot \frac{3}{11} = \frac{2}{11}$$

$$I_{e1} = -\frac{1}{3} - \frac{5}{3} \cdot \frac{2}{11} = -\frac{1}{3} - \frac{10}{33} = \frac{-11 - 10}{33} = \frac{-21}{33} = \frac{-7}{11}$$

best

read

$$-\frac{7}{11} + \frac{2}{11} - V_I = -1 \Rightarrow -V_I = -1 + \frac{5}{11} \Rightarrow V_I = \frac{6}{11}$$

$$I_V = 2 + I_{C2} = 2 + \frac{2}{11} = \frac{24}{11}$$

$$I_1 = I_0 + I_{E1} + I_{C2} = 2 + \frac{2}{11} - \frac{7}{11} = \frac{22 + 2 - 7}{11} = \frac{17}{11}$$

$$I_2 = I_{E1} = -\frac{7}{11}$$


$$I_3 = I_{C2} + I_{E1} = -\frac{5}{11}$$

$$I_4 = I_{E2} = \frac{2}{11}$$

$$V_I = \frac{6}{11}$$
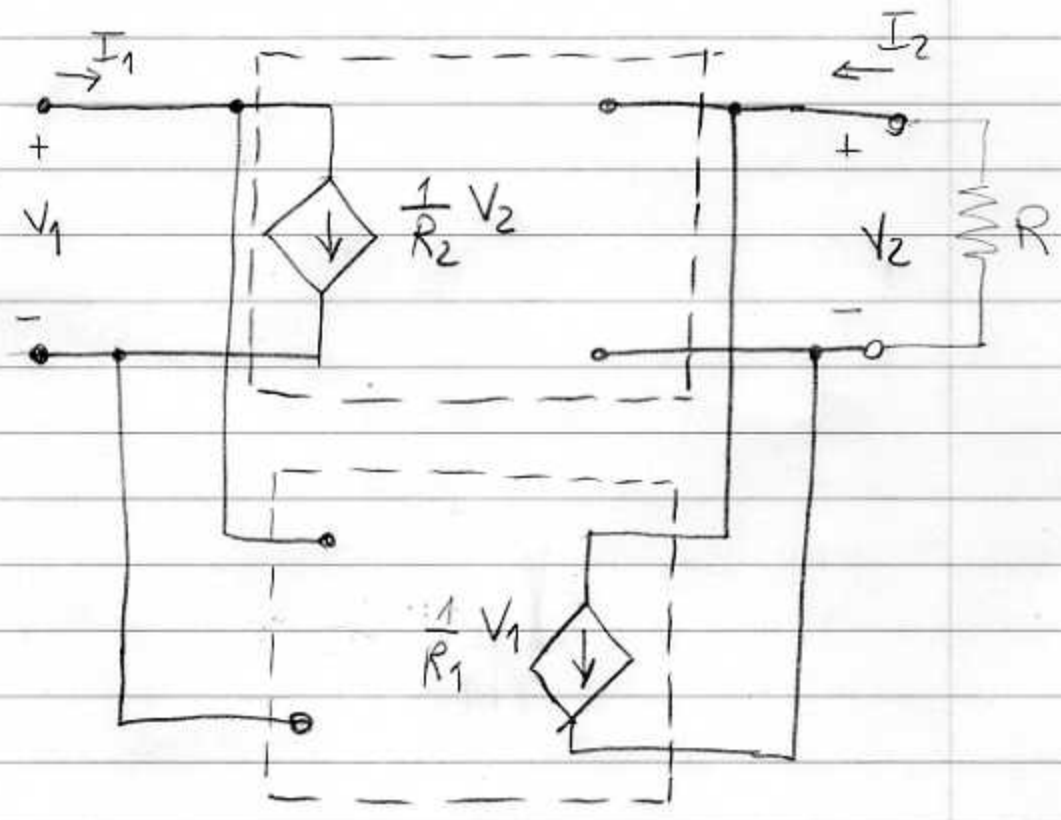
### 3) Negative impedance converter

Using controlled sources we can change a passive resistor  $R$  in an active resistor  $-R'$



Compute  $\frac{V_1}{I_1}$




$$3) \quad I_1 = \frac{V_2}{R_2} = - \frac{R I_2}{R_2} = - R \frac{V_1}{R_1 R_2}$$

$$\frac{V_1}{I_1} = - \frac{R_1 R_2}{R} = - R'$$

### 4) NULLOR

Define a new component:

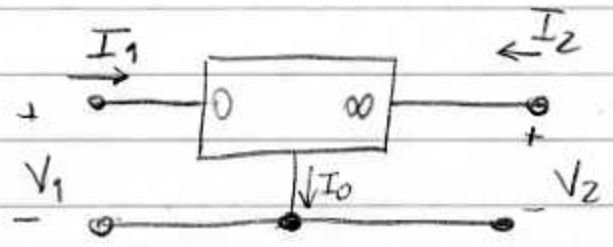

the nullor


The constitutive equations are

$$V_1 = 0, I_1 = 0$$


$V_2$  and  $I_2$  are determined by the rest of the circuit.

4.1) Using the generalization of KCL compute  $I_0$ .

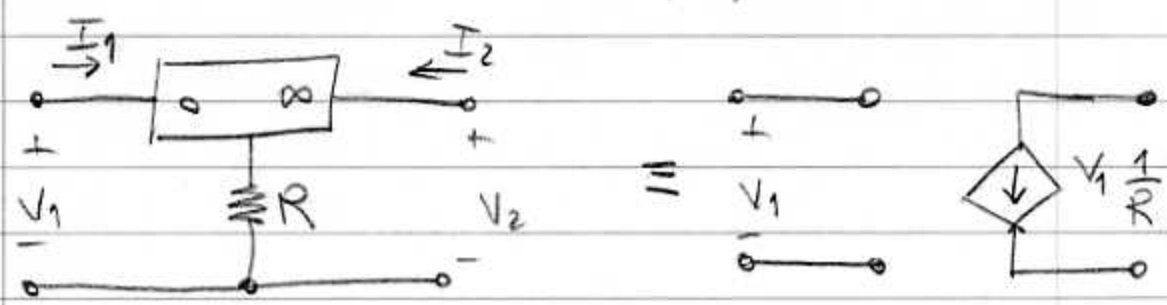
4.2) Show that the two circuits are equivalent



Mead

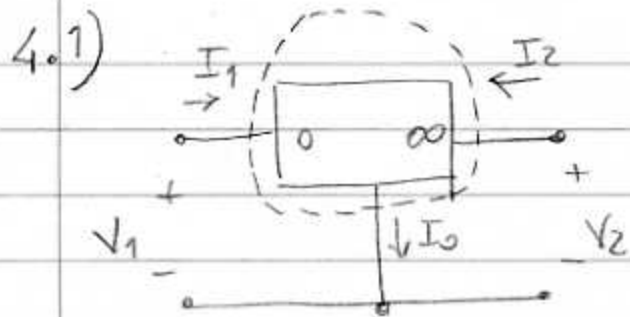

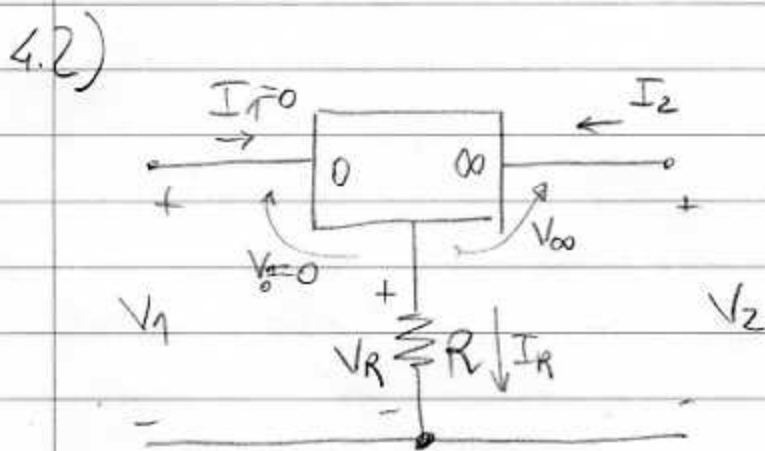
$$I_0 = I_1 + I_2 = I_2 \quad \text{because } I_1 = 0$$



$$V_R + V_0 = V_1 \Rightarrow V_R = V_1 \Rightarrow I_R = \frac{V_1}{R}$$


$$I_R = I_2 \Rightarrow I_2 = \frac{V_1}{R}$$

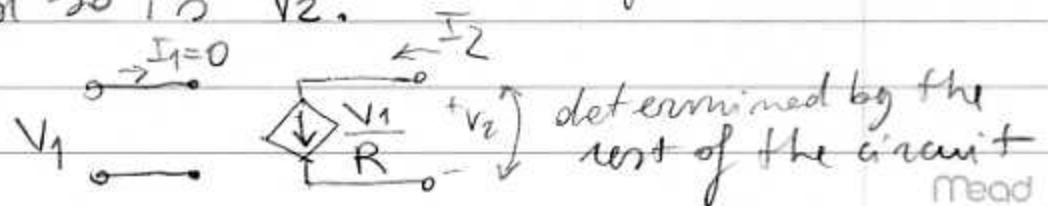$V_2 = V_R + V_0$  but  $V_0$  is determined by the rest of the circuit and so is  $V_2$ .



Mead

5)

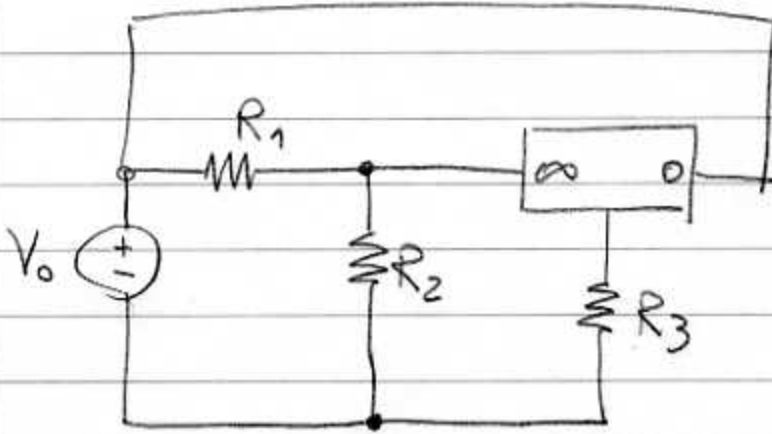


$$V_0 = 2 \text{ V}$$

$$R_1 = 1 \Omega$$

$$R_2 = \frac{1}{3} \Omega$$

$$R_3 = \frac{1}{10} \Omega$$

5.1) Solve the circuit

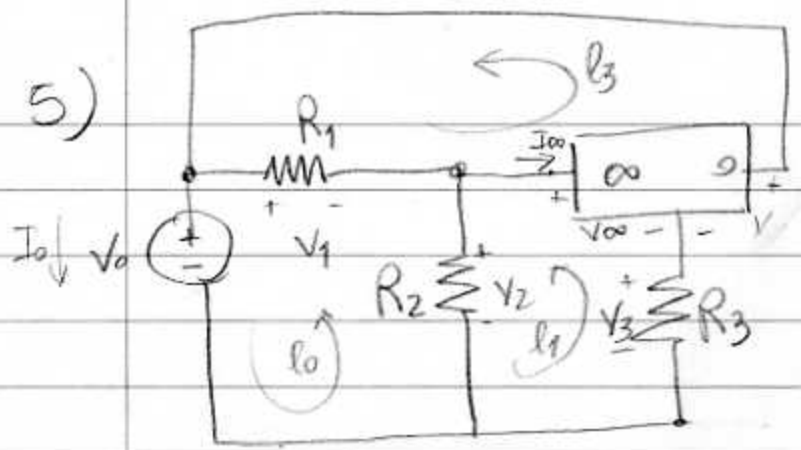

Using mesh-current

$$\begin{cases} l_0 : & V_0 - V_2 - V_1 = 0 \\ l_1 : & -V_3 - V_{\infty} + V_2 = 0 \\ l_3 : & (V_{\infty} - V) + V_1 = 0 \end{cases}$$

$$\begin{cases} V_0 - R_2(I_{l_1} - I_{l_0}) - R_1(I_{l_3} - I_{l_0}) = 0 \\ +I_{l_1}R_3 - V_{\infty} + R_2(I_{l_1} - I_{l_0}) = 0 \\ (V_{\infty} - V) + R_1(I_{l_3} - I_{l_0}) = 0 \end{cases}$$

but  $I_{l_3} = 0$  and  $V = 0$

$$\begin{cases} l_0 & V_0 - R_2(I_{l_1} - I_{l_0}) - R_1I_{l_0} = 0 \\ l_1 & I_{l_1}R_3 - V_{\infty} + R_2(I_{l_1} - I_{l_0}) = 0 \\ l_3 & V_{\infty} - R_1I_{l_0} = 0 \end{cases}$$

We have 3 eqns in 3 unknowns

$$V_{oc} = R_1 I_{c0} \quad (\text{from } I_3)$$

$$\left\{ \begin{aligned} V_0 - R_2 I_{L1} + I_{c0} (R_2 - R_1) &= 0 \end{aligned} \right.$$

$$\left\{ \begin{aligned} I_{L1} (R_3 + R_2) - R_2 I_{c0} - R_1 I_{c0} &= 0 \end{aligned} \right.$$

$$I_{L1} = \frac{I_{c0} (R_2 + R_1)}{R_2 + R_3} = I_{c0} \frac{4/3}{13/30} = I_{c0} \frac{4}{3} \frac{30}{13} =$$

$$= I_{c0} \frac{40}{13}$$

$$V_0 - R_2 \frac{40}{13} I_{c0} - \frac{2 I_{c0}}{3} = 0 \rightarrow$$

$$\Rightarrow 2 - I_{c0} \left( \frac{40}{39} + \frac{2}{3} \right) = 0 \Rightarrow I_{c0} \frac{66}{39} = 2$$

$$\Rightarrow I_{c0} = \frac{39}{33} = \frac{13}{11}$$

$$I_{L1} = \frac{13}{11} \frac{40}{13} = \frac{40}{11}$$

$$I_0 = \frac{13}{11} ; I_1 = -\frac{13}{11} ; I_2 = \frac{40}{11} - \frac{13}{11} = \frac{27}{11}$$

$$I_3 = -\frac{40}{11} \quad I_{\infty} = -\frac{40}{11}$$

also you can compute all the voltages.