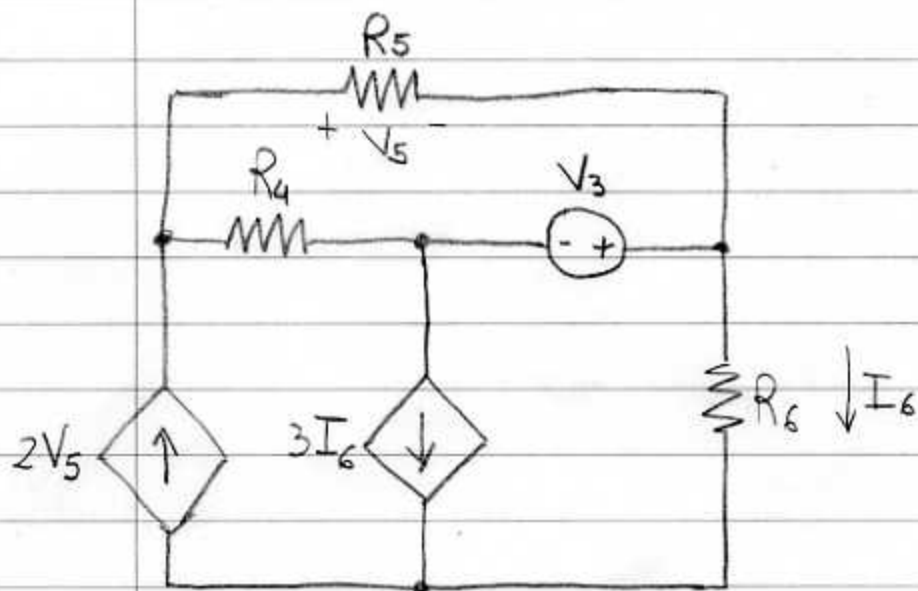


## EE 40 HW 1: Circuits Analysis



$$R_4 = 1 \, \Omega$$

$$R_5 = \frac{1}{2} \, \Omega$$


$$R_6 = \frac{1}{3} \, \Omega$$

$$V_3 = 1 \, \text{V}$$

Definition: Given a circuit  $C$ ,  
Solve the circuit means to find  
 current through and voltage  
 across each element of the  
 circuit.

- 1) Solve the circuit using  
Node-Voltage Analysis
- 2) Solve the circuit using  
Mesh-Current Analysis

## EE40 HW1 SOLUTION

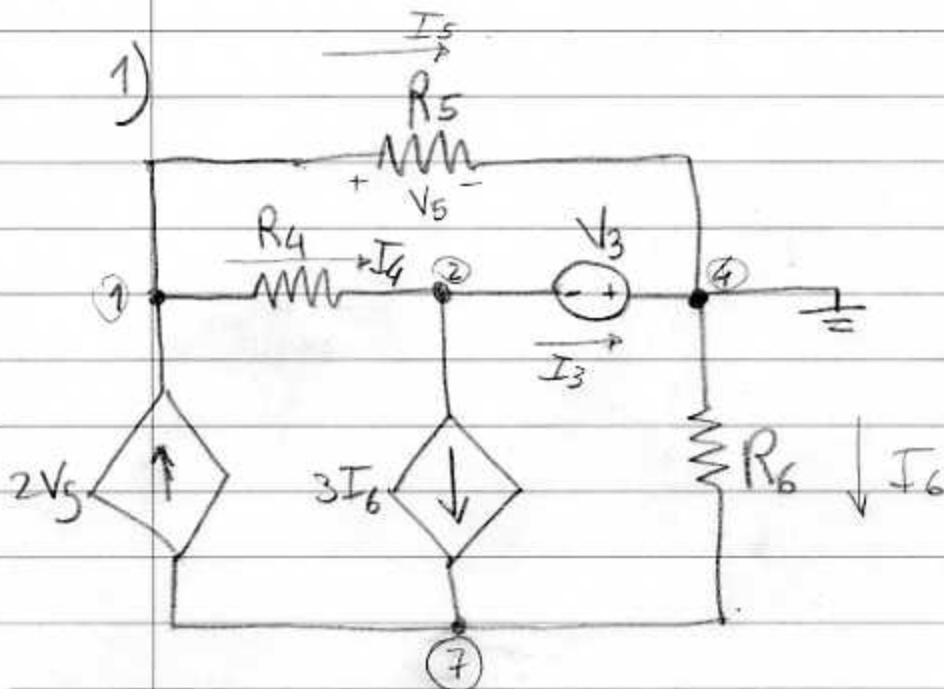

I pick node 4 to be the reference node so that  $V_2 = -V_3$  and it is no longer an unknown. Also I have fixed reference directions and polarities.

$$\textcircled{1} \quad I_5 + I_4 - 2V_5 = 0$$

$$\textcircled{2} \quad 3I_6 + I_3 - I_4 = 0$$

$$\textcircled{7} \quad 2V_5 - 3I_6 - I_6 = 0$$

Note that  $V_5 = V_1$ , and  $V_2 = -V_3$

$$\textcircled{1} \quad \frac{V_1}{R_5} + \frac{V_1 - V_2}{R_4} - 2V_1 = 0$$

$$\textcircled{2} \quad -\frac{3V_7}{R_6} + I_3 - \frac{(V_1 - V_2)}{R_4} = 0$$

$$\textcircled{7} \quad 2V_1 + \frac{3V_7}{R_6} + \frac{V_7}{R_6} = 0$$

$$\Downarrow V_2 = -V_3$$

$$\textcircled{1} \quad \frac{V_1}{R_5} + \frac{V_1 + V_3}{R_4} - 2V_1 = 0$$

$$\textcircled{2} \quad -\frac{3V_7}{R_6} + I_3 - \frac{(V_1 + V_3)}{R_4} = 0$$

$$\textcircled{7} \quad 2V_1 + 4\frac{V_7}{R_6} = 0$$

We have 3 eqns in 3 unknowns:  
 $V_1, V_7, I_3$

$$\text{from } \textcircled{1} \rightarrow V_1 \left( \frac{1}{R_5} + \frac{1}{R_4} - 2 \right) = -\frac{V_3}{R_4}$$


$$\Rightarrow V_1 = -1$$

from ⑦  $\rightarrow -2 + \frac{4V_7}{R_6} = 0 \Rightarrow V_7 = \frac{2}{12} = \frac{1}{6}$

from ②  $\rightarrow$   

$$-\frac{9}{6} + I_3 - 0 = 0$$
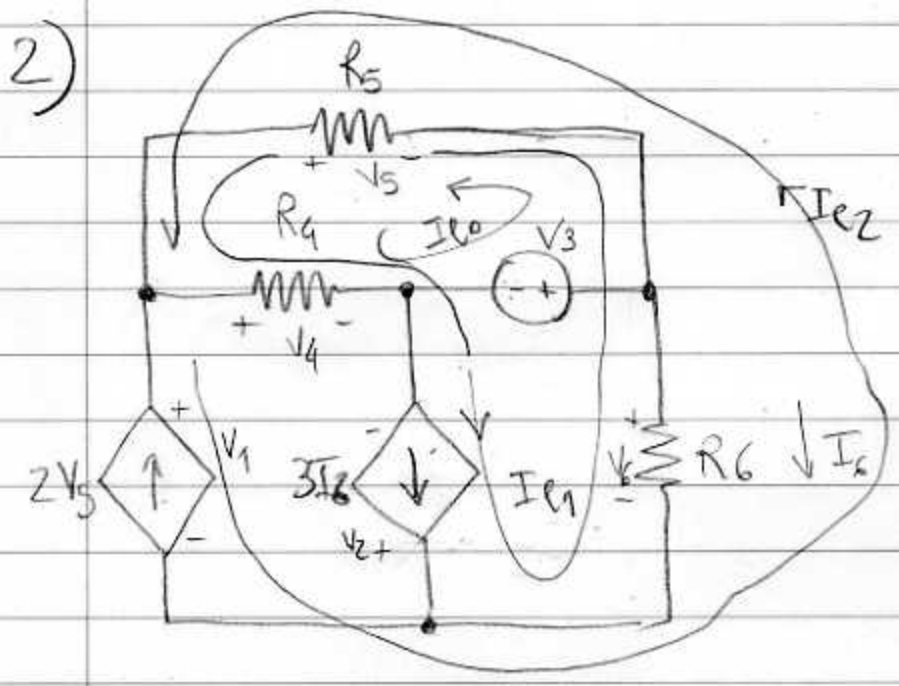
$$\Rightarrow I_3 = \frac{9}{6} = \frac{3}{2}$$



$$I_{e2} = -2V_5 \Rightarrow V_5 = -\frac{I_{e2}}{2}$$

$$I_{e1} = 3I_6 \Rightarrow I_6 = \frac{I_{e1}}{3}$$

$$\textcircled{l_0} \quad V_4 - V_3 - V_5 = 0$$

$$\textcircled{l_1} \quad V_4 - V_2 - V_6 - V_5 = 0$$

$$\textcircled{l_2} \quad V_1 - V_6 - V_5 = 0$$

$$\textcircled{l_0} \quad R_4(I_{l_0} + I_{e_1}) - V_3 + I_{e_2}/2 = 0$$

$$\textcircled{l_1} \quad R_4(I_{e_0} + I_{e_1}) - V_2 - \frac{R_6 I_{e_1}}{3} + \frac{I_{e_2}}{2} = 0$$

$$\textcircled{l_2} \quad V_1 - \frac{R_6 I_{e_1}}{3} + \frac{I_{e_2}}{2} = 0$$

$$I_{e_2} = +2R_5(I_{e_0} + I_{e_1} + I_{e_2}) \Rightarrow I_{e_2}(1 - 2R_5) = 2R_5(I_{e_0} + I_{e_1})$$

$$I_{e_1} = -3(I_{e_1} + I_{e_2}) \Rightarrow 4I_{e_1} = -3I_{e_2}$$

$$I_{e_2}(1 - 2R_5) = 2R_5(I_{e_0} - 3I_{e_2}/4)$$

$$I_{e_2}(1 - 2R_5 + 3R_5/2) = 2R_5 I_{e_0}$$

$$\frac{3I_{e_2}}{4} = I_{e_0} \Rightarrow I_{e_2} = \frac{4I_{e_0}}{3}$$

$$I_{e_1} = -I_{e_0}$$

$$\text{from } l_0 \rightarrow R_4(I_{l_0} - I_{l_2}) - V_3 + \frac{2I_{l_0}}{3} = 0$$

$$\Rightarrow I_{l_0} = \frac{3V_3}{2} = \frac{3}{2}$$

$$\Rightarrow I_{l_1} = -\frac{3}{2}, \quad I_{l_2} = 2$$

$$\text{from } l_2 \rightarrow V_1 + \frac{R_6}{2} + 1 = 0$$

$$\Rightarrow V_1 + \frac{1}{6} + 1 = 0 \Rightarrow V_1 = -\frac{7}{6}$$

$$\text{from } l_1 \rightarrow -V_2 + \frac{3}{2} \frac{R_6}{3} + 1 = 0$$

$$-V_2 + \frac{1}{6} + 1 = 0$$

$$V_2 = \frac{7}{6}$$

Now you can compute all the other currents.