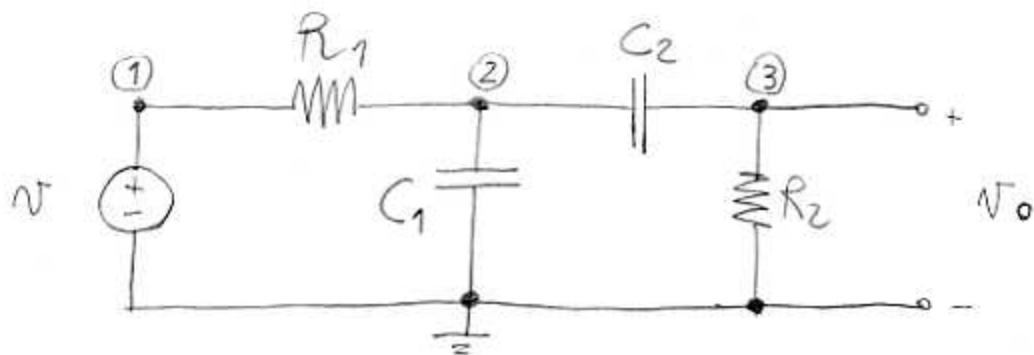


A) 2nd order circuits

Consider the circuit:



Follow the steps that I tell you to find the answer:

- A.1) Pick a reference point like in figure and consider the three nodes ①, ②, ③. Pick reference directions and polarities for all branches.

Write KCL for each node.

- A.2) You have to find now the equation for v_3 and v_2

I) Take derivative of equation at node ②.

- II) From equation at node ③, write $\frac{dv_2}{dt}$ as function of v_3 and $\frac{dv_3}{dt}$ (call this equation ④)
- III) take derivative of equation ④ to find an expression for $\frac{d^2v_2}{dt^2}$

IV) Substitute $\frac{dV_2}{dt}$ or $\frac{d^2V_2}{dt^2}$ found in II and III
in equation obtained in I. Call this new
equation (2')

A.3) We want to study the steady state response
when $v(t) = \sin(\omega_0 t)$ where $\omega_0 = 2\pi f_0$.

As usual, assume $V_3(t) = A \sin(\omega_0 t) + B \cos(\omega_0 t)$.

I) Substitute $V_3(t) = A \sin(\omega_0 t) + B \cos(\omega_0 t)$ in (2')

II) Compute A and B

We know that $A \sin x + B \cos x = \sqrt{A^2+B^2} \sin(x + \tan^{-1}(\frac{A}{B}))$
We are interested in $\sqrt{A^2+B^2}$


III) Compute A^2+B^2

A.4) We want to know the cut off frequencies.

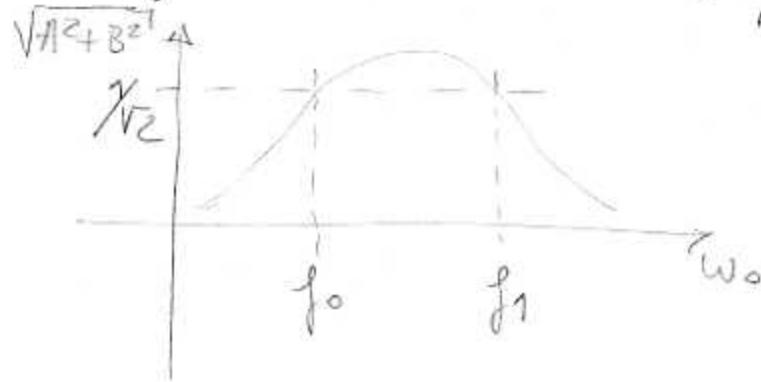I) Solve the equation:

$$\sqrt{A^2+B^2} = \frac{1}{\sqrt{Z}}$$


You should get two solutions for ω_0 meaning



it is a
bandpass filter!!
(cool, isn't it?)


B) Op-Amps : current source

Given the following circuit

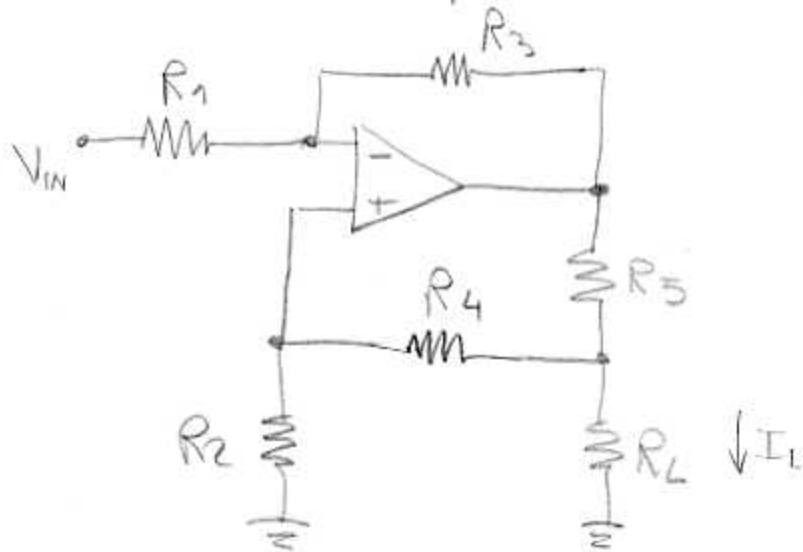

B.1) Compute I_L as a function of V_{IN}
in the case where $\begin{cases} R_3 = R_4 + R_5 \\ R_1 = R_2 \end{cases}$

C) Op-Amps: non linear circuit

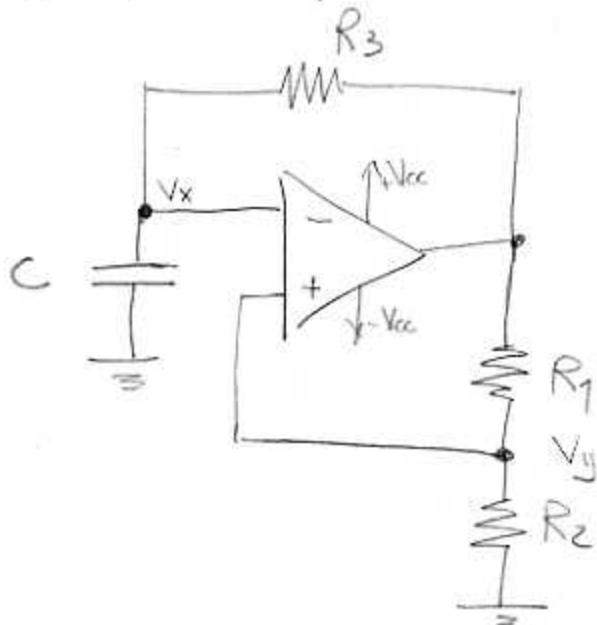

C.1) Consider $V_x = V_{cc} \frac{R_2}{R_1 + R_2}$ and the output to be $-V_{cc}$.

What is going to happen?

Describe how the circuit works

C.2) Compute the frequency of the output oscillation