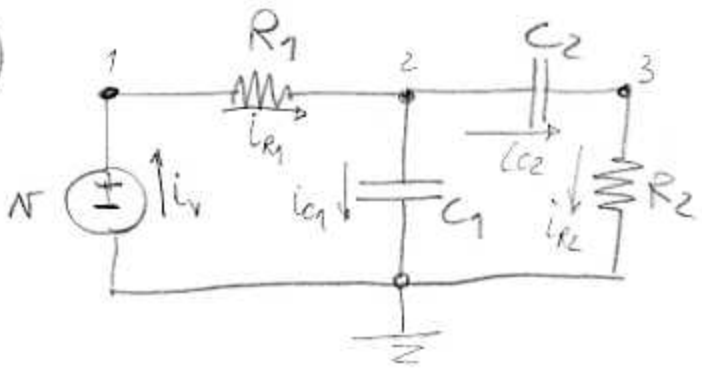


A.1)



$$\begin{cases}
 \textcircled{1} & i_V - i_{R1} = 0 \\
 \textcircled{2} & i_{R1} - i_{C1} - i_{C2} = 0 \\
 \textcircled{3} & i_{C2} - i_{R2} = 0
 \end{cases}
 \begin{cases}
 i_V - \frac{V_1 - V_2}{R_1} = 0 \\
 \frac{V_1 - V_2}{R_1} - C_1 \frac{dV_2}{dt} - C_2 \frac{d(V_2 - V_3)}{dt} = 0 \\
 C_2 \frac{d(V_2 - V_3)}{dt} - \frac{V_3}{R_2} = 0
 \end{cases}$$

$$V_1 = V$$

$$\begin{cases}
 \textcircled{1} & i_V - \frac{V - V_2}{R_1} = 0 \\
 \textcircled{2} & \frac{V - V_2}{R_1} - C_1 \frac{dV_2}{dt} - C_2 \frac{d(V_2 - V_3)}{dt} = 0 \\
 \textcircled{3} & C_2 \frac{d(V_2 - V_3)}{dt} - \frac{V_3}{R_2} = 0
 \end{cases}$$

A.2) taking derivative of ②:

$$\frac{1}{R_1} \frac{dV}{dt} - \frac{1}{R_1} \frac{dV_2}{dt} - C_1 \frac{d^2 V_2}{dt^2} - C_2 \frac{d^2 V_2}{dt^2} + C_2 \frac{d^2 V_3}{dt^2} = 0$$

$$\Rightarrow \frac{1}{R_1} \frac{dV}{dt} - \frac{1}{R_1} \frac{dV_2}{dt} - (C_1 + C_2) \frac{d^2 V_2}{dt^2} + C_2 \frac{d^2 V_3}{dt^2} = 0$$

from (3):

2
5/12

$$C_2 \frac{dv_2}{dt} - C_2 \frac{dv_3}{dt} - \frac{v_3}{R_2} = 0 \Rightarrow \frac{dv_2}{dt} = \frac{dv_3}{dt} + \frac{1}{R_2 C_2} v_3$$

and also taking derivative

$$\frac{d^2 v_2}{dt^2} = \frac{d^2 v_3}{dt^2} + \frac{1}{R_2 C_2} \frac{dv_3}{dt}$$

Now we substitute $\frac{dv_2}{dt}$ and $\frac{d^2 v_2}{dt^2}$ in (2) to obtain an equation in v_3 only:

$$\frac{1}{R_1} \frac{dv}{dt} - \frac{1}{R_1} \frac{dv_3}{dt} - \frac{1}{R_1 R_2 C_2} v_3 - (C_1 + C_2) \frac{d^2 v_3}{dt^2} - \frac{C_1 + C_2}{R_2 C_2} \frac{dv_3}{dt} +$$

$$+ C_2 \frac{d^2 v_3}{dt^2} = 0 \Rightarrow$$

$$\Rightarrow -C_1 \frac{d^2 v_3}{dt^2} - \left(\frac{1}{R_1} + \frac{C_1 + C_2}{R_2 C_2} \right) \frac{dv_3}{dt} - \frac{v_3}{R_1 R_2 C_2} + \frac{1}{R_1} \frac{dv}{dt} = 0 \quad (2)$$

A.3) $v_3 = A \sin(\omega t) + B \cos(\omega t)$, $v(t) = \sin(\omega t)$

$$-C_1 \left(-A \omega^2 \sin(\omega t) - B \omega^2 \cos(\omega t) \right) - \left(\frac{1}{R_1} + \frac{C_1 + C_2}{R_2 C_2} \right) \left(A \omega \cos(\omega t) - B \omega \sin(\omega t) \right)$$

$$- \frac{1}{R_1 R_2 C_2} \left[A \sin(\omega t) + B \cos(\omega t) \right] + \frac{1}{R_1} \omega \cos(\omega t) = 0$$

$$\sin(\omega t) \left[C_1 A \omega^2 + B \omega \left(\frac{1}{R_1} + \frac{C_1 + C_2}{R_2 C_2} \right) - \frac{A}{R_1 R_2 C_2} \right] + \cos(\omega t) \left[-C_1 B \omega^2 + \frac{B \omega}{R_1} - \frac{B}{R_1 R_2 C_2} \right] = 0$$

$$\cos(\omega_0 t) \left[C_1 B \omega_0^2 - \left(\frac{1}{R_1} + \frac{C_1 + C_2}{R_2 C_2} \right) \omega_0 A - \frac{B}{R_1 R_2 C_2} + \frac{\omega_0}{R_1} \right] = 0 \quad \text{Sol 3}$$

$$\begin{cases} C_1 A \omega_0^2 + B \omega_0 \left(\frac{1}{R_1} + \frac{C_1 + C_2}{R_2 C_2} \right) - \frac{A}{R_1 R_2 C_2} = 0 \\ C_1 B \omega_0^2 - \left(\frac{1}{R_1} + \frac{C_1 + C_2}{R_2 C_2} \right) \omega_0 A - \frac{B}{R_1 R_2 C_2} + \frac{\omega_0}{R_1} = 0 \end{cases}$$

$$\begin{cases} R_1 R_2 C_1 C_2 A \omega_0^2 + B \omega_0 (R_2 C_2 + R_1 C_1 + R_1 C_2) - A = 0 \\ R_1 R_2 C_1 C_2 B \omega_0^2 - (R_2 C_2 + R_1 C_1 + R_1 C_2) \omega_0 A - B + \omega_0 R_2 C_2 = 0 \end{cases}$$

$$\tau_1 = R_1 C_1 ; \tau_2 = R_2 C_2 ; (\tau_1 + \tau_2 + R_1 C_2) = \tau^*$$

$$\begin{cases} \tau_1 \tau_2 \omega_0^2 A + B \omega_0 \tau^* - A = 0 \longrightarrow B = A \frac{(1 - \tau_1 \tau_2 \omega_0^2)}{\omega_0 \tau^*} \\ \tau_1 \tau_2 \omega_0^2 B - \tau^* \omega_0 A - B = -\omega_0 \tau_2 \end{cases}$$

↓

$$\tau_1 \tau_2 \omega_0^2 \frac{A(1 - \tau_1 \tau_2 \omega_0^2)}{\omega_0 \tau^*} - \tau^* \omega_0 A - A \frac{(1 - \tau_1 \tau_2 \omega_0^2)}{\omega_0 \tau^*} = -\omega_0 \tau_2$$

$$\Rightarrow A \left(\frac{\tau_1 \tau_2 \omega_0^2 (1 - \tau_1 \tau_2 \omega_0^2) - \omega_0^2 \tau^{*2} - 1 + \tau_1 \tau_2 \omega_0^2}{\omega_0 \tau^*} \right) = -\omega_0 \tau_2$$

$$\Rightarrow A = \frac{-\tau_2 \tau^* \omega_0^2}{\tau_1 \tau_2 \omega_0^2 - \tau_1^2 \tau_2^2 \omega_0^4 - 1 + \tau_1 \tau_2 \omega_0^2 - \omega_0^2 \tau^{*2}} = \mathcal{A}$$

$$= \frac{\tau_2 \tau^* \omega_0^2}{(1 - \omega_0^2 \tau_1 \tau_2)^2 + \omega_0^2 \tau^{*2}} = \frac{N_A}{D_A} \quad \text{4 Solz}$$

$$B = \frac{N_A}{D_A} \frac{(1 - \tau_1 \tau_2 \omega_0^2)}{\omega_0 \tau^*}$$

↓

$$\begin{aligned} \sqrt{A^2 + B^2} &= \sqrt{\frac{N_A^2}{D_A^2} + \frac{N_A^2}{D_A^2} \frac{(1 - \tau_1 \tau_2 \omega_0^2)^2}{(\omega_0 \tau^*)^2}} = \frac{N_A}{D_A \omega_0 \tau^*} \sqrt{D_A} = \\ &= \frac{\tau_2 \tau^* \omega_0^2}{\omega_0 \tau^* \sqrt{D_A}} = \frac{\omega_0 \tau_2}{\sqrt{(1 - \tau_1 \tau_2 \omega_0^2)^2 + \omega_0^2 \tau^{*2}}} \end{aligned}$$

A.4)

$$\sqrt{A^2 + B^2} = \frac{1}{\sqrt{2}} \Rightarrow 2 \omega_0^2 \tau_2^2 = (1 - \tau_1 \tau_2 \omega_0^2)^2 + \omega_0^2 \tau^{*2}$$

$$\Rightarrow 2 \omega_0^2 \tau_2^2 = 1 + \tau_1^2 \tau_2^2 \omega_0^4 - 2 \tau_1 \tau_2 \omega_0^2 + \omega_0^2 \tau^{*2}$$

$$\omega_0^2 = x$$


$$\Rightarrow \tau_1 \tau_2 x^2 - (2\tau_2^2 + 2\tau_1 \tau_2 - \tau^{*2}) x + 1 = 0$$

a
 b
 c

$$x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$b^2 - 4ac = (2\tau_2^2 + 2\tau_1 \tau_2 - \tau^{*2})^2 - 4\tau_1 \tau_2$$

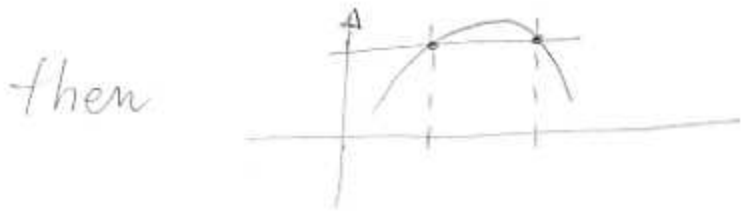if $b^2 - 4ac > 0 \Rightarrow 2\tau_2^2 + 2\tau_1\tau_2 - \tau^{*2} > 2\sqrt{\tau_1\tau_2}$



we have two real solutions for x

and 4 solutions for w_0 (only the positive solutions count).


if $b^2 - 4ac < 0 \Rightarrow 2\tau_2^2 + 2\tau_1\tau_2 - \tau^{*2} < 2\sqrt{\tau_1\tau_2}$

then there are no real solutions

if $b^2 - 4ac = 0 \Rightarrow (2\tau_2^2 + 2\tau_1\tau_2 - \tau^{*2})^2 = 4\tau_1\tau_2$

\Rightarrow there is only one solution for w_0

B) Let's use the pair nullator-morator

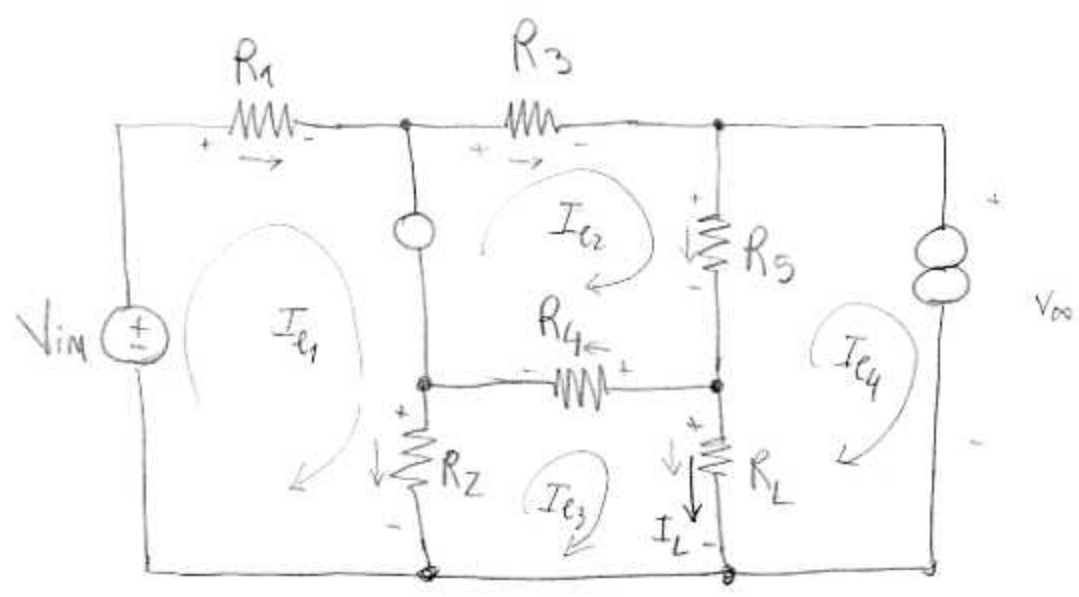

There are 4 meshes so we will have 4 equations plus 2 equations from the nullator.

The unknown are the four mesh currents, the voltage across the morator and the current through the morator.

$$\left\{ \begin{array}{l} -V_{im} + V_{R1} + 0 + V_{R2} = 0 \\ 0 + V_{R3} + V_{R5} + V_{R4} = 0 \\ -V_{R2} - V_{R4} + V_{R_L} = 0 \\ -V_{R_L} - V_{R5} + V_{\infty} = 0 \\ I_{e1} - I_{e2} = 0 \end{array} \right. \left\{ \begin{array}{l} -V_{im} + R_1 I_{e1} + R_2 (I_{e1} - I_{e3}) = 0 \\ R_3 I_{e2} + R_5 (I_{e2} - I_{e4}) + R_4 (I_{e2} - I_{e3}) = 0 \\ R_2 (I_{e3} - I_{e1}) + R_4 (I_{e3} - I_{e2}) + R_L (I_{e3} - I_{e4}) = 0 \\ R_L (I_{e4} - I_{e3}) + R_5 (I_{e4} - I_{e2}) + V_{\infty} = 0 \\ I_{e1} - I_{e2} = 0 \end{array} \right.$$

Since $R_3 = R_4 + R_5$ and $R_1 = R_2$

7
5/2

$$\begin{cases} -V_{im} + 2R_1 I_{e1} - R_1 I_{e3} = 0 & 1 \\ 2R_3 I_{e2} - R_5 I_{e4} - R_4 I_{e3} = 0 & 2 \\ (R_2 + R_4 + R_6) I_{e3} - R_2 I_{e1} - R_4 I_{e2} - R_6 I_{e4} = 0 & 3 \\ I_{e1} = I_{e2} & 4 \end{cases}$$


We actually need only eq. 1, 2, 4 :

$$\begin{cases} -V_{im} + 2R_1 I_{e1} - R_1 I_{e3} = 0 \\ 2R_3 I_{e1} - R_5 I_{e4} - R_4 I_{e3} = 0 \end{cases} \begin{cases} I_{e3} = -\frac{V_{im}}{R_1} + 2I_{e1} \\ I_{e4} = \frac{2R_3}{R_5} I_{e1} + \frac{V_{im} R_4}{R_1 R_5} - \frac{2R_4}{R_5} I_{e1} \end{cases}$$

$$I_L = I_{e3} - I_{e4} = -\frac{V_{im}}{R_1} + 2I_{e1} - \left(\overset{\downarrow 2R_5}{\frac{2R_3 - 2R_4}{R_5}} I_{e1} + \frac{V_{im} R_4}{R_1 R_5} \right)$$


$$= -\frac{V_{im}}{R_1} + \cancel{2I_{e1}} - \cancel{2I_{e1}} - \frac{V_{im} R_4}{R_1 R_5} =$$
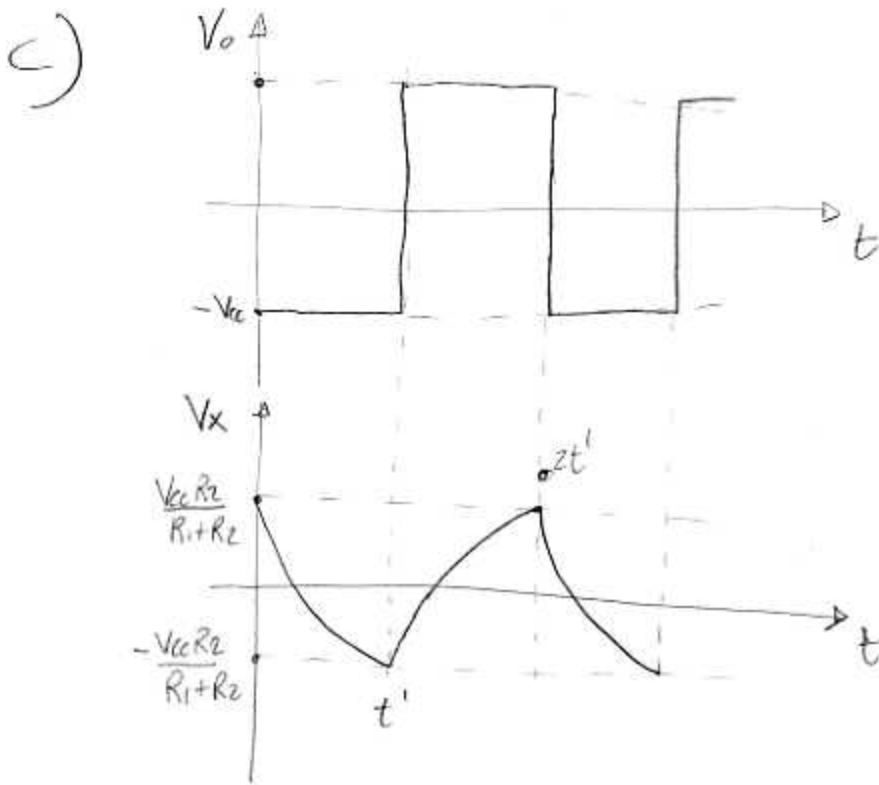
$$= -\frac{R_5 V_{im} + R_4 V_{im}}{R_1 R_5} = -\frac{V_{im} R_3}{R_1 R_5}$$



We need t' and then $f = \frac{1}{2t'}$

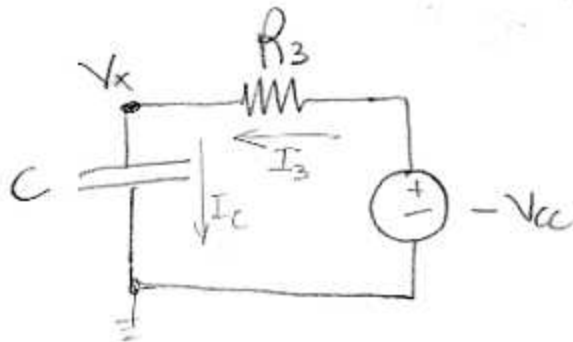The capacitor discharges on R_3 so the circuit is like



$$V_c(0) = V_{cc} \frac{R_2}{R_1 + R_2}$$

We need an expression for V_x

$$I_3 - I_c = 0 \Rightarrow \frac{-V_{cc} - V_x}{R_3} - C \frac{dV_x}{dt} = 0$$

$$R_3 C \frac{dV_x}{dt} + V_x = -V_{cc}$$

consider $V_x = A e^{\alpha t} + B$ as our guess:

$$R_3 C A \alpha e^{\alpha t} + A e^{\alpha t} + B = -V_{cc}$$

$$B = -V_{cc}$$

$$R_3 C A \alpha e^{\alpha t} + A e^{\alpha t} = 0 \Rightarrow \alpha = -\frac{1}{R_3 C}$$

$$V_x(0) = V_{cc} \frac{R_2}{R_1 + R_2} \Rightarrow A - V_{cc} = V_{cc} \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow A = V_{cc} \left(\frac{R_2}{R_1 + R_2} + 1 \right)$$

Now we want to know the time when

$$V_x = -V_{cc} \frac{R_2}{R_1 + R_2} :$$

$$-\frac{V_{cc} R_2}{R_1 + R_2} = V_{cc} \left(\frac{R_2}{R_1 + R_2} + 1 \right) e^{-\frac{t}{R_3 C}} - V_{cc}$$

$$\cancel{V_{cc}} \left(1 - \frac{R_2}{R_1 + R_2} \right) = \cancel{V_{cc}} \left(\frac{R_2}{R_1 + R_2} + 1 \right) e^{-\frac{t}{R_3 C}}$$

$$\frac{R_1}{R_1 + R_2} = \frac{2R_2 + R_1}{R_1 + R_2} e^{-t'/R_3C}$$

$$e^{-t'/R_3C} = \frac{R_1}{2R_2 + R_1} \Rightarrow -\frac{t'}{R_3C} = \ln\left(\frac{R_1}{2R_2 + R_1}\right)$$

$$\Rightarrow t' = -R_3C \ln\left(\frac{R_1}{2R_2 + R_1}\right)$$

$$\frac{1}{f} = \frac{1}{2t'} = -\frac{1}{2R_3C \ln\left(\frac{R_1}{2R_2 + R_1}\right)}$$