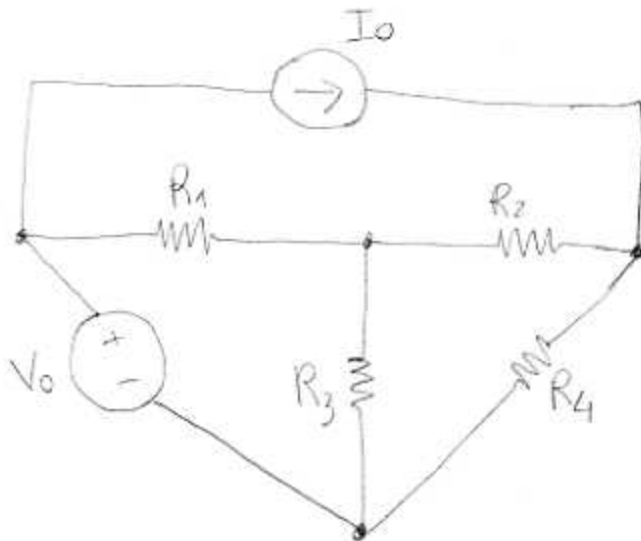


## A) CIRCUIT ANALYSIS



$$R_1 = R_2 = 2 \Omega$$

$$R_3 = R_4 = 1 \Omega$$


$$V_0 = 2 \text{ V}$$

$$I_0 = \frac{6}{7} \text{ A}$$

A.1) Using the method that you like most, solve the circuit.

## B) THEVENIN/NORTON EQUIVALENCE

2

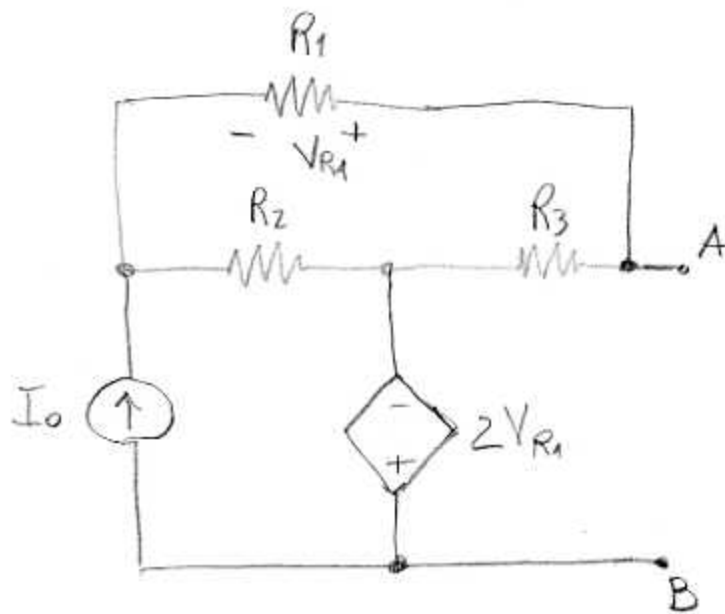

$$R_1 = 1 \Omega$$

$$R_2 = 2 \Omega$$


$$R_3 = 1 \Omega$$

$$I_0 = 2 \text{ A}$$


B.1) Find the thevenin equivalent circuit at nodes A, B

B.2) Find the Norton equivalent circuit at node A, B

# C) OP-AMPS

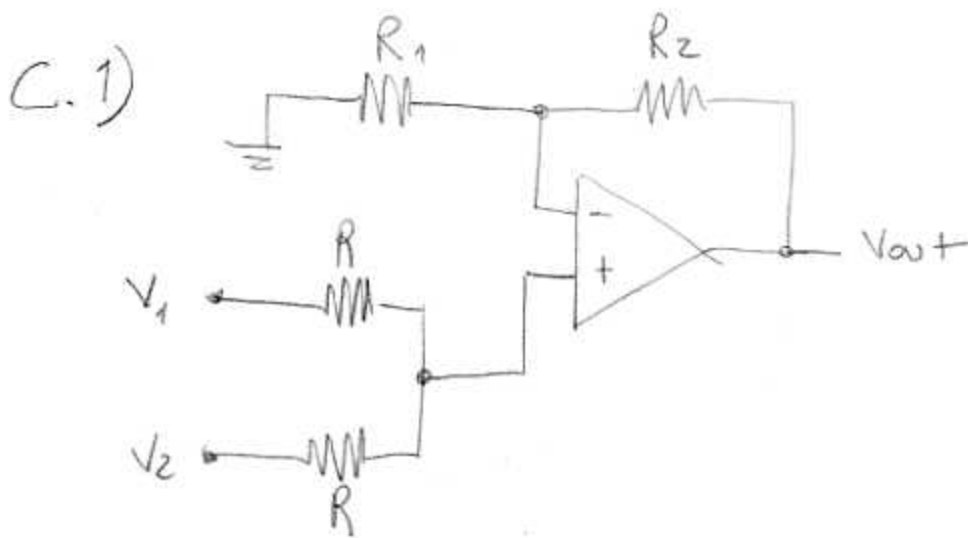

compute  $V_{out}$

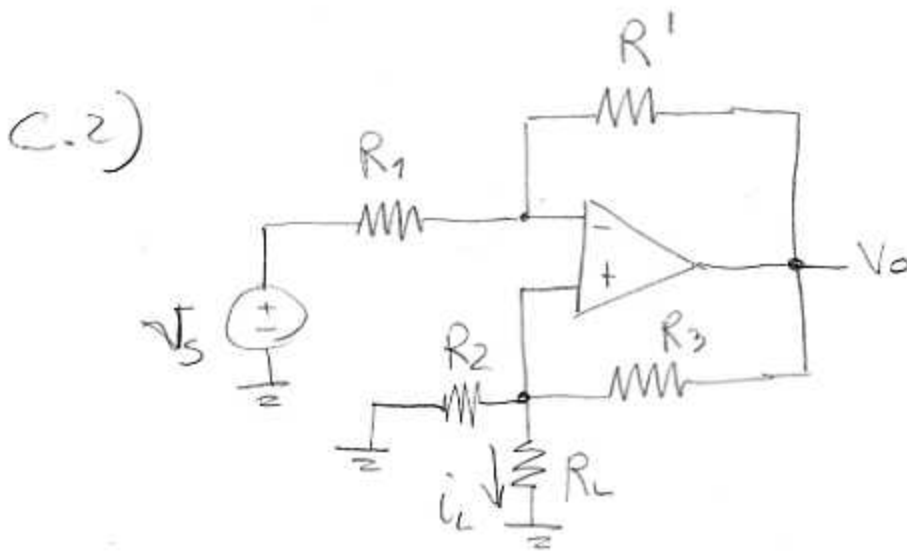


Prove that if  $\frac{R_3}{R_2} = \frac{R'}{R_1}$  then

$$i_L = -\frac{V_s}{R_2}$$

(Of course, you should first compute  $i_L = f(V_s)$ )

# MIDTERM 1 SOLUTIONS

A) Using Node - Voltage

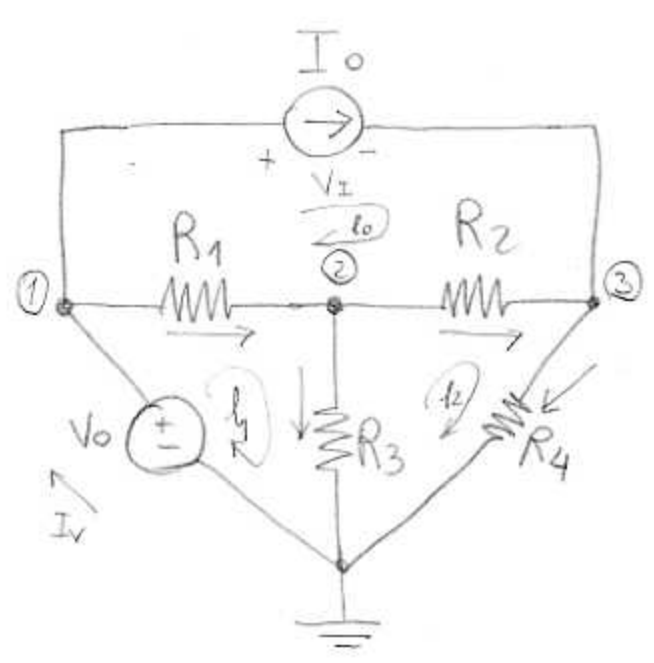

$$R_1 = R_2 = 2 \Omega$$

$$R_3 = R_4 = 1 \Omega$$

$$V_0 = 2 \text{ V}$$

$$I_0 = \frac{6}{7} \text{ A}$$

$$\begin{cases} I_v - I_1 - I_0 = 0 \\ I_1 - I_3 - I_2 = 0 \\ I_2 - I_4 + I_0 = 0 \end{cases} \quad \begin{cases} I_v - \frac{V_0 - V_2}{R_1} - I_0 = 0 \\ \frac{V_0 - V_2}{R_1} - \frac{V_2}{R_3} - \frac{V_2 - V_3}{R_2} = 0 \\ \frac{V_2 - V_3}{R_2} - \frac{V_3}{R_4} + I_0 = 0 \end{cases}$$

$$\begin{cases} I_v - \frac{V_0 - V_2}{R_1} - I_0 = 0 \\ 1 - \frac{V_2}{2} - \frac{V_2}{1} - \frac{V_2 - V_3}{2} = 0 \\ \frac{V_2 - V_3}{2} - \frac{V_3}{1} + \frac{6}{7} = 0 \end{cases} \quad \begin{cases} I_v - \frac{2}{2} + \frac{V_2}{2} - \frac{6}{7} = 0 \\ 1 - 2V_2 - \frac{V_3}{2} = 0 \\ \frac{V_2}{2} = -\frac{6}{7} + \frac{3}{2} V_3 \end{cases}$$

$$\begin{cases} I_V - 1 + V_2/2 - 6/7 = 0 \\ V_3 = 4V_2 - 2 \\ V_2/2 = 6/7 + 3/2(4V_2 - 2) \Rightarrow -\frac{11}{2}V_2 + \frac{27}{7} = 0 \end{cases}$$

$$\Rightarrow V_2 = \frac{27}{7} \cdot \frac{2}{11} = \frac{54}{77}$$

$$V_3 = 4 \frac{54}{77} - 2 = \frac{4 \cdot 54 - 154}{77} = \frac{216 - 154}{77} = \frac{62}{77}$$

$$I_V = 1 - \frac{54}{77} \cdot \frac{1}{2} + \frac{6}{7} = \frac{77 - 27 + 66}{77} = \frac{116}{77}$$

$$I_1 = \left(2 - \frac{54}{77}\right) \frac{1}{R_1} = \frac{154 - 54}{77} \cdot \frac{1}{2} = \frac{50}{77}$$

$$I_3 = \frac{V_2}{R_3} = \frac{54}{77}$$

$$I_2 = \frac{V_2 - V_3}{R_2} = \frac{1}{2} \left( \frac{54}{77} - \frac{62}{77} \right) = -\frac{4}{77}$$

$$V_I = V_1 - V_3 = 2 - \frac{62}{77} = \frac{154 - 62}{77} = \frac{92}{77}$$

Using mesh-current

$$\begin{cases} V_E - R_2 I_2 - R_1 I_1 = 0 \\ R_1 I_1 + R_3 I_3 - V_0 = 0 \\ R_2 I_2 + R_4 I_4 - R_3 I_3 = 0 \end{cases} \quad \begin{cases} V_E - R_2 (I_{e1} - I_{e0}) - R_1 (I_{e1} - I_{e0}) = 0 \\ R_1 (I_{e1} - I_{e0}) + R_3 (I_{e1} - I_{e2}) - V_0 = 0 \\ R_2 (I_{e2} - I_{e0}) + R_4 (I_{e2}) - R_3 (I_{e1} - I_{e2}) = 0 \end{cases}$$

$$I_{e0} = I_0$$

from the last two:

$$\begin{cases} I_{e1} (R_1 + R_3) - I_{e2} R_3 = V_0 + R_1 I_0 \\ -I_{e1} R_3 + I_{e2} (R_2 + R_4 + R_3) = R_2 I_0 \end{cases}$$

$$\begin{cases} 3I_{e1} - I_{e2} = 2 + \frac{12}{7} \\ -I_{e1} + 4I_{e2} = \frac{12}{7} \end{cases} \quad \begin{cases} 12I_{e2} - \frac{36}{7} - I_{e2} = \frac{26}{7} \\ I_{e1} = 4I_{e2} - \frac{12}{7} \end{cases}$$

$$11I_{e2} = \frac{62}{7} \Rightarrow I_{e2} = \frac{62}{77}$$

$$I_{e1} = 4 \frac{62}{77} - \frac{12}{7} = \frac{4 \cdot 62 - 11 \cdot 12}{77} = \frac{248 - 132}{77} = \frac{116}{77}$$


$$I_v = I_{e_1} = \frac{116}{77}$$

$$I_1 = I_{e_1} - I_{e_0} = \frac{116}{77} - \frac{6}{7} = \frac{116 - 66}{77} = \frac{50}{77}$$

$$I_3 = I_{e_1} - I_{e_2} = \frac{116}{77} - \frac{62}{77} = \frac{54}{77}$$

$$I_2 = I_{e_2} - I_{e_0} = \frac{62}{77} - \frac{66}{77} = -\frac{4}{77}$$

$$I_4 = I_{e_2} = \frac{62}{77}$$

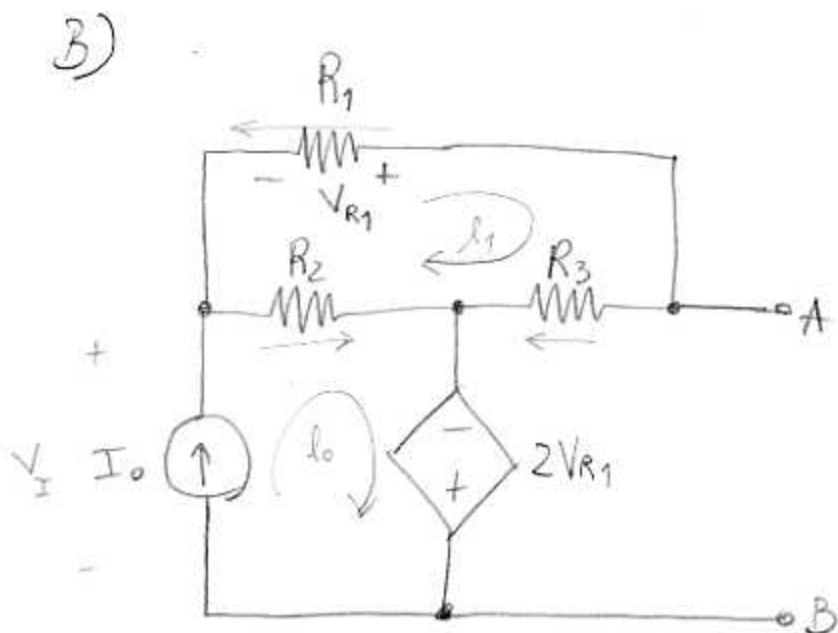

B.1) Compute  $V_{oc}$  which is the  $V_{TH}$ :

$$\left\{ \begin{array}{l} -V_I + R_2 I_2 - 2V_{R1} = 0 \\ -V_{R1} + R_3 I_3 - R_2 I_2 = 0 \end{array} \right. \left\{ \begin{array}{l} -V_I + R_2 (I_{l_0} - I_{l_1}) - 2R_1 (-I_{l_1}) = 0 \\ +R_1 I_{l_1} + R_3 I_{l_1} - R_2 (I_{l_0} - I_{l_1}) = 0 \end{array} \right.$$


$$I_{l_0} = I_0$$

$$\left\{ \begin{array}{l} -V_I + R_2 I_0 + I_{l_1} (+2R_1 - R_2) = 0 \\ I_{l_1} (R_1 + R_3 + R_2) - R_2 I_0 = 0 \end{array} \right. \Rightarrow I_{l_1} = \frac{R_2 I_0}{R_1 + R_3 + R_2}$$

$$= \frac{2 \cdot 2}{4} = 1$$
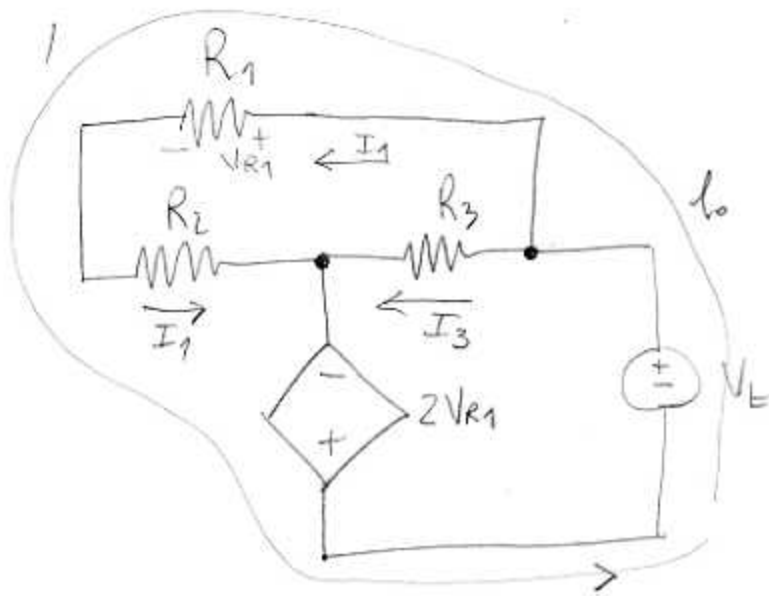
$$\begin{aligned} V_{oc} &= R_3 I_{l_1} - 2V_{R1} = \\ &= R_3 I_{l_1} + 2R_1 I_{l_1} = 3 \end{aligned}$$





write KVL at  $l_0$

$$-V_t + R_1 I_1 + R_2 I_1 - 2R_1 I_1 = 0$$

$$I_1 (R_1 + R_2 - 2R_1) = V_t \Rightarrow I_1 = \frac{V_t}{R_2 - R_1}$$

then


$$I_3 = \frac{V_t + 2V_{r1}}{R_3} = \frac{V_t + 2R_1 I_1}{R_3} = \frac{V_t + \frac{2R_1 V_t}{R_2 - R_1}}{R_3} =$$

$$= V_t \frac{R_2 + R_1}{R_3 (R_2 - R_1)} =$$


$$\Rightarrow I_t = I_1 + I_3 = V_t \left( \frac{1}{R_2 - R_1} + \frac{R_1 + R_2}{R_3 (R_2 - R_1)} \right) =$$

$$= V_t (1 + 3) = V_t 4 \Rightarrow \frac{V_t}{I_t} = \frac{1}{4} = R_{TH}$$

The thevenin equivalent circuit is then

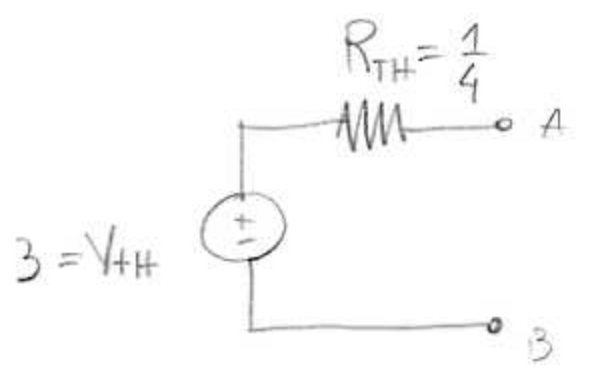


Hence the norton eq. circuit is

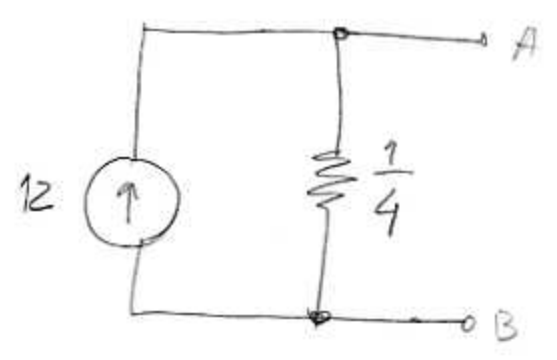

c)

c.1)

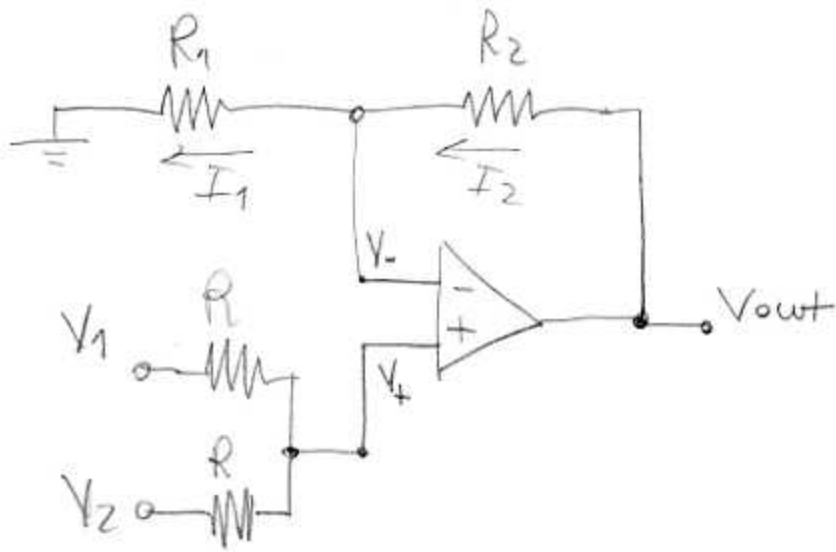

$$V_+ = V_1 \frac{R}{R+R} + V_2 \frac{R}{R+R} = \frac{V_1}{2} + \frac{V_2}{2}$$

↑ by superposition of  $V_1$  and  $V_2$


Virtual short circuit  $V_+ = V_-$

$$\bar{I}_1 = \frac{V_-}{R_1} = \frac{V_+}{R_1} = \frac{1}{R_1} \left( \frac{V_1}{2} + \frac{V_2}{2} \right)$$

$$I_2 = \bar{I}_1 \Rightarrow V_{out} = (R_1 + R_2) I_1 =$$

$$= \frac{R_1 + R_2}{2R_1} (V_1 + V_2) = \frac{1}{2} \left( 1 + \frac{R_2}{R_1} \right) (V_1 + V_2)$$

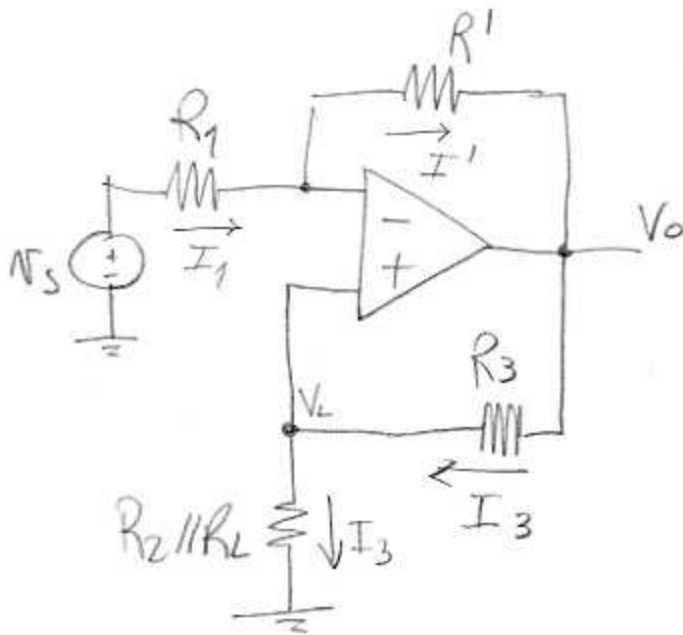C.2) 1<sup>st</sup> method (direct method):



$$V_L = V_o \frac{R_2 // R_L}{R_3 + R_2 // R_L} \quad *$$

$$\begin{aligned} V_o - V_L &= -R' I' = -R' I_1 = \\ &= -R' \frac{V_s - V_L}{R_1} \Rightarrow \end{aligned}$$

$$\Rightarrow V_o = V_L \left( 1 + \frac{R'}{R_1} \right) - \frac{R'}{R_1} V_s$$

Substituting in \*:

$$V_L = V_L \left( 1 + \frac{R'}{R_1} \right) \frac{R_2 // R_L}{R_3 + R_2 // R_L} - \frac{R'}{R_1} \frac{R_2 // R_L}{R_3 + R_2 // R_L} V_s$$

$$V_L \left( 1 - \left( 1 + \frac{R_1'}{R_1} \right) \frac{R_2 // R_L}{R_3 + R_2 // R_L} \right) = - \frac{R_1'}{R_1} \frac{R_2 // R_L}{R_3 + R_2 // R_L} V_S$$

$$V_L = - \frac{\frac{R_1'}{R_1} \frac{R_2 // R_L}{R_3 + R_2 // R_L}}{1 - \left( 1 + \frac{R_1'}{R_1} \right) \frac{R_2 // R_L}{R_3 + R_2 // R_L}} V_S$$

Now  $\frac{R_2 // R_L}{R_3 + R_2 // R_L} = \frac{R_2 R_L}{R_3(R_2 + R_L) + R_2 R_L}$

$$V_L = - \frac{\frac{R_1'}{R_1} \frac{R_2 R_L}{R_3(R_2 + R_L) + R_2 R_L}}{1 - \left( 1 + \frac{R_1'}{R_1} \right) \frac{R_2 R_L}{R_3(R_2 + R_L) + R_2 R_L}} V_S$$

$$= - \frac{\frac{R_1'}{R_1}}{\frac{R_3(R_2 + R_L) + R_2 R_L}{R_2 R_L} - \left( 1 + \frac{R_1'}{R_1} \right)} V_S =$$

$$= - \frac{\frac{R_1'}{R_1} R_2 R_L R_1}{R_1 R_3 (R_2 + R_L) + R_2 R_L R_1 - R_2 R_L R_1 - R_2 R_L R_1'} V_S =$$

$$= - \frac{\frac{R_1'}{R_1} R_2 R_L R_1}{R_1 R_3 R_2 + R_1 R_3 R_L - R_2 R_L R_1'} V_S =$$

$$\therefore \text{Since } \frac{R_3}{R_2} = \frac{R_1'}{R_1} \Rightarrow R_3 R_1 = R_2 R_1'$$


$$V_L = \frac{\frac{R_1'}{R_1} R_2 R_L R_1}{\cancel{R_2 R_1' R_L} - \cancel{R_2 R_L R_1'} + R_1 R_3 R_2} V_S = \frac{R_1' R_L}{R_1 R_3} V_S =$$

$$= - R_L V_S \frac{R_1'}{R_1} \frac{1}{R_3} = - V_S R_L \frac{R_3}{R_2} \frac{1}{R_3} =$$

$$= - \frac{R_L}{R_2} V_S$$

$$\text{Now } I_L = \frac{V_L}{R_L} = - \frac{V_S}{R_2}$$

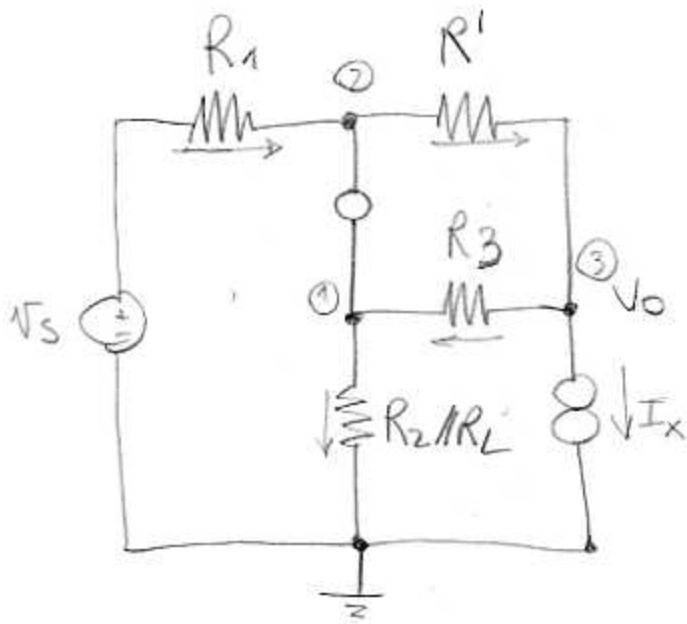2<sup>nd</sup> method (nullator, norator):



node-Voltage Analysis:

$$\left\{ \begin{array}{l} -\frac{V_1}{R_2 \parallel R_L} + \frac{V_3 - V_1}{R_3} = 0 \\ \frac{V_5 - V_2}{R_1} - \frac{V_2 - V_3}{R'} = 0 \\ -\frac{V_3 - V_1}{R_3} + \frac{V_2 - V_3}{R'} - I_x = 0 \end{array} \right.$$

$V_2 = V_1$  (this is imposed by the nullator)

$$\left\{ \begin{array}{l} -\frac{V_1}{R_2 \parallel R_L} + \frac{V_3 - V_1}{R_3} = 0 \\ \frac{V_5 - V_1}{R_1} - \frac{V_1 - V_3}{R'} = 0 \\ -\frac{V_3 - V_1}{R_3} + \frac{V_1 - V_3}{R'} - I_x = 0 \end{array} \right.$$

Using the first two equations:

$$V_3 = R_3 \left( \frac{V_1}{R_2 // R_L} + \frac{1}{R_3} \right) = V_1 \left( 1 + \frac{R_3}{R_2 // R_L} \right)$$

and substituting into the second equation:

$$\frac{V_s - V_1}{R_1} - \frac{V_1}{R'} + \frac{V_3}{R'} = 0$$

⇓

$$\frac{V_s - V_1}{R_1} - \frac{V_1}{R'} + \frac{V_1}{R'} \left( 1 + \frac{R_3}{R_2 // R_L} \right) = 0$$

$$V_1 \left( \cancel{\frac{1}{R'}} + \frac{R_3}{R' (R_2 // R_L)} - \cancel{\frac{1}{R'}} - \frac{1}{R_1} \right) = - \frac{V_s}{R_1}$$

$$V_1 \left( \frac{R_3 (R_2 + R_L)}{R' R_2 R_L} - \frac{1}{R_1} \right) = - \frac{V_s}{R_1}$$

$$V_1 \left( \frac{R_3 R_1 R_2 + R_L R_1 R_3 - R' R_2 R_L}{R' R_2 R_L R_1} \right) = - \frac{V_s}{R_1}$$

$$V_1 = -V_s \frac{R' R_2 R_L}{R_1 R_2 R_3} = -V_s \frac{R_L}{R_2} \Rightarrow I_L = \frac{V_1}{R_L} = -\frac{V_s}{R_2}$$