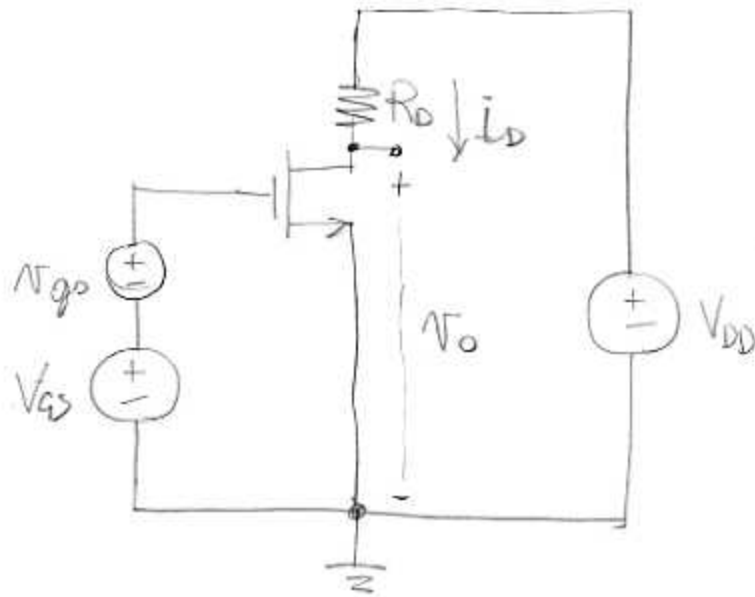


COMMON SOURCE CONFIGURATION

1

In this configuration the source is connected to ground:



We first consider $v_{gs} = 0$, which means performing a DC analysis and computing the quiescent operating point.

We assume the transistor in saturation:

$$I_{DQ} = \frac{K}{2} (V_{GS} - V_T)^2$$



(V_{GS} is basically fixing the quiescent drain current)

$$V_{DSQ} = V_{DD} - R_D I_{DQ} =$$

$$= V_{DD} - R_D \frac{K}{2} (V_{GS} - V_T)^2$$


In order for the transistor to be in saturation, it must be $V_{GS} > V_T$ and $V_{DSQ} \geq V_{GS} - V_T$

Using the load line:

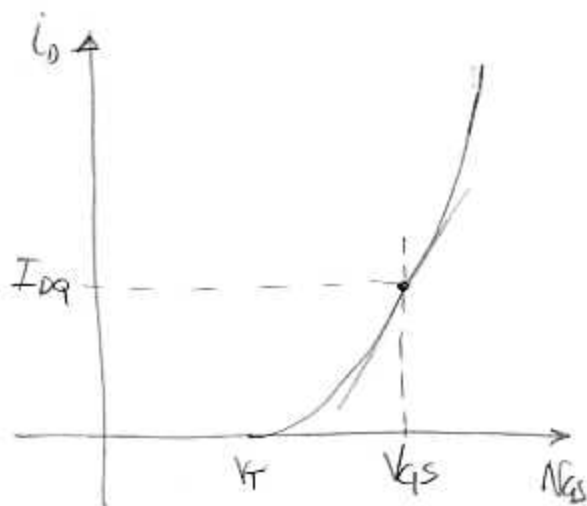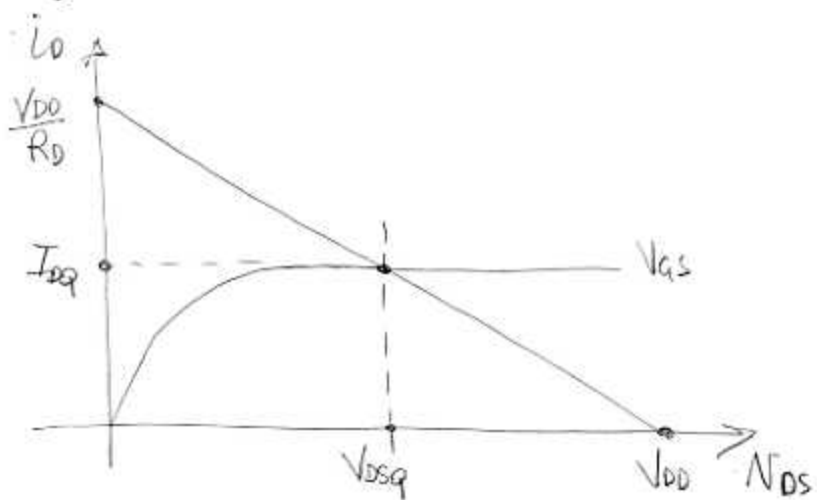


Now we compute $g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS}} = K(V_{GS} - V_T)$

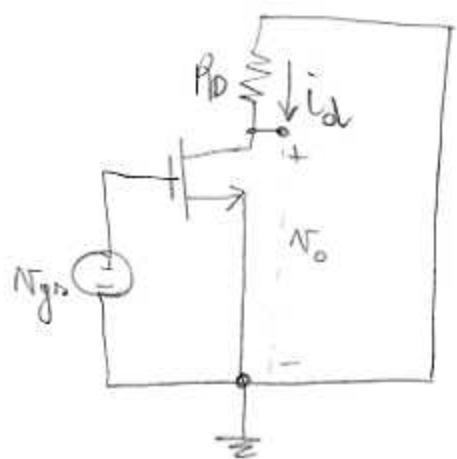and we consider all DC sources equal zero:



eq. model

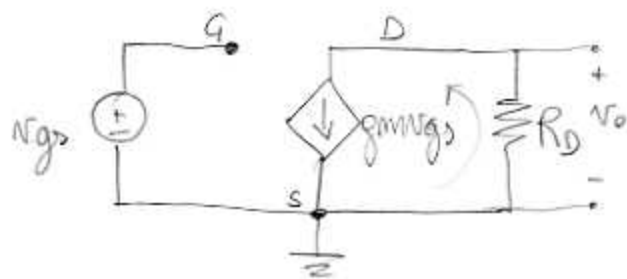

$$V_O = -g_m V_{GS} R_D \Rightarrow \frac{V_O}{V_{GS}} = A_v = -g_m R_D$$

where A_v is the voltage gain.

Graphically the following thing is happening:

