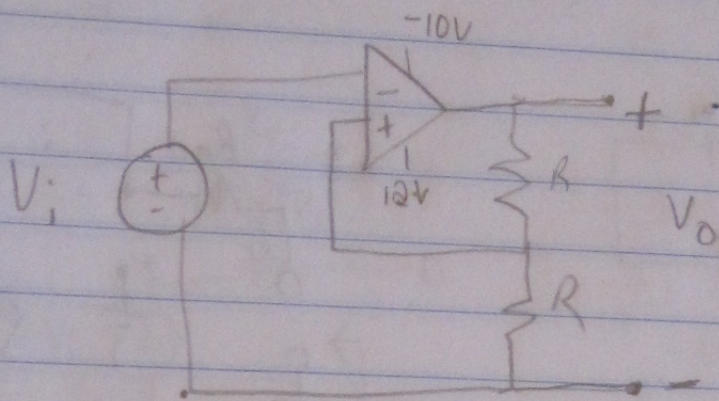



Positive Feedback:



F
-10, 12

$$V_{min} = -10V$$


$$V_{max} = 12V$$

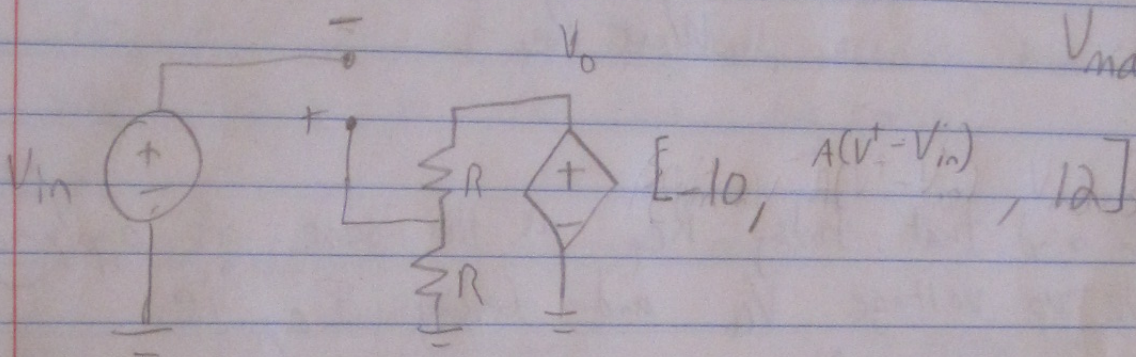

$$V_o = [-10, A(V^+ - V_{in}), 12]$$

$$V^+ \text{ node: } \frac{V^+}{R} + \frac{V^+ - V_o}{R} = 0$$

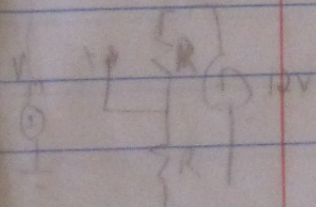
$$\frac{V^+}{R} + \frac{V^+ - [-10, A(V^+ - V_{in}), 12]}{R} = 0$$




$$2V^+ = \frac{[-10, A(V^+ - V_{in}), 12]}{2}$$

Step back and think!

Consider $V_{in} = 0$:

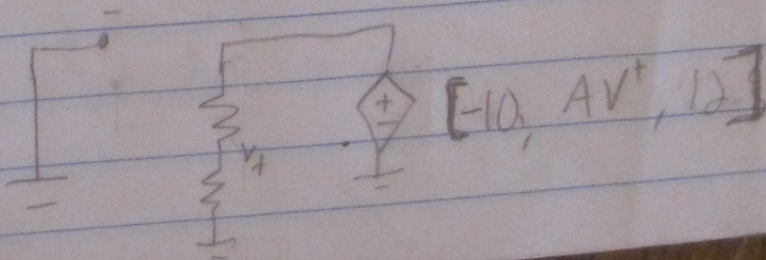

If $V^+ = -5V$

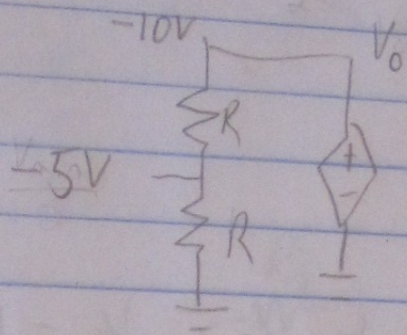


Voltage divider says $V_0 = -10V$
Op-amp says:

$$V_0 = [-10V, \overset{-5V}{\text{gain}}, 12V] = 10V$$

gain not
amps!

Everything is consistent!

If $V^+ = -6V$

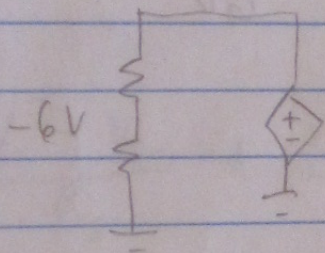


Voltage divider says $V_0 = -12V$

Op-amp says:


$$V_0 = [-10V, \overset{-6V}{\text{gain}}, 12V] = -10V$$

disagreement

Interestingly, if we have:

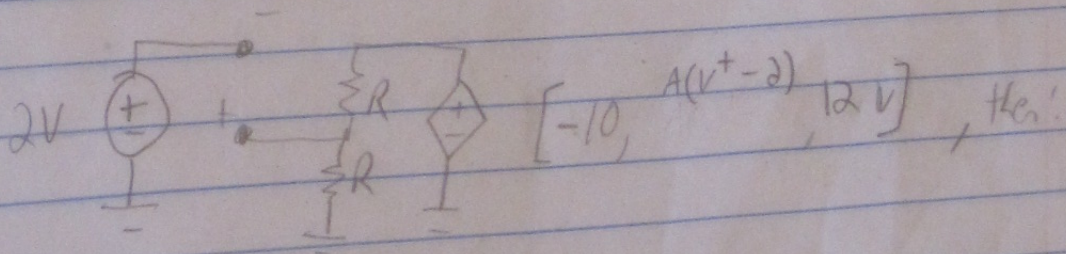

If $V^+ = -5V$

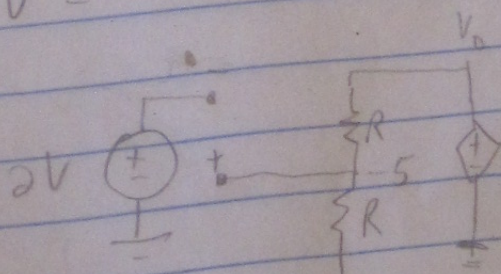


Current divider says $V_0 = -10V$

Op-amp says:

$$[-10, \overset{+(-7)}{\text{gain}}, 10V] = -10V$$

OK!

And if we assume $V^+ = 6V$

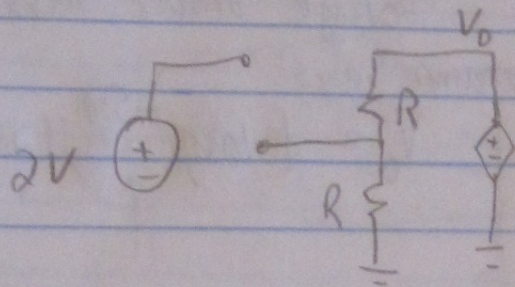

Current divider says $V_o = 12V$
op amp says:

$$[-10, A \cdot (3V), 12] = 12V$$

Consistent! V^+ can be -5V or 6V.

