
EE40
Lecture 7
Josh Hug

7/7/2010

Blackboard Stuff

- HW3 concerns
- Any general questions people might have

General Info

- No lab today
- Midterm on Friday in class
 - **12:10-1:30 [be on time!]**
 - No electronic devices
 - One 8.5"x11" (or A4) sheet of paper
 - Handwritten anything you want, both sides
- HW4 due next Friday (will be posted Friday)
- No positive feedback circuits on the midterm (but there might be on the final)

Project 2

- Project 2 spec to be posted over the weekend
- If you'd like to do something other than the official project, you can submit a specification for your Project 2:
 - Team members (up to 3)
 - Parts list
 - Schematic
- Must have substantial hardware component
 - Microcontrollers are OK, but your project shouldn't be about assembly programming
 - MyDAQ is also OK, but your project shouldn't be about LabVIEW programming
- Custom project proposals due **WEDNESDAY** by 5 PM

Guest Mini-Lecture Today


- Jeff Jansen from National Instruments will be talking today for the last half hour
 - MyDAQ data acquisition device
 - USB device that lets you use your computer in lieu of big bulky specialized test equipment
 - Can use this device to do labs from home or anywhere else a laptop functions
 - If anyone wants to use these in labs, we will have 10 of them available
 - Could be handy for Project 2
 - Must have substantial hardware component (can't just be LabVIEW software written for MyDAQ)

Course Website

- I am assured that the rest of the calendar and the other 5 labs will be posted shortly. Most likely schedule is:
 - 7/13: Project 1 (buzzer)
 - 7/14: Sound synthesizer
 - 7/20: Power supply
 - 7/21: Active filter lab
 - 7/27-8/11: Project 2
- Future reading assignments will be posted 3 days before they're due
 - Micro-deadlines are needed for me, too!





Op-Amp Saturation

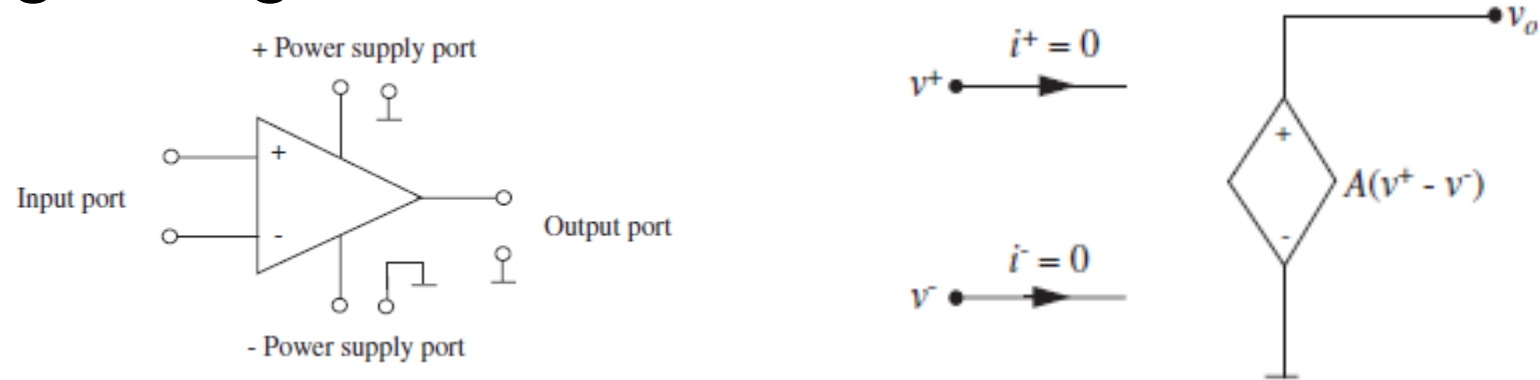- Remember those power ports we've been ignoring?




- They specify the maximum and minimum voltage that our op-amp can deliver
 - If $v_{\min} < A(v^+ - v^-) < v_{\max}$
 - Op-Amp output is $A(v^+ - v^-)$
 - If $A > v_{\max}$,
 - Op-Amp output is v_{\max}
 - If $A < v_{\min}$,
 - Op-Amp output is v_{\min}

Op-Amp Saturation Example

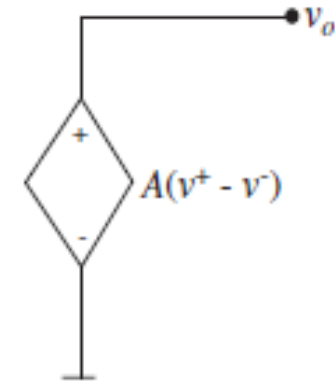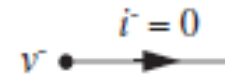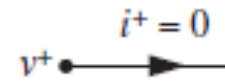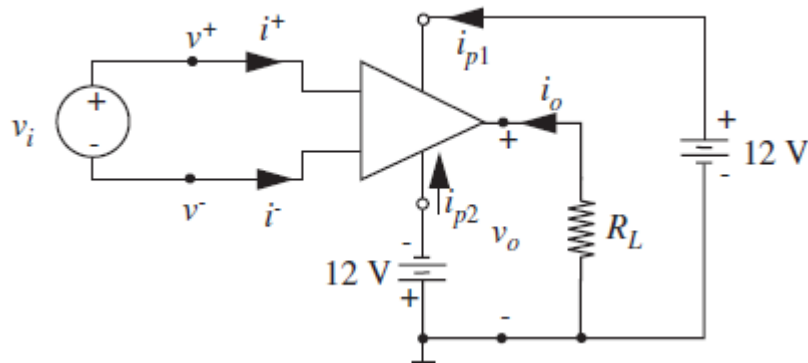


- $v_{max} = 12V, v_{min} = -12V$
- If $A=3$:

V_{in}	V_o
-5 V	-12V
-1V	-3V
2V	6V
1,512,312V	12V

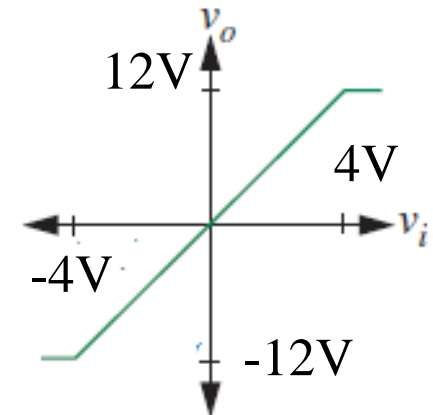

Positive Feedback

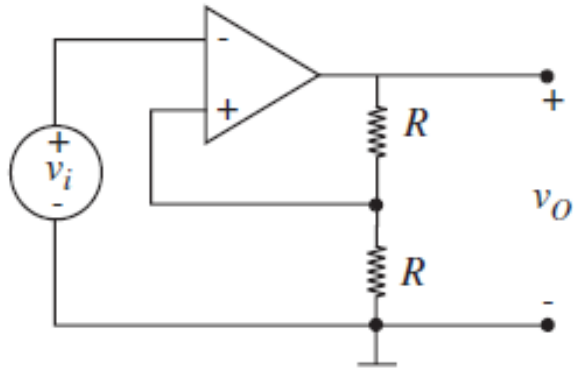


On the board

Another Op-Amp Model Revision

- Real amplifiers deviate from the ideal
 - Input resistance between V^+ and V^-
 - Output resistance at the output of the dependent source
- Another significant problem is “common mode signal amplification”


Common Mode Signal

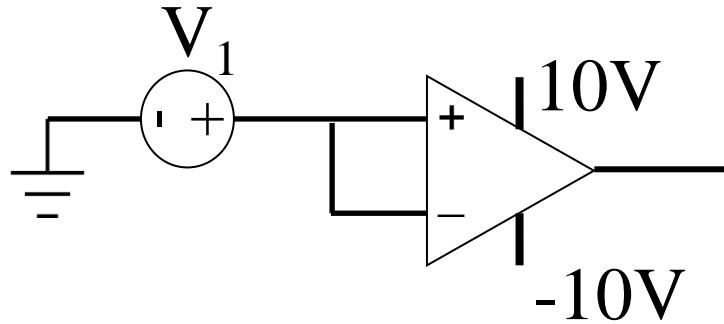

- In theory, the above amplifier would have an output voltage of **0V**
- In practice, even an equal signal will leak through a little

- $$V_{out} = A_d(V^+ - V^-) + \underbrace{\frac{A_c(V^+ + V^-)}{2}}_{\text{New Term}}$$

Common Mode Signal

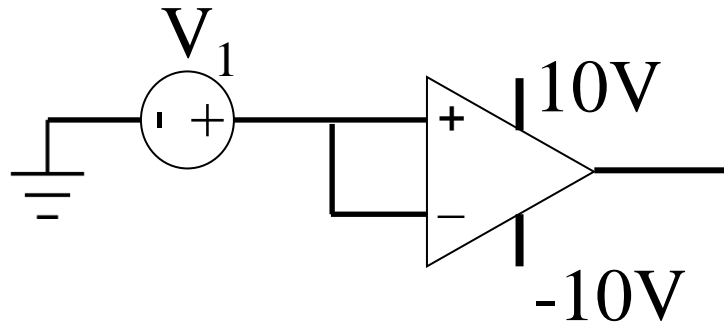

- $V_{out} = A_d(V^+ - V^-) + \frac{A_c(V^+ + V^-)}{2}$
- A_d and A_c are typically not explicitly considered
- Instead, we consider the “Common Mode Rejection Ratio” $CMRR = \frac{A_d}{A_c}$
- Big is good, less common mode signal



Example of using CMRR

- Find V_o as a function of R_s , R_f , CMRR

- (On board)

One of many Op-Amp parameters

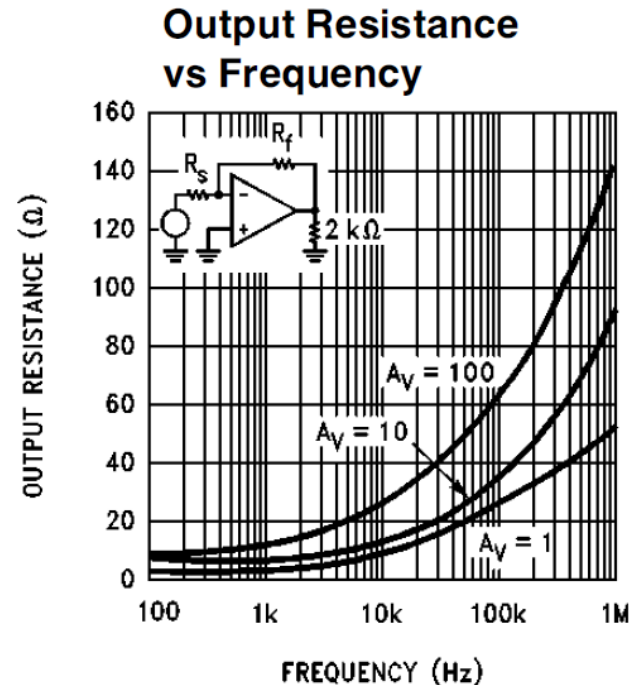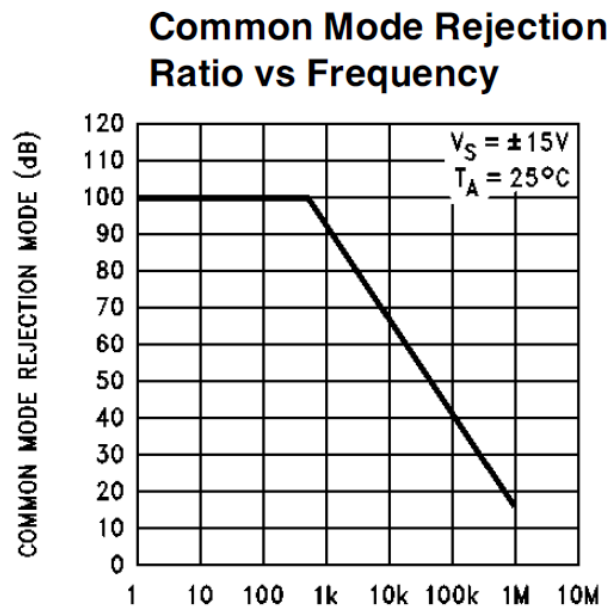- Typical CMRR is 35,000 (~90 dB)
 - Usually measured in db
 - $CMRR_{db} = 20 \cdot \log_{10}(CMRR)$
- In real life, Op-Amps come with multipage data sheets (as do everything else)



How are you feeling about...

- How are you feeling about Node Voltage and solving basic circuits?
 - A. Completely lost
 - B. A little behind
 - C. Alright
 - D. Pretty good
 - E. Feel like I've attained mastery

How are you feeling about...

- How are you feeling about I-V characteristics and Thevenin and Norton equivalents?
 - A. Completely lost
 - B. A little behind
 - C. Alright
 - D. Pretty good
 - E. Feel like I've attained mastery

How are you feeling about...

- How are you feeling about Op-Amp circuits?
 - A. Completely lost
 - B. A little behind
 - C. Alright
 - D. Pretty good
 - E. Feel like I've attained mastery

How are you feeling about...

- How are you feeling about the midterm?
 - A. Terrified
 - B. A little scared
 - C. Neutralish
 - D. Feel prepared
 - E. Feel like I will do excellently

Make up Labs

- Do you need a make up lab?
- A. Yes
- B. No

-
- This is where we stopped

UNIT 2

Elements with Memory a.k.a. Energy Storage Elements

Preview of Unit 2


- In the next major unit of the class, starting next Monday, we'll be discussing elements with memory
 - Capacitor: Gives relationship between I and $\frac{dv}{dt}$
 - Inductor: Gives relationship between V and $\frac{di}{dt}$
- Fundamental mathematical difference is that their IV relationship changes with time
- Fundamental physical difference is that they can store energy
- For the rest of today, we'll give a sneak preview of this material

RC Circuits

- Taking the Live Demo risk, let's check out a quick qualitative circuit simulation

The Capacitor

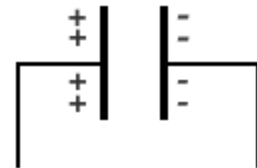
- The basic idea is pretty simple
 - Imagine you have two parallel metal plates, both of which have equal and opposite excess charges
 - Plates are separated by an insulating layer (air, glass, wood, etc)



- The charges would love to balance out
- Insulator blocks them (just as the ground blocks you from falling into the center of the earth)


The Capacitor

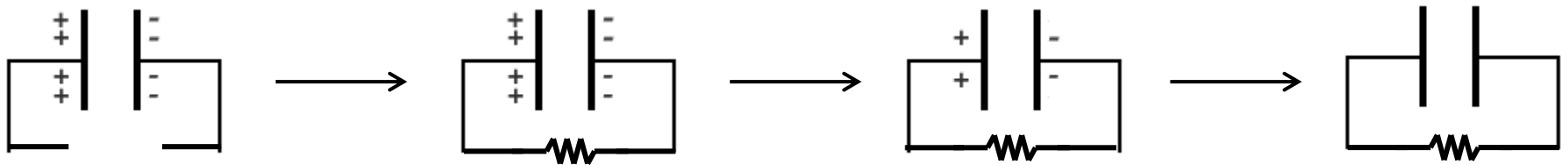- If you were to connect a resistive wire to the plates
 - Charges would flow through the wire
 - Charge flow is current
 - $P = I^2 R$
 - Energy has been released as heat



The Capacitor

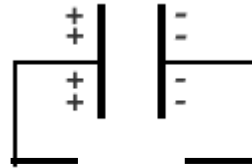- Remember that a voltage is the electrical potential between two points in space



- Here, we have an imbalance of charge, and thus an electric field, and thus a voltage


$$V = EL$$

- Field strength is dependent on number and distribution of charges as well as material properties
- Field length is dependent on size of capacitor
- Capacitor size and material properties lumped into single “capacitance” C

- $V = QC$

The Capacitor

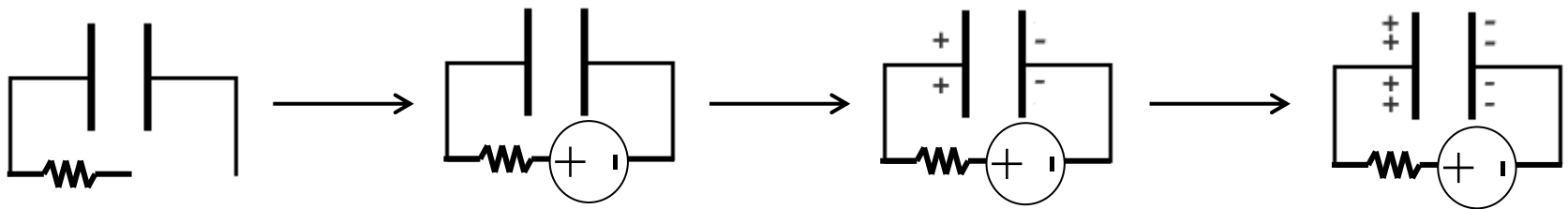
- Thus, if you connect a voltage source to the plates
 - Like charges will move to get away from the source
 - Charge flow is current
 - Current will stop once charges reach equilibrium with voltage source, i.e. $V_C = V_S$
 - Energy has been stored



The Capacitor

Lots of current

Zero current

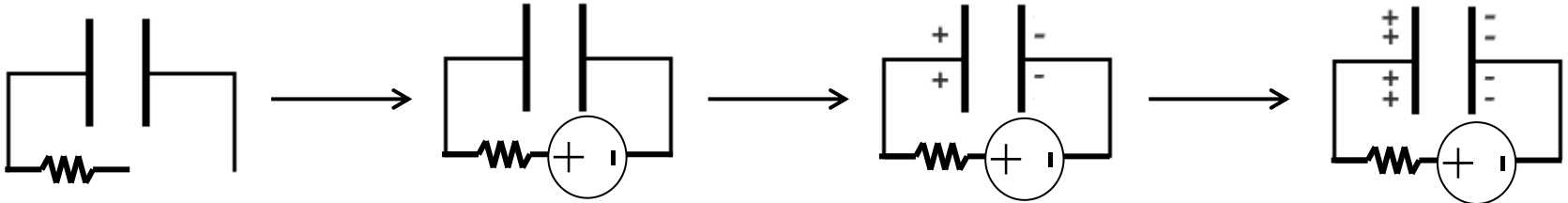


Zero V_C

$V_C = V_S$

$$I = C \frac{dV}{dt}$$

Lots of current


Zero of current

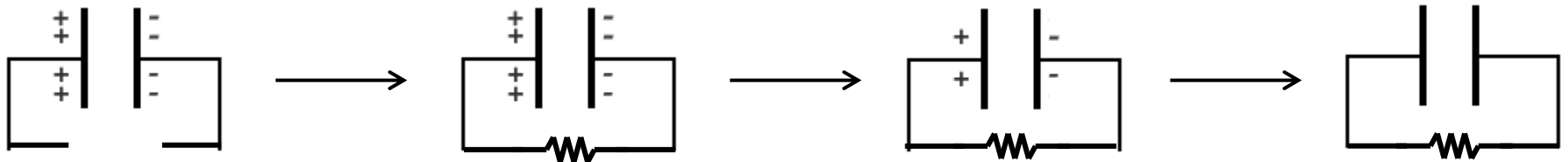

High V_C

Zero V_C


Capacitor

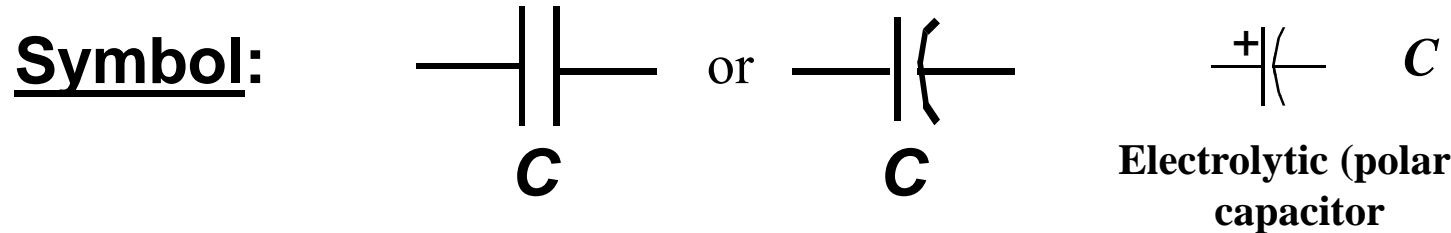

Units: Farads (Coulombs/Volt) These have high capacitance and cannot support voltage drops of the wrong polarity
(typical range of values: 1 pF to 1 μ F; for “supercapacitors” up to a few F!)

Current-Voltage relationship:

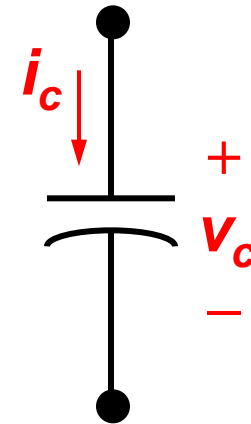
$$i_c = \frac{dQ}{dt} = C \frac{dv_c}{dt}$$



Note: v_c must be a continuous function of time since the charge stored on each plate cannot change suddenly

Node Voltage with Capacitors
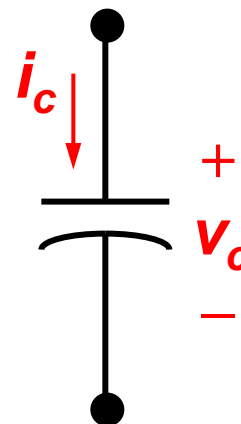
$$i_c = \frac{dQ}{dt} = C \frac{dv_c}{dt}$$




- On board

Ordinary Differential Equations

- Inductors, too, give us a simple 1st order relationship between voltage and current
- Node Voltage with memoryless circuits gave us algebraic equations
- Node voltage with elements with memory will give us Ordinary Differential Equations (ODEs)
- Next week will be a bunch of setting up and solving 1st and 2nd order linear ODEs
- Higher order and especially nonlinear ODEs are tough to solve. For example...

Chua's Circuit

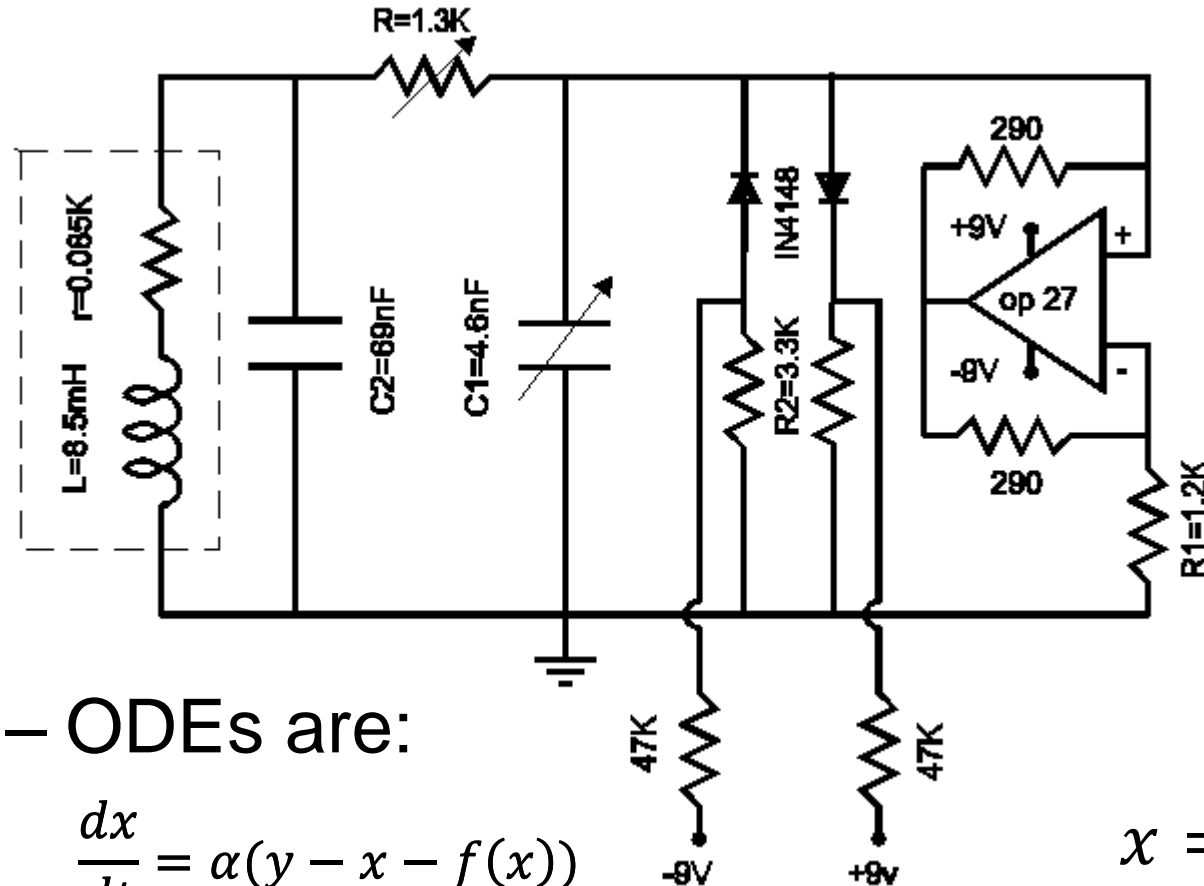

$f(x)$ – response of diodes and resistor block

– ODEs are:

$$\frac{dx}{dt} = \alpha(y - x - f(x))$$

$$\frac{dy}{dt} = x - y + z$$

$$\frac{dz}{dt} = -\beta y$$

$$x = v_{C1}$$

$$y = v_{C2}$$

$$z = i_L$$

Chua's Circuit

- Despite simplicity of ODEs


$$\frac{dx}{dt} = \alpha(y - x - f(x))$$

$$\frac{dy}{dt} = x - y + z$$

$$\frac{dz}{dt} = -\beta y$$

- Exhibits chaos!

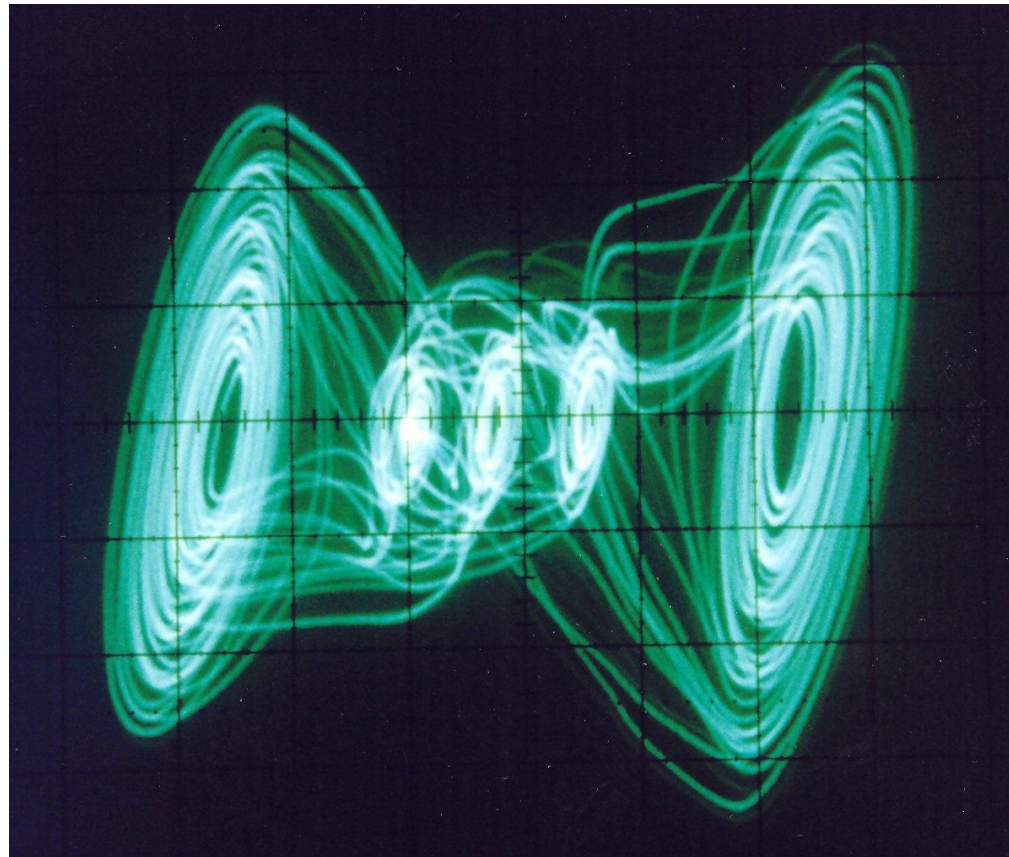Invented by current
UC Berkeley EECS
professor Leon
Chua in 1983



Capacitors

- Useful for
 - Storing Energy
 - Filtering
 - Modeling unwanted capacitive effects, particularly delay

Good luck on your midterm!

- Now on to Jeff's presentation