



EECS 42 – Introduction to Electronics for Computer Science

Fall 2001,
Dept. EECS,
UC Berkeley
Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee42/>

Prof. A. R. Neureuther
510 Cory 642-4590
Tentative OH M, Tu, W, (Th), F 11

Solutions Midterm #2 November 7th, 2001

**Closed Book, Closed Notes
Write on the Exam paper**

Print Your Name: _____

Sign Your Name: _____

Show your work so that the method as well as the answer can be graded for correctness and completeness. Correct answers alone are only worth 70% of full credit.

Problem	Possible	Score
I	30	
II	25	
III	22	
IV	23	
Total	100	


I (30 Points) Logic and Timing Diagrams

Inputs A, B, and C have all been zero (low) for a long time and then at $t = 0$, A, B and C go to (high) for a long time.

- a) (5 Points) Find the values of X, Y and Z just before $t = 0$, and then as t goes to infinity.


	Before $t = 0$	As $t \rightarrow \infty$
X	1	0
Y	1	1
Z	1	0

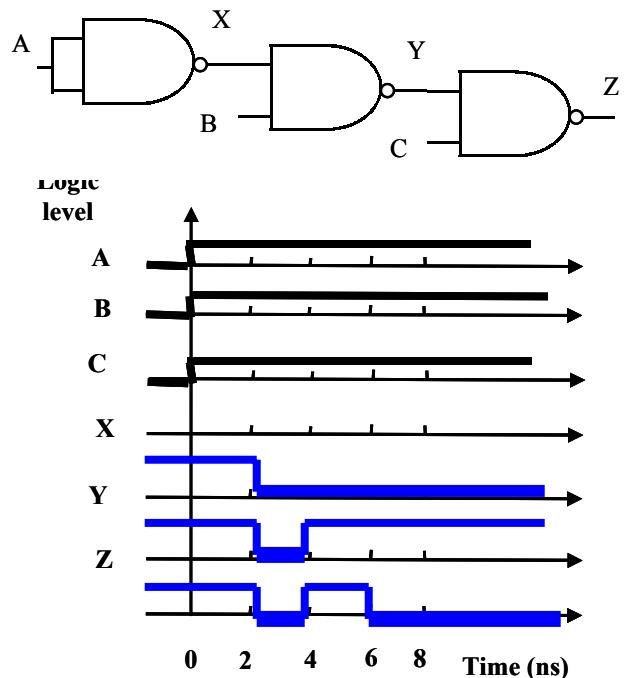- b) (10 points) Complete the timing diagram to the right assuming that each gate has a propagation delay of 2 ns before the correct output appears at its output.



- c) (7 Points) For the CMOS circuit implementation to the right of the NAND gate logic circuit above and the signal changes in part a), **find the time at which the change reaches V_{OUT_1}** . State the delay in terms of $0.69RC$ using R_U and R_D (from the switched resistor device models) and the capacitors shown.

$$\tau = 0.69(2R_D)C_{OUT1}$$

 


- d) (10 points) (8 Points) For the CMOS circuit implementation to the right of the NAND gate logic circuit above and the signal changes in part a), **find the time at which the change reaches V_{OUT_3}** . State the delay in terms of combinations of $0.69RC$ using R_U and R_D (from the switched resistor device models) and the capacitors shown.

$$\tau = 0.69(2R_D)C_{OUT1} + 0.69(R_U)C_{OUT2} + 0.69(2R_D)C_{OUT3}$$

II (25 Points) Ideal Op-Amp Analysis

Use the ideal op-amp analysis method in this problem.

 - a) (8 Points) Find V_{OUT1} in terms of the resistances and input voltages.



$$\frac{(V_1 - V_2)}{R_1} + \frac{(V_{OUT1} - V_2)}{R_3} = 0$$

$$V_{OUT1} = V_2 + \frac{R_3}{R_1} (V_2 - V_1)$$

- b) (9 Points) Give sufficient additional equations for finding V_{OUT2} in terms of the resistances and input voltages. Do not solve.

$$V_{+2} = V_4 + (V_3 - V_4) \frac{R_7}{R_6 + R_7}$$



$$V_{OUT2} = V_{+2} + \frac{R_8}{R_5} (V_{+2} - V_{OUT1})$$

- c) (8 Points) Assume that $V_{OUT2} = k_1 V_1 + k_2 V_2 + k_3 V_3 + k_4 V_4$. For $i = 1, 4$ complete the table below by determining the sign of k_i and listing the resistors that will contribute to k_i . Hint: Start with what you know from part a) to reach V_{OUT1} and then apply this principle again.

Term	Sign	Contributing Resistors
V_1	+	R1, R3, R5, R8
V_2	-	R1, R3, R5, R8
V_3	+	R5, R6, R7, R8
V_4	+	R5, R6, R7, R8


III (22 Points) Device I vs. V Curves

  - a) (10 Points) For the logic circuit and device characteristics shown find V_{OUT} when $V_{IN} = 3V$.




$V_{oc} = 40 \mu\text{A} \times 100\text{k ohms} = 4\text{V}$
 $I_{in} = 40 \mu\text{A}$
Intersection with $V_{in} = 3\text{V}$ at $V_{out} = 1.5\text{V}$

 - b) (12 Points) For the logic circuit shown approximately sketch the voltage transfer function V_{OUT} vs. V_{IN} . Specify values of V_{OUT} for $V_{IN} = 0, 3$ and 5V .



IV (23 Points) Advanced Circuits with Dependent Sources

a) (10 Points) Find V_{OUT}/V_{IN} .

 

Node equation (KCL) at the output node.

$$i_{IN} + \beta i_{IN} + \frac{(0 - V_{OUT})}{R_E} = 0$$

$$i_{IN} = \frac{(V_S - V_{OUT})}{R_{IN}}$$

Substitute

$$(\beta + 1) \frac{(V_S - V_{OUT})}{R_{IN}} + \frac{(0 - V_{OUT})}{R_E} = 0$$

Rearrange

$$V_{OUT} = \frac{(\beta + 1)R_E}{(R_{IN} + (\beta + 1)R_E)} V_S$$

=> Gain is less than but close to 1 so the output follows the input.

b) (13 Points) Find the Thevenin resistance looking into the output.

$$i_{OUT} = \frac{V_{OUT}}{R_{IN}} + \frac{V_{OUT}}{R_E} - \beta i_{IN}$$

$$i_{IN} = -\frac{V_{OUT}}{R_{IN}}$$

$$i_{OUT} = \left(\frac{1}{R_E} + \frac{(\beta + 1)}{R_{IN}} \right) V_{OUT}$$

=> sees R_E in parallel with $R_{IN}/(\beta + 1)$ which is a low output impedance

Looking in the output RE and RIN are in parallel and current flows backward through RIN. However the dependent source draws β times more current than goes backward through RIN and by drawing a current proportional to the conductance of RIN it increases the conductance and reduces the resistance by a factor of $(\beta + 1)$. It is a form of a current supply that sucks in additional current.