



# EECS 42 – Introduction to Electronics for Computer Science

Fall 2001,  
Dept. EECS,  
UC Berkeley  
Course Web Site <http://www-inst.EECS.Berkeley.EDU/~ee42/>

Prof. A. R. Neureuther  
510 Cory 642-4590  
Tentative OH M, Tu, W, (Th), F 11


## Quiz #1 September 26, 2001

Show your work so that the method can be graded for correctness and completeness and all of the points do not depend on just the final numerical value.

### I (20 Points) Basic Circuit Analysis

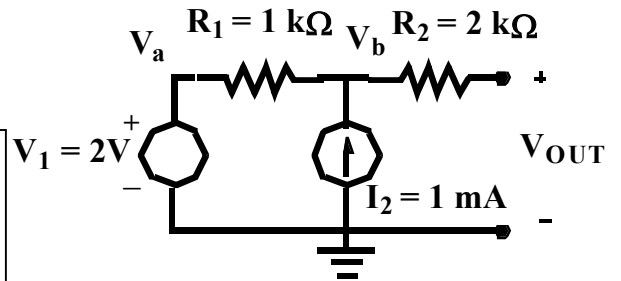a) For the circuit shown find  $V_b$ .

No current in the output.  $I_2$  goes through  $R_1$ .  
 $V_b = V_1 + I_2 R_1 = 2V + (1mA)(1k\Omega)$   
 $= 2V + 1V = 3V$




b) Find the Thevenin resistance seen looking into the output terminals.

Turn  $V_1$  to zero = short; Turn  $I_2$  to zero = open  
 See  $R_2$  in series with  $R_1$   
 $R_{THEVENIN} = R_1 + R_2 = 3k\Omega$
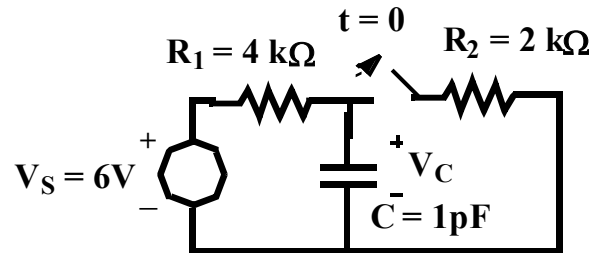
### II (20 Points) Transient Analysis

The switch in the circuit to the right is opened at  $t = 0$ . Find an equation that describes  $V_C(t)$ .



$V_C(t) = A + Be^{-t/\tau}$   
 $V_C(0) = \text{Voltage Divider} = V_S (R_2 / (R_1 + R_2))$   
 $= 6 (2k\Omega / (4k\Omega + 2k\Omega)) = 2V = A + B$   
 $V_C(\text{infinity}) = V_S = 6V = A$   
 Time constant  $\tau = R_1 C = 4k\Omega \cdot 1pF = 4 \text{ ns}$

$$V_C(t) = 6V - 4e^{-t/4ns}$$