

EE 42
Midterm Exam No. 1
27 February 2002

Put your name (printed, signed), your student identification number, and the number of the Discussion Section that you attend here:

Print Name (last, first) _____ Sign Name _____
S. I. D. _____ Discussion Section No. _____


NOTE: THERE ARE SEVERAL DIFFERENT VERSIONS OF THIS EXAM IN THE ROOM. Your responses will be different from those of your neighbors. Keep your eyes on your own paper.

PLEASE DON'T OPEN THE TEST UNTIL THE PROCTOR SAYS YOU MAY BEGIN

Table 1:

Page	Points/ Possible
2	/15
3	/15
4	/35
5	/15
6	/10
7	/10
TOTAL	/100

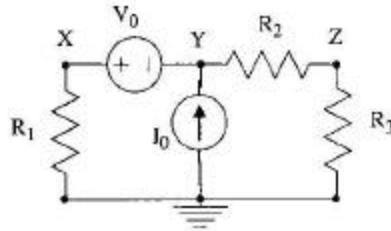1 (15 points). Write enough nodal equations to solve for all unknown currents and voltages in the circuit shown below. (IT IS NOT NECESSARY TO SOLVE THESE EQUATIONS.)



Nodes X and Y

We have a supernode.

$$\boxed{V_X - V_Y = V_0} \quad (1)$$

$$\boxed{\frac{V_X}{R_1} - I_0 + \frac{V_Y - V_Z}{R_2} = 0} \quad \text{or} \quad \frac{V_X}{R_1} - I_0 + \frac{V_Y}{R_2 + R_3} = 0 \quad (2)$$


Node Z

$$\boxed{\frac{V_Z - V_Y}{R_2} + \frac{V_Z}{R_3} = 0} \quad (3)$$



3 Unknown voltages = V_X, V_Y, V_Z

3 Equations.

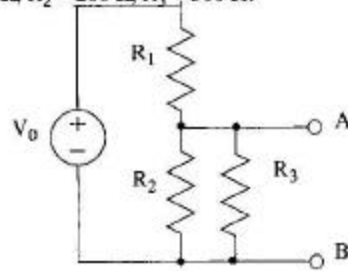2. (15 points). Draw the Norton equivalent circuit, and find its I_N and R_N , that is equivalent to the circuit to the left of the terminals A-B shown below. The values of the elements are: $V_0 = 6V$, $R_1 = 100 \Omega$, $R_2 = 200 \Omega$, $R_3 = 300 \Omega$.



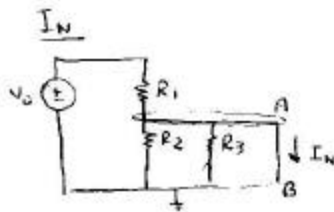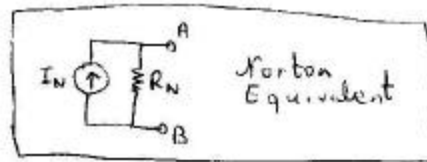- a. Draw Norton equivalent circuit here \rightarrow
 b. $I_N = 60 \text{ mA}$
 c. $R_N = 54.5 \Omega$




1st way: Nodal Analysis

$$\frac{V_A - V_0}{R_1} + \frac{V_A}{R_2} + \frac{V_A}{R_3} + I_N = 0 \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} I_N = \frac{V_0}{R_1} = \frac{6V}{100\Omega} \\ \Rightarrow I_N = 60 \text{ mA} \end{array}$$


$V_A = 0$ (Goes to ground through a wire)

2nd way: The wire takes out R_2, R_3

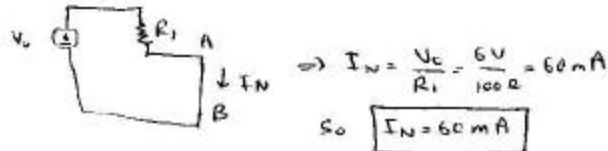

R_N

- 1) Deactivate sources

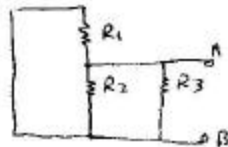

So, we have R_1, R_2, R_3 in parallel $\Rightarrow R_N = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \frac{600}{11} \Omega$
 $\Rightarrow R_N = 54.5 \Omega$


True-False Questions:

- 3. (5 points) The equivalent resistance of six resistors connected in parallel is larger than the value of any of the individual resistors. True False
- 4. (5 points) The equivalent resistance of six resistors connected in series is smaller than the value of any of the individual resistors. True False
- 5. (5 points) The prefixes used to represent 1000, 1/1000, and 10^{-9} , respectively, are mezza, milli, and nano, respectively. True False
- 6. (5 points). To measure current flowing in a circuit element you connect an ammeter across the circuit element. *False.*
- 7. (5 points) An ideal voltmeter is electrically equivalent to a short circuit (zero resistance). True False
- 8. (5 points) The electrical units for capacitance, inductance and voltage are henries, farads and volts. True False
- 9. (5 points) If a 4-volt supply delivers current through a switch, resistor, and inductor connected in series, the voltage generated when the switch is operated cannot exceed 4 V. True False

3. It should have been smaller than

4. It should have been larger than


5. kilo, milli and nano

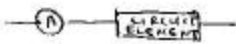6. The ammeter is connected in series : 

7. It is electrically equivalent to an open circuit


8. Farads, Henries, Volts

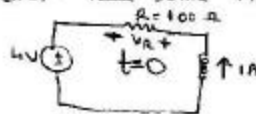9. If the inductor had some initial current ~~of 1A~~ ^{of 1A} stored in it then:




At $t=0$ this is what the circuit looks like, as the inductor holds on to its current value of 1A temporarily. Then at $t=0$, $V_R = (1A)(100\Omega) = 100V > 4V$

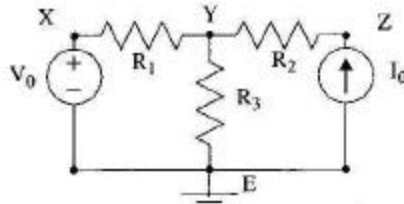
10. (5 points) Redraw the circuit below to show its electrical equivalent after you have "turned off" the independent sources (which you might do in order to find the Thevenin equivalent resistance, R_T , or in order to use superposition to analyze the circuit).




with the voltage source off

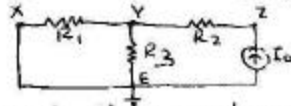

with the current source off

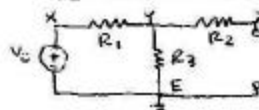

OR with both of them off

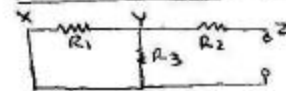


Note


R_2 does not really affect voltage calculation but it does affect Thevenin resistance calculation so it is not removed

11. (5 points) An uncharged $60 \mu\text{F}$ capacitor is suddenly connected to a 9V battery in series with a 100Ω resistor, at time $t = 0$.

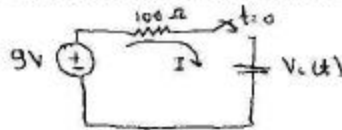- a. The maximum current that flows is 90 (give units mA) and it occurs at time $t = \underline{0}$.
 b. The minimum current that flows is 0 (give units mA) and it occurs at time $t = \underline{\infty}$.



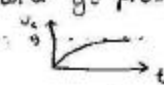After switching, V_c will go from 0V to 9V like so:



The current I flowing through is $\frac{9 - V_c(t)}{100}$ (By applying Ohm's law on the 100Ω resistor)

So: $I = \frac{9 - V_c(t)}{100}$

max I : when $V_c(t) = 0$ which happens at $t = 0$ (Initially uncharged capacitor)
 $\Rightarrow I_{\text{max}} = \frac{9\text{V}}{100 \Omega} = 90\text{mA}$


min I : when $V_c(t) = 9\text{V}$ which happens at $t = \infty$ (capacitor behaves like an open circuit)
 $\Rightarrow I_{\text{min}} = 0\text{mA}$

12. (5 points) When analyzing a first-order transient circuit problem, which of these quantities cannot change instantaneously (check all that apply)::

- a. Voltage across a resistor
- b. Current flowing through a capacitor
- c. Voltage across a capacitor
- d. Energy stored in an inductor
- e. Current flowing in an inductor
- f. Charge in a capacitor
- g. None of these

13. (6 points) A 120V supply is connected to a 500 Ω and a 700 Ω resistor connected in series. What is the rate of energy dissipation in

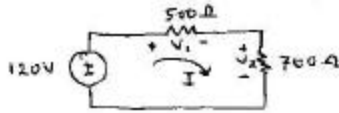- a. The 500 Ω resistor: 5 (give units: W).
 b. The 700 Ω resistor: 7 (give units: W).
 c. The 120-V supply: -12 (give units: W).



$$I = \frac{120V}{500\Omega + 700\Omega} = 0.1A$$

$$\text{Power}_{500\Omega} = I^2 \cdot (R_{500\Omega}) = (0.1A)^2 \cdot (500\Omega) = \boxed{5W}$$

$$\text{Power}_{700\Omega} = I^2 \cdot (R_{700\Omega}) = (0.1A)^2 \cdot (700\Omega) = \boxed{7W}$$


$$\text{Power}_{\text{source}} = (\text{Voltage across source}) \times \left(\begin{array}{l} \text{current flowing from} \\ \text{its +ve term} \\ \text{straight to} \\ \text{the -ve.} \end{array} \right)$$

$$= (120V)(-I) = (120V)(-0.1A) = \boxed{-12W}$$

(so the source dissipates negative power so it actually produces power)

A quick check: The sum of all powers has to be zero: $5 + 7 - 12 = 0$

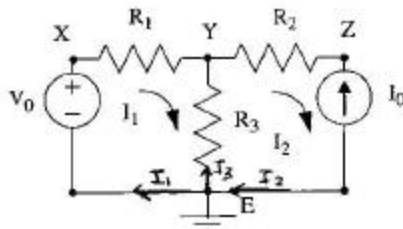14. (4 points) Write an equation for the voltage V_{EY} across resistor R_3 in terms of the loop (mesh) currents indicated in this circuit:




Apply Kirchoff's Law at E: $I_2 = I_3 + I_1 \Rightarrow I_3 = I_2 - I_1$

$$V_{EY} = R_3 (\text{current flowing through } R_3 \text{ from E to Y}) = R_3 \cdot (I_2 - I_1)$$

$$\Rightarrow \boxed{V_{EY} = R_3 \cdot (I_2 - I_1)}$$

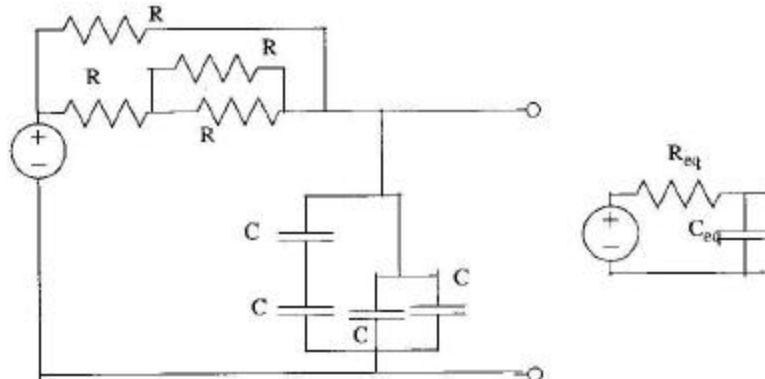
15. (10 points) The circuit below shows a number of resistors and capacitors, in addition to an independent ideal voltage source. Combine the resistors into a single resistor R_{eq} that is in series with the voltage source and an equivalent capacitor C_{eq} (so that you could apply transient analysis to the circuit whose time constant would be $R_{eq}C_{eq}$). Note: all resistors are $1\text{ k}\Omega$ and all capacitors are $2\text{ }\mu\text{F}$.



Deactivate the source

a. $R_{eq} = 600\ \Omega$

b. $C_{eq} = 5\ \mu\text{F}$

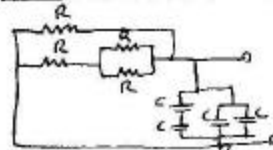


$$R_{\text{series}} = R_1 + R_2 + R_3 + \dots + R_N$$

$$R_{\parallel} = R_{\text{parallel}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)^{-1}$$

$$C_{\text{series}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right)^{-1}$$

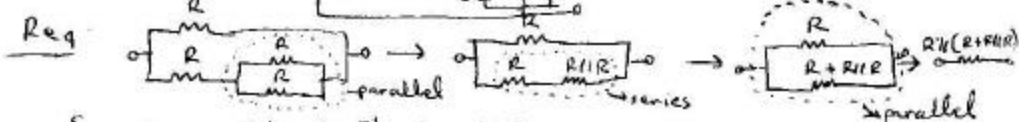
$$C_{\parallel} = C_1 + C_2 + \dots + C_N$$



So $R_{\parallel} = \left(\frac{1}{R} + \frac{1}{R} \right)^{-1} = \frac{R}{2} = \frac{1\text{ k}\Omega}{2} = 500\ \Omega$

$R + R_{\parallel} = 1\text{ k}\Omega + 500\ \Omega = 1500\ \Omega$

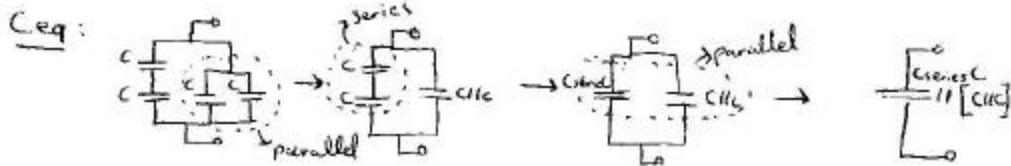$R_{\parallel} (R + R_{\parallel}) = \left(\frac{1}{1000\ \Omega} + \frac{1}{1500\ \Omega} \right)^{-1} = 600\ \Omega \Rightarrow \boxed{R_{eq} = 600\ \Omega}$



$C_{\parallel} = C + C = 4\ \mu\text{F}$

$C_{\text{series}} = \left(\frac{1}{C} + \frac{1}{C} \right)^{-1} = 1\ \mu\text{F}$

$[C_{\text{series}}] \parallel [C_{\parallel}] = 4\ \mu\text{F} + 1\ \mu\text{F} = 5\ \mu\text{F} \Rightarrow \boxed{C_{eq} = 5\ \mu\text{F}}$