

PRACTICE PROBLEMS

(eddieng@eeecs)

Draw logic gates implementation of the following equations

1, $F = AB \oplus C$, " \oplus " = XOR






2, $G = A\bar{B} + (\bar{C} + D)(E)$

3, $F = A\bar{B} + ABC$

4, $G = \bar{X}Y\bar{Z} + YZ + \bar{Y}X$

5, $F = \overline{(X \oplus Y)(\bar{Z})}$

     Derive Boolean equations from the following circuits and simplify results if you can :



10, Obtain Boolean equations from the truth table :


inputs			outputs : I, J, K, L, M, N					
X	Y	Z	I	J	K	L	M	N
0	0	0	0	0	1	1	0	0
0	0	1	0	1	1	0	0	1
0	1	0	0	1	1	1	0	1
0	1	1	0	0	1	1	0	1
1	0	0	0	1	1	0	1	1
1	0	1	0	0	1	0	0	1
1	1	0	1	0	1	1	0	1
1	1	1	1	1	1	0	1	1

11, a, Consider $F = (A+B) \cdot C$. Draw function F using one OR gate and one AND gate.

b, Draw F using only NOR gates. (Hint: use De Morgan's Theorem)

c, Draw F using only NAND gates.

12, Consider the following inverter :

 

If $R_P = 1.5k\Omega$, $R_N = 1.0k\Omega$, $C_{LOAD} = 1pF$, what is the delay from IN to OUT when OUT is making a low to high transition? A High to low transition? What is the average?