


SOLUTIONS

(eddieng@eeecs)

1, $F = AB \oplus C$



2, $G = A\bar{B} + (\bar{C} + D)(E)$

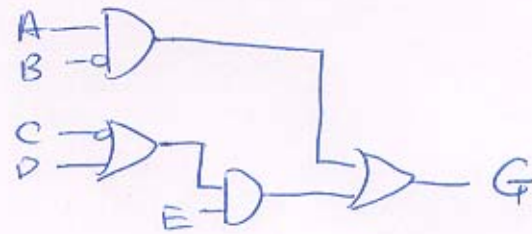

3, $F = A\bar{B} + ABC$

Before start drawing this one, we can simplify F by:

$$F = A(\bar{B} + BC)$$

redundant $\Rightarrow \bar{B} + BC \equiv \bar{B} + C$

BC	\bar{B}	BC	$\bar{B} + BC$	$\bar{B} + C$
00	1	0	1	1
01	1	0	1	1
10	0	0	0	0
11	0	1	1	1

↑ SAME

$$F = A(\bar{B} + C)$$



4, $G = \bar{X}Y\bar{Z} + YZ + \bar{Y}X = Y(\bar{X}\bar{Z} + Z) + \bar{Y}X$


$$= Y(\bar{X} + Z) + \bar{Y}X$$

$$= Y\bar{X} + YZ + \bar{Y}X$$

$$= X \oplus Y + YZ$$

(combine 1st & 3rd terms)


4 (cont)

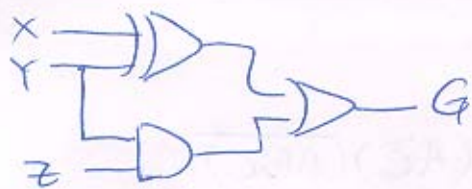


5, $F = \overline{(X \oplus \bar{Y})Z}$



6,

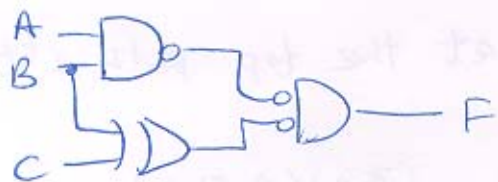

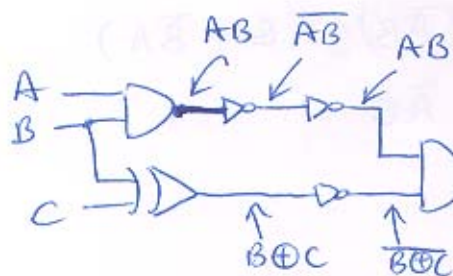If you have problem with the circle notations, replace them with inverters:



$$F = (AB)(\overline{B \oplus C})$$

$$= (AB)(BC + \bar{B}\bar{C})$$


$$= AB \cdot BC + AB \cdot \bar{B}\bar{C}$$

$x \cdot \bar{x} \equiv 0$ guarantee!
 $x \cdot x \equiv x$

$$\overline{(\overline{ABC})} = ABC$$


$$YX + (Y+X)S = YX + YS + XS = 1$$

7,

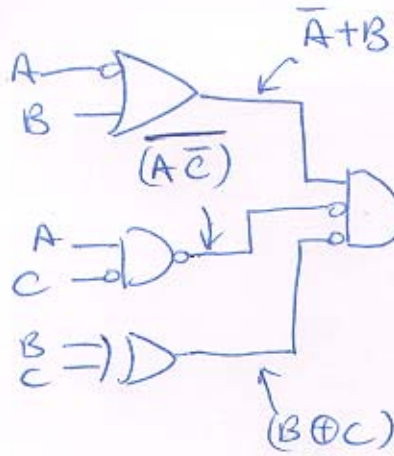


$$\begin{aligned}
 G &= (\bar{A} + B)(A\bar{C})(B \oplus C) \\
 &= (\bar{A} \cdot A\bar{C} + B \cdot A\bar{C})(\bar{B}\bar{C} + BC) \\
 &= (A\bar{B}\bar{C})(\bar{B}\bar{C} + BC) \\
 &= \underbrace{A\bar{B}\bar{C}}_0 \cdot \bar{B}\bar{C} + \underbrace{A\bar{B}\bar{C}}_0 \cdot BC \\
 &= \boxed{0} \quad ! \quad \text{No matter what the inputs, } G=0 \text{ always are}
 \end{aligned}$$

8,

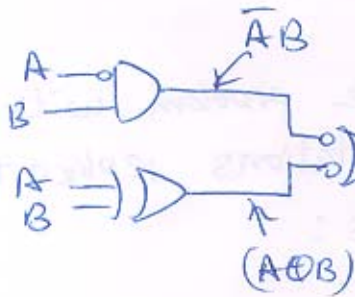


(let's look at the top path 1st.)
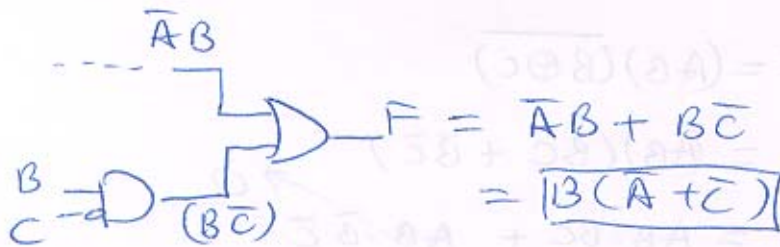
$$\begin{aligned}
 &(\overline{AB + A \oplus B}) = (\bar{A}\bar{B})(A \oplus B) \\
 &= (\bar{A}\bar{B})(\bar{A}B + \bar{B}A) \\
 &= \bar{A}\bar{B}
 \end{aligned}$$



$$\begin{aligned}
 F &= \bar{A}B + B\bar{C} \\
 &= \boxed{B(A + \bar{C})}
 \end{aligned}$$

9,

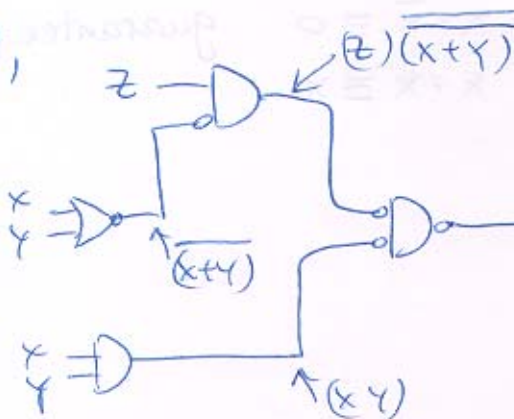


$$K = \overline{z(x+y)(x+y)}$$

$$= z(x+y) + xy$$

$$\boxed{K = zx + zy + xy}$$


9 (cont)

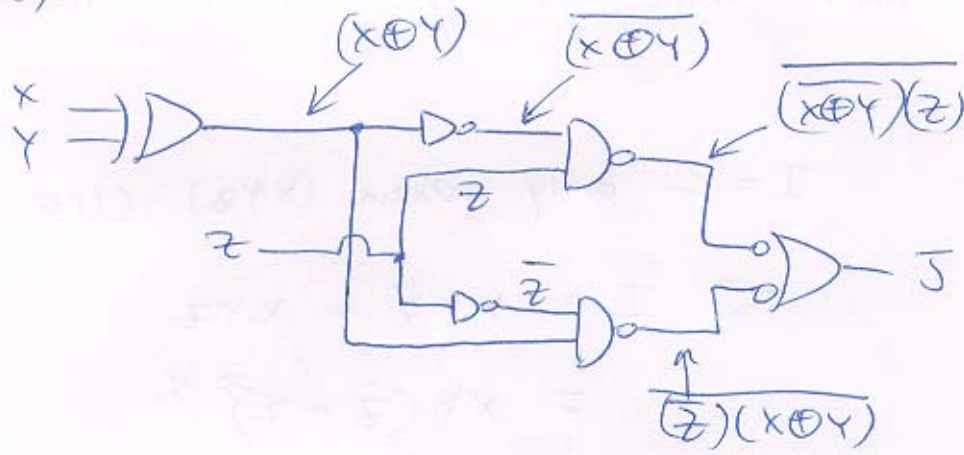

$$J = (X \oplus Y)z + \bar{z}(X \oplus Y)$$

$$J = X \oplus Y \oplus z$$

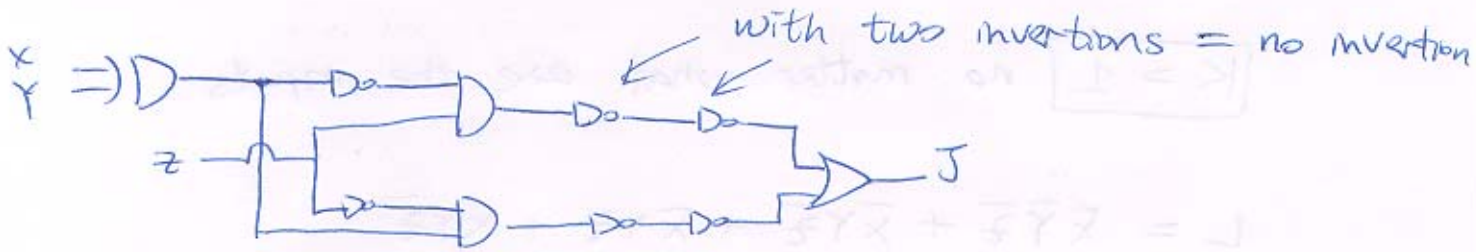Again the circles can be replaced by inverters ...



if x is replaced by A

Y " " by B

Z " " by Ci

K " " by Cout

J " " by SUM

⇒ This is a 1-bit

FULL ADDER

$$\bar{B}Y + Y\bar{B} + \bar{B}Y = J$$

$$\bar{B}Y + \bar{B}Y = M$$

$$(\bar{B} + \bar{B})Y =$$

$$(\bar{B} \oplus \bar{B})Y = M$$

10, From the truth table, always focus on the 1's

X	Y	Z	I
1	1	0	1
1	1	1	1

$X\bar{Y}\bar{Z}$	\rightarrow	110	1
$X\bar{Y}Z$	\rightarrow	111	1

$I = 1$ only when $(XYZ) = (110 \text{ \& } 111)$

$$\Rightarrow I = X\bar{Y}\bar{Z} + X\bar{Y}Z$$

$$= X\bar{Y}(\bar{Z} + Z) \quad 1$$

$$I = \boxed{X\bar{Y}}$$

$J = 1$ when there is odd number of 1's.

$$\boxed{J = X \oplus Y \oplus Z}$$

$K = 1$ no matter what are the inputs.

$$L = \bar{X}\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z}$$

$$= \bar{X}\bar{Z}(\bar{Y} + Y) \quad 1 + \bar{X}YZ + X\bar{Y}\bar{Z}$$

$$= \bar{X}(\bar{Z} + Z) + X\bar{Y}\bar{Z}$$

$$= \bar{X} + \bar{X} + Y + X\bar{Y}\bar{Z}$$

$$= \bar{X} + Y(\bar{X} + \bar{Z})$$

$$\boxed{L = \bar{X} + Y + Y\bar{Z}}$$

$$M = X\bar{Y}\bar{Z} + X\bar{Y}Z$$

$$= X(\bar{Y}\bar{Z} + \bar{Y}Z)$$

$$\boxed{M = X(\bar{Y} \oplus Z)}$$

$N = 1$ in all cases except when $x=y=z=0$

in this case it's easier to obtain \bar{N}

$$\bar{N} = \bar{x} \bar{y} \bar{z} \quad \text{or} \quad \boxed{N = \overline{(\bar{x} \bar{y} \bar{z})}}$$

11a, $F = (A+B)C$





b, De Morgan's theorem states that =

$$X + Y = \overline{(\bar{X} \bar{Y})}$$

$$F = (A+B)C = \overline{(\bar{A} \bar{B})} C$$

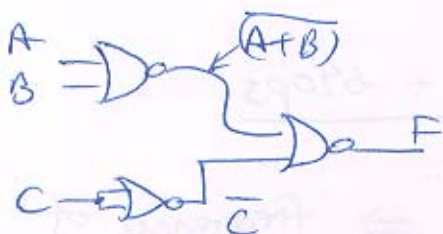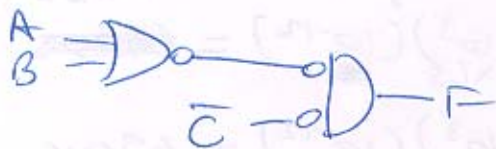it would be easier to look at the circuit.





↳ this behaves like an inverter

	NOR	
00	1	←
01	0	
10	0	
11	0	←

inputs are the same

(6)

11c

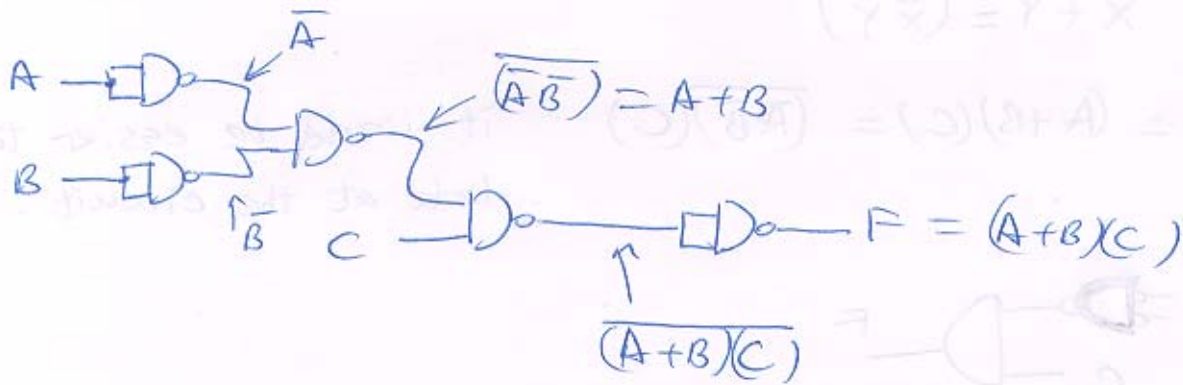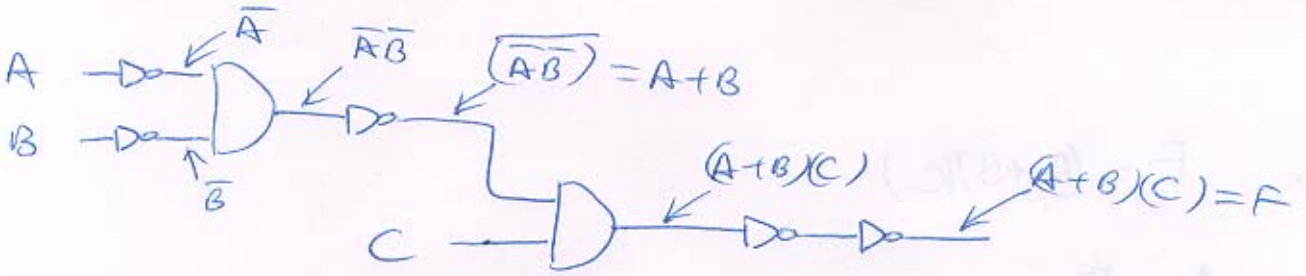

12, t_{PLH} (propagation delay from low to high) 1.035ns
 $= (0.69)(R_p)(C_L) = (0.69)(10^3)(10^{-12}) = \text{~~69ps~~}$

$t_{PHL} = (0.69)(R_n)(C_L) = (0.69)(10^3)(10^{-12}) = 690ps$

$t_p = \frac{t_{PLH} + t_{PHL}}{2} = \frac{1.035ns + 690ps}{2}$

$= \boxed{863ps} \Rightarrow \text{frequency of } 1.16GHz$