



a.  $F = \overline{(\bar{A} \cdot B)}$

b. Truth table

A	$\bar{A}$	B	F
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1

c.  $C_G = C_{ox} \cdot \text{gate electrode area} = C_{ox} \cdot W \cdot L$

$C_{ox} = 2.3 \text{ fF}/\mu\text{m}^2$

Use  $W_s$  and  $L_s$  as on diagram in notes of 29.04.02 (see second page), i.e.,

PMOS  $12 \mu\text{m}$  and  $1.5 \mu\text{m}$

NMOS  $6 \mu\text{m}$  and  $1.5 \mu\text{m}$

Let  $R_p = \underline{\underline{\quad}}$ ,  $R_n = 4 \text{ k}\Omega$

(2)

$$\text{Find } C_{GP} = 23 \text{ fF} \cdot 12 \times 1.5 = 41.4 \text{ fF}$$

$$C_{GN} = 2.3 \text{ fF} \cdot 6 \cdot 1.5 = 20.7 \text{ fF}$$

- d. what is fanout of the inverter (1)  
e. what gate capacitance does the inverter drive?

$$C_{GP} + C_{GN} = 41.4 + 20.7 = 62.1 \text{ fF}$$

- f. In NAND gate what is the <sup>source</sup> resistance when F goes from 1 to 0?

$$R = 2R_N = 8 \text{ k}\Omega$$

- g. In NAND gate what is the <sup>maximum</sup> resistance when F goes from 0 to 1?

max if only one PMOS is ~~at~~ changes state  $\rightarrow 4 \text{ k}\Omega$

- h. ~~In terms of  $R_P$  and  $R_N$ , and~~ what is the time delay in the inverter?

$$\tau_{inv} = R (C_P + C_N) = 4 \text{ k}\Omega (62.1 \text{ fF}) = 248 \text{ ps}$$

$$\text{gate delay} = 0.69\tau = 171 \text{ ps}$$

- i. If the load capacitance  $C_L = 100 \text{ fF}$ , what is the maximum delay in the NAND gate?  $\tau_{max} = R_{max} \cdot C_L = 8 \text{ k}\Omega \cdot 100 \text{ fF}$

i. What values of  $\tau$   $\rightarrow 800 \text{ ps}$ ; delay =  $0.69\tau = 552 \text{ ps}$   $\rightarrow$  this

K. If A goes from a 0 to a 1 ~~how~~  
much energy is stored in ~~the~~ <sup>one</sup> gate  
~~of inverter~~ capacitance of the inverter.

L. Which one (PMOS or NMOS)? <sup>NMOS</sup>  
How much energy (assuming  $V_{DD} = +5V$ )

$$U = \frac{1}{2} CV^2 = \frac{1}{2} (20.7 \text{ fF}) (25) \\ = 2.6 \times 10^{-13} \text{ J}$$

M. If change occurs once each clock  
cycle in a 500 MHz ~~the~~ processor,  
how much power is expended?

$$P = U \cdot f = 2.6 \times 10^{-13} \times 5 \times 10^8 = \\ 129 \mu\text{W}$$

N. If there are

$$60 \text{ watts} \rightarrow \frac{60}{129 \times 10^{-6}} = 464,000 \text{ gates}$$