



EE 42 Introduction to Digital Electronics

Fall 2003

Prof. A. R. Neureuther

Dept EECS 510 Cory, 642-4590

neureuth@eecs.berkeley.edu

UC Berkeley


Office Hours M 1, Tu/Th 10:30-11:30, F 11

Course Website

www-inst.eecs.Berkeley.edu/~ee42/

EE42 Midterm #1 – Solutions 2 October 2003

I. (25 points) Basic Circuit Analysis

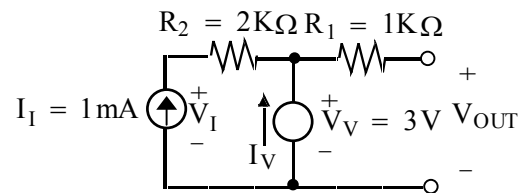

- a) (13 pts.) Find V_{OUT} and voltage on the current source V_I when the output is open circuited.

$$I_{R_1} = 0 \Rightarrow V_{OUT} = V_V = 3\text{V}$$
$$V_I = I_I R_2 + V_V = (1\text{mA})(2K) + 3 = 5\text{V}$$


- b) (12 pts.) Find the current on the voltage source I_V when the output is shorted.

$$\text{Short} \Rightarrow I_{R_1} = \frac{3\text{V}}{1K\Omega} = 3\text{mA}.$$

$$I_I + I_V - I_{R_3} = 0$$

$$I_V = I_{R_3} - I_I = 3\text{mA} - 1\text{mA} = 2\text{mA}$$

II. (25 points) Load Lines

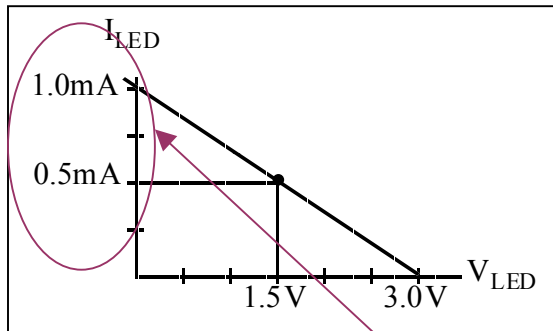

LED Device
Desired operating point
 $V_{LED} = 1.5$
 $I_{LED} = 5\text{mA}$

- a) (15 pts.) Choose a Thévenin voltage in the range from 1 to 4 volts and a Thévenin resistance in the range 400 to 4k ohms to operate the LED device at the desired operating point given above. Values found from a graphical solution are adequate.

$$V_{Th} = 3V$$

$$R_{Th} = \frac{3V}{1\text{mA}} = 3k\Omega$$


Error in Solution: Point is 5 mA and intercept is 10 mA. This make the resistance 10 times smaller at 300 ohms. A workable solution is 4V and 500 ohms. This problem will be graded on the methodology that you used and the values that you show.

- b) (10 pts.) For your choice in a), above, what fraction of the power delivered by the Thévenin voltage source is consumed by the load?

$$\frac{P_{LED}}{P_{SUP}} = \frac{I_{LED}V_{LED}}{I_{LED}V_{SUP}} = \frac{V_{LED}}{V_{SUP}} = 0.50$$

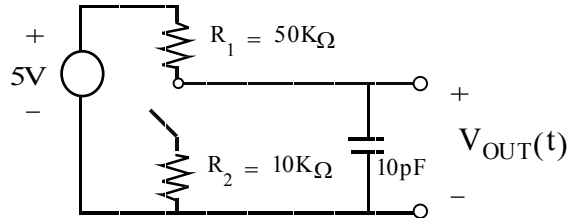III. (25 points) Transient

This circuit charges when the switch is open and discharges when the switch is closed.



- a) (6 pts.) Determine the maximum and minimum voltage on the capacitor.

$$\begin{aligned} \text{MAX} &= 5\text{V} & I_{R_1} &= 0 \\ \text{MIN} &= \frac{R_2}{R_1 + R_2} 5\text{V} = \frac{10}{10 + 50} 5\text{V} = \frac{5}{6} \text{V} \end{aligned}$$


- b) (13 pts.) Find $V_{\text{OUT}}(t)$ in discharging the capacitor.

$$\begin{aligned} V_{\text{OUT}}(t) &= V_{\text{FINAL}} + (V_{\text{INITIAL}} - V_{\text{FINAL}}) e^{-t/\tau} \\ V_{\text{FINAL}} &= \frac{5}{6} \text{V} & V_{\text{INITIAL}} &= 5\text{V} \\ \tau &= \frac{R_1 R_2}{R_1 + R_2} c = \frac{10 \cdot 50}{10 + 50} c = \frac{50}{6} \text{K}\Omega 10\text{pF} = \frac{500}{6} \text{ns} \\ V_{\text{OUT}}(t) &= \frac{5}{6} \text{V} + \left(\frac{25}{6} \text{V} \right) e^{-t/833\text{ns}} \end{aligned}$$

- c) (6 pts.) Find the initial current out of the capacitor when discharging the capacitor.

$$\begin{aligned} \text{At } t = 0^+ & \quad V_c = 5\text{V}, \text{ so } I_{R_1} = 0 \\ I_{R_2} &= \frac{5\text{V}}{R_2} = \frac{5\text{V}}{10\text{K}\Omega} = 0.5\text{mA} \end{aligned}$$

IV. (25 points) Node Equations

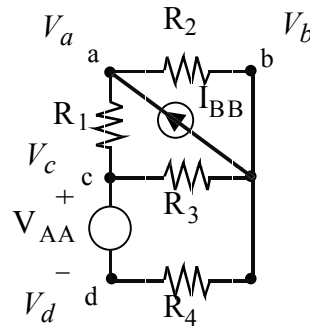

a) (5 pts.) Six nodes are shown. Determine the nodes that have potentially different voltages and assign only these nodes a label $a, b, c \dots$ and voltage $V_a, V_b, V_c \dots$

b) (5 pts.) Choose one of the remaining nodes as a reference and set its voltage to zero. Which of your remaining nodes have nonzero voltages that cannot be found directly from the voltages of the other nodes? In other words, how many unknown node voltages are there and node equations are you going to need?

$$V_b = 0 \quad V_a, V_c \quad \text{as } V_d \text{ easy to get}$$

c) (15 pts.) Using the node equation method and your node labeling in a), above, write a sufficient set of equations to solve for the unknown node voltages. [Only V_{AA}, I_{BB} , the resistors and your node voltages from b) should appear.]

$$\frac{V_a - 0}{R_2} - I_{BB} + \frac{V_a - V_c}{R_1} = 0$$

$$\frac{V_c - V_a}{R_1} + \frac{V_c - 0}{R_3} + \frac{V_c - V_{AA}}{R_4} = 0$$