

# EECS 42 – Introduction to Electronics for Computer Science



Spring 2003,  
Dept. EECS, 510 Cory  
UC Berkeley  
Course Web Site

[Prof. A. R. Neureuther](mailto:neureuth@eecs.berkeley.edu)  
[neureuth@eecs.berkeley.edu](mailto:neureuth@eecs.berkeley.edu) 642-4590  
Office Hours (Tentative M, Tu, W, (Th), F 11  
<http://www-inst.eecs.berkeley.edu/~ee42/>

## Problem Set # 3 Due 2:30 PM Feb 12th, 240 Cory

**Reading:** Section 5.1, 2.2, 3.1-3.4 Schwarz and Oldham. 4th week 8.1 and Handout

**3.1 Capacitance.** An airplane has a capacitance to the clouds around it of  $1 \text{ mF} = 0.001 \text{ F}$ . It flies through a thunderstorm at  $900 \text{ km/hr}$  picking up  $10^{17}$  electrons per meter. It was uncharged before entering the storm.

- Find the charge on the plane as a function of time.
- Find voltage on the plane as a function of time.
- If lightning strikes when the potential of the airplane reaches  $100 \text{ KV}$ , find the distance it will go into the thunderstorm before lightning strikes?
- If the lightning strike discharges the plane find the energy that is released.

Note: Airplanes have thin wires with points that continuously discharge the plane. The values in this problem are just guesses.

**3.2 Capacitance and voltage versus time.** A  $1 \text{ pF}$  capacitance from a  $1 \text{ cm}$  wire on a PC board is charged by a current of  $1 \text{ } \mu\text{A}$  for  $2 \text{ } \mu\text{s}$ . At  $2 \text{ } \mu\text{s}$  the current increases to  $2 \text{ } \mu\text{A}$  for an additional  $2 \text{ } \mu\text{s}$ . At  $4 \text{ } \mu\text{s}$  the current reverses to  $-4 \text{ } \mu\text{A}$ .

- Find the voltage versus time from  $0$  to  $6 \text{ } \mu\text{s}$ .
- Find the energy supplied during the interval  $0$  to  $2 \text{ } \mu\text{s}$ .
- Find the energy supplied during the interval  $2$  to  $4 \text{ } \mu\text{s}$ .
- Explain why is c) not proportional to the square of the change in voltage?

Now the answers will be between  $0$  and  $10 \text{ V}$ .

$I_{SS} = 1 \text{ mA}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $R_3 = 3 \text{ k}\Omega$

**3.3 Equivalent Circuits.** Consider the circuit in Fig. P3.3.

- Assume  $V_{OUT} = 1.2 \text{ V}$ ,  $0.6 \text{ V}$  and  $0 \text{ V}$  are caused by three different external loads. Find the corresponding current  $I_{OUT}$ .
- Which of the above values were the easiest to find?
- Sketch  $I_{OUT}$  versus  $V_{OUT}$  from your data.
- Use your graphical results to find a voltage supply and one resistor in series (Thevenin equivalent) that could be used to replace the three resistors and current source.
- Show that  $R_T = -V_{OC}/I_{SC}$ .
- What combination of  $R_1$ ,  $R_2$  and  $R_3$  gives  $R_T$ ? Verify that turning the current source to zero and evaluating the resistance looking into the output gives this same result.

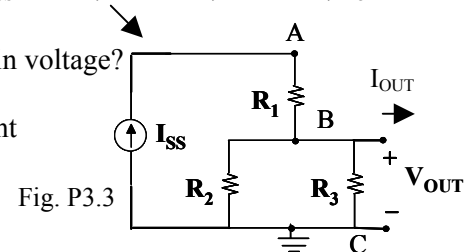


Fig. P3.3

**3.4 Equivalent Circuits and Ideal Supplies.** Consider the circuit in Fig. P3.4.

- Find  $V_{OC}$ .
- Find  $I_{SC}$ .
- Find the Norton equivalent circuit.
- Find the voltage on the current source when  $I_{OUT} = 0$ .
- Find the current through the voltage source when  $V_{OUT} = 0$ .

$V_{AA} = 1 \text{ V}$ ,  $I_{SS} = 1 \text{ mA}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$

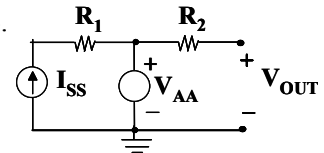


Fig. P3.4

**3.5 Nonlinear Load and Power.** Use a graphical method to find the solution for the following loads when attached to  $V_{OUT}$  in Fig. P3.3. (No algebra please. Accuracy to 5% is fine. Use your graph from Problem 3.3.)

- Find  $V_{OUT}$  and  $I_{OUT}$  and then the power into the load when the load is a  $4 \text{ k}\Omega$  resistor.
- Find  $V_{OUT}$  and  $I_{OUT}$  and then the power into the load when the load has  $I_{LOAD} = 1 \text{ (mA/V}^2)(V_{OUT})^2$ .
- Find  $V_{OUT}$  and  $I_{OUT}$  and then the power into the load when the load has  $I_{LOAD} = -2 \text{ mA} + 1 \text{ (mA/V}^2)(V_{OUT})^2$ .