

EECS 42 – Introduction to Electronics for Computer Science



Spring 2003,
Dept. EECS, 510 Cory
UC Berkeley
Course Web Site

Prof. A. R. Neureuther
neureuth@eecs.berkeley.edu 642-4590
Office Hours (Tentative M, Tu, W, (Th), F 11
http://www-inst.eecs.berkeley.edu/~ee42/

Problem Set # 4 Due 2:30 PM Feb 19th, 240 Cory

Reading: Week #4 Section 8.1 Schwarz and Oldham, Viewgraphs in HANDOUT_RC available on the web. Week #5 Feb. 17th is a UC Holiday, Feb 19th Node Eq.

4.1 Sketch/Trend. Consider the circuit in Fig. P4.1. At $t = 0$, the capacitor voltage $V_C = 1V$.

- Find V_{OUT} as t goes to infinity.
- Evaluate the time constant RC in ns.
- Evaluate the initial slope $dV/dt = (1/C)(V_{FINAL} - V_{INITIAL})/R$
- Draw axes for $V_{OUT}(t)$ vs t where t goes from 0 to 20 ns. Draw horizontal lines for $V_{INITIAL}$ and V_{FINAL} . Draw a slanted line with the slope found in part c).
- Sketch $V_{OUT}(t)$ on the graph.
- What one-by-one fractional changes (i.e. doubling or reduction by half) of the individual parameters C , $V_{FINAL} - V_{INITIAL}$ and R will cause the slope to double?

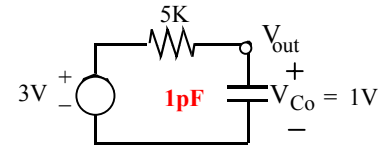


Fig. P4.1

4.2 General Exponential Form. Use the circuit in Fig. P4.1 and values from Problem 4.1.

- Assume that $V_{OUT}(t)$ is a known function and find an equation for the current through the resistor in terms of $V_{OUT}(t)$.
- Assume that $V_{OUT}(t)$ is a known function and find an equation for the current through the capacitor in terms of the time derivative of $V_{OUT}(t)$.
- Equate a) and b) to obtain a differential equation for $V_{OUT}(t)$.
- Substitute $V_{OUT}(t) = A + B e^{-t/\tau}$ and carry out the derivatives.
- Group the equations into constant terms and terms times $e^{-t/\tau}$.

Set these two groups of terms equal to zero to get two equations.

Which two of the three parameters A , B and τ do they determine?

- Use the initial value to determine the third parameter.

$I_{SS} = 1mA$, $R_1 = 1k\Omega$, $R_2 = 2k\Omega$, $R_3 = 3k\Omega$

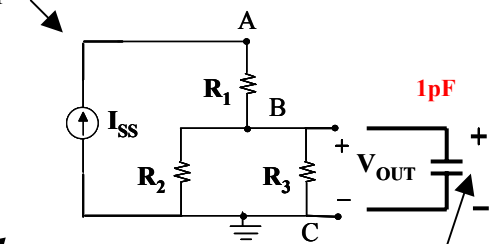


Fig. P4.3

$V_{INITIAL} = -1.0V$

4.3 Nonzero levels and resistors. A capacitor is precharged to -1.0 volts and connected at $t=0$ to the circuit in Fig. P4.3. This makes $V_{OUT}(0) = -1V$.

- Find the voltage on the capacitor as t goes to infinity.
- Determine the Thevenin resistance seen by the capacitor by setting $I_{SS} = 0$.
- Find I_{OUT} and dV_{OUT}/dt at $t=0$.
- Assume $V_{OUT}(t) = A + B e^{-t/\tau}$ and use the initial condition and a) and b) to find A , B , and τ .

These values are the same as in Problem 4.1

4.4 Pulse shape. In the circuit in Fig. P4.4 the switch has been in the upward position connecting to R_U for a long time. At $t=0$ the switch changes such that it is connected to R_D .

- Find $V_{OUT}(t)$ as t goes to infinity and the RC time constant.
- Find $V_{OUT}(t)$ for $t > 0$.
- Determine the fraction of a time constant and the actual time that it takes for $V_{OUT}(t)$ to reach $2.5V$.
- Find $V_{OUT}(t = 1.5 ns)$.
- Assume the switch returns to the upward position at $t = 1.5 ns$ and determine $V_{OUT}(t)$ for $t > 1.5 ns$. (Be aware that there is a different time constant going upward.)

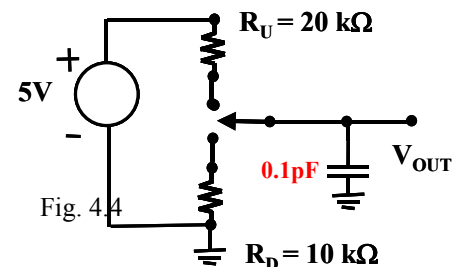


Fig. 4.4

Brain teaser for fun for good students: determine the time at which $V_{OUT}(t)$ reach $4V$ on its way back upward!