

EECS 42 – Introduction to Electronics for Computer Science



Spring 2003,
Dept. EECS, 510 Cory
UC Berkeley
Course Web Site

[Prof. A. R. Neureuther](mailto:neureuth@eecs.berkeley.edu)
642-4590
Office Hours (Tentative M, Tu, W, (Th), F 11
<http://www-inst.eecs.berkeley.edu/~ee42/>

Solution to Problem Set # 4 (by Farinaz Koushanfar)

4.1 Sketch/Trend. (Using $C = 1\text{pF}$).

- As ' t ' goes to infinity the capacitor voltage stops changing and the current goes to zero. Without current there is no voltage on the 5k resistor and $V_{\text{out}} = 3\text{V}$.
- $RC = (1\text{pF})(5\text{k}\Omega) = 5\text{ ns}$.
- The initial slope $dV/dt = (1/C)(V_{\text{FINAL}} - V_{\text{INITIAL}})/R = 0.6\text{V/ns}$.
- {Show horizontal line at 0 and at 3V, line from 0 to 3V at 5 ns.}
- refer to the graph below:


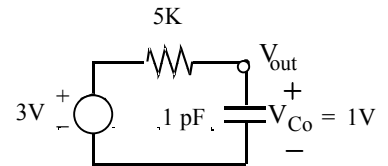


Fig. P4.1

Voltage (V)

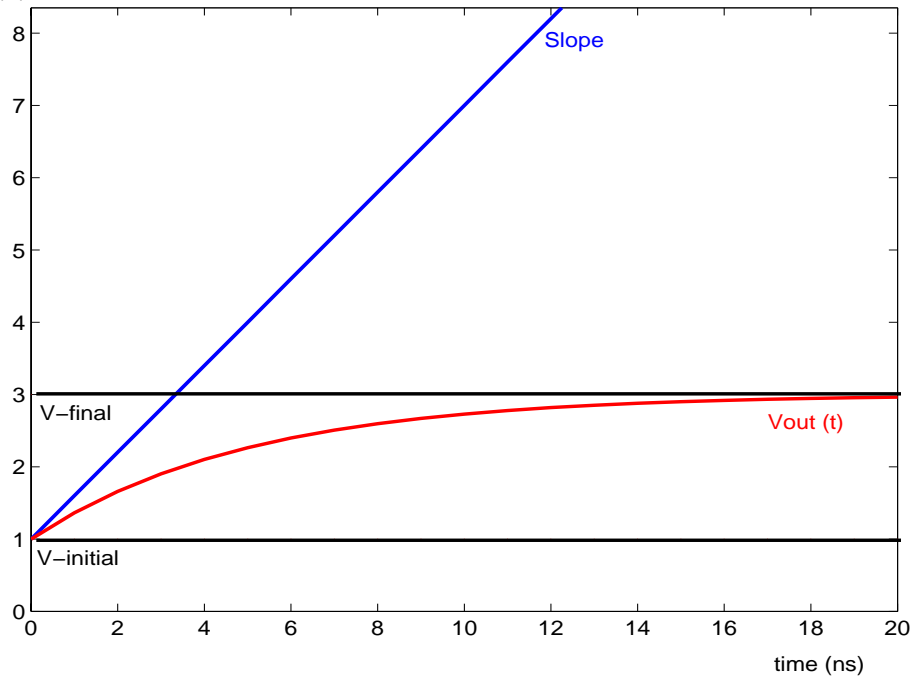

- The slope doubles when C is cut in Half or $(V_{\text{FINAL}} - V_{\text{INITIAL}})$ doubles or R is cut in half.

4.2 General Exponential Form.

- $I_R = (3\text{ V} - V_0(t))/R$.
- $I_C = C dV_0/dt$
- $C dV_0/dt = (3\text{ V} - V_0(t))/R$
- $C(1/\tau)B e^{-(t/\tau)} = (3\text{ V} - A - B e^{-(t/\tau)})/R$
- $0 = \{(3\text{ V} - A)/R\} + \{[-B(C/\tau) - B/R]\} (e^{-(t/\tau)})$ Since this equation holds for $t > 0$ both the constant and the exponential term coefficients must be individually zero. $A = 3\text{V}$ and $\tau = RC = 1\text{pF} \times 5\text{k}\Omega = 5\text{ ns}$.
- $V_0(0) = 0 \Rightarrow B = -A = -3\text{V}$

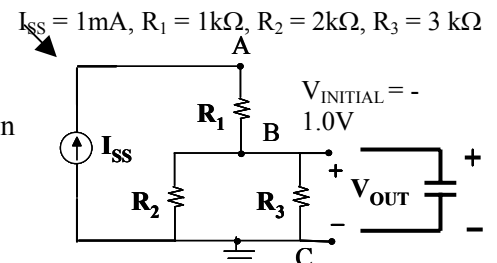


Fig. P4.3

4.3 Nonzero levels and resistors. (Using $C = 1\text{ pF}$)

- a) As t goes to infinity, $I_C = 0$, thus $V_0 = I_{SS}(R_2 || R_3) = 1\text{mA} \times (1.2\text{k}\Omega) = 1.2\text{V}$
- b) Setting $I_{SS} = 0$ leaves R_1 without current so $R_{TH} = (R_2 || R_3) = 1.2\text{k}\Omega$
- c) At $t = 0$, $I_{OUT} = I_{SS} - V_0/R_3 - V_0/R_2 = 1\text{mA} + 0.5\text{mA} + 0.33\text{mA} = 1.83\text{mA}$
 $dV_{OUT}/dt = (1/C) \times I = (1/\text{pF})(1.83\text{mA}) = 1.83\text{V/ns}$
- d) a) $\Rightarrow A = 1.2\text{V}$, b) $\Rightarrow t = RC = 1.2\text{k}\Omega \times 1\text{pF} = 1.2\text{ns}$, $V_0(0) = -1 \Rightarrow B = -2.2\text{V}$.

4.4 Pulse shape. (Using $C = 0.1\text{pF}$)

- a) With switch at R_D , $V_{OUT}(t)$ goes to zero as t goes to infinity.
- b) $\tau = R_D C = 10\text{k}\Omega \times 0.1\text{pF} = 1\text{ns}$.
 $V_{OUT}(t) = 5 e^{-(t/1\text{ns})}\text{V}$ for $t > 0$.
- c) To decay to 50%, $e^{-(t/1\text{ns})} = 0.5$. Taking the $\ln()$ of both sides gives, $t = 2\text{ns}$, $\ln(2) = 0.69 \times (1\text{ns}) = 0.69\text{ns}$.
- d) $V_{OUT}(t = 1.5\text{ns}) = 5 e^{-(1.5\text{ns}/1\text{ns})} = 5 e^{-1.5} = 1.12\text{V}$.
- e) When the switch is up again $\tau = R_U C = 20\text{k}\Omega \times 0.1\text{pF} = 2\text{ns}$
 $V_{OUT}(t) = 5\text{V} - 3.88\text{V} e^{-((t-1.5\text{ns})/2\text{ns})}$ for $t > 1.5\text{ns}$.
 [For fun $5\text{V} - 3.88\text{V} e^{-((t-1.5\text{ns})/2\text{ns})} = 4\text{V} \Rightarrow 3.88 e^{-((t-1.5\text{ns})/2\text{ns})} = 1 \Rightarrow ((t-1.5\text{ns})/2\text{ns}) = \ln(3.88)$, $(t-1.5\text{ns}) = (1.36)(2\text{ns}) = 2.71\text{ns} \Rightarrow t = 1.5\text{ns} + 2.71\text{ns} = 4.21\text{ns}$.

