

EE42 - Problem Set #7


Solution

7.1.a Voltage divider formed by R1 and R2: $V_2 = V_{in} \cdot \frac{R_2}{R_1 + R_2}$

Voltage gain of VCVS: $A \cdot V_2 = V_{in} \cdot \frac{A \cdot R_2}{R_1 + R_2}$

Voltage divider by R3 and R4: $V_{out} = A \cdot V_2 \cdot \frac{R_4}{R_3 + R_4}$

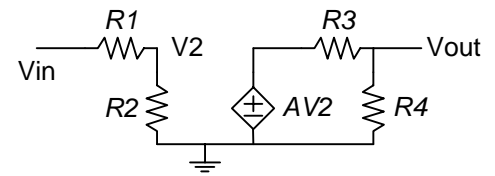So, $V_{out} = V_{in} \cdot \frac{A \cdot R_2}{R_1 + R_2} \cdot \frac{R_4}{R_3 + R_4}$ (1)



7.1

7.1.b Let $V_{out} = V_{out_DC} + \Delta V_{out}$, $V_{in} = V_{in_DC} + \Delta V_{in}$ in Eq. (1),

$$V_{out_DC} + \Delta V_{out} = (V_{in_DC} + \Delta V_{in}) \cdot \frac{A \cdot R_2}{R_1 + R_2} \cdot \frac{R_4}{R_3 + R_4}$$

Sort terms of DC and Δ , we get,

$$V_{out_DC} = V_{in_DC} \cdot \frac{A \cdot R_2}{R_1 + R_2} \cdot \frac{R_4}{R_3 + R_4}$$

$$\Delta V_{out} = \Delta V_{in} \cdot \frac{A \cdot R_2}{R_1 + R_2} \cdot \frac{R_4}{R_3 + R_4} \quad (2)$$

Derive the small-signal gain from (2):

$$A_{ac} = \frac{\Delta V_{out}}{\Delta V_{in}} = A \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{R_4}{R_3 + R_4}$$


7.2.a KCL at node V- : $\frac{V_- - V_{out}}{R_2} + \frac{V_-}{R_1} = 0$ (3)

We also know: $V_{out} = A \cdot V_i = A \cdot (V_{in} - V_-)$ (4)

Given $\frac{V_- - V_{out}}{R_2} + \frac{V_-}{R_1} = 0$

$$V_{out} = A \cdot (V_{in} - V_-)$$
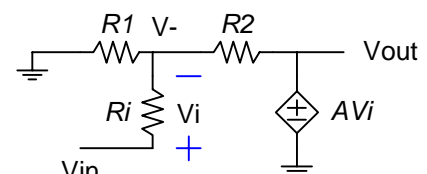
$$\text{Find}(V_{out}, V_-) \rightarrow \begin{bmatrix} A \cdot V_{in} \cdot \frac{(R_1 + R_2)}{(R_1 + R_1 \cdot A + R_2)} \\ R_1 \cdot A \cdot \frac{V_{in}}{(R_1 + R_1 \cdot A + R_2)} \end{bmatrix}$$



7.2

So,
$$V_{out} = V_{in} \cdot \frac{R1 + R2}{R1 + \frac{R1 + R2}{A}} = 10.999395 \quad (5)$$

Note: 1) In (5), term contains A in the denominator is the error term due to finite gain of VCVS.
 2) If $A = \infty$, then V_{out} reduces to the form assuming op amp is ideal.

7.2.b A is large, so the term contains A in the denominator is small compared to R1. Apply Taylor expansion to (5), we have:

$$V_{out} = V_{in} \cdot \frac{R1 + R2}{R1 + \frac{R1 + R2}{A}} = V_{in} \cdot \left(\frac{R1 + R2}{R1} \right) \cdot \left(1 - \frac{R1 + R2}{A \cdot R1} \right)$$


The fraction of deviation from ideal gain is:
$$\frac{\Delta V_{out}}{V_{out(ideal)}} = -\frac{R1 + R2}{A \cdot R1} = \frac{-1}{A \cdot \frac{R1}{R1 + R2}} = -5.5 \cdot 10^{-5} \quad (6)$$

Note: The term in the denominator of (6) is called "loop gain", i.e., the gain derived when going around the feedback loop of the op amp, including the resistive network forming a divider.

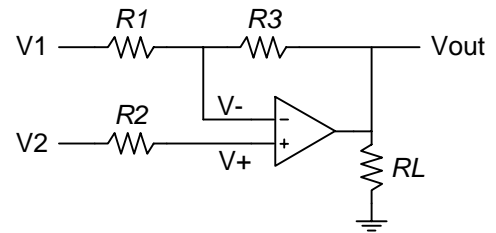7.3.a Assuming ideal op amp, 1) $V+ = V-$; 2) no current into + and - terminals, so $V- = V+ = V2$ holds.

KCL at node $V-$, we get:
$$\frac{V2 - V1}{R1} + \frac{V2 - Vout}{R3} = 0$$

Solve, we have:
$$Vout = V2 \cdot \left(1 + \frac{R3}{R1} \right) - V1 \cdot \frac{R3}{R1}$$




7.3

7.3.b Op amp is ideal, no current flowing through R2, so $V+ = V2$ holds independent to the value of R2.

7.3.c VCVS is a voltage source, so R_L at output in parallel to the VCVS will not affect the its voltage.

7.4.a

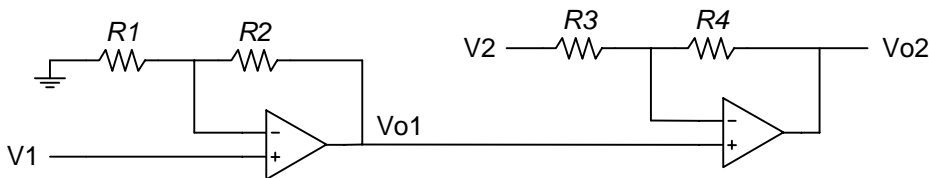

$$Vo1 = V1 \cdot \left(1 + \frac{R2}{R1} \right)$$

7.4.b

$$Vo2 = Vo1 \cdot \left(1 + \frac{R4}{R3} \right) - V2 \cdot \frac{R4}{R3} = V1 \cdot \left(1 + \frac{R2}{R1} \right) \cdot \left(1 + \frac{R4}{R3} \right) - V2 \cdot \frac{R4}{R3}$$

7.5.a KCL at node V2:
$$\frac{V_{in} - V_2}{R_1} + I_B - \frac{V_2}{R_2} = 0$$

KCL at node Vout:
$$\frac{V_{out}}{R_4} + \frac{V_{out} - V_{cc}}{R_3} + g_m \cdot V_2 = 0$$

Given
$$\frac{V_{in} - V_2}{R_1} + I_B - \frac{V_2}{R_2} = 0$$

$$\frac{V_{out}}{R_4} + \frac{V_{out} - V_{cc}}{R_3} + g_m \cdot V_2 = 0$$

Find(Vout, V2) →
$$\left[\begin{array}{c} -R_4 \cdot \frac{(-V_{cc} \cdot R_1 - V_{cc} \cdot R_2 + g_m \cdot R_2 \cdot R_3 \cdot V_{in} + g_m \cdot R_2 \cdot R_3 \cdot R_1 \cdot I_B)}{(R_3 \cdot R_1 + R_3 \cdot R_2 + R_4 \cdot R_1 + R_4 \cdot R_2)} \\ R_2 \cdot \frac{(V_{in} + R_1 \cdot I_B)}{(R_1 + R_2)} \end{array} \right]$$

So,
$$V_{out} = \frac{-g_m \cdot R_2 \cdot R_3 \cdot R_4 \cdot (V_{in} + I_B \cdot R_1)}{(R_1 + R_2) \cdot (R_3 + R_4)} + \frac{V_{cc} \cdot R_4}{R_3 + R_4} \quad (7)$$

Note: If superposition is applied to the analysis, it is very easy to eyeball the solution in (7) consisting of 3 terms:

- 1) V_{in} term, due to the cascade of divider R_1 & R_2 , VCCS gain g_m , output resistance $R_3 \parallel R_4$;
- 2) I_B term, similar to V_{in} , but need to go through a Thevenin equivalent transform at V_{in} ;
- 3) V_{cc} term, simply a divider formed by R_3 and R_4 .

7.5.b Set $I_B = V_{cc} = 0$, rewrite KCL's

KCL at node V2:
$$\frac{V_{in} - V_2}{R_1} - \frac{V_2}{R_2} = 0$$

KCL at node Vout:
$$\frac{V_{out}}{R_4} + \frac{V_{out}}{R_3} + g_m \cdot V_2 = 0$$

Solve, we have
$$V_{out} = \frac{-g_m \cdot R_2 \cdot R_3 \cdot R_4 \cdot V_{in}}{(R_1 + R_2) \cdot (R_3 + R_4)} \quad (8)$$

7.5.c If we set $I_B = V_{cc} = 0$ in (7), we see we get exactly (8).