

EECS 42 – Introduction to Electronics for Computer Science



Spring 2003,
Dept. EECS, 510 Cory
UC Berkeley
Course Web Site

Prof. A. R. Neureuther
neureuth@eecs.berkeley.edu 642-4590
Office Hours (Tentative M, Tu, W, (Th), F 11
http://www-inst.eecs.berkeley.edu/~ee42/

Solution to Problem Set # 8 (by Farinaz Koushanfar)

8.1 (a) Let's call the current of R_0 , i_0 . Since at the output node, $\beta i_B = i_0$, then at the node v_E , the currents between v_E and v_{out} cancel out each other, so the current i_B goes into the resistance R_E . If we write the KVL of the input loop, we get:

$$v_{in} - i_B(R_s + R_{in} + R_E) = 0 \Rightarrow v_{in} / (R_s + R_{in} + R_E) = i_B$$

At the output node, $i_0 = \beta i_B$, $v_{out} = v_E + i_0 R_0 = i_B R_E - R_0 \beta i_B = (R_E - R_0 \beta) v_{in} / (R_s + R_{in} + R_E)$

$$v_{out} / v_{in} = (R_E - R_0 \beta) / (R_s + R_{in} + R_E) = (100 \Omega - 100 \text{ K}\Omega \cdot 100) / (1 \text{ K}\Omega + 10 \text{ K}\Omega + 100 \Omega) = -$$

$$9999.9 / 11.1 = -900.8$$

(b) The input resistance at AA' while output is short circuit, is v_{IN} / i_B . Now, the resistances R_E and R_0 are in parallel with each other and parallel with the dependent source βi_B . The voltage at the node v_E is $v_{IN} - i_B R_{in}$. The KCL at node v_E now becomes:

$$i_B = (v_{IN} - i_B R_{in}) / (R_E || R_0) - \beta i_B \rightarrow i_B (1 + \beta + R_{in} / (R_E || R_0)) = v_{IN} / (R_E || R_0)$$

$$\rightarrow R(AA') = v_{IN} / i_B = (R_E || R_0) (1 + \beta + R_{in} / (R_E || R_0)) = R_{IN} + (\beta + 1)(R_E || R_0)$$

The physical significance is that the extra dependent source current through $R_E || R_0$ magnifies the value.

c) Short circuit A and A' and look at the output resistance.

Putting a bag around the dependent source and R_0 shows that the current i_{out} flows through R_{in} and R_E in parallel and $v_E = i_{out} (R_E || R_{IN})$ and $i_b = -i_{out} (R_E / (R_{IN} + R_E))$.

The current downward through $R_0 = i_{R_0} = -\beta i_b + i_{out}$

$$v_{OUT} = i_{R_0} R_0 + v_E = R_0 (-\beta i_b + i_{out}) + i_{out} (R_E || R_{IN})$$

$$v_{OUT} = R_0 (\beta i_{out} (R_E / (R_{IN} + R_E)) + i_{out}) + i_{out} (R_E || R_{IN})$$

$$\text{Solving } v_{OUT} / i_{out} = (\beta R_E / (R_{IN} + R_E) + 1) R_0 + (R_E || R_{IN})$$

The physical significance is that the extra dependent source current adjusted for the fraction that makes it through through R_{IN} , magnifies the value of R_0 by raising the top to bottom voltage drop on R_0 . The dependent source in some sense 'burps' and current flows upward through it when ever current flows into the output. The resistance is nonetheless still positive.

8.2 (a) the sketch is shown :

(b) The voltage at the Op-AMP input is:

$$V_- = (V_{REF} + V_{IN}) / 2$$

Voltage V_{OUT} is an amplified version of V_{IN} .

for this condition to hold, we should have

$$V_{REF} + V_{IN} \leq 0. \text{ In other words, } V_{REF} = -1 \text{ V.}$$

(c) $V_{RAIL-} = 0, V_{RAIL+} = 2$



(d) $v_- = v_{IN} / 2, v_{OUT} = v_- + v_- \cdot R_2 / R_1 =$

$$v_- (1 + R_2 / R_1) = v_{IN} (1 + R_2 / R_1) / 2$$


$$v_{OUT} / v_{IN} = (1 + R_2 / R_1) / 2 = 1000, R_1 = 1 \text{ K}\Omega \Rightarrow$$

$$R_2 = 1999 \text{ K}\Omega$$

(e)

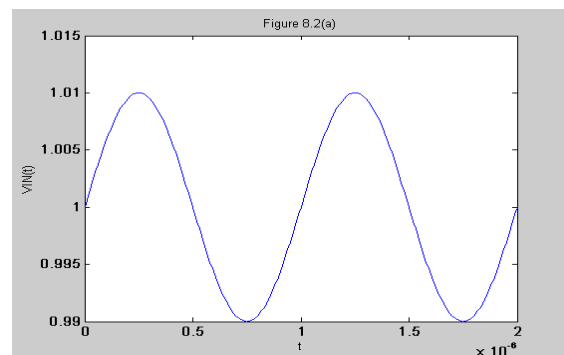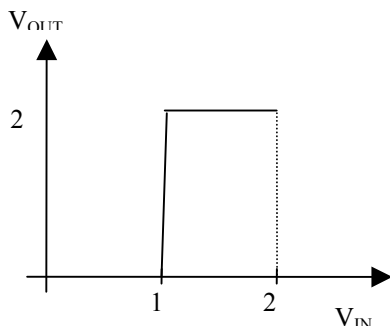

(f)

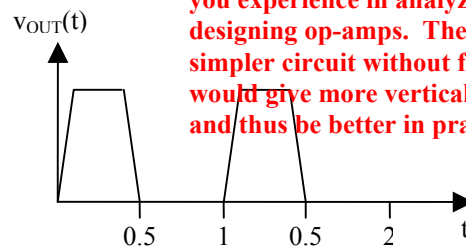

Please note that this problem gave you experience in analyzing and designing op-amps. The much simpler circuit without feedback would give more vertical transitions and thus be better in practice.