



b)  $V_{out} = 4.5V > V_{out-SAT-D} = 1V$   
 $\Rightarrow$   $x_{tor}$  is in SAT region.  
 $\Rightarrow$   $I_{out} = K_D (V_{in} - V_{T0}) V_{out-SAT-D}$   
 $= 25 \mu A/V^2 \times (3V - 1V) \times 1V$   
 $= 50 \mu A$

c)  $V_{out} = 0.5V < V_{out-SAT-D} = 1V$   
 $\Rightarrow$   $x_{tor}$  is in LIN region  
 $\Rightarrow$   $I_{out} = \frac{I_{out-SAT-D}}{2} = 25 \mu A$

d) Same as c), but equivalent to find out  $V_{in}$  for  $I_{out} = 30 \mu A$  ( $\because V_{out} = 0.5V = \frac{1}{2} V_{out-SAT-D}$ )

$\Rightarrow 30 \mu A = 25 \mu A/V^2 \times (V_{in} - 1V) \times 1V$   
 $\Rightarrow V_{in} = 2.2V$

9.2

  

9.2


Calculate intercepts for the loadline of the resistors:

$$\begin{cases} I_{out} = \phi \Rightarrow V_{out} = \frac{100}{100+100} \times 5V = 2.5V \\ V_{out} = \phi \Rightarrow I_{out} = \frac{5V}{100k\Omega} = 50 \mu A \end{cases}$$

b) Read from the plot (approximately).


$V_{in}$	0V	1V	2V	3V	4V	5V
$V_{out}$	2.5V	2.5V	1V	0.7V	0.5V	0.4V

c)

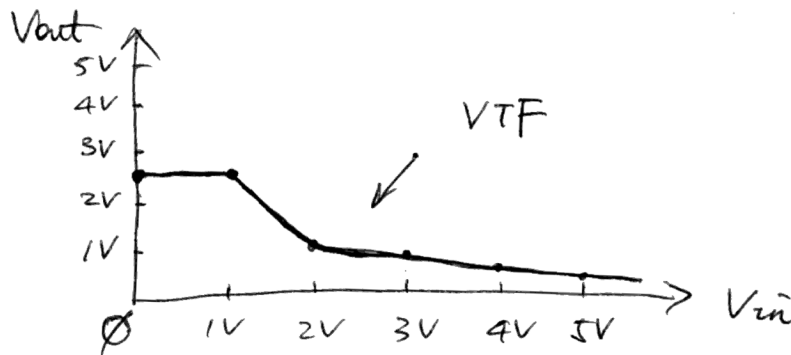

9.3

a)

 

b)  $V_{out} = 4.5V \Rightarrow$   $x_{tor}$  is in LIN region.

$$I_{out} = \frac{I_{out-SAT-PD}}{2} = \frac{20\mu A}{2} \times (5V - 3V - 1V) \times 1V / 2$$
$$= 10\mu A$$

c)  $V_{out} = 0.5V \Rightarrow$   $x_{tor}$  is in SAT region.

$$I_{out} = \frac{20\mu A}{2} \times (5V - 3V - 1V) \times 1V = 20\mu A$$


d) same as in c).

$$15\mu A = \frac{20\mu A}{2} (5V - V_{in} - 1V) \times 1V$$

$$\Rightarrow V_{in} = 3.25V$$

Q.4


a)

 

$$V_m = 2.5V, \quad I_{out} \approx 30\mu A$$

$$V_{out} \approx 0.8V$$

 b) Since CMOS inverter output current looks like a bell shape. There should be 2 solns possible for this question.



#1 NMOS SAT, PMOS LIN.  
 $\Rightarrow$  NMOS determine current.

$$NMOS: 15\mu A = 25\mu A (V_m - 1) \Rightarrow V_m = 1.6V$$

$$PMOS: 15\mu A = 20\mu A (5 - 1 - V_m) \cdot (5 - V_{out}) \Rightarrow V_{out} = 4.6875V$$

#2 NMOS LIN, PMOS SAT.

$$NMOS: 15\mu A = 25\mu A (V_m - 1) V_{out} \Rightarrow V_{out} = 0.2667V$$

$$PMOS: 15\mu A = 20\mu A (5 - 1 - V_m) \Rightarrow V_m = 3.25V$$

c) Since NMOS pull-down is stronger than PMOS pull-up,  $V_m$  has to be less than 2.5V. So PMOS must be in SAT region. Assume NMOS is also in SAT.

$$\Rightarrow I_{out} = I_{NMOS} = 25\mu A (V_m - 1) \Rightarrow V_m = \frac{7}{3}V$$

$$= I_{PMOS} = 20\mu A (5 - V_m - 1)$$

Note: Double check our assumption validity.

d)

