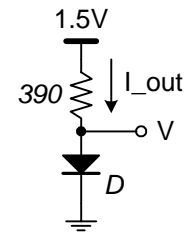


EE42 - Problem Set #11 Solution



11.1.a-c output voltage: $v := 0, 0.001.. 3$

Diode current: $I_{diode}(v) := 1000 \times 10^{-14} \cdot \left(e^{\frac{v}{0.025}} - 1 \right)$ mA

Resistor current: $I_{out}(v) := 1000 \frac{(1.5 - v)}{390}$ mA




11.1

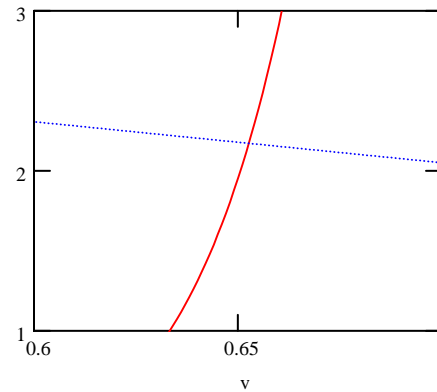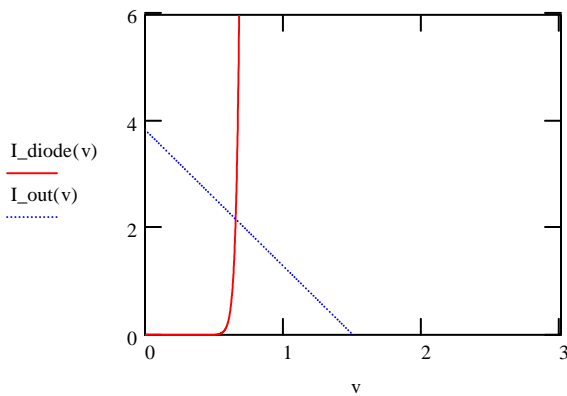

The soln read from the zoom-in plot is: $I_{diode} = I_{out} = 2.2\text{mA}$

11.1.d-e

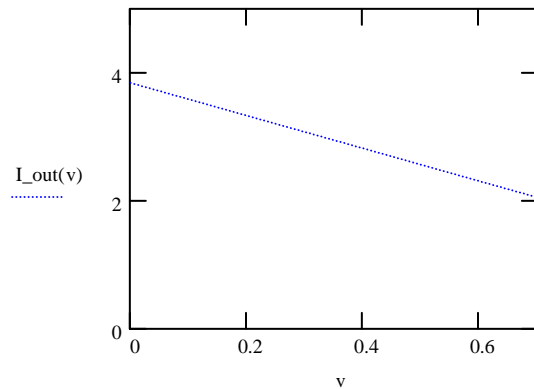

d) intercept to $V=0.7$ line is large-signal diode model soln: $I_{out} = 2.1\text{mA}$

e) intercept to $V=0$ line is perfect rectifier model soln: $I_{out} = 3.8\text{mA}$



Note, obviously, the large-signal diode model yields a better accuracy.

11.2.a-b

D1 turns on when:
 $V_{out} = V_{AA} + V_{turn_on_D1} + V_{BB} = 0.7 + 0.7 + 1 = 2.4V$
 => sets the upper clamping voltage


D2 turns on when:
 $V_{out} = 0.7 - 0.7 = 0V$
 => sets the lower clamping voltage

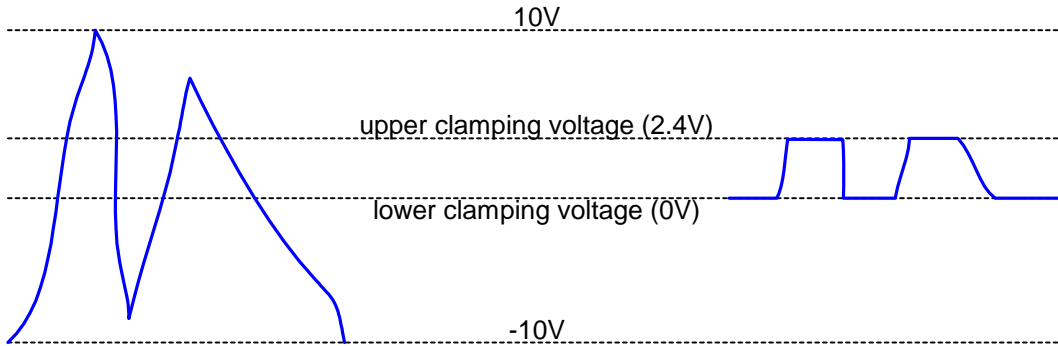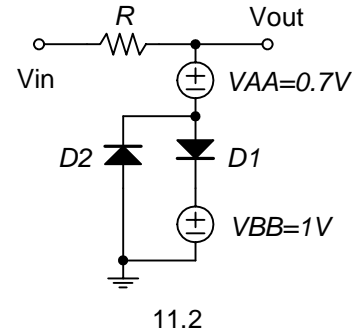Note that R value does not matter in the problem as diode is treated as "ideal".



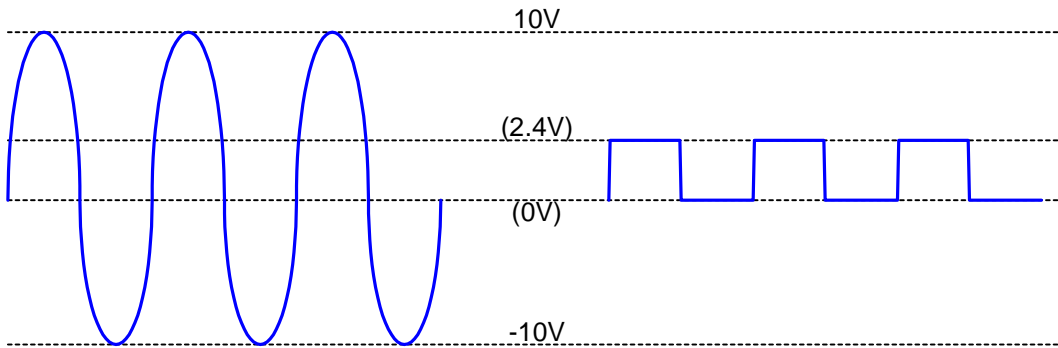11.2.c

The slow varying top and bottom of the sinewave will be clipped, so the output waveform is more square-waving.



11.3.a

Assume every donor atom is ionized and each donor contributes one electron,

$$N = \frac{10^{13} \text{ cm}^{-2}}{t} = \frac{10^{13} \cdot \text{cm}^{-2}}{0.1 \mu\text{m}} = 10^{18} \text{ cm}^{-3}$$

11.3.b

$$\sigma = q \cdot \mu \cdot N = 1.6 \cdot 10^{-19} \text{ C} \cdot 400 \frac{\text{cm}^2}{\text{V} \cdot \text{s}} \cdot 10^{18} \text{ cm}^{-3} = 64 \frac{\text{C}}{\text{V} \cdot \text{s} \cdot \text{cm}} = 64 \cdot \frac{1}{\Omega \cdot \text{cm}}$$

11.3.c

$$R_{\text{square}} = \frac{\rho}{t} = \frac{1}{\sigma \cdot t} = \frac{1}{64} \cdot \Omega \cdot \text{cm} \cdot \frac{1}{0.1 \mu\text{m}} = 1562.5 \Omega$$

11.3.d

$$R = \frac{L}{W} \cdot R_{\text{square}} = \frac{3 \mu\text{m}}{0.2 \mu\text{m}} \cdot 1562.5 \Omega = 23.4 \text{ k}\Omega$$

$$11.4.a \quad C_{\text{ox}} = \frac{\epsilon_R \cdot \epsilon_0}{t} = 3.9 \cdot 8.85 \cdot 10^{-14} \frac{\text{F}}{\text{cm}} \cdot \frac{1}{10\text{nm}} = 3.45 \cdot 10^{-7} \frac{\text{F}}{\text{cm}^2} = 3.45 \cdot \frac{\text{fF}}{\mu\text{m}^2}$$

$$11.4.b \quad C_G = (LW) \cdot C_{\text{ox}} = 1\mu\text{m} \cdot 0.25\mu\text{m} \cdot 3.45 \cdot 10^{-7} \cdot \frac{\text{F}}{\text{cm}^2} = 0.8625\text{fF}$$

$$11.4.c \quad Q_G = C_G \cdot (V_{\text{GS}} - V_T) = 0.8625 \cdot \text{fF} \cdot (3\text{V} - 1\text{V}) = 1.725\text{fC}$$

$$11.4.d \quad N_e = \frac{Q_G}{e} = \frac{1.725\text{fC}}{1.6 \cdot 10^{-19}\text{C}} = 10781$$

$$11.4.e \quad R_{\text{square}} = \frac{1}{q \cdot \mu \cdot N \cdot t} = \frac{1}{1.6 \cdot 10^{-19}\text{C} \cdot 1000 \frac{\text{cm}^2}{\text{V} \cdot \text{s}} \cdot \frac{10781}{0.25 \cdot \mu\text{m}^2}} = 1449.3 \cdot \Omega$$

$$R = \frac{W}{L} \cdot R_{\text{square}} = \frac{1\mu\text{m}}{0.25\mu\text{m}} \cdot 1449.3\Omega = 5.8\text{k}\Omega$$

Note the conduction of a MOSFET is along the width direction by definition.

$$11.4.f \quad k_D = \frac{W}{L} \cdot \mu \cdot C_{\text{ox}} = \frac{1\mu\text{m}}{0.25\mu\text{m}} \cdot 1000 \frac{\text{cm}^2}{\text{V} \cdot \text{s}} \cdot 3.45 \frac{\text{fF}}{\mu\text{m}^2} = 1.38 \cdot \frac{\text{mA}}{\text{V}^2}$$

Note that V_{D_SAT} is not useful in deriving k_D in this problem.