

EE 42


Homework #6

Due Friday, May 7 at 4pm in drop box

 Problem 1:

Imagine that you are fabricating a CMOS inverter from scratch. You want your inverter to have a midpoint of 2.5 V when the supply voltage is 5 V. This means when the input is 2.5 V, the output should be 2.5 V, as shown.

Your fabrication process determines that:
 $C_{OX} = 5 \text{ fF}/\mu\text{m}^2$ for both PMOS and NMOS
 $\mu_n = 500 \text{ cm}^2/(\text{Vs})$
 $\mu_p = 400 \text{ cm}^2/(\text{Vs})$
 $V_{TH(n)} = 1 \text{ V}$
 $V_{TH(p)} = -1 \text{ V}$
 $\lambda_n = 0.1 \text{ V}^{-1}$
 $\lambda_p = -0.1 \text{ V}^{-1}$



You have already decided on the lengths of the transistors; $L_n = L_p = 1.5 \mu\text{m}$.


With $W_n = 10 \mu\text{m}$, what is the value of W_p (the width of the PMOS) needed for this midpoint?

Problem 2:

Find V_{OUT} for the circuit shown at right.

Assume the large-signal model for the diode,
 With $V_F = 2 \text{ V}$.

$W/L\mu_n C_{ox} = W/L\mu_p C_{ox} = 1 \text{ mA}/\text{V}^2$
 $V_{TH(n)} = 1 \text{ V}$
 $V_{TH(p)} = -1 \text{ V}$
 $\lambda_n = \lambda_p = 0 \text{ V}^{-1}$

 

Problem 3:

Consider a CMOS NAND gate.
 Suppose we attach n CMOS logic gate inputs to the output of this NAND gate (fanout of n).

What is the maximum value of n allowed if the worst-case propagation delay t_p through the NAND is not to exceed 100 ns?

Note: The propagation delay varies with different input combinations. You need to find the worst-case combination.

$R_n = 1 \text{ k}\Omega$ $R_p = 3 \text{ k}\Omega$ $C_G = 10 \text{ pF}$

Problem 4:

Let's explore how transistor design, through the choice of the transistor dimensions W and L , as well as the choice of power supply voltage V_{DD} , contributes to gate delay.

R_n and R_p , the pull-down/pull-up transistor resistances, are calculated in the following way:

$R = \text{average value of } (V_{DS} / I_D) \text{ over the time period } 0 \text{ to } t_p \text{ (during pull-up for PMOS or pull-down for NMOS)}$

In other words, average V_{DS} / I_D from the start of the pull, when $V_{DS} = \pm V_{DD}$, to the halfway point of the pull, when $V_{DS} = \pm V_{DD}/2$. During this time, V_{DS} is bigger in magnitude than $V_{DD}/2$, so you can assume saturation mode (Why? Review our inverter analysis of Lecture 20 where we talked about the possible modes during transitions.) You can also neglect the effect of λ .

C_G is calculated in the following way, via the parallel-plate capacitor formula:

$$C_G = (W)(L)(C_{ox}) = (W)(L)(\epsilon_0 k_{ox}) / (t_{ox})$$

where ϵ_0 is a physical constant, and k_{ox} and t_{ox} are fixed by the fabrication process.

In view of these facts, fill in the following table, and provide justification for your answers:

Fill in "increases" or "decreases" in each blank below.			
As W increases,	R _____	C_G _____	t_p _____
As L increases,	R _____	C_G _____	t_p _____
As V_{DD} increases,	R _____	C_G _____	t_p _____

Problem 5:

Suppose you have a DRAM cell, with capacitance $C_{cell} = 25 \text{ fF}$.

In order to read a logic 1 (3 V) from this cell, the bit line must be able to achieve a voltage of at least 0.1 V so the sense amplifier can detect it.

How big can the bit line capacitance C_{line} be?

If $C_{line} = (W)(L)(C_{ox}) = (1 \mu\text{m})(L)(150 \mu\text{F}/\text{m}^2)$ where L is the length of the bit line in meters, how long can the bit line be?