

EE 42

Homework #5 Solutions

Problem 1:

For there to be between 20 mA and 100 mA of current flowing, the diode must be forward biased. The diode will take 2 V of V_{digital} , and the resistor will take the rest of V_{digital} .

The current flowing through the circuit will thus be


$$I_{\text{diode}} = (V_{\text{digital}} - 2 \text{ V})/R_{\text{limit}}$$

R_{limit} must be small enough so that I_{diode} is at least 20 mA when V_{digital} is at its smallest, 4 V.


$$(4 \text{ V} - 2 \text{ V})/R_{\text{limit}} \geq 20 \text{ mA} \quad R_{\text{limit}} \leq 100 \Omega$$

R_{limit} must be big enough so that I_{diode} is less than 100 mA when V_{digital} is at its biggest, 5 V.

$$(5 \text{ V} - 2 \text{ V})/R_{\text{limit}} \leq 100 \text{ mA} \quad R_{\text{limit}} \geq 30 \Omega$$

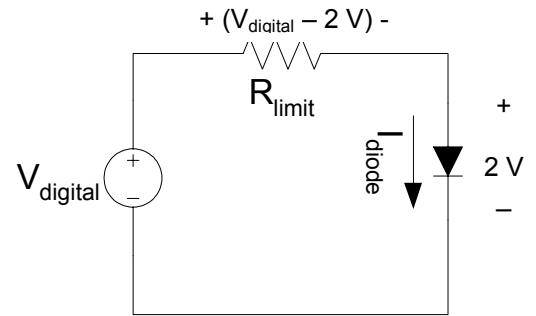

Problem 2:

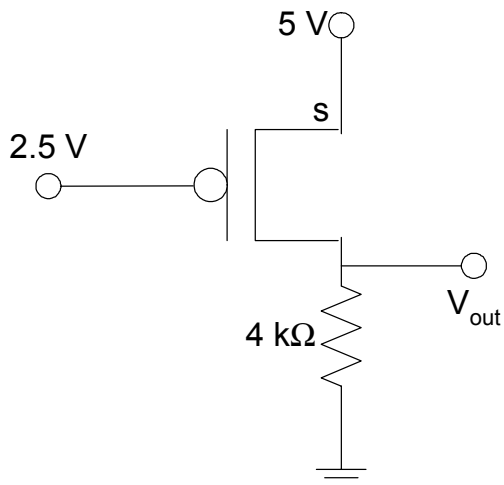

$$V_{\text{GS}} = 2.5 \text{ V} - 5 \text{ V} = -2.5 \text{ V}$$

Transistor is not cutoff.

Guess saturation mode:

$$I_{\text{D}} = -(1 \text{ mA/V}^2)(1/2)(-2.5 \text{ V} - -1 \text{ V})^2(1 + 0 V_{\text{DS}})$$

$$I_{\text{D}} = -1.125 \text{ mA}$$

By KVL,

$$(4 \text{ k}\Omega)I_{\text{D}} + V_{\text{DS}} + 5 \text{ V} = 0 \quad \text{so} \quad V_{\text{DS}} = -0.5 \text{ V}$$

For saturation, $V_{\text{DS}} < V_{\text{GS}} - V_{\text{TH(p)}}$ **Not true!**

So transistor must be in triode mode.

$$I_{\text{D}} = -(1 \text{ mA/V}^2)(-2.5 \text{ V} - -1 \text{ V} - (V_{\text{DS}}/2))(V_{\text{DS}})$$

It's still true that $(4 \text{ k}\Omega)I_{\text{D}} + V_{\text{DS}} + 5 \text{ V} = 0$ so substitute to get

$$-(5 \text{ V} + V_{\text{DS}})/4 \text{ k}\Omega = -(1 \text{ mA/V}^2)(-2.5 \text{ V} - -1 \text{ V} - (V_{\text{DS}}/2))(V_{\text{DS}})$$

$$\text{Solutions: } V_{\text{DS}} = \{-1 \text{ V}, -2.5 \text{ V}\}$$


$V_{\text{DS}} = -2.5 \text{ V}$ not possible for triode mode (need $V_{\text{DS}} > V_{\text{GS}} - V_{\text{TH(p)}}$) so $V_{\text{DS}} = -1 \text{ V}$

$$I_{\text{D}} = -(1 \text{ mA/V}^2)(-2.5 \text{ V} - -1 \text{ V} - (-1 \text{ V}/2))(-1 \text{ V}) = -1 \text{ mA}$$

$$V_{out} = V_{DS} + 5 V = 4 V$$

(Typically, the numbers do not work out this nicely!)

Problem 3:

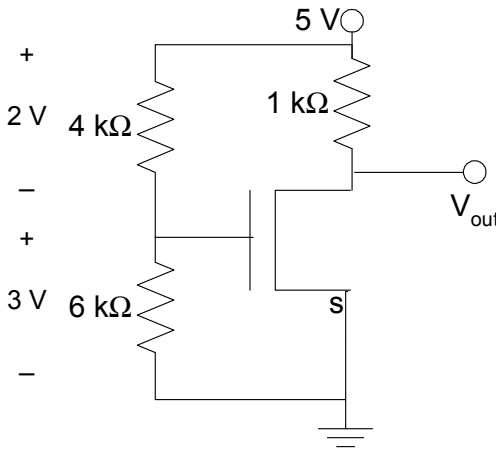

Notice that no current goes into or out of the gate.
So the 4 k and 6 k resistors have the same current.

Voltage division or Ohm's law tells us that the 4 k resistor has 2 V and the 6 k resistor has 3 V as shown.

So $V_{GS} = 3 V$ (over the 6 k resistor).

The transistor is not cutoff.


Guess saturation mode:

$$I_D = (1 \text{ mA/V}^2)(1/2)(3 V - 1 V)^2(1+0 V_{DS}) \quad I_D = 2 \text{ mA}$$

By KVL, $(1 \text{ k}\Omega)I_D + V_{DS} - 5 V = 0$ so $V_{DS} = 3 V$

For saturation, $V_{DS} > V_{GS} - V_{TH(n)}$ **Yes!** Saturation was the right guess. $V_{out} = V_{DS} = 3 V$

Problem 4:

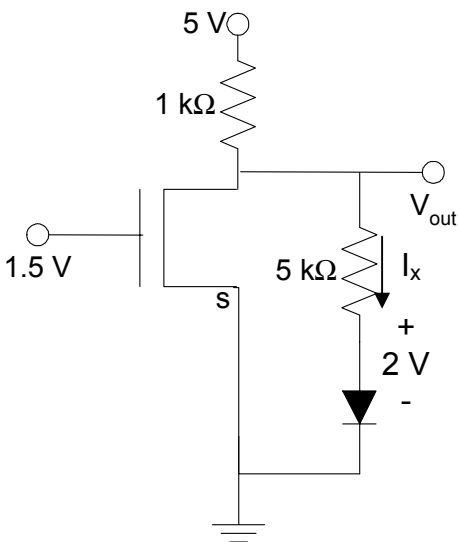

$V_{GS} = 1.5 V$ Transistor is not cutoff. Guess saturation:

$$I_D = (1 \text{ mA/V}^2)(1/2)(1.5 V - 1 V)^2(1+0 V_{DS}) \quad I_D = 125 \mu A$$

Now we must find V_{DS} . The only way to do this is by KVL.
Guess that the diode is forward biased (small V_{in} means big V_{out} for our inverter). For large-signal model, this means diode has $V_F = 2 V$ and some positive current. Now starting KVL at ground and going clockwise,

$$-V_{DS} + 5 \text{ k}\Omega I_x + 2 V = 0 \quad \text{Need to find } I_x.$$

KVL again, starting at ground, going up diode branch and 1k resistor branch, dropping back to ground over 5 V source:

$$-2 V - 5 \text{ k}\Omega I_x - 1 \text{ k}\Omega (I_x + 125 \mu A) + 5 V = 0$$

$$I_x = 479 \mu A$$

$V_{DS} = 5 \text{ k}\Omega I_x + 2 V$ (by previous KVL) $V_{DS} = 4.395 V$

For saturation, $V_{DS} > V_{GS} - V_{TH(n)}$ **Yes!** Saturation was the right guess. $V_{out} = V_{DS} = 4.395 V$