

EECS 40/43
Pre-Lab
DMM


Name: _____

TA: _____

Section: _____


1. If $V=10V$ and $R = 10k\Omega$, find I .

$I =$ _____

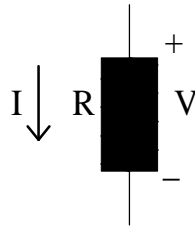

2. Should the DMM, set up to measure current, ever be placed in parallel with the DC power supply? Explain.

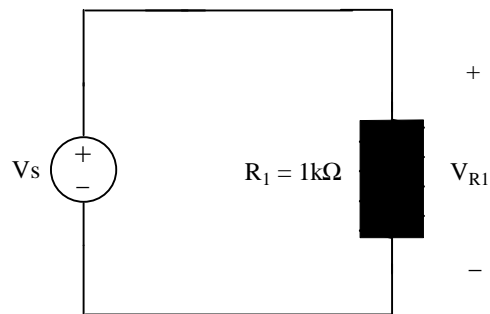3. Given the circuit below, what would you expect V_{R1} to be with each of the following DC power supply settings?



- a) $V_s = 5V$, current limit = 10mA
b) $V_s = 5V$, current limit = 2mA

$V_{R1} =$ _____

$V_{R1} =$ _____

4. Find V_X .

$V_X =$ _____

