

EECS151/251A Discussion 11

Christopher Yarp


Apr. 19, 2019

Plan for Today

- Adders
- Multipliers
- Pipelining
- Questions

Adders

- Earlier in the term, we discussed the Carry Ripple Adder
 - Replicates how we add by hand
 - Compute $\text{sum}[i]$ and $\text{carry_out}[i]$ based on $A[i]$, $B[i]$, and $\text{carry_in}[i]$
 - $\text{carry_in}[i] = \text{carry_out}[i-1]$, $\text{carry_in}[0] = 0$ if unsigned.
- Primary Downside: Long Critical Path
 - The carry ripple results in a critical path that goes through each FA
 - Grows linearly with the number of bits added
- How do we make adders faster?
 - Cut the critical path!
 - How?
 - Change how we work with carries!

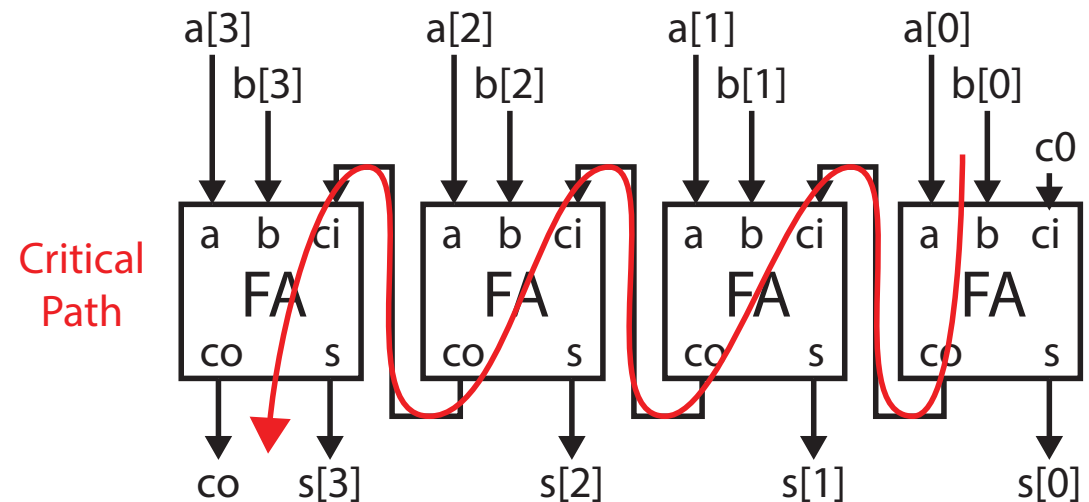

Carry Select Adder

- One way to reduce critical path is to cut the adder into 2 parts, severing the carry chain.
 - Problem: The LSB side of the adder will work as expected but the MSB side still depends on the value of the carry!
 - Solution: There are 2 possibilities for the carry-in to the MSB adder, 0 and 1. Calculate the result of **BOTH** cases and pick the correct one
 - Allows the MSB computations to occur in parallel with the LSB calculation with a small delay to select the correct value
 - Downside: Replicated logic, wasted effort (energy) on result that is not used


Carry Select Example:

Example:

4' b0111 (7)


+ 4' b0101 (5)

5' b01100 (12)

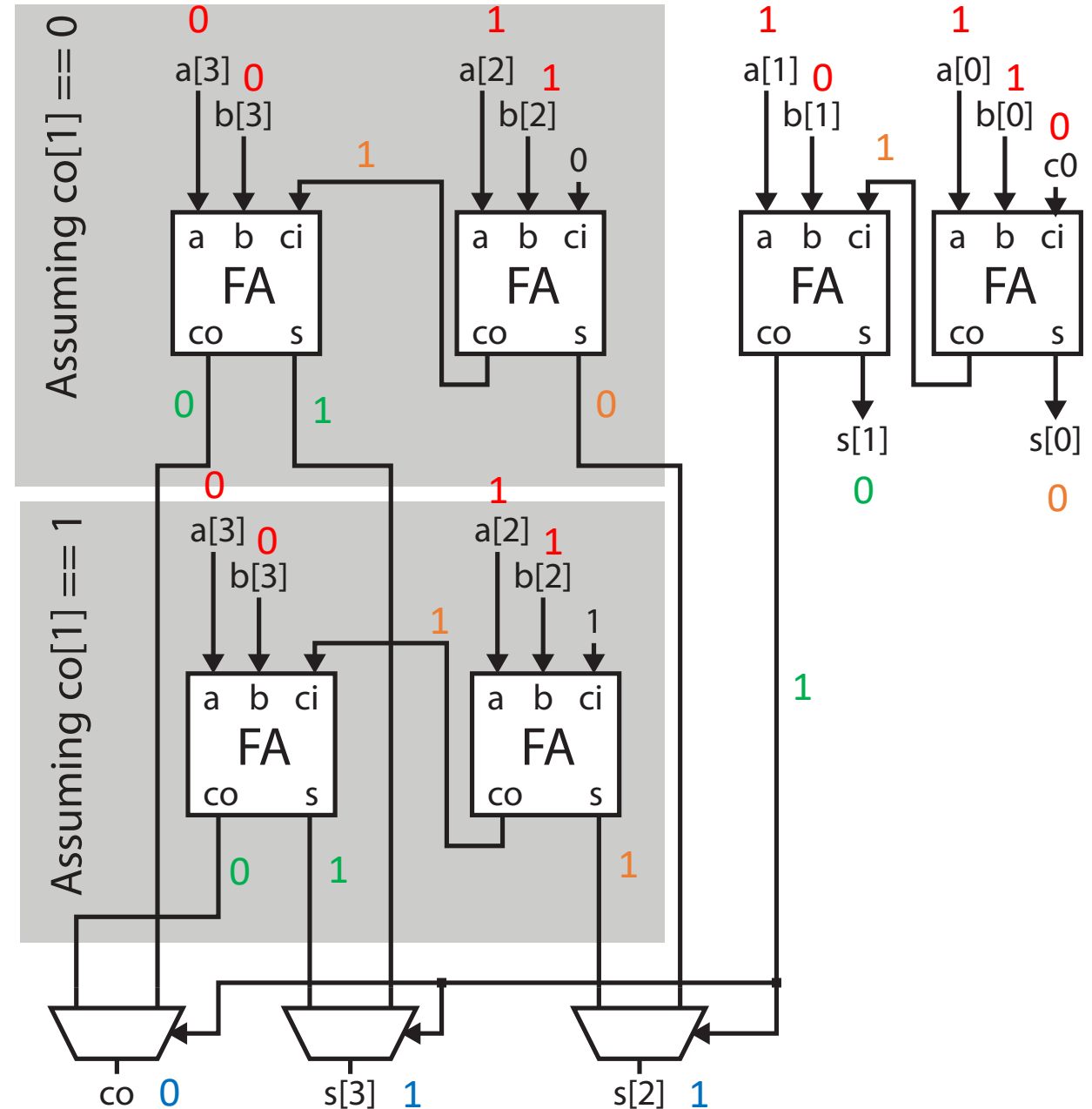

Quick Aside: Associativity

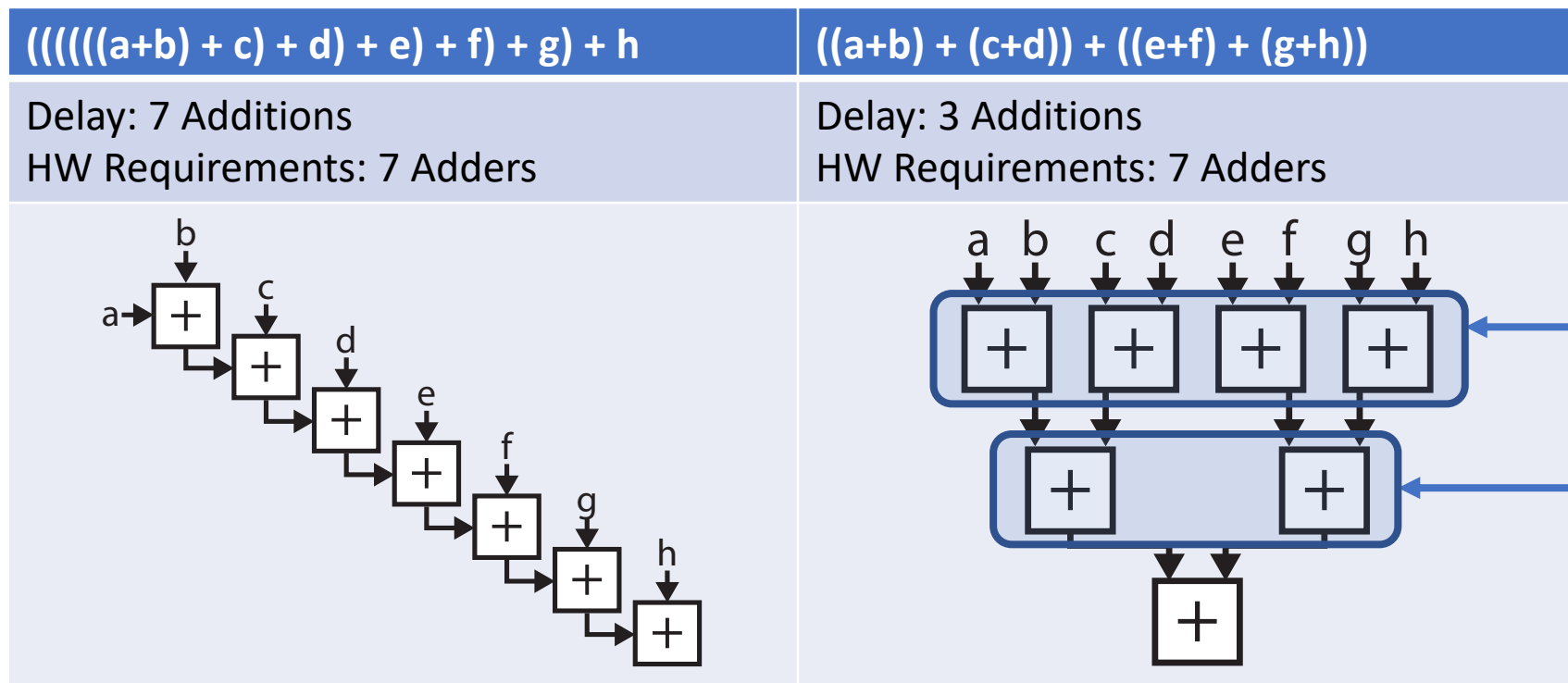- An operator, #, is associative if the following is true: $(a \# b) \# c = a \# (b \# c)$
- Addition*, multiplication, AND, OR, XOR, are associative
- This allows us to compute them in a tree structure
 - Ex. Compute: $a+b+c+d+e+f+g+h$



Adders in same layer can be computed in parallel!

See: [Weisstein, Eric W. "Associative." From MathWorld--A Wolfram Web Resource. http://mathworld.wolfram.com/Associative.html](http://mathworld.wolfram.com/Associative.html)

* Addition of floating point numbers is generally not considered associative

Carry Lookahead Adder

- The carry logic, as we have presented it, is not associative
 - We need to compute the bits in order from LSB to MSB, since each FA needs the carry-out of the previous stage
- This is a problem as it limits us to a linear chain of FAs, preventing us from doing work in parallel
- Solution: Make the carry logic associative through re-defining the FAs

Redefining FAs: Carry Generate and Propagate

- Each FA Now Generates 2 New Signals
 - g (Generate): True if the adder is guaranteed to **generate a carry**, regardless of the value of the carry-in
 - If both operands have a 1 in this position, it is guaranteed that a carry will be generated
 - $g_i = a_i \cdot b_i$
 - p (Propagate): True if the carry-out of this stage will equal the carry-in (**propagate carry-in**)
 - If exactly one of the inputs is true, the carry-out will equal the carry-in
 - $p_i = a_i \oplus b_i$

Redefining FAs: Carry Generate and Propagate

- The sum and carry-out of a FA can now be defined in terms of these new signals
 - The sum is true if:
 - A single input is true and the carry-in is false
 - The inputs are both 0 or both 1, and the carry-in is true
 - $s_i = p_i \oplus c_i$, where c_i is the carry-in for this digit
 - The carry-out is true if:
 - Carry generate is true
 - Propagate is true and the carry-in is true
 - $c_{i+1} = g_i + p_i \cdot c_i$

What good did that do?



- Note that the sum and carry-out bits in each FA still depend on the values of the carry-in.
 - This means that we still need to compute the carry-in value for each bit position and have logic to generate the sum
- However, the p and g values can all be computed simultaneously
 - There is **no dependence** on carry-in when computing p and g !
- We leverage this property in the carry lookahead adder by grouping together adders and creating P and G signals for the entire group
 - P represents if the entire group will propagate a carry signal
 - G represents if the entire group generates a carry signal
- The P and G signals can be processed in a tree structure

Carry Look-ahead Adder

- The smaller blocks are modified full adders.
 - Can calculate g and p immediately
 - Must wait for carry-in to compute sum bit
 - Some FAs are required to create a carry-out
 - $g_i = a_i \cdot b_i$
 - $p_i = a_i \oplus b_i$
 - $s_i = p_i \oplus c_i$
 - $c_{i+1} = g_i + p_i \cdot c_i$



No Dependence on carry-in

Depend on carry-in

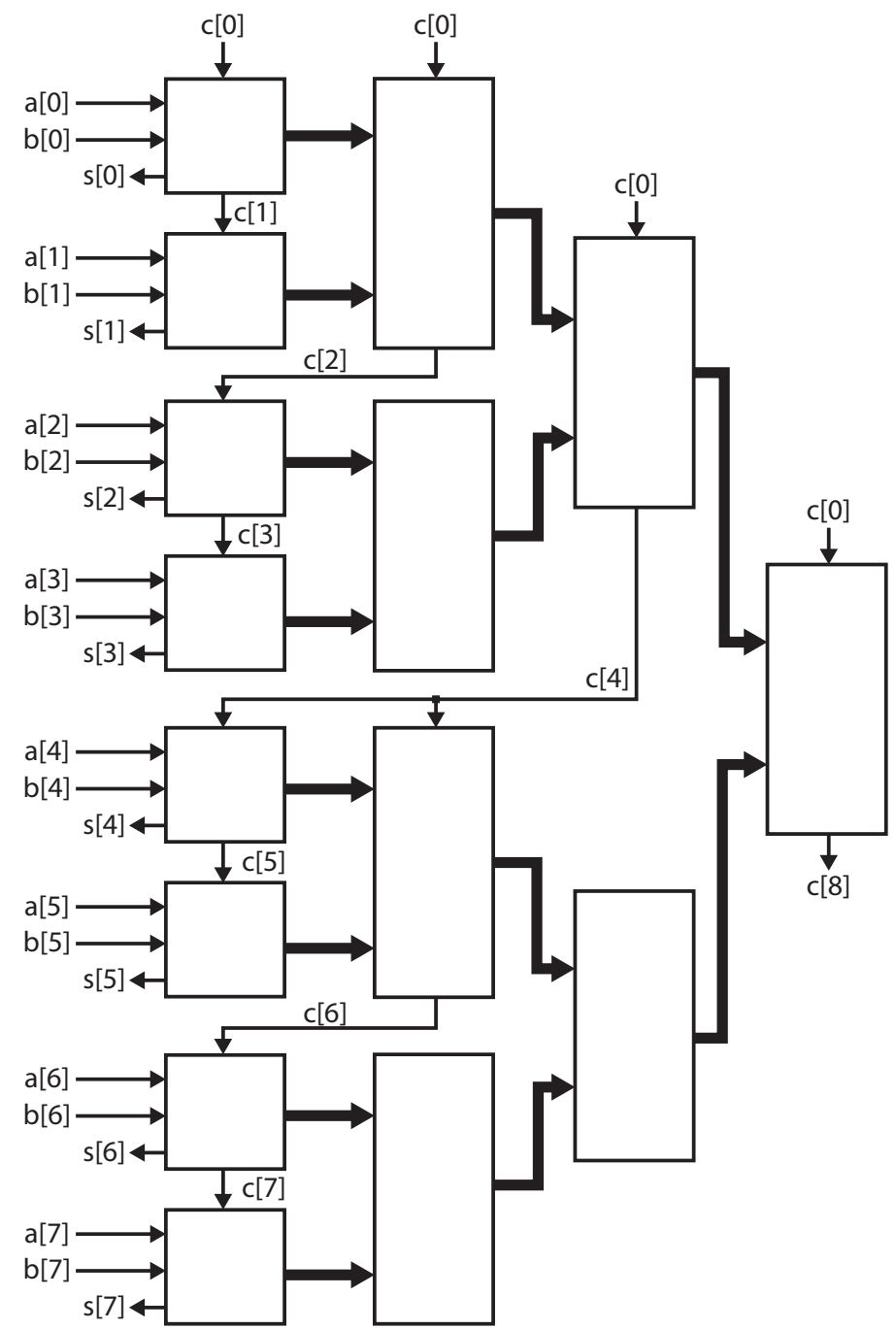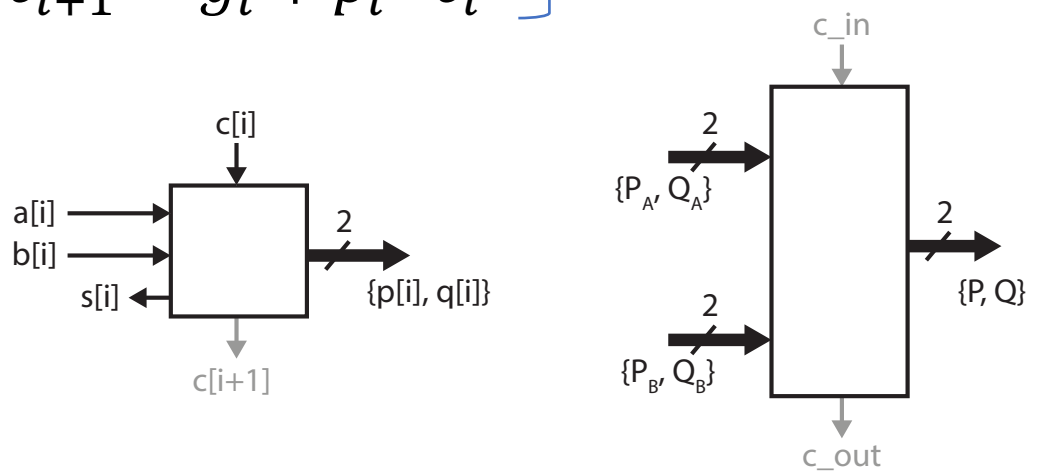

Carry Look-ahead Adder

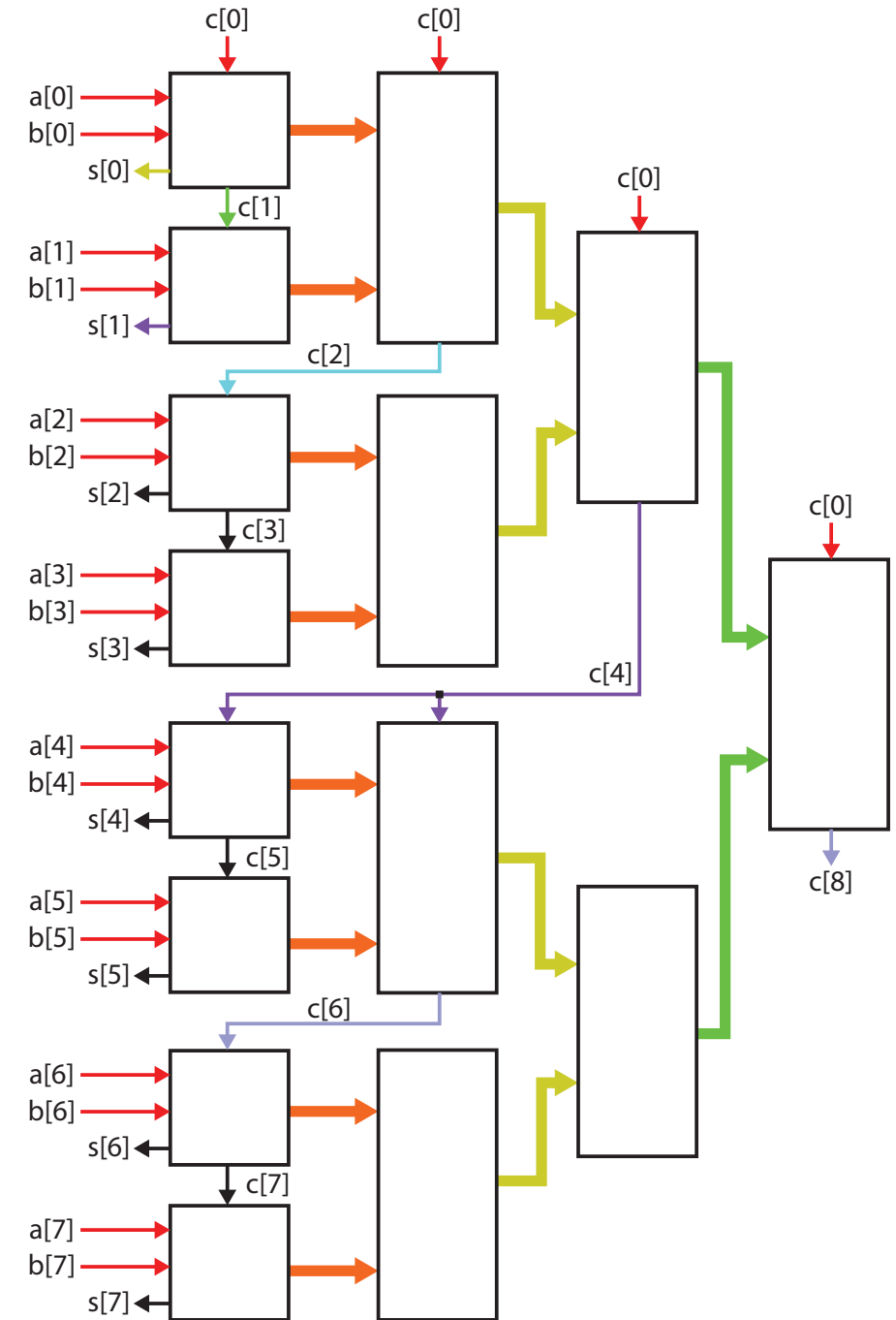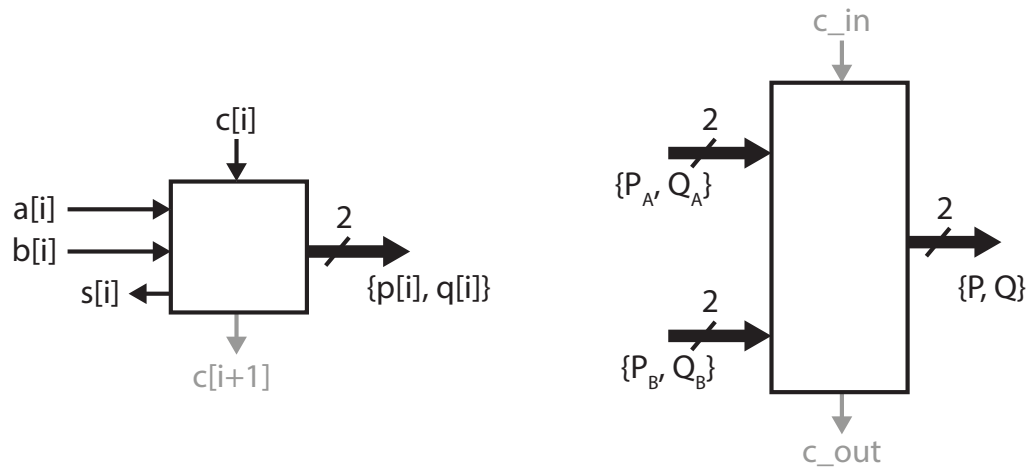- The larger blocks compute P & G for higher levels of the hierarchy.
 - P & G can be computed without carry-in
 - Carry-in is required to generate carry-out
 - $P = P_A P_B$
 - $G = G_B + G_A P_B$ } No Dependence on carry-in
 - $C_{out} = G + C_{in} P$ } Depend on carry-in



Parallel Prefix Adder

- One disadvantage of the carry lookahead adder as described in the lecture slides is that the carry-out bit still ripple through the groups in the first layer
- An alternative is to compute the carry bits directly without any grouping
 - However, we don't want to fall back to a carry ripple solution.
 - Trick: unroll the expression for the carry bit

Unrolling the Carry-in


- Recall: $c_{i+1} = g_i + p_i \cdot c_i$
- Let's compute the carries using unrolling
 - $c_0 = 0$ (unsigned)
 - $c_1 = g_0 + p_0 \cdot c_0 = g_0$
 - $c_2 = g_1 + p_1 \cdot c_1 = g_1 + p_1(g_0) = g_1 + p_1g_0$
 - $c_3 = g_2 + p_2 \cdot c_2 = g_2 + p_2(g_1 + p_1g_0) = g_2 + p_2g_1 + p_2p_1g_0$
 - $c_4 = g_3 + p_3 \cdot c_3 = g_3 + p_3(g_2 + p_2g_1 + p_2p_1g_0) = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0$
- Computing the carries involves ANDs and ORs of individual p and g signals
 - These p and g signals can all be computed in parallel since they do not depend on carry-ins
- These operations are associative!
 - We can change the order in which they are evaluated
 - Allows us to compute them in a tree (parallel computation)!

Parallel Prefix Trees


- Similar to a reduction tree except that you want to keep the intermediate values
 - Intermediate values are re-used when computing
- In our case, we *could* use a reduction tree to compute the last carry.
 - This would be of limited use to us because we need all of the intermediate carry bits that would be computed as part of the reduction tree
- Parallel prefix trees give us these intermediate values!
 - Work on operators that are associative

Different Parallel Prefix Trees

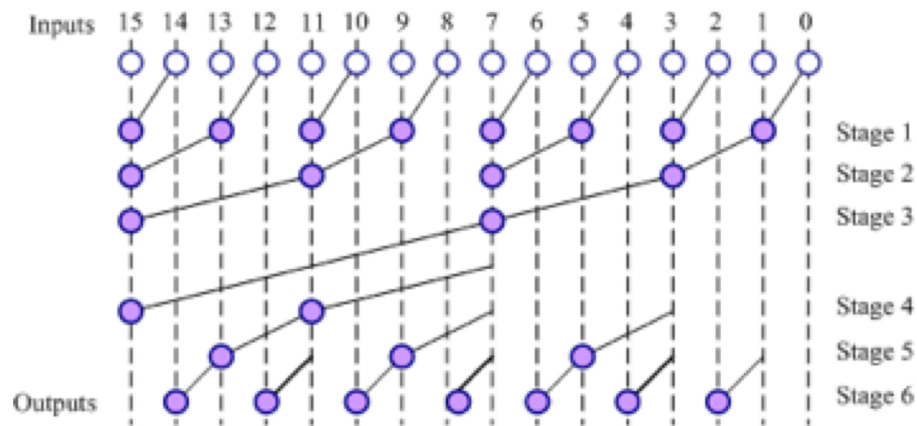- There is a tradeoff in parallel prefix trees in how intermediate values are computed/reused
- Note that both of these graphs produce the same outputs (the partial results)



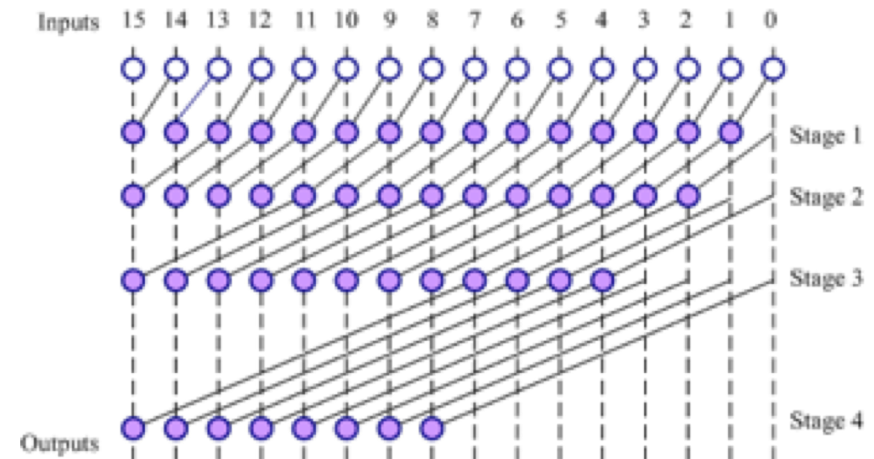Brent-Kung (Diagram from Lecture Slides)
Most reuse (minimal logic) but with a longer critical path



Kogge-Stone (Diagram from Lecture Slides)
Requires more resources but has a shorter critical path.

Parallel Prefix Adder

- The Parallel Prefix Tree Described Above is for computing the **carry bits**
- We **still need full adders** to produce the p & g signals and to calculate the final sum
 - Modified **full adders feed the parallel prefix tree** with p and g values
 - **Full adders receive the carry in from the parallel prefix tree** to compute the sum bit

Multipliers

- Remember, the mechanics of multiplication in binary are generally the same as decimal multiplication (signed multiply requires a slight tweak).
- 2 Steps to Multiplication:
 - Generation of partial products
 - Adding partial products
- Making faster multipliers mostly involves changing how we deal with generating and adding the partial products

Unsigned Multiplication Example


$$\begin{array}{r} 4'b0011 \quad (3) \\ * 4'b0110 \quad (6) \end{array}$$

- Partial Products can be generated in parallel
- Let's try to improve the addition of the partial products

$$\begin{array}{r} 4'b0011 \quad (3) \\ * 4'b0110 \quad (6) \\ \hline \quad \quad 0000 \\ \quad \quad 0011 \\ \quad 0011 \\ + 0000 \\ \hline \quad 00010010 \quad (18) \end{array} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \text{Partial Products}$$

Carry Save Addition

- When we generate a carry in a given column of an addition, we add it to the 2 values in the next column.
 - This addition may in turn generate its own carry
- If adding carries is just like another addition, can we delay adding the carry bits until later?
 - Yes, so long as we remember what the carry bits need to be added
- This is the basis of the carry save adder:
 - Takes in a, b, and carry_in (multi-bit)
 - Produces a sum and carry_out (multi-bit)


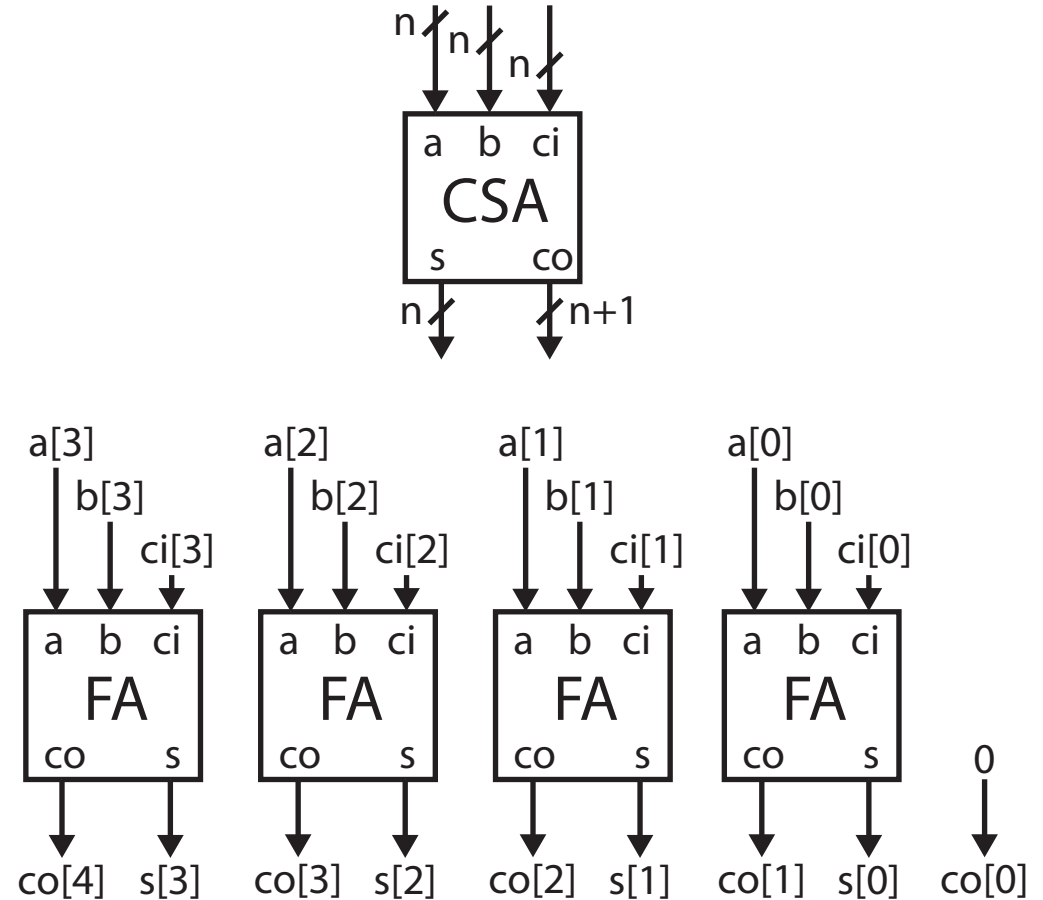


Using Carry Save Addition

- Using Carry Save Addition Allows us to create a multi-input adder that is:
 - Relatively fast: Carry Save Adders do not have a carry ripple
 - Relatively small: do not need the logic to handle the carry logic to create a fast adder
- However, still need a standard adder at the end to add the final carry-out and sum.
 - This is one of the fast adders such as the Carry Lookahead or Parallel Prefix Adders
 - Good news! We only need one of them.

Using Carry Save Addition

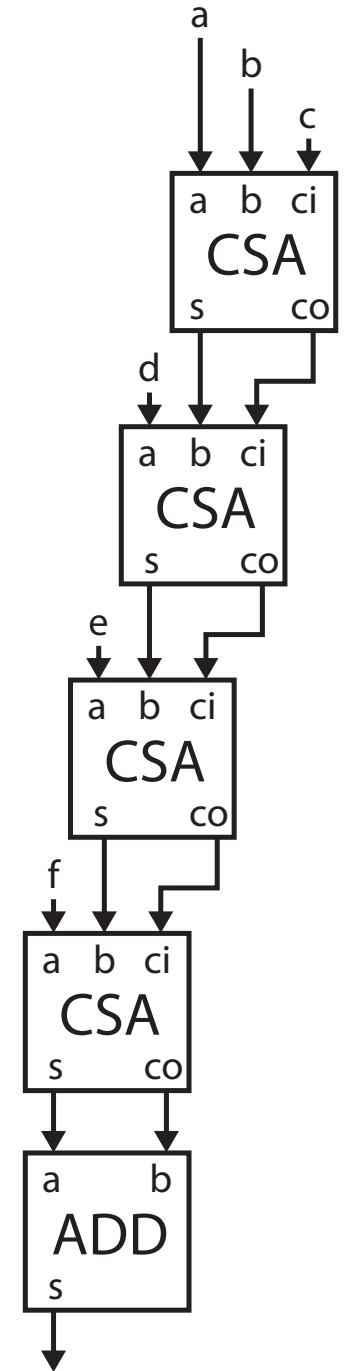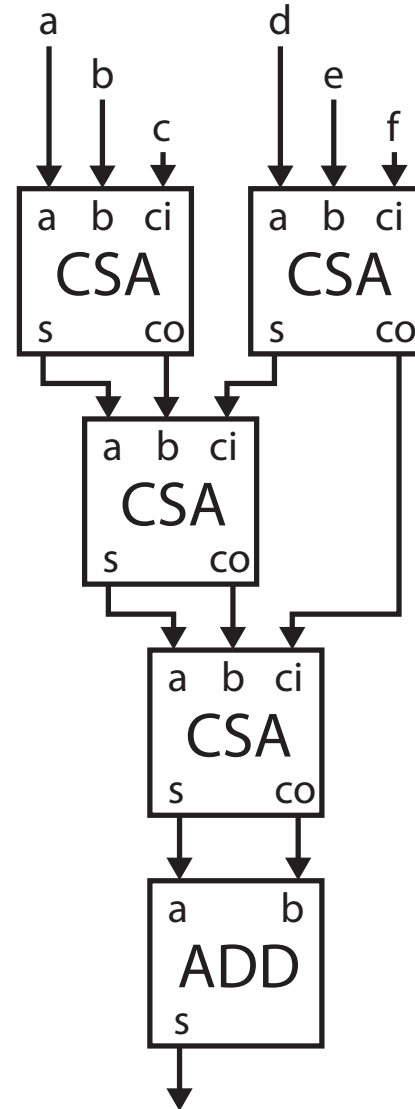
- Because addition is associative, it actually does not matter what order the carry bits are added back into the sum
 - Can use a tree structure




Quick Note on Pipelining With Feedback

- Pipelining in the presence of feedback is problematic due to the dependence
- However, if the feedback loop includes operators that are associative and commutative, we may be able to make the feedback loop shorter.
 - Tightening the feedback path pushes some logic outside of the loop
 - Logic outside of the feedback loop (feed forward) can usually be pipelined relatively easily.


Example from Lecture

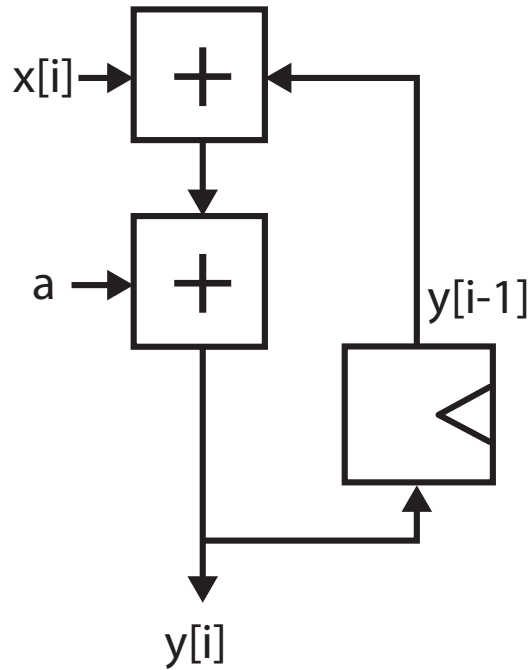

Orig: $y[i] = (y[i-1] + x[i]) + a$

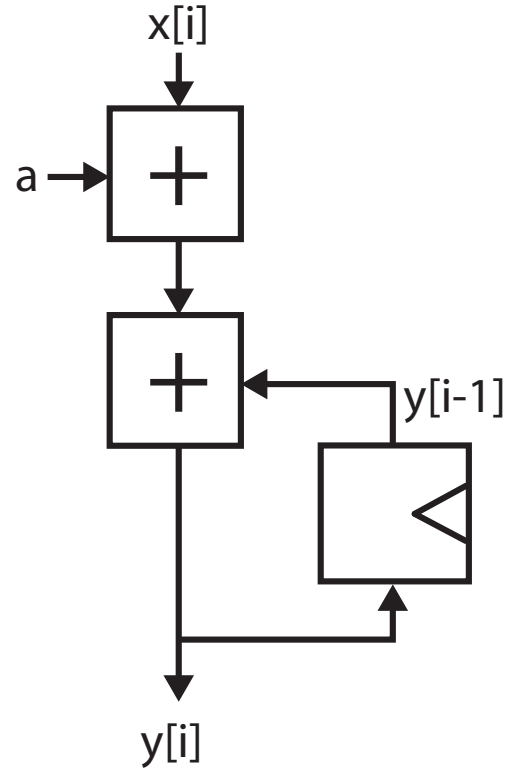

Reorg: $y[i] = y[i-1] + (x[i] + a)$

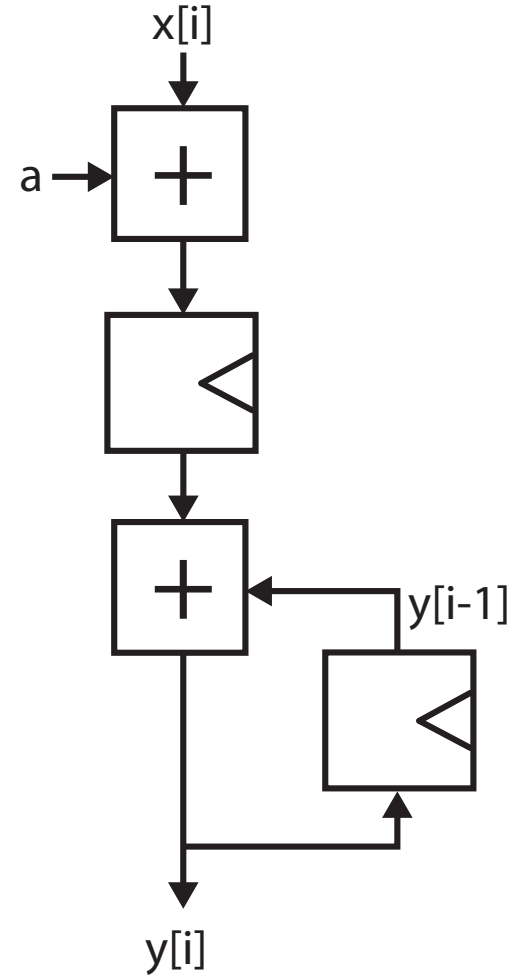

Feed Forward Section Pipelined