

EECS 151/251A Homework 2

Due Monday, Feb 11th, 2019

Suggestions for this HW Assignment

You will be asked to write several Verilog modules as part of this HW assignment. You are highly encouraged to test your modules by running them through a simulator. Several simulator options were discussed in Discussion 2 including <https://www.edaplayground.com> which is a free, online, Verilog simulator.

Problem 1: Interpreting Verilog [4,2 pts.]


- (a) Sketch a gate-level schematic of the circuit described by the Verilog code below. [4 pts]
- (b) Try to simplify the schematic by sharing gates when possible. [2 pts]

```
module circuit1(a, b, c, y z)
  input a, b, c;
  output y,z;

  assign y = a & b & c | a & b & ~c | a & ~b & c;
  assign z = a & b | ~a & ~b;
endmodule
```

Solution:

Part (a):

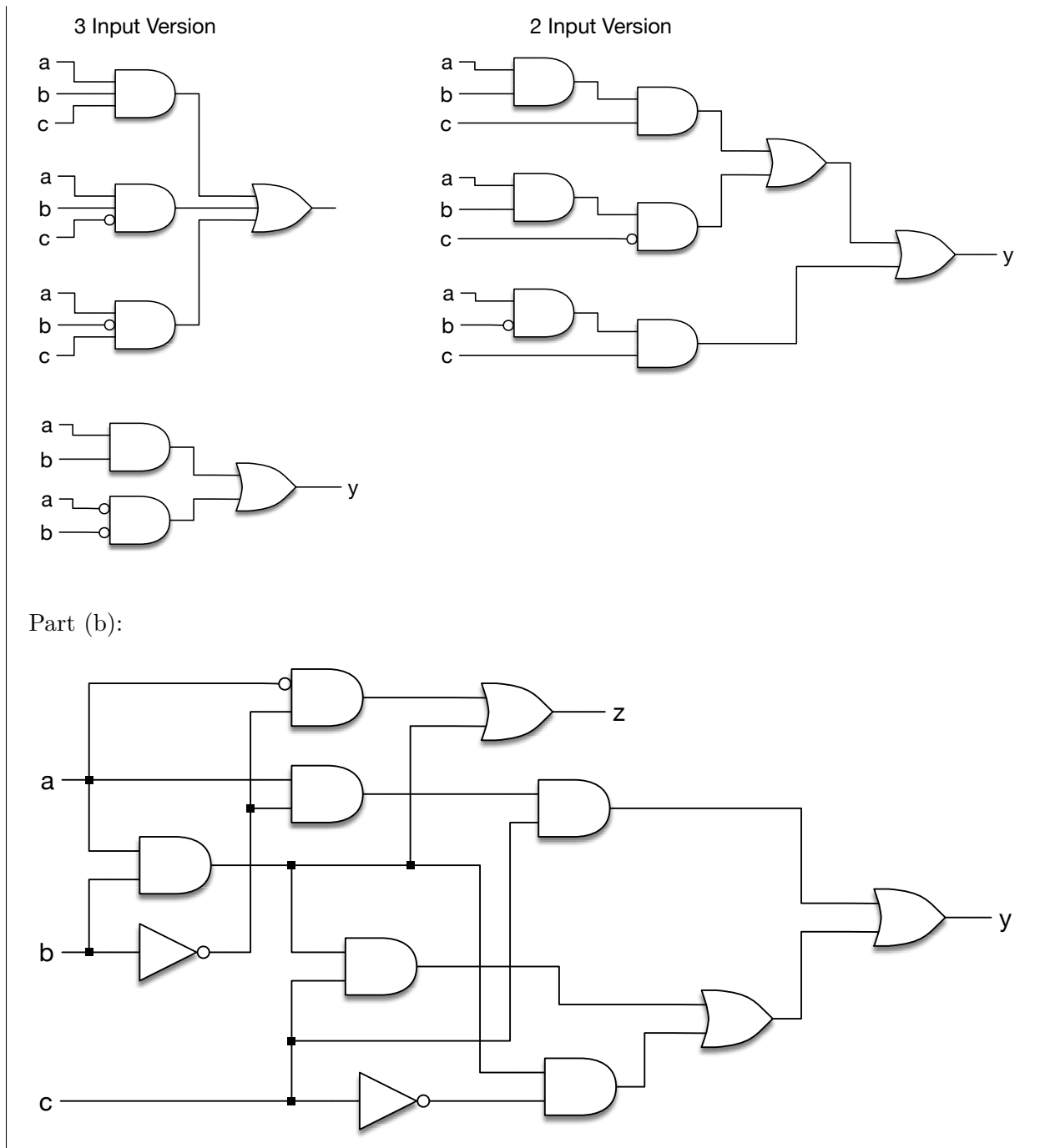

Problem 2: Interpreting and Re-Implementing Verilog [4,3,4 pts.]

- (a) Sketch a gate-level schematic of the circuit described by the Verilog code below (using only simple logic gates)
- (b) Try to simplify the schematic by sharing gates and eliminating unnecessary gates.
- (c) Write an equivalent implementation of circuit2 that uses the Verilog “case” construct.

```


module circuit2(a, y)
  input [3:0] a;
  output [1:0] y;

  always @(*)
    if (a[0]) y = 2'b11;
    else if (a[1]) y=2'b10;
    else if (a[2]) y=2'b01;
    else if (a[3]) y=2'b00;
    else
      y=a[1:0];
endmodule


```

Solution:

Part (a):

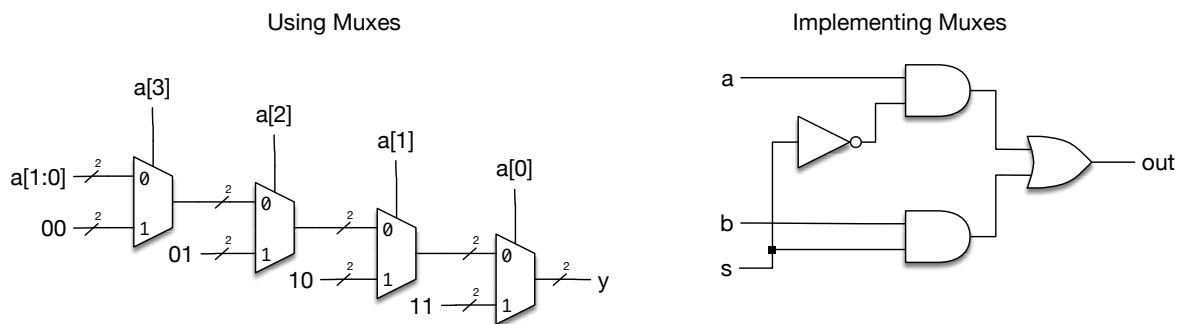

Part (b):

 

Part (c): Verilog Modules:

```

1  module circuit2_case(a, y);
2    input [3:0] a;
3    output reg [1:0] y;
4
5    always @(*)
6      //Need to handle the precedence in the if/else
7      case(a)
8        //First if

```

```

9      4'b0001: y = 2'b11; //The actual greyscale
10     //4'b0011: y = 2'b11; Handled by default
11     4'b0101: y = 2'b11;
12     //4'b0111: y = 2'b11; Handled by default
13     4'b1001: y = 2'b11;
14     //4'b1011: y = 2'b11; Handled by default
15     4'b1101: y = 2'b11;
16     //4'b1111: y = 2'b11; Handled by default
17
18     //Second if
19     4'b0010: y = 2'b10; //The actual greyscale
20     //4'b0110: y = 2'b10; Handled by default
21     //4'b1010: y = 2'b10; Handled by default
22     //4'b1110: y = 2'b10; Handled by default
23
24     //Third if
25     4'b0100: y = 2'b01; //The actual greyscale
26     4'b1100: y = 2'b01;
27
28     //Fourth if
29     4'b1000: y = 2'b00; //The actual greyscale
30     default: y = a[1:0];
31 endcase
32 endmodule

```

There is a more concise way of describing this circuit using a casez statement. The casez allows you to specify don't cares with '?'s in case statements.

```

1  module circuit2_casez(a, y);
2      input [3:0] a;
3      output reg [1:0] y;
4
5      always @(*)
6          //Need to handle the precedence in the if/else
7          casez(a)
8              //First if
9              4'b???1: y = 2'b11;
10             //Second if
11             4'b??10: y = 2'b10;
12             //Third if
13             4'b?100: y = 2'b01;
14             //Fourth if
15             4'b1000: y = 2'b00;
16             default: y = a[1:0];
17         endcase
18     endmodule

```

Problem 3: Translating to Verilog [3,3 pts.]

Consider the decoder examples presented in lecture 3, page 5 of the notes. These examples used a fake HDL. Rewrite these examples in proper Verilog.

Solution:

Verilog Modules:

```
1  //Structural
2  module Decoder_structural(
3      output x0,
4      output x1,
5      output x2,
6      output x3,
7      input  a,
8      input  b);
9
10     wire abar, bbar;
11     not(bbar, b);
12     not(abar, a);
13     and(x0, abar, bbar);
14     and(x1, abar, b);
15     and(x2, a, bbar);
16     and(x3, a, b);
17 endmodule
18
19 //Behavioral
20 module Decoder_behavioral(
21     output reg x0,
22     output reg x1,
23     output reg x2,
24     output reg x3,
25     input  a,
26     input  b);
27
28     always @(*) begin
29         case({a,b})
30             //You can concatenate on the left hand side
31             2'b00: {x3, x2, x1, x0} = 4'h1;
32             2'b01: {x3, x2, x1, x0} = 4'h2;
33             2'b10: {x3, x2, x1, x0} = 4'h4;
34             2'b11: {x3, x2, x1, x0} = 4'h8;
35         endcase
36     end
37
38 endmodule
```

See the appendix for an example testbench.

Problem 4: Testing a Grey-code to Binary Converter [6,4 pts.]

- (a) Write a Verilog testbench that would instantiate and exhaustively test a 4-bit Gray-code to binary-code converter. (Hint: you may use the generator presented in class.)
- (b) Draw the gate-level circuit diagram of the 4-bit Gray-code to binary converter.

Solution:

Part (a): Verilog Module:

```
1 // From Slides
2 module gray2bin1 (bin, gray);
3     parameter SIZE = 8;
4     output [SIZE-1:0] bin;
5     input [SIZE-1:0] gray;
6
7     genvar i;
8
9     generate for (i=0; i<SIZE; i=i+1) begin:bitchain
10         assign bin[i] = ^gray[SIZE-1:i];
11     end endgenerate
12 endmodule
```

Verilog Testbench:

```
1 `timescale 1ns/1ns
2 module bin_gray_tester();
3     reg [3:0] in;
4     reg [3:0] out_bin2gray;
5     wire [3:0] out_gray2bin;
6     wire match;
7
8     reg fail;
9
10    initial in = 0;
11    initial fail = 0;
12
13    always @(*) begin
14        case(in)
15            4'b0000: out_bin2gray = 4'b0000;
16            4'b0001: out_bin2gray = 4'b0001;
17            4'b0010: out_bin2gray = 4'b0011;
```

```
18     4'b0011: out_bin2gray = 4'b0010;
19     4'b0100: out_bin2gray = 4'b0110;
20     4'b0101: out_bin2gray = 4'b0111;
21     4'b0110: out_bin2gray = 4'b0101;
22     4'b0111: out_bin2gray = 4'b0100;
23     4'b1000: out_bin2gray = 4'b1100;
24     4'b1001: out_bin2gray = 4'b1101;
25     4'b1010: out_bin2gray = 4'b1111;
26     4'b1011: out_bin2gray = 4'b1110;
27     4'b1100: out_bin2gray = 4'b1010;
28     4'b1101: out_bin2gray = 4'b1011;
29     4'b1110: out_bin2gray = 4'b1001;
30     4'b1111: out_bin2gray = 4'b1000;
31     endcase
32 end
33
34 //Instantiate the DUTs
35 gray2bin1 orig(.gray(out_bin2gray), .bin(out_gray2bin));
36
37 assign match = (in == out_gray2bin);
38
39 always #2 begin
40     in = in + 4'd1;
41 end
42
43 initial begin
44     $dumpfile("dump.vcd"); //Setup file dump (for waveform viewer)
45     $dumpvars; //Dump signals to dumpfile
46
47     #33
48     if(fail)
49         $display("Test FAIL");
50     else
51         $display("Test PASS");
52     $finish();
53 end
54
55 initial begin
56     #1
57     forever begin
58         $strobe("time: %4d, in: %b, out_bin2gray: %b, out_bin2gray: %b,
59             ↪ match %b", $time, in, out_bin2gray, out_gray2bin, match);
60     end
61 end
62
63 initial begin
```

```

64     #1
65     forever begin
66         if(!match)
67             fail = 1;
68         #2;
69     end
70 end
71 endmodule

```

Another method is to use a binary to Gray-code converter to produce a series of gray codes. These Gray-codes can be fed to our Gray-code to binary converter which should convert to the original binary number. The binary to Gray-code converter used here comes from Weste & Harris pg 471.

```

1  //Weste & Harris pg 471
2  //Binary -> Gray Code
3  //G_{N-1} = B_{N-1}
4  //G_{i} = B_{i+1} ^ B_{i} for N-1>i>=0
5
6  module bin2gray #(parameter N = 4)(
7      input  [N-1:0] bin,
8      output [N-1:0] gray);
9
10     //Implementing Weste & Harris pg 471
11
12     //Calculate the N-1 bit
13     assign gray[N-1] = bin[N-1];
14
15     genvar i;
16     generate
17         for(i = N-2; i>=0; i = i-1) begin:gray_chain
18             assign gray[i] = bin[i+1] ^ bin[i];
19         end
20     endgenerate
21 endmodule

```

```


1  `timescale 1ns/1ns
2  module bin_gray_tester();
3      reg [3:0] in;
4      wire [3:0] out_bin2gray;
5      wire [3:0] out_gray2bin;
6      wire match;
7
8      reg fail;
9

```



```
10  initial in = 0;
11  initial fail = 0;
12
13  //Instantiate the DUTs
14  bin2gray dut(.bin(in), .gray(out_bin2gray));
15  gray2bin1 orig(.gray(out_bin2gray), .bin(out_gray2bin));
16
17  assign match = (in == out_gray2bin);
18
19  always #2 begin
20      in = in + 4'd1;
21  end
22
23  initial begin
24      $dumpfile("dump.vcd"); //Setup file dump (for waveform viewer)
25      $dumpvars; //Dump signals to dumpfile
26
27      #33
28      if(fail)
29          $display("Test FAIL");
30      else
31          $display("Test PASS");
32      $finish();
33  end
34
35  initial begin
36      #1
37      forever begin
38          $strobe("time: %4d, in: %b, out_bin2gray: %b, out_bin2gray: %b,
39              ↪ match %b", $time, in, out_bin2gray, out_gray2bin, match);
40          #2;
41      end
42  end
43
44  initial begin
45      #1
46      forever begin
47          if(!match)
48              fail = 1;
49          #2;
50      end
51  end
52 endmodule
```

Part (b):

 

Problem 5: Implementing an Adder/Subtractor [7 pts.]

Subtraction, for instance $A-B$, can be implemented as $A+(-B)$. Therefore, any adder circuit can be converted to a subtractor by converting B to its 2's complement, defined as $\sim B+1$.

Write a *structural* Verilog module as follows: `module add_sub(A, B, R, add)` which produces $A+B$ if “add” is equal to 1 and produces $A-B$ otherwise.

(hint, for an adder, the carry-in to the first stage provides an easy way to add 1 to the final result).

Solution:

Verilog Modules:

```

1  module full_adder (
2      input a,
3      input b,
4      input carry_in,
5      output sum,
6      output carry_out
7  );
8
9      wire aXORb;
10     xor(aXORb, a, b);
11     xor(sum, aXORb, carry_in);
12
13     wire carryAB;
14     and(carryAB, a, b);
15
16     wire carryCIN;
17     and(carryCIN, aXORb, carry_in);
18
19     or(carry_out, carryAB, carryCIN);
20 endmodule
21

```

```

22 module structural_adder_subtractor
23     #(parameter N=14)(
24         input [N-1:0] A,
25         input [N-1:0] B,
26         output [N-1:0] R,
27         input add);
28
29     wire [N:0] carry;
30     assign carry[0] = ~add;
31
32     wire [N-1:0] second_operand;
33
34     genvar i;
35     generate
36         for(i = 0; i<N; i = i + 1) begin:adder_chain
37             xor(second_operand[i], B[i], ~add);
38
39             full_adder fa(.a(A[i]),
40                         .b(second_operand[i]),
41                         .carry_in(carry[i]),
42                         .sum(R[i]),
43                         .carry_out(carry[i+1]));
44         end
45     endgenerate
46
47 endmodule

```

Problem 6: 251A only — *Optional Challenge Question for 151 [5,5 pts.]*

- Write the Verilog description for a LUT3 (3 input LUT with 1 output) module. It will have 4 inputs. The first three are the single bit LUT inputs: a, b, c. The last input, F, specifies the LUT function as an 8 bit number. For instance if $F=8'h01$, the LUT implements an AND gate. If $F = 8'h7F$, it implements an OR gate.
- Using only the LUT3 module you created, write a LUT4 module using *structural* Verilog.

Solution:

Verilog Modules:

```

1 module lut3(
2     input a,
3     input b,
4     input c,
5     input [7:0] F,

```

```

6   output out);
7
8   wire [2:0] index;
9   assign index = {~c, ~b, ~a};
10
11  //The index of F is the opposite of that of the index wire
12  //The LSB of F is the case when a, b, and c are all true
13  //The MSB of F is the case when a, b, and c are all false
14  //This can be addressed by inverting the inputs
15
16  //Slice based on the index (this synthesizable - at least in Vivado -
17  ↪ infers a bit selector with index port -> becomes luts and muxes)
18  assign out = F[index];
19  endmodule
20
21  module lut4(
22      input a,
23      input b,
24      input c,
25      input d,
26      input [15:0] F,
27      output out);
28      //Assuming d is the MSB of the input
29
30      //=== Build a Tree with LUT3s ===
31      wire d_true_lut_out;
32      wire d_false_lut_out;
33
34      //The lower half of F is when d is true. Within that half, the LSB is
35      ↪ when a, b, c are true
36      lut3 f_true_lut(.a(a), .b(b), .c(c), .F(F[7:0]), .out(d_true_lut_out));
37
38      //The upper half of F is when d is false. Within that half, the LSB is
39      ↪ when a, b, c are true
40      lut3 f_false_lut(.a(a), .b(b), .c(c), .F(F[15:8]),
41      ↪ .out(d_false_lut_out));
42
43      //Use a LUT3 as a mux
44      //With LSB = All false, F would be 8'b11100100. With LSB = all true, F
45      ↪ is 8'b00100111
46      lut3 mux_lut(.a(d), .b(d_false_lut_out), .c(d_true_lut_out),
47      ↪ .F(8'b00100111), .out(out));
48  endmodule

```

Appendix

Solution:

Problem 2: Example Testbench:

```
1  `timescale 1ns/1ns
2  module circuit2_tester();
3      reg [3:0] in;
4      wire [1:0] out_orig;
5      wire [1:0] out_case;
6
7      wire match;
8      reg fail;
9
10     initial in = 0;
11     initial fail = 0;
12
13     //Instantiate the DUTs
14     circuit2_case dut(.a(in), .y(out_case));
15     circuit2_orig orig(.a(in), .y(out_orig));
16
17     assign match = out_orig == out_case;
18
19     //Increment Input Every 2 Steps (Check Between Increments)
20     always #2 begin
21         in = in + 4'd1;
22     end
23
24     initial begin
25         $dumpfile("dump.vcd"); //Setup file dump (for waveform viewer)
26         $dumpvars; //Dump signals to dumpfile
27
28         #33
29         if(fail)
30             $display("Test FAIL");
31         else
32             $display("Test PASS");
33         $finish();
34     end
35
36     //Print
37     initial begin
38         #1
39         forever begin
40             $strobe("time: %4d, in: %b, out_orig: %b, out_case: %b, match %b",
41                 ↪ $time, in, out_orig, out_case, match);
42             #2;
43         end
44     end
```

```
43     end
44
45     //Check for Failure 1 Step After Input Change
46     initial begin
47         #1
48         forever begin
49             if(!match)
50                 fail = 1;
51             #2;
52         end
53     end
54
55 endmodule
```

Problem 3: Example Testbench:

```
1  `timescale 1ns/1ns
2  module decoder_tester();
3      reg  [1:0] in;
4
5      wire x0_stru;
6      wire x1_stru;
7      wire x2_stru;
8      wire x3_stru;
9      wire [3:0] out_stru;
10
11     wire x0_behu;
12     wire x1_behu;
13     wire x2_behu;
14     wire x3_behu;
15     wire [3:0] out_behu;
16
17     reg fail;
18     wire match;
19
20     initial in = 0;
21     initial fail = 0;
22
23     assign out_stru = {x0_stru, x1_stru, x2_stru, x3_stru};
24     assign out_behu = {x0_behu, x1_behu, x2_behu, x3_behu};
25
26     //Instantiate the DUTs
27     Decoder_structural stru(.x0(x0_stru), .x1(x1_stru), .x2(x2_stru),
28     ↪ .x3(x3_stru), .a(in[1]), .b(in[0]));
29     Decoder_behavioral behu(.x0(x0_behu), .x1(x1_behu), .x2(x2_behu),
30     ↪ .x3(x3_behu), .a(in[1]), .b(in[0]));
```

```

29
30   assign match = out_stru == out_beha;
31
32   always #2 begin
33       in = in + 2'd1;
34   end
35
36   initial begin
37       $dumpfile("dump.vcd"); //Setup file dump (for waveform viewer)
38       $dumpvars; //Dump signals to dumpfile
39
40       #9
41       if(fail)
42           $display("Test FAIL");
43       else
44           $display("Test PASS");
45       $finish();
46   end
47
48   initial begin
49       #1
50       forever begin
51           $strobe("time: %4d, in: %b, out_stru: %b, out_beha: %b, match %b",
52               ↪ $time, in, out_stru, out_beha, match);
53       end
54   end
55
56   initial begin
57       #1
58       forever begin
59           if(!match)
60               fail = 1;
61       end
62   end
63 endmodule
64

```

Problem 5: Example Testbench:

```

1  module behavioral_adder_subtractor
2      #(parameter N=14)(
3      input  [N:0] A,
4      input  [N:0] B,
5      output [N:0] R,
6      input add);

```

```
7
8   assign R = add ? A+B : A-B;
9
10  endmodule
11
12  `timescale 1ns/1ns
13  module adder_tester();
14    reg [6:0] in;
15
16    wire signed [2:0] out_stru;
17    wire signed [2:0] out_beha;
18
19    reg fail;
20    wire match;
21
22    initial in = 0;
23    initial fail = 0;
24
25    wire signed [2:0] op_a;
26    wire signed [2:0] op_b;
27    wire op_add;
28    assign op_a = in[2:0];
29    assign op_b = in[5:3];
30    assign op_add = in[6];
31
32
33    //Instantiate the DUTs
34    structural_adder_subtractor #(.N(3)) stru (.A(op_a), .B(op_b),
35    ↪ .R(out_stru), .add(op_add));
36    behavioral_adder_subtractor #(.N(3)) beha (.A(op_a), .B(op_b),
37    ↪ .R(out_beha), .add(op_add));
38
39    assign match = out_stru == out_beha;
40
41    always #2 begin
42      in = in + 2'd1;
43    end
44
45    initial begin
46      $dumpfile("dump.vcd"); //Setup file dump (for waveform viewer)
47      $dumpvars; //Dump signals to dumpfile
48
49      #257
50      if(fail)
51        $display("Test FAIL");
52      else
53        $display("Test PASS");
```



```
52     $finish();
53 end
54
55 initial begin
56     #1
57     forever begin
58         $strobe("time: %4d, a: %2d, b: %2d, add: %b, out_stru: %2d,
59             ↪ out_beha: %2d, match %b", $time, op_a, op_b, op_add, out_stru,
60             ↪ out_beha, match);
61     #2;
62     end
63 end
64
65 initial begin
66     #1
67     forever begin
68         if(!match)
69             fail = 1;
70     #2;
71     end
72 end
73 endmodule
```

Problem 6: Example Testbench:

```
1  `timescale 1ns/1ns
2  module lut4_tester();
3      reg [5:0] in;
4
5      wire out_lut4;
6
7      reg fail;
8      wire match;
9
10     initial in = 0;
11     initial fail = 0;
12
13     wire op_a;
14     wire op_b;
15     wire op_c;
16     wire op_d;
17     wire [1:0] func_ind;
18
19     assign op_a = in[0];
20     assign op_b = in[1];
21     assign op_c = in[2];
```

```

22  assign op_d = in[3];
23  assign func_ind = in[5:4];
24
25  //Set the function to test (we'll test 4 different functions)
26  reg [15:0] func;
27  initial func = 0;
28  always @(*) begin
29      case(func_ind)
30          2'd0: func = 16'h7FFF; //OR all
31          2'd1: func = 16'h0001; //AND all
32          2'd2: func = 16'b0010001000000011; //dcb+(!d)b(!a)
33          2'd3: func = 16'b0100000000000000; //(!d)(!c)(!b)a
34          default: func = 16'h0000;
35      endcase
36  end
37
38  //Test against static
39  reg out_static;
40  initial out_static = 0;
41  always @(*) begin
42      case(func_ind)
43          2'd0: out_static = op_a | op_b | op_c | op_d; //OR all
44          2'd1: out_static = op_a & op_b & op_c & op_d; //AND all
45          2'd2: out_static = (op_d & op_c & op_b) | ((~op_d) & op_b &
46              ↪ (~op_a)); //dcb+(!d)b(!a)
47          2'd3: out_static = (~op_d) & (~op_c) & (~op_b) & op_a;
48              ↪ //(!d)(!c)(!b)a
49          default: out_static = 16'h0000;
50      endcase
51  end
52
53  //Instantiate the DUTs
54  lut4 lut(.a(op_a), .b(op_b), .c(op_c), .d(op_d), .F(func),
55      ↪ .out(out_lut4));
56
57  assign match = out_lut4 == out_static;
58
59  always #2 begin
60      in = in + 6'd1;
61  end
62
63  initial begin
64      $dumpfile("dump.vcd"); //Setup file dump (for waveform viewer)
65      $dumpvars; //Dump signals to dumpfile
66
67      #129
68      if(fail)

```

```
66     $display("Test FAIL");
67     else
68     $display("Test PASS");
69     $finish();
70 end
71
72 initial begin
73     #1
74     forever begin
75     $strobe("time: %4d, a: %b, b: %b, c: %b, d: %b, func_ind: %d, func:
76     ↪ %b, out_lut4: %b, out_static: %b, match %b", $time, op_a, op_b,
77     ↪ op_c, op_d, func_ind, func, out_lut4, out_static, match);
78     #2;
79     end
80 end
81
82 initial begin
83     #1
84     forever begin
85     if(!match)
86     fail = 1;
87     #2;
88     end
89 end
90 endmodule
```