

EECS 151/251A Homework 4

Due Monday, Feb 25th, 2019

Problem 1: Correct JohnW's lecture mistake! [5 pts]

For the "BCD Incrementer Example" presented in lecture 6, derive the minimized logic equations for the outputs, expressed in sum-of-products (SOP) form.

Solution:

From the truth tables for w , x , y and z :

		w			
		ab	00	01	11
cd	00	0	0	x	1
	01	0	0	x	0
	11	0	1	x	x
	10	0	0	x	x

		x			
		ab	00	01	11
cd	00	0	1	x	0
	01	0	1	x	0
	11	1	0	x	x
	10	0	1	x	x

		y			
		ab	00	01	11
cd	00	0	0	x	0
	01	1	1	x	0
	11	0	0	x	x
	10	1	1	x	x

		z			
		ab	00	01	11
cd	00	1	1	x	1
	01	0	0	x	0
	11	0	0	x	x
	10	1	1	x	x

$$w = bcd + a\bar{d}$$

$$x = b\bar{c} + b\bar{d} + \bar{b}cd$$


$$y = \bar{a}\bar{c}d + c\bar{d}$$

$$z = \bar{d}$$


Problem 2: Bubble Pushing [14 pts]

Two-level OR/AND circuits can be implemented as two-level NOR/NOR circuits.

 - (a) For the example below, using the "bubble pushing" technique, show the series of steps that you would take to convert the circuit to use only NORs. [4pts]




 - (b) Now convert the OR/AND circuit to use only NANDs (and possibly inverters). [5pts]
 (c) Convert the following circuit to all NANDs (and possibly inverters). [5pts]




Solution:


(a) :

 

(b) :

 

(c) :

 

Problem 3: SOP, POS, and Minimum Expressions [9pts]

Consider the function f defined with the truth-table below:

x_0	x_1	x_2	x_3	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

- (a) Write out the sum-of-products (SOP) and product-of-sums (POS) canonical forms. [3pts]
 (b) Derive the minimized expressions for f and for f' in SOP and POS forms (four answers required here). Hint: use a K-map. [6pts]

Solution:


(a) *Sum-of-products (SOP):*

$$f = \overline{x_0} \overline{x_1} \overline{x_2} x_3 + \overline{x_0} \overline{x_1} x_2 x_3 + x_0 \overline{x_1} \overline{x_2} x_3 + x_0 \overline{x_1} x_2 x_3 + x_0 x_1 \overline{x_2} \overline{x_3} + x_0 x_1 \overline{x_2} x_3 + x_0 x_1 x_2 \overline{x_3} + x_0 x_1 x_2 x_3$$

Product-of-sums (POS):

$$f = (x_0 + x_1 + x_2 + x_3)(x_0 + x_1 + \overline{x_2} + x_3)(x_0 + \overline{x_1} + x_2 + x_3)(x_0 + \overline{x_1} + x_2 + \overline{x_3})(x_0 + \overline{x_1} + \overline{x_2} + x_3)(x_0 + \overline{x_1} + \overline{x_2} + \overline{x_3})(\overline{x_0} + x_1 + x_2 + x_3)(\overline{x_0} + x_1 + \overline{x_2} + x_3)$$

 (b) Build a Karnaugh map for f and \overline{f} :



From the map for f we can derive:

$$f = x_0x_1 + \bar{x}_1x_3 \quad (\text{SOP, solid line})$$

$$f = (x_0 + \bar{x}_1)(x_1 + x_3) \quad (\text{POS, dotted line})$$

And from the map for \bar{f} we can derive:

$$\bar{f} = \bar{x}_1\bar{x}_3 + \bar{x}_0x_1 \quad (\text{SOP, solid line})$$

$$\bar{f} = (\bar{x}_0 + \bar{x}_1)(x_1 + \bar{x}_3) \quad (\text{POS, dotted line})$$

Notice that the SOP form for f and the POS form for \bar{f} are equivalent under De Morgan's law - likewise the POS form for f and the SOP form for \bar{f} .

Problem 4: Simplification with Boolean Algebra [6pts]

For the following function g defined with the truth-table below, use algebraic manipulation to derive its minimized form.

x_0	x_1	x_2	g
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Solution:

The algebraic derivation starts by reading the SOP form from the truth table and then proceeds as follows:

$$\begin{aligned}
 g &= \overline{x_0} \overline{x_1} \overline{x_2} + \overline{x_0} x_1 \overline{x_2} + x_0 x_1 \overline{x_2} \\
 &= \overline{x_0} x_1 \overline{x_2} + \overline{x_0} \overline{x_1} \overline{x_2} + \overline{x_0} x_1 \overline{x_2} + x_0 x_2 \overline{x_2} \\
 &= \overline{x_0} \overline{x_2} (x_1 + \overline{x_1}) + x_1 \overline{x_2} (x_0 + \overline{x_0}) \\
 &= \overline{x_0} \overline{x_2} (1) + x_1 \overline{x_2} (1) \\
 &= \overline{x_0} \overline{x_2} + x_1 \overline{x_2}
 \end{aligned}$$

We can confirm this by looking at the Karnaugh-map:

g

	$x_0 x_1$	00	01	11	10
x_2	0	1	1	1	0
1		0	0	0	0

... from which the simplified expression is also:

$$g = \overline{x_0} \overline{x_2} + x_1 \overline{x_2}$$

Problem 5: Building a Better Saturating Incrementer [10pts]

Consider the design of a 3-bit binary unsigned incrementer with saturating output. Saturating in this case means that if the input is the maximum representable value (in this case 111_2), then it is passed through unchanged. In Verilog we might try defining the incrementer with:

```
assign y = (x == 3'b111) ? 3'b111 : x + 1;
```

A naive logic synthesizer might turn this into a comparator, a multiplexor, and an adder. Your job is to derive a simpler circuit by hand.

Show your derivation of logic equations for the 3-output bits, $y[0]$, $y[1]$, $y[2]$.

Solution:

First derive an expression for g as a function of the current value x :

x_2	x_1	x_0	y_2	y_1	y_0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	1	1	1

Then derive simplified expressions for each signal in y using a Karnaugh-map (or otherwise):

y_2 :

		y_2			
		x_2x_1 00	01	11	10
x_0	0	0	0	1	1
	1	0	1	1	1

$$y_2 = x_0x_1 + x_2$$

y_1 :

		y_1			
		x_2x_1 00	01	11	10
x_0	0	0	1	1	0
	1	1	0	1	1

$$y_1 = \overline{x_0}x_1 + x_2x_1 + x_0\overline{x_1}$$

 y_0 :

		y_0			
		x_2x_1 00	01	11	10
x_0	0	1	1	1	1
	1	0	0	1	0

$$y_0 = \overline{x_0} + x_2x_1$$

Problem 6: Writing a FSM in Verilog [8pts]

Write the behavior Verilog description for the Combinational Lock FSM example presented in lecture 7.

Solution:

```

module CombinationalLock(clk, reset, code, enter, open, error);
    input clk, reset;
    input [7:0] code; // Assume code is 8 bits.
    input enter;

```



```
output open, error;

parameter START = 3'd0;
parameter OK1   = 3'd1;
parameter OK2   = 3'd2;
parameter BAD1  = 3'd3;
parameter BAD2  = 3'd4;

// Let's pretend that the code is '12'.
parameter CODE1 = 8'd1;
parameter CODE2 = 8'd2;

reg open;
reg error;
reg [2:0] present_state, next_state;

always @(posedge clk)
    if (reset) present_state <= START;
    else      present_state <= next_state;

always @(present_state or enter)
    case (present_state)
        START: begin
            open = 1'b0;
            error = 1'b0;
            if (enter == 1'b0)    next_state = START;
            else if (code == CODE1) next_state = OK1;
            else                   next_state = BAD1;
        end
        OK1: begin
            open = 1'b0;
            error = 1'b0;
            if (enter == 1'b0)    next_state = OK1;
            else if (code == CODE2) next_state = OK2;
            else                   next_state = BAD2;
        end
        OK2: begin
            open = 1'b1;
            error = 1'b0;
            next_state = START;
        end
        BAD1: begin
            open = 1'b0;
            error = 1'b0;
            if (enter == 1'b1)    next_state = BAD2;
            else                   next_state = BAD1;
        end
    end
```

```

BAD2: begin
  open = 1'b0;
  error = 1'b1;
  next_state = BAD2;
end
default: begin
  open = 1'b0;
  error = 1'b0;
  next_state = START;
end
endcase
endmodule

```


Problem 7: Designing an FSM [11pts]

Consider the design of a Moore-style FSM with a 1-bit input (x), and a 1-bit output (y). The FSM accepts inputs one bit at a time and outputs a 0 until it sees the sequence 0101 (with no other bit values in between). After seeing the second 1 in the sequence it outputs a 1 and then starts over.

- Draw the state transition diagram. Label all nodes and arcs. [3pts]
- Derive the next state logic and the output logic equations. [8pts]

Solution:

(a) :

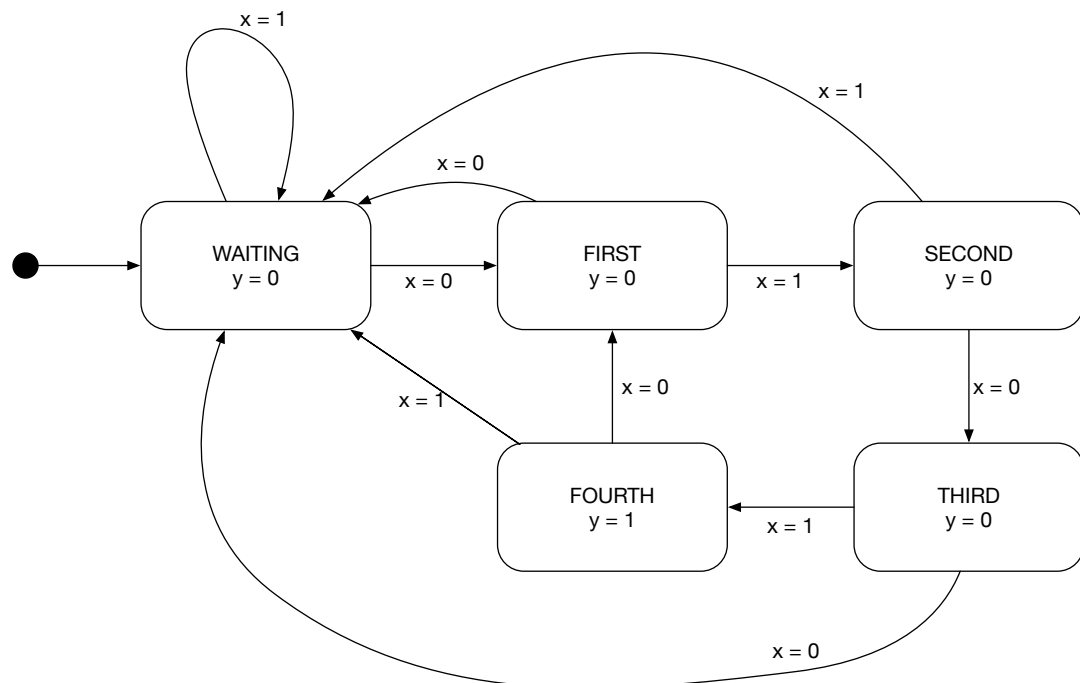

(b) One way is to use one-hot encoding and 5 bits to express states:

$$S_{WAITING} = 00001$$

$$S_{FIRST} = 00010$$

$$S_{SECOND} = 00100$$

$$S_{THIRD} = 01000$$

$$S_{FOURTH} = 10000$$

Then each of the 5 bits of the next state (n) are derived from the current state c and input x as follows, also assuming that there is a reset r :

$$\begin{aligned} y &= c_4 \\ n_0 &= r + c_1\bar{x} + c_2x + c_3\bar{x} + c_4x + c_0 \\ &= r + x(c_2 + c_4 + c_0) + \bar{x}(c_1 + c_3) \\ n_1 &= \bar{r}c_0\bar{x} \\ n_2 &= \bar{r}c_1x \\ n_3 &= \bar{r}c_2\bar{x} \\ n_4 &= \bar{r}c_3x \end{aligned}$$

Another way is to express states as integers, S_0 through S_4 , using only 3 bits of state.

$$S_0 = 000$$

$$S_1 = 001$$

$$S_2 = 010$$

$$S_3 = 011$$


$$S_4 = 100$$

You can then use Karnaugh-maps to derive simplified expressions for each bit of the next state n from the current state c and input x in the same way as was done for problem 5.

$$\begin{aligned} y &= n_2\bar{n}_1\bar{n}_0 \\ n_2 &= c_1c_0x \\ n_1 &= \bar{c}_1c_0x + c_1\bar{c}_0\bar{x} \\ n_0 &= \bar{c}_0\bar{x} + \bar{x}_1\bar{x} \end{aligned}$$

 Problem 8: Implementing an FSM [13pts]

Consider the state transition diagram shown below:



- (a) Write the Verilog behavior description for the corresponding circuit. [5pts]
- (b) Draw the circuit diagram for one-hot encoded implementation. (You may assume that flip-flops have both "set" and "reset" inputs, but you must label which one you would use for each flip-flop.) [8pts]

Solution:

```

(a) module Problem(clk, rst, in, out);
    input clk, rst;
    input in;
    output out;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    parameter S3 = 2'b11;

    reg out;
    reg [1:0] present_state, next_state;

    always @(posedge clk)
        if (rst) present_state <= S0;
        else present_state <= next_state;


    always @(present_state or in)
        case (present_state)
            S0: begin
                out = 1'b0;
  
```

```

    if (in == 1'b1) next_state = S1;
    else             next_state = S3;
end
S1: begin
    out = 1'b1;
    if (in == 1'b1) next_state = S3;
    else             next_state = S2;
end
S2: begin
    out = 1'b1;
    if (in == 1'b1) next_state = S2;
    else             next_state = S0;
end
S3: begin
    out = 1'b0;
    if (in == 1'b1) next_state = S2;
    else             next_state = S0;
end
    // No 'default' case needed.
endcase
endmodule


```

(b) :

 

 Problem 9: Converting from Mealy to Moore Style [6pts]

Convert the Mealy-style state transition diagram to a Moore-style.



Solution:

