



**EECS151/251A**  
**Fall 2019**  
**Digital Design and**  
**Integrated Circuits**

Instructors:  
John Wawrzynek

**Lecture 20:**  
**Adders**

# Outline




- ❑ *“tricks with trees”*
- ❑ *Adder review, subtraction, carry-select*
- ❑ *Carry-lookahead*
- ❑ *Bit-serial addition, summary*




*Tricks with Trees*

# Reductions with Trees

 


*If each node (operator) is  $k$ -ary instead of binary, what is the delay?*

# Trees for optimization

 

$$T = O(N)$$
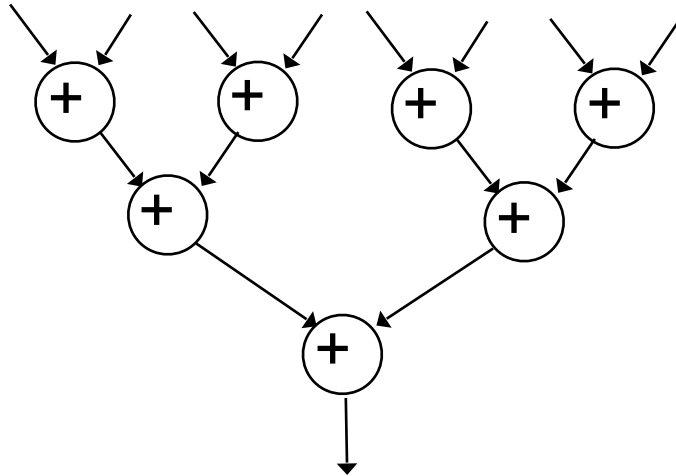
$$(((((((X_0 + X_1) + X_2) + X_3) + X_4) + X_5) + X_6) + X_7)$$




$$T = O(\log N)$$

$$((X_0 + X_1) + (X_2 + X_3)) + ((X_4 + X_5) + (X_6 + X_7))$$

- What property of “+” are we exploiting?
- Other associate operators? Boolean operations? Division? Min/Max?
 
# Parallel Prefix, or "Scan"

- If "+" is an associative operator, and  $x_0, \dots, x_{p-1}$  are input data then parallel prefix operation computes:  $y_j = x_0 + x_1 + \dots + x_j$  for  $j=0, 1, \dots, p-1$





*Adder review,  
subtraction, carry-select*

# 4-bit Adder Example

- Motivate the adder circuit design by hand addition:

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 c \ r_3 \ r_2 \ r_1 \ r_0
 \end{array}$$

- Add  $a_0$  and  $b_0$  as follows:

a	b	r	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

*carry to next stage*

$$r = a \text{ XOR } b = a \oplus b$$

$$c = a \text{ AND } b = ab$$

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 c \ r_3 \ r_2 \ r_1 \ r_0
 \end{array}$$

- Add  $a_1$  and  $b_1$  as follows:

$c_i$	a	b	r	$co$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$r = a \oplus b \oplus c_i$$

$$co = ab + ac_i + bc_i$$



# Algebraic Proof of Carry Simplification

$$\begin{aligned} \text{Cout} &= a'bc + ab'c + abc' + abc \\ &= a'bc + ab'c + abc' + abc + abc \\ &= a'bc + abc + ab'c + abc' + abc \\ &= (a' + a)bc + ab'c + abc' + abc \\ &= (1)bc + ab'c + abc' + abc \\ &= bc + ab'c + abc' + abc + abc \\ &= bc + ab'c + abc + abc' + abc \\ &= bc + a(b' + b)c + abc' + abc \\ &= bc + a(1)c + abc' + abc \\ &= bc + ac + ab(c' + c) \\ &= bc + ac + ab(1) \\ &= bc + ac + ab \end{aligned}$$

	ab			
c	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$\text{cout} = ab + bc + ac$$

# 4-bit Adder Example

## Gate Representation of FA-cell




$$r_i = a_i \oplus b_i \oplus c_{in}$$

$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in}$$

- Alternative Implementation (with 2-input gates):

$$r_i = (a_i \oplus b_i) \oplus c_{in}$$
   
$$c_{out} = c_{in}(a_i + b_i) + a_i b_i$$




# Carry-ripple Adder Revisited
 
## □ Each cell:


$$r_i = a_i \oplus b_i \oplus c_{in}$$

$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in} = c_{in}(a_i + b_i) + a_i b_i$$



*“Full adder cell”*

## □ 4-bit adder:

 


## □ What about subtraction?

# Subtractor/Adder

$$A - B = A + (-B)$$


How do we form  $-B$ ?

1. complement  $B$
2. add 1

 
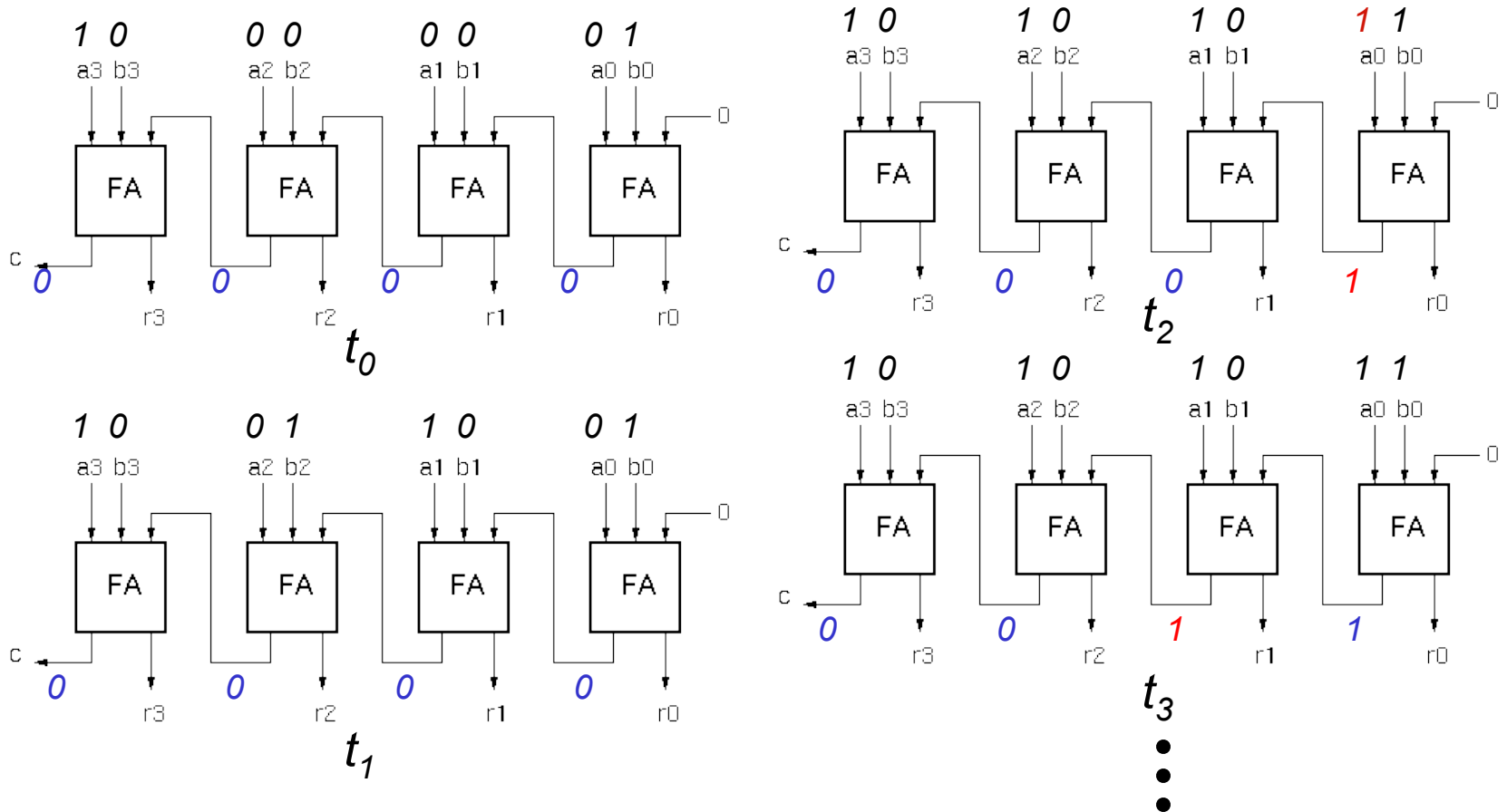
# Delay in Ripple Adders


- Ripple delay amount is a function of the data inputs:



- However, we usually only consider the worst case delay on the critical path. There is always at least one set of input data that exposes the worst case delay.

# Adders (cont.)

## Ripple Adder

 


*Ripple adder is inherently slow because, in worst case  $s_7$  must wait for  $c_7$  which must wait for  $c_6$  ...*

$$T \propto n, \text{ Cost} \propto n$$

*How do we make it faster, perhaps with more cost?*

# Carry Select Adder

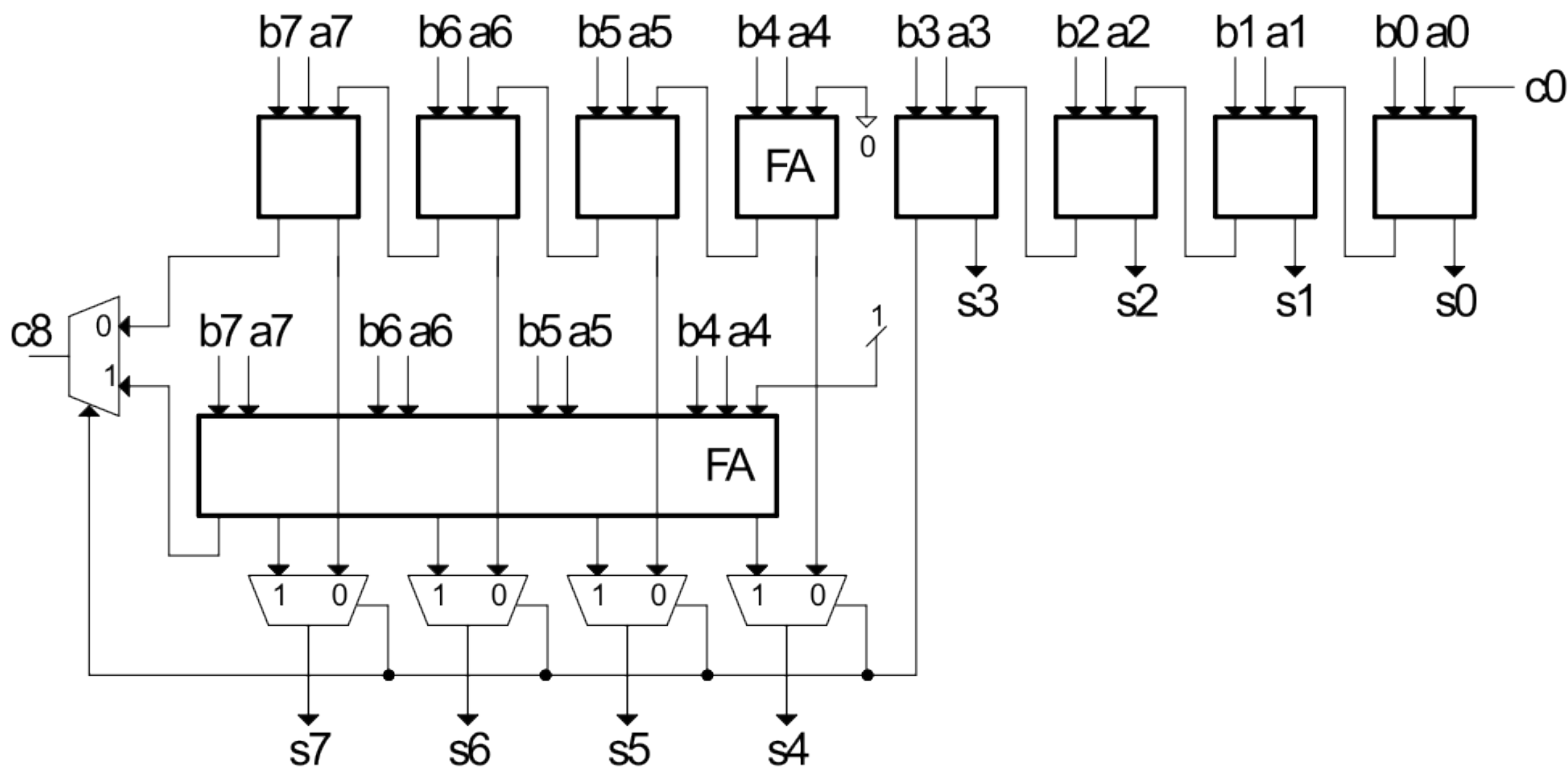


$$T = T_{\text{ripple\_adder}} / 2 + T_{\text{MUX}}$$

$$\text{COST} = 1.5 * \text{COST}_{\text{ripple\_adder}} + (n/2 + 1) * \text{COST}_{\text{MUX}}$$

# Carry Select Adder
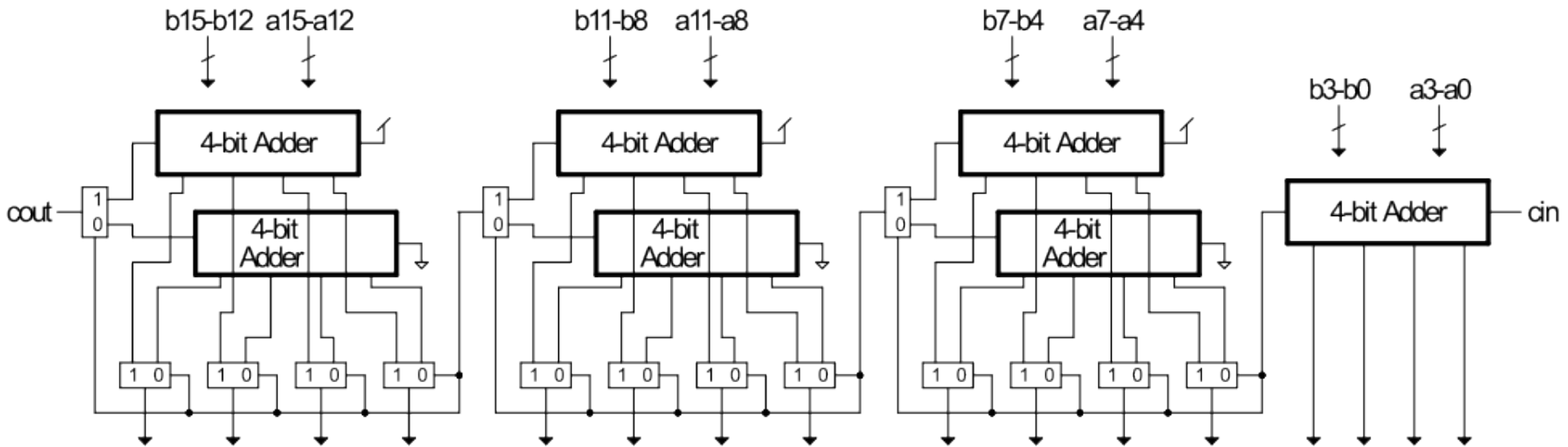
## Extending Carry-select to multiple blocks



## What is the optimal # of blocks and # of bits/block?


- If blocks too small delay dominated by total mux delay
- If blocks too large delay dominated by adder ripple delay

$\sqrt{N}$  stages of  $\sqrt{N}$  bits

$T \propto \text{sqrt}(N)$ ,  
 $\text{Cost} \approx 2 * \text{ripple} + \text{muxes}$



# Carry Select Adder

 

- Compare to ripple adder delay:

$$T_{total} = 2 \sqrt{N} T_{FA} - T_{FA}, \text{ assuming } T_{FA} = T_{MUX}$$

$$\text{For ripple adder } T_{total} = N T_{FA}$$

“cross-over” at  $N=3$ , Carry select faster for any value of  $N > 3$ .

- Is  $\sqrt{N}$  really the optimum?

- From right to left increase size of each block to better match delays
- Ex: 64-bit adder, use block sizes [12 11 10 9 8 7 7], the exact answer depends on the relative delay of mux and FA





*Carry-lookahead and  
Parallel Prefix*

# Adders with Delay $\propto \log(n)$

Can carry generation be made to be a kind of “reduction operation”?

Lowest delay for a reduction is a balanced tree.

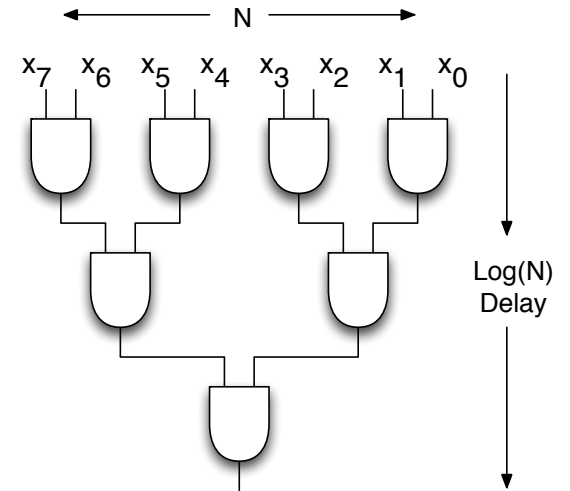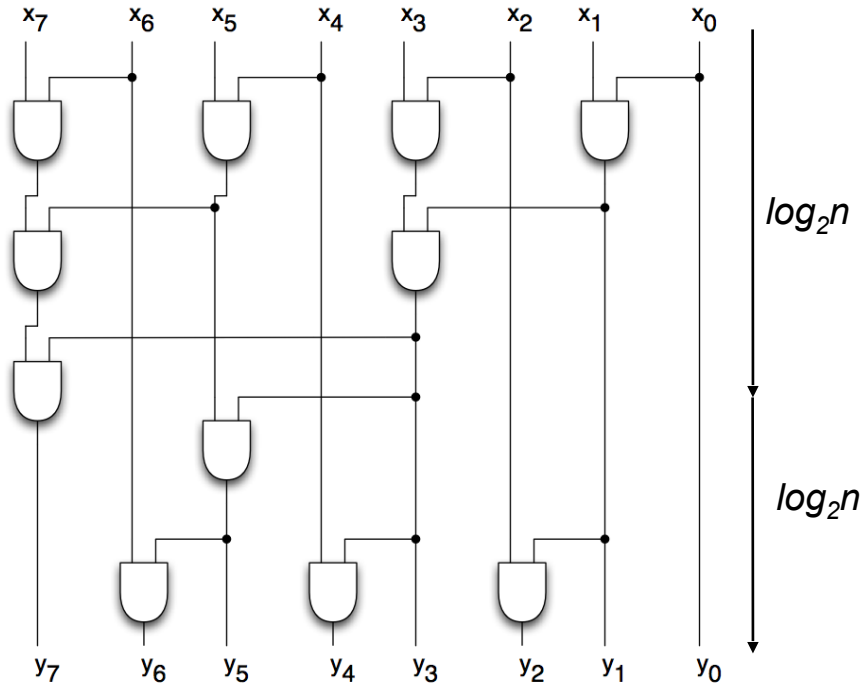- *But in this case all intermediate values are required.*
- *One way is to use “Parallel Prefix” to compute the carries.*



$$y_0 = x_0$$

$$y_1 = x_0 x_1$$

$$y_2 = x_0 x_1 x_2$$

# Carry Look-ahead Adders

- How do we arrange carry generation to be associative?
- Reformulate basic adder stage:


$a$	$b$	$c_i$	$c_{i+1}$	$s$	
0	0	0	0	0	carry "kill"
0	0	1	0	1	$k_i = a_i' b_i'$
0	1	0	0	1	
0	1	1	1	0	carry "propagate"
1	0	0	0	1	$p_i = a_i \oplus b_i$
1	0	1	1	0	
1	1	0	1	0	carry "generate"
1	1	1	1	1	$g_i = a_i b_i$

$$c_{i+1} = g_i + p_i c_i$$
$$s_i = p_i \oplus c_i$$
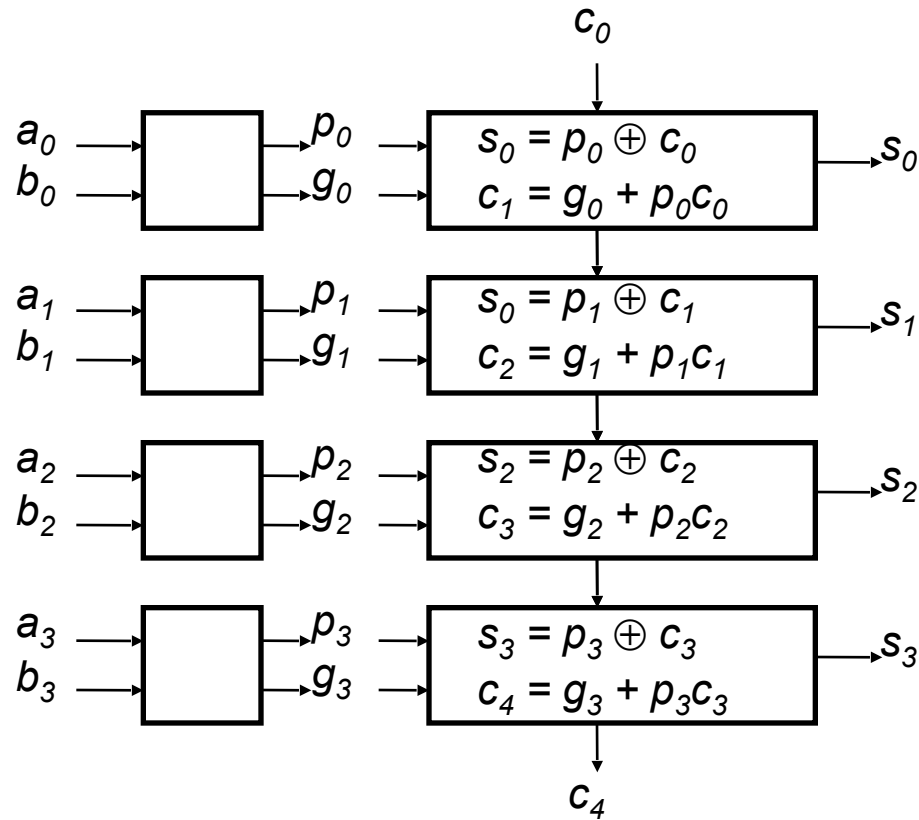
# Carry Look-ahead Adders

- Ripple adder using p and g signals:


$$p_i = a_i \oplus b_i$$
$$g_i = a_i b_i$$



- So far, no advantage over ripple adder:  $T \propto N$
 
# Carry Look-ahead Adders

- “Group” propagate and generate signals:




- P true if the group as a whole propagates a carry to  $c_{out}$
- G true if the group as a whole generates a carry

$$c_{out} = G + Pc_{in}$$

- Group P and G can be generated hierarchically.

# Carry Look-ahead Adders


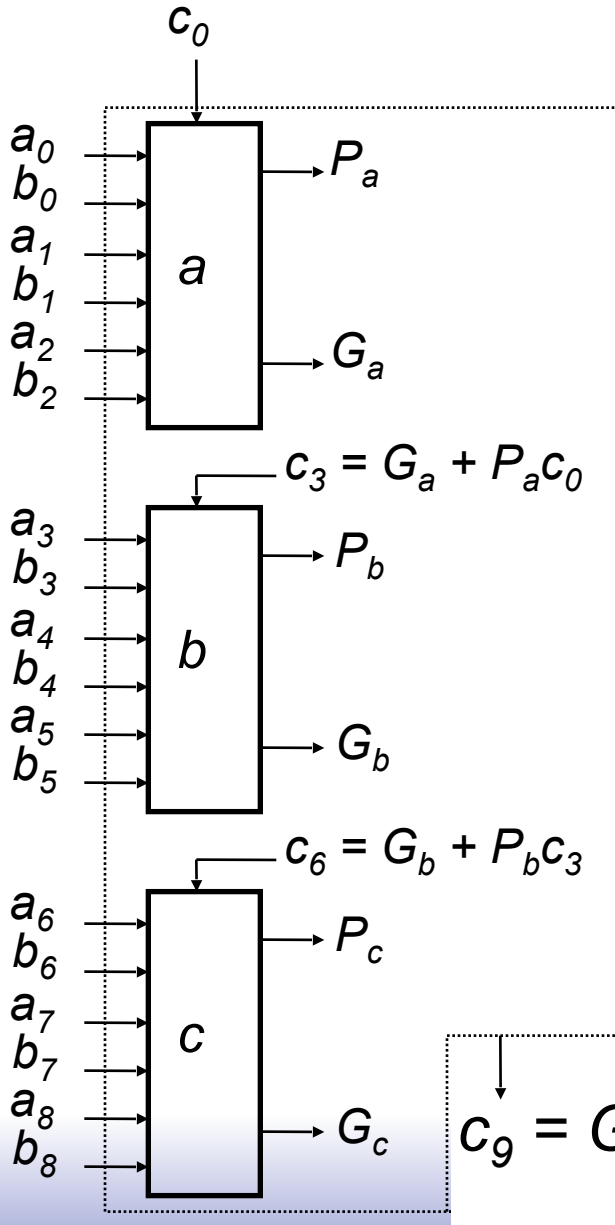


9-bit Example of hierarchically generated  $P$  and  $G$  signals:


$$P = P_a P_b P_c$$

$$G = G_c + P_c G_b + P_b P_c G_a$$


$$c_9 = G + P c_0$$

  


# 8-bit Carry Look-ahead Adder

 



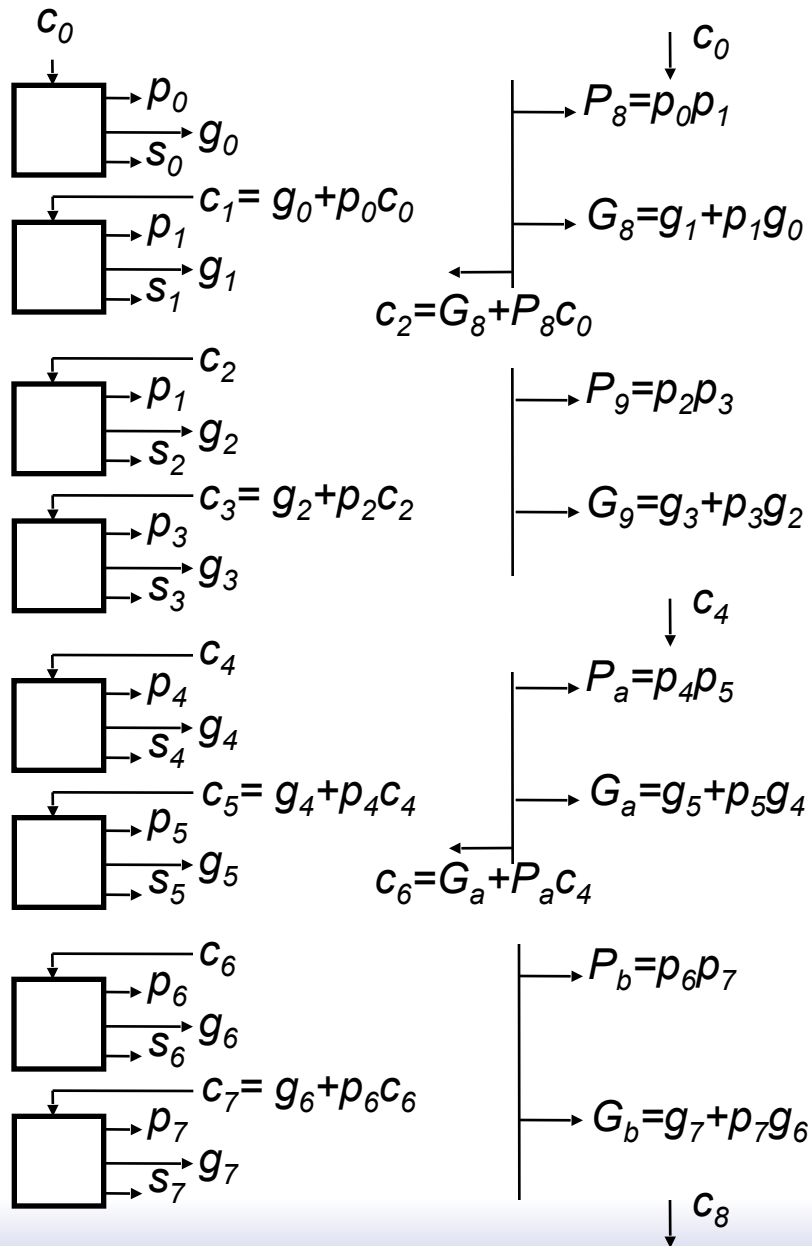
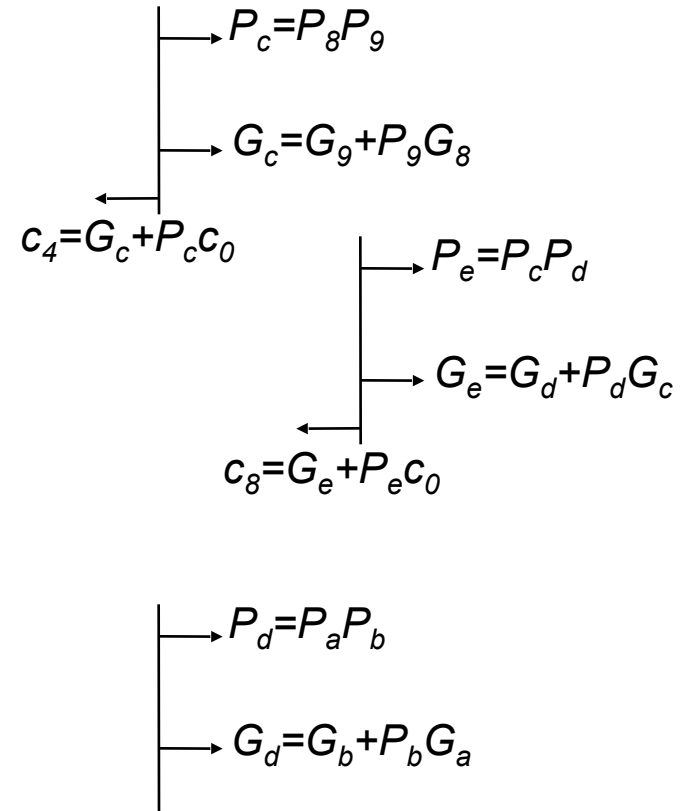
## 8-bit Carry Look-ahead Adder with 2-input gates.



# Parallel-Prefix Carry Look-ahead Adders

- Generate all carries directly (no grouping):

$$c_0 = 0$$

$$c_1 = g_0 + p_0 c_0 = g_0$$


$$c_2 = g_1 + p_1 c_1 = g_1 + p_1 g_0$$

$$c_3 = g_2 + p_2 c_2 = g_2 + p_2 g_1 + p_1 p_2 g_0$$

$$c_4 = g_3 + p_3 c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_4 p_3 p_2 g_0$$

⋮  
⋮  
⋮



$$c_{i+1} = g_i + p_i c_i$$

 

*Binary (G, P)  
associative operator*

*Use binary (G,P) operator to form parallel prefix tree*


# Parallel Prefix Adder Example

  


$$\begin{aligned}
 G &= g_3 + g_2 p_3 + (g_1 + g_0 p_1) p_3 p_2 \\
 &= g_3 + g_2 p_3 + g_1 p_3 p_2 + g_0 p_3 p_2 p_1 \\
 &= c_4
 \end{aligned}$$

$$s_i = a_i \oplus b_i \oplus c_i = p_i \oplus c_i$$

 
# Other Parallel Prefix Adder Architectures



 
**Kogge-Stone adder:** minimum logic depth, and full binary tree with minimum fan-out, resulting in a fast adder but with a large area



 **Ladner-Fischer adder:** minimum logic depth, large fan-out requirement up to  $n/2$



 **Brent-Kung adder:** minimum area, but high logic depth



**Han-Carlson adder:** hybrid design combining stages from the Brent-Kung and Kogge-Stone adder


# *Carry look-ahead Wrap-up*

- ❑ Adder delay  $O(\log N)$ .
- ❑ Cost?
- ❑ Can be applied with other techniques. Group P & G signals can be generated for sub-adders, but another carry propagation technique (for instance ripple) used within the group.
  - For instance on FPGA. Ripple carry up to 32 bits is fast, CLA used to extend to large adders. CLA tree quickly generates carry-in for upper blocks.



***Bit-serial Addition, Adder  
summary***

# Bit-serial Addder

 


- *A, B, and R held in shift-registers. Shift right once per clock cycle.*
- *Reset is asserted by controller.*

## □ Addition of 2 n-bit numbers:

- takes n clock cycles,
- uses 1 FF, 1 FA cell, plus registers
- the bit streams may come from or go to other circuits, therefore the registers might not be needed.
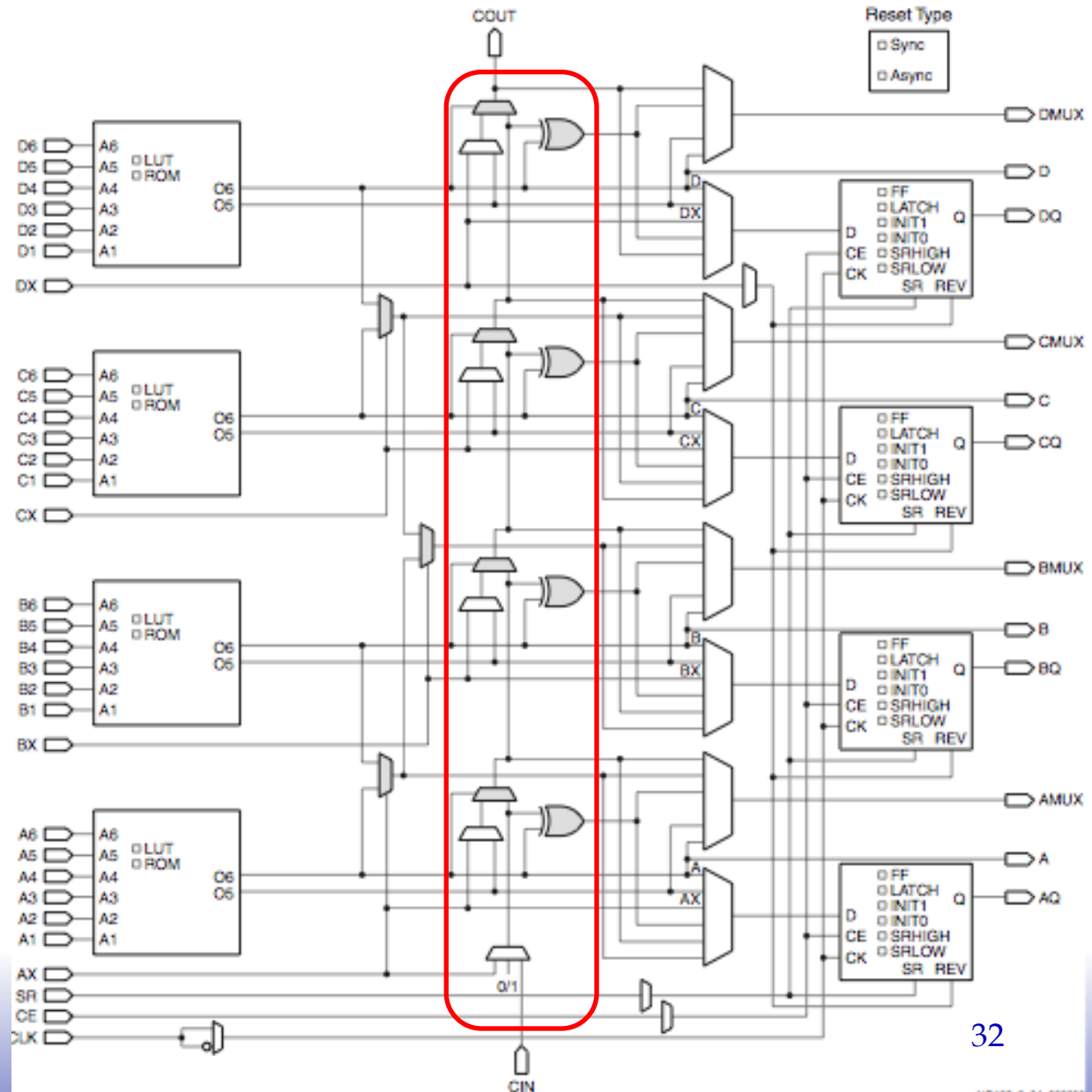
# Adders on FPGAs

- Dedicated carry logic provides fast arithmetic carry capability for high-speed arithmetic functions.
- On Virtex-5
  - Cin to Cout (per bit) delay = 40ps, versus 900ps for F to X delay.
  - 64-bit add delay = 2.5ns.





# Adder Final Words

Type	Cost	Delay
Ripple	$O(N)$	$O(N)$
Carry-select	$O(N)$	$O(\sqrt{N})$
Carry-lookahead	$O(N)$	$O(\log(N))$
Bit-serial	$O(1)$	$O(N)$

- ❑ Dynamic energy per addition for all of these is  $O(n)$ .
- ❑ “O” notation hides the constants. Watch out for this!
- ❑ The “real” cost of the carry-select is at least 2X the “real” cost of the ripple. “Real” cost of the CLA is probably at least 2X the “real” cost of the carry-select.
- ❑ The actual multiplicative constants depend on the implementation details and technology.
- ❑ FPGA and ASIC synthesis tools will try to choose the best adder architecture automatically - assuming you specify addition using the “+” operator, as in “`assign A = B + C`”