



**EECS 151/251A**  
**Spring 2019**  
**Digital Design and**  
**Integrated Circuits**

Instructor:  
John Wawrzynek

**Lecture 6**

# Outline




- *Three representations for combinational logic:*
  - *truth tables,*
  - *graphical (logic gates), and*
  - *algebraic equations*
- *Boolean Algebra*
- *Boolean Simplification*
- *Multi-level Logic, NAND/NOR, XOR*



## Representations of Combinational Logic

# Combinational Logic (CL) Defined

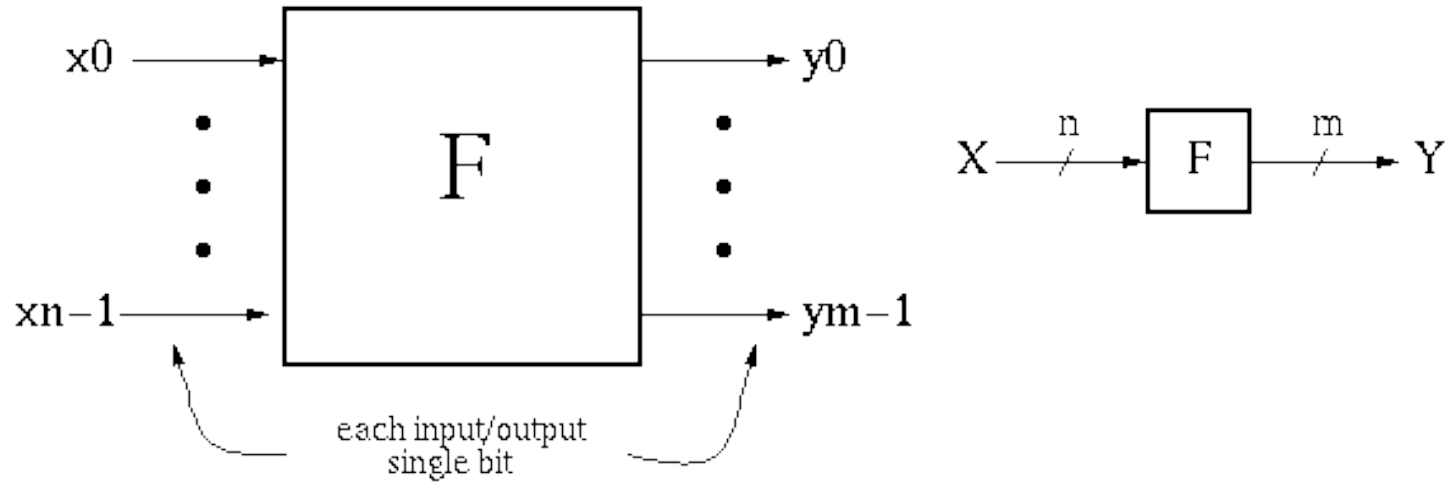


$y_i = f_i(x_0, \dots, x_{n-1})$ , where  $x, y$  are  $\{0,1\}$ .

$Y$  is a function of only  $X$ .

- If we change  $X$ ,  $Y$  will change immediately (well almost!).
  - There is an **implementation dependent** delay from  $X$  to  $Y$ .

# CL Block Example #1

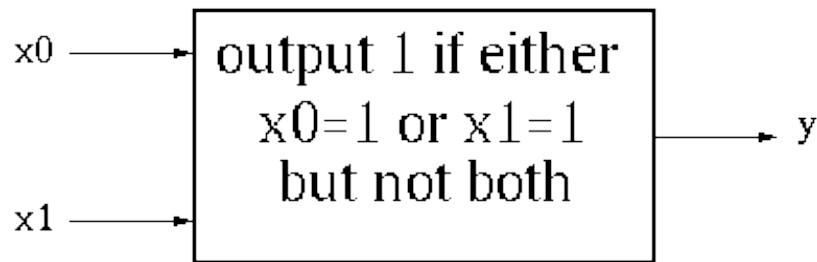


Boolean Equation:

$$y_0 = (x_0 \text{ AND not}(x_1)) \\ \text{OR } (\text{not}(x_0) \text{ AND } x_1) \\ y_0 = x_0x_1' + x_0'x_1$$

Truth Table Description:

$x_0$	$x_1$	$y$
0	0	0
0	1	1
1	0	1
1	1	0

Gate Representation:

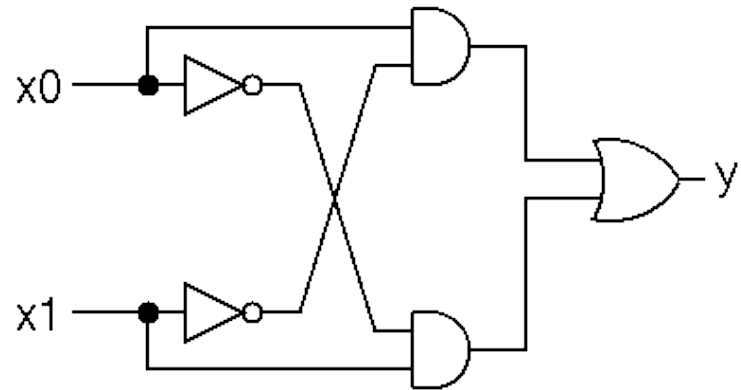


*How would we prove that all three representations are equivalent?*

# Boolean Algebra/Logic Circuits

- ❑ Why are they called “logic circuits”?
- ❑ Logic: The study of the principles of reasoning.
- ❑ The 19th Century Mathematician, George Boole, developed a math. system (algebra) involving logic, Boolean Algebra.
- ❑ His variables took on TRUE, FALSE
- ❑ Later Claude Shannon (father of information theory) showed (in his Master's thesis!) how to map Boolean Algebra to digital circuits:
- ❑ Primitive functions of Boolean Algebra:



a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

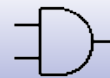

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1



a	NOT
0	1
1	0







# Other logic functions of 2 variables (x,y)

x y	f0	f1														
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1



0
AND
X
Y
 $\oplus$ 
OR
NOR
XNOR
NAND
1

Look at NOR and NAND:

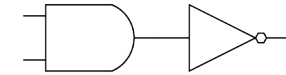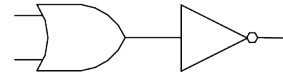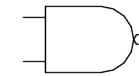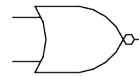

- Theorem: Any Boolean function that can be expressed as a truth table can be expressed using NAND and NOR.


- Proof sketch:

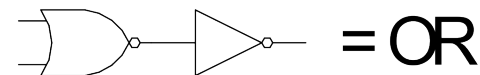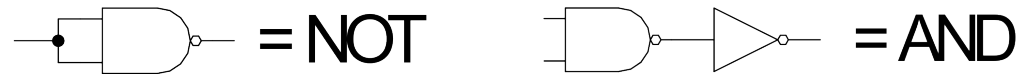

- How would you show that either NAND or NOR is sufficient?
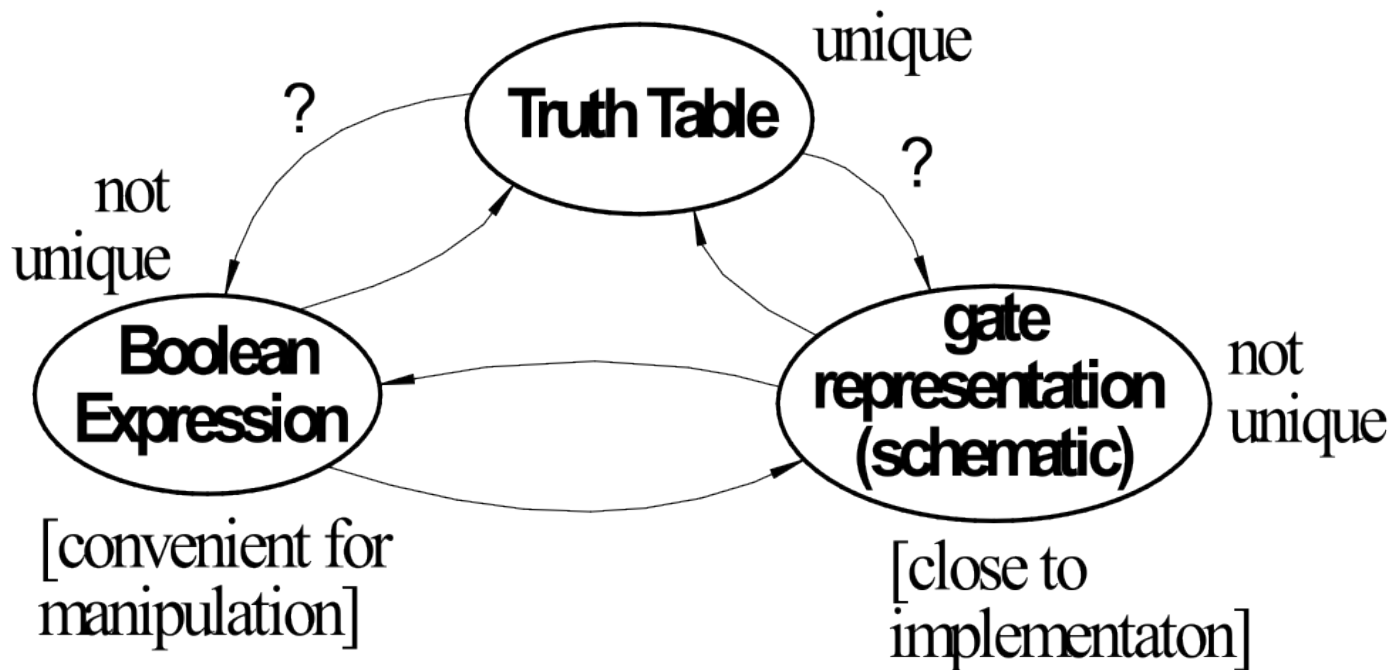
# Relationship Among Representations


- \* Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



*How do we convert from one to the other?*



# CL Block Example – 4 Bit Adder

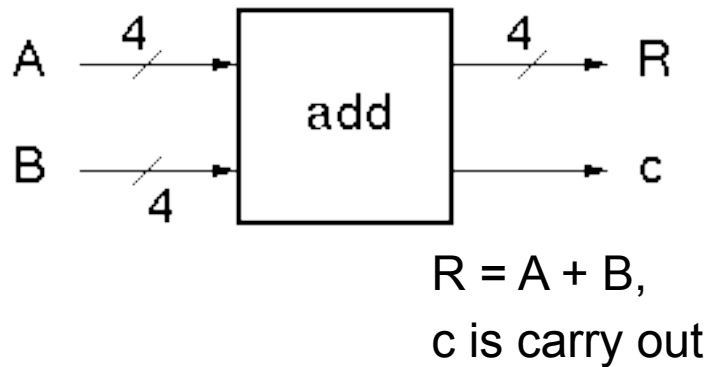

- Truth Table Representation:

a3	a2	a1	a0	b3	b2	b1	b0	r3	r2	r1	r0	c
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	0	1	1	0	0	1	1	0
0	0	0	0	0	1	0	0	0	1	0	0	0
					•							
					•							
					•							
0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	1	0	0	0	1	1	0	1	0	1	0
					•							
					•							
					•							
0	0	0	1	1	1	1	1	0	0	0	0	1

*In general:  $2^n$  rows for  $n$  inputs.*

*256 rows!*

*Is there a more efficient (compact) way to specify this function?*

# 4-bit Adder Example

- Motivate the adder circuit design by hand addition:

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 c \ r_3 \ r_2 \ r_1 \ r_0
 \end{array}$$

- Add  $a_0$  and  $b_0$  as follows:

a	b	r	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

*carry to next stage*

$$r = a \text{ XOR } b = a \oplus b$$

$$c = a \text{ AND } b = ab$$

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 c \ r_3 \ r_2 \ r_1 \ r_0
 \end{array}$$

- Add  $a_1$  and  $b_1$  as follows:

ci	a	b	r	co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$r = a \oplus b \oplus c_i$$


$$co = ab + ac_i + bc_i$$

# 4-bit Adder Example

□ In general:


$$r_i = a_i \oplus b_i \oplus c_{in}$$
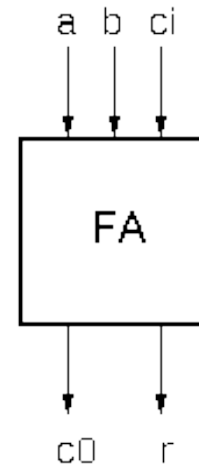
$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in} = c_{in}(a_i + b_i) + a_i b_i$$



*“Full adder cell”*

□ Now, the 4-bit adder:

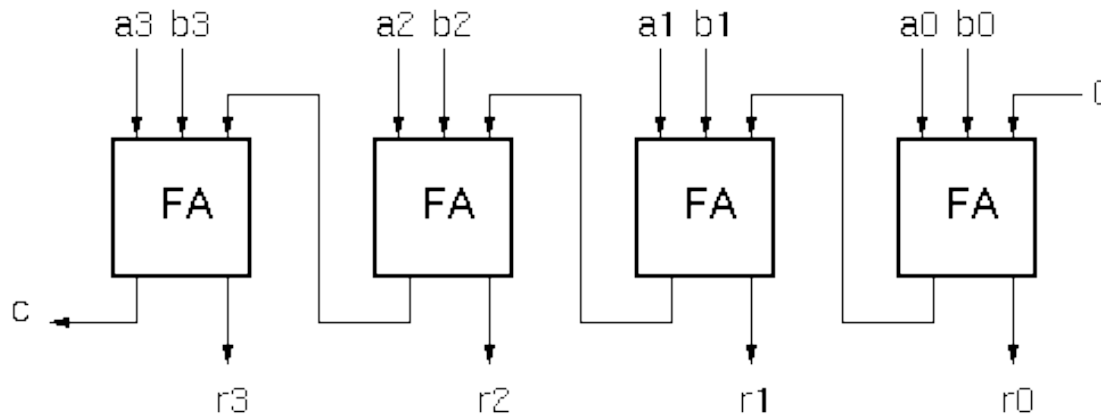


*“ripple” adder*

# 4-bit Adder Example
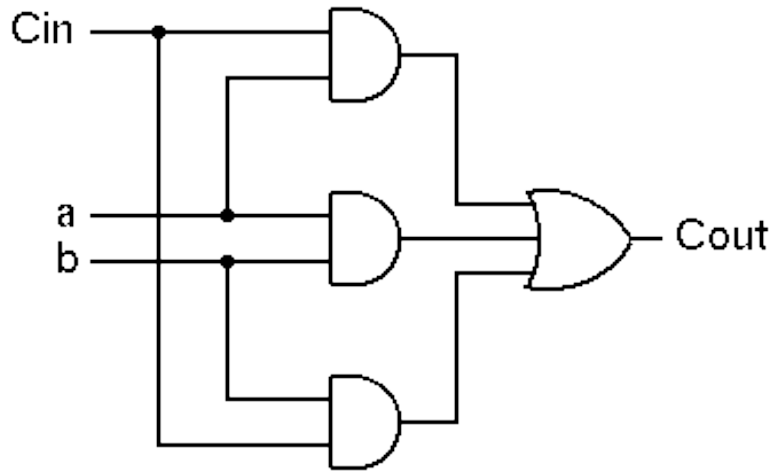
## Graphical Representation of FA-cell

$$r_i = a_i \oplus b_i \oplus c_{in}$$



$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in}$$



- Alternative Implementation (with only 2-input gates):

$$r_i = [a_i \oplus b_i] \oplus c_{in}$$
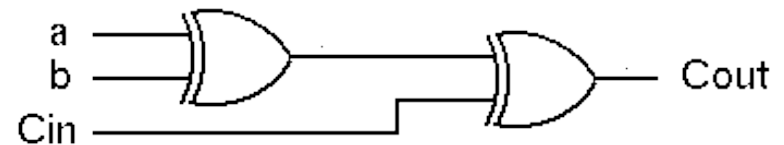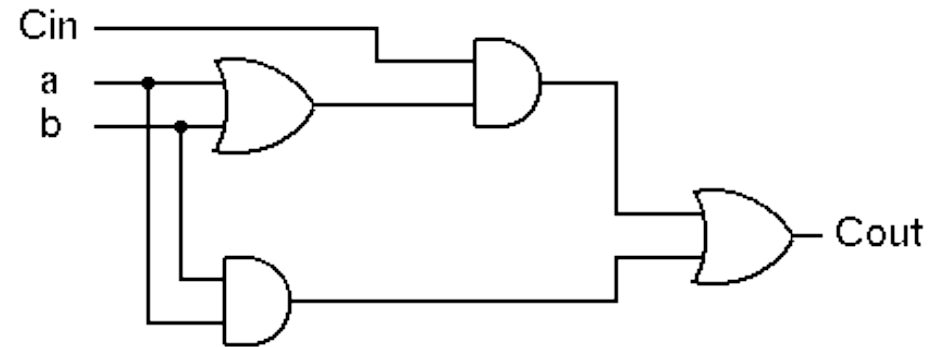
$$c_{out} = c_{in}(a_i + b_i) + a_i b_i$$





# Boolean Algebra

# Boolean Algebra

Set of elements  $B$ , binary operators  $\{+, \bullet\}$ , unary operation  $\{'\}$ , such that the following axioms hold :

1.  $B$  contains at least two elements  $a, b$  such that  $a \neq b$ .

2. Closure :  $a, b$  in  $B$ ,  
 $a + b$  in  $B$ ,  $a \bullet b$  in  $B$ ,  $a'$  in  $B$ .


3. Communitive laws :  
 $a + b = b + a$ ,  $a \bullet b = b \bullet a$ .

4. Identities :  $0, 1$  in  $B$   
 $a + 0 = a$ ,  $a \bullet 1 = a$ .


5. Distributive laws :  
 $a + (b \bullet c) = (a + b) \bullet (a + c)$ ,  $a \bullet (b + c) = a \bullet b + a \bullet c$ .

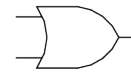6. Complement :  
 $a + a' = 1$ ,  $a \bullet a' = 0$ .


$B = \{0,1\}$ ,  $+$  = OR,  $\bullet$  = AND,  $'$  = NOT  
is a valid Boolean Algebra.



00		0
01		1
10		1
11		1

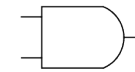

00		0
01		0
10		0
11		1

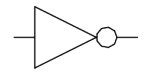

0		1
1		0

# Some Laws of Boolean Algebra

Duality: A dual of a Boolean expression is derived by interchanging OR and AND operations, and 0s and 1s (literals are left unchanged).

$$\{F(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)\}^D = \{F(x_1, x_2, \dots, x_n, 1, 0, \bullet, +)\}$$

Any law that is true for an expression is also true for its dual.

Operations with 0 and 1:

$$\mathbf{x + 0 = x} \quad \mathbf{x * 1 = x}$$

$$\mathbf{x + 1 = 1} \quad \mathbf{x * 0 = 0}$$

Idempotent Law:

$$\mathbf{x + x = x} \quad \mathbf{x x = x}$$

Involution Law:

$$\mathbf{(x')' = x}$$

Laws of Complementarity:

$$\mathbf{x + x' = 1} \quad \mathbf{x x' = 0}$$

Commutative Law:

$$\mathbf{x + y = y + x} \quad \mathbf{x y = y x}$$

# Some Laws of Boolean Algebra (cont.)

Associative Laws:

$$(x + y) + z = x + (y + z)$$

$$x y z = x (y z)$$

Distributive Laws:

$$x (y + z) = (x y) + (x z)$$

$$x +(y z) = (x + y)(x + z)$$

“Simplification” Theorems:

$$x y + x y' = x$$

$$x + x y = x$$

$$(x + y) (x + y') = x$$

$$x (x + y) = x$$

DeMorgan's Law:

$$(x + y + z + \dots)' = x'y'z'$$

$$(x y z \dots)' = x' + y' + z'$$

Theorem for Multiplying and Factoring:

$$(x + y) (x' + z) = x z + x' y$$

Consensus Theorem:


$$x y + y z + x' z = (x + y) (y + z) (x' + z)$$

$$x y + x' z = (x + y) (x' + z)$$



# DeMorgan's Law


$$(x + y)' = x' y'$$

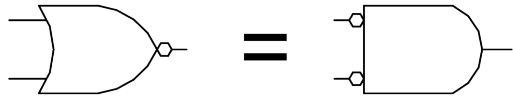

*Exhaustive  
Proof*

x	y	x'	y'	(x+y)'	x'y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(x y)' = x' + y'$$

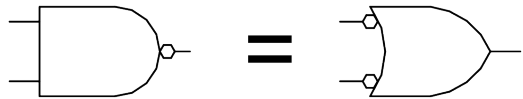


*Exhaustive  
Proof*

x	y	x'	y'	(xy)'	x'+y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0
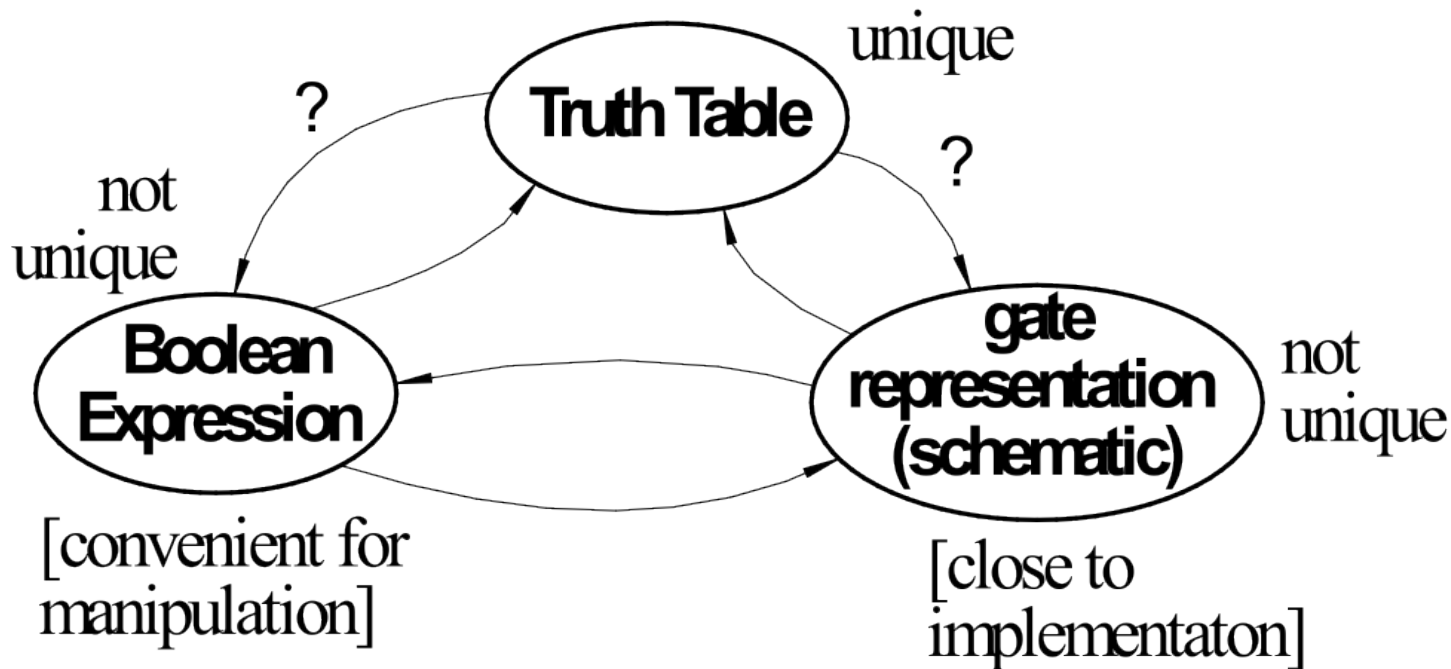
# Relationship Among Representations

- \* Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



*How do we convert from one to the other?*

# Canonical Forms

- Standard form for a Boolean expression - unique algebraic expression directly from a true table (TT) description.
- Two Types:
  - \* **Sum of Products (SOP)**
  - \* **Product of Sums (POS)**
- Sum of Products (disjunctive normal form, minterm expansion). Example:

Minterms	a	b	c	f	f'
a'b'c'	0	0	0	0	1
a'b'c	0	0	1	0	1
a'bc'	0	1	0	0	1
a'bc	0	1	1	1	0
ab'c'	1	0	0	1	0
ab'c	1	0	1	1	0
abc'	1	1	0	1	0
abc	1	1	1	1	0

One product (and) term for each 1 in f:

$$f = a'bc + ab'c' + ab'c + abc' + abc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

*What is the cost?*

# Sum of Products (cont.)

Canonical Forms are usually not minimal:

Our Example:

$$f = a'bc + ab'c' + ab'c + abc' + abc \quad (xy' + xy = x)$$

$$= a'bc + ab' + ab$$

$$= a'bc + a$$

$$= a + bc$$

$$(x'y + x = y + x)$$

$$f' = a'b'c' + a'b'c + a'bc'$$

$$= a'b' + a'bc'$$

$$= a' ( b' + bc' )$$

$$= a' ( b' + c' )$$

$$= a'b' + a'c'$$

# Canonical Forms

- Product of Sums (conjunctive normal form, maxterm expansion).

Example:

maxterms	a	b	c	f	f'
$a+b+c$	0	0	0	0	1
$a+b+c'$	0	0	1	0	1
$a+b'+c$	0	1	0	0	1
$a+b'+c'$	0	1	1	1	0
$a'+b+c$	1	0	0	1	0
$a'+b+c'$	1	0	1	1	0
$a'+b'+c$	1	1	0	1	0
$a'+b'+c'$	1	1	1	1	0

One sum (**or**) term for each **0** in f:

$$f = (a+b+c) (a+b+c') (a+b'+c)$$

$$f' = (a+b'+c') (a'+b+c) (a'+b+c') \\ (a'+b'+c) (a+b+c')$$



## **Boolean Simplification**

# *Algebraic Simplification Example*

Ex: full adder (FA) carry out function (in canonical form):

$$C_{out} = a'bc + ab'c + abc' + abc$$

# Algebraic Simplification

$$\begin{aligned} \text{Cout} &= a'bc + ab'c + abc' + abc \\ &= a'bc + ab'c + abc' + abc + abc \\ &= a'bc + abc + ab'c + abc' + abc \\ &= (a' + a)bc + ab'c + abc' + abc \\ &= (1)bc + ab'c + abc' + abc \\ &= bc + ab'c + abc' + abc + abc \\ &= bc + ab'c + abc + abc' + abc \\ &= bc + a(b' + b)c + abc' + abc \\ &= bc + a(1)c + abc' + abc \\ &= bc + ac + ab(c' + c) \\ &= bc + ac + ab(1) \\ &= bc + ac + ab \end{aligned}$$



# *Outline for remaining CL Topics*

- K-map method of two-level logic simplification
- Multi-level Logic
- NAND/NOR networks
- EXOR revisited

# Algorithmic Two-level Logic Simplification

Key tool: The Uniting Theorem:

$$xy' + xy = x(y' + y) = x(1) = x$$

<i>ab</i>	<i>f</i>
00	0
01	0
10	1
11	1

$$f = ab' + ab = a(b' + b) = a$$

b values change within the on-set rows

a values don't change

b is eliminated, a remains

<i>ab</i>	<i>g</i>
00	1
01	0
10	1
11	0

$$g = a'b' + ab' = (a' + a)b' = b'$$


b values stay the same

a values changes


b' remains, a is eliminated
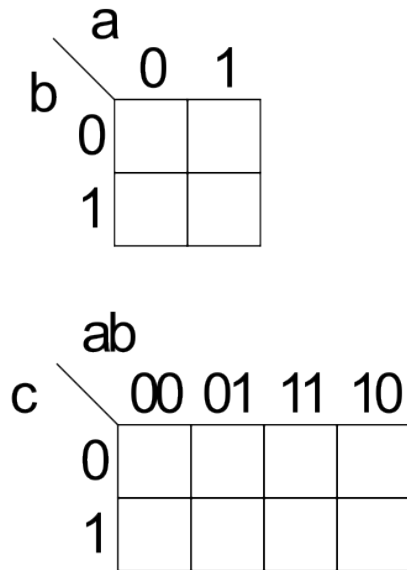
# Karnaugh Map Method

- K-map is an alternative method of representing the TT and to help visual the adjacencies.



Note: "gray code" labeling.

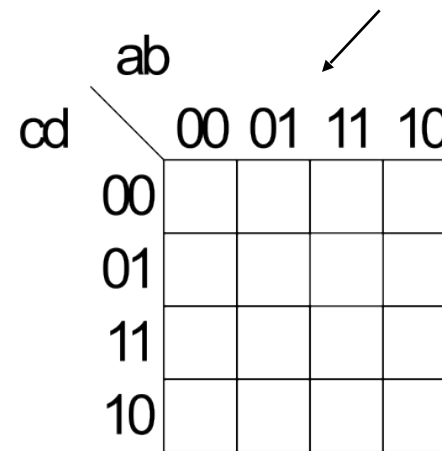

5 & 6 variable k-maps possible

# Karnaugh Map Method

- Adjacent groups of 1's represent product terms

a

b \ a	0	1
0	0	1
1	0	1

f = a

a

b \ a	0	1
0	1	1
1	0	0

g = b'

ab

c \ ab	00	01	11	10
0	0	0	1	0
1	0	1	1	1

cout = ab + bc + ac

ab

c \ ab	00	01	11	10
0	0	0	1	1
1	0	0	1	1

f = a

## *K-map Simplification*

1. Draw K-map of the appropriate number of variables (between 2 and 6)
2. Fill in map with function values from truth table.
3. Form groups of 1's.
  - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
  - ✓ Form as large as possible groups and as few groups as possible.
  - ✓ Groups can overlap (this helps make larger groups)
  - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
  - the term includes the “constant” variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

# K-maps (cont.)

	ab			
c	00	01	11	10
0	1	0	0	1
1	0	0	1	1

$$f = b'c' + ac$$

	ab			
cd	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

$$f = c + a'bd + b'd'$$

(bigger groups are better)

## Product-of-Sums Version

1. Form groups of 0's instead of 1's.
2. For each group write a sum term.
  - the term includes the “constant” variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
3. Form Boolean expression as product-of-sums.

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = (b' + c + d)(a' + c + d')(b + c + d')$$


# BCD incrementer example

## Binary Coded Decimal

	<i>a b c d</i>	<i>w x y z</i>
0	0000	0001
1	0001	0010
2	0010	0011
3	0011	0100
4	0100	0101
5	0101	0110
6	0110	0111
7	0111	1000
8	1000	1001
9	1001	0000
	1010	- - - -
	1011	- - - -
	1100	- - - -
	1101	- - - -
	1110	- - - -
	1111	- - - -

$\{a,b,c,d\}$

4 ↓

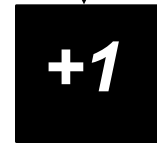

4 ↓

$\{w,x,y,z\}$



## *BCD Incrementer Example*

- ❑ Note one map for each output variable.
- ❑ Function includes “don’t cares” (shown as “-” in the table).
  - These correspond to places in the function where we don’t care about its value, because we don’t expect some particular input patterns.
  - We are free to assign either 0 or 1 to each don’t care in the function, as a means to increase group sizes.
- ❑ In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.

# BCD incrementer example

**W**

	ab	00	01	11	10
cd		<u>00</u>	<u>01</u>	<u>11</u>	<u>10</u>
00		0	0	-	1
01		0	0	-	0
11		0	1	-	-
10		0	0	-	-

**X**

	ab	00	01	11	10
cd		<u>00</u>	<u>01</u>	<u>11</u>	<u>10</u>
00		0	1	-	0
01		0	1	-	0
11		1	0	-	-
10		0	1	-	-

w =

x =

**y**

	ab	00	01	11	10
cd		<u>00</u>	<u>01</u>	<u>11</u>	<u>10</u>
00		0	0	-	0
01		1	1	-	0
11		0	0	-	-
10		1	1	-	-



**Z**

	ab	00	01	11	10
cd		<u>00</u>	<u>01</u>	<u>11</u>	<u>10</u>
00		1	1	-	1
01		0	0	-	0
11		0	0	-	-
10		1	1	-	-

y =

z =

# Higher Dimensional K-maps

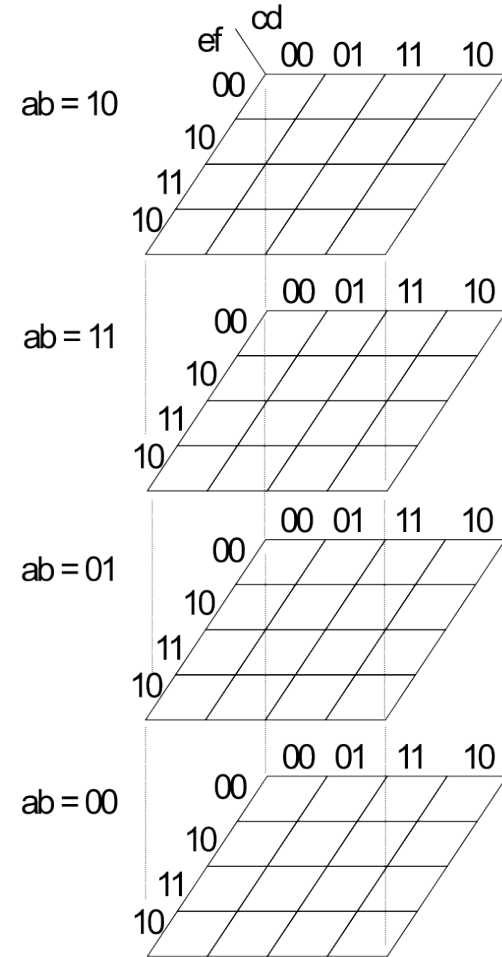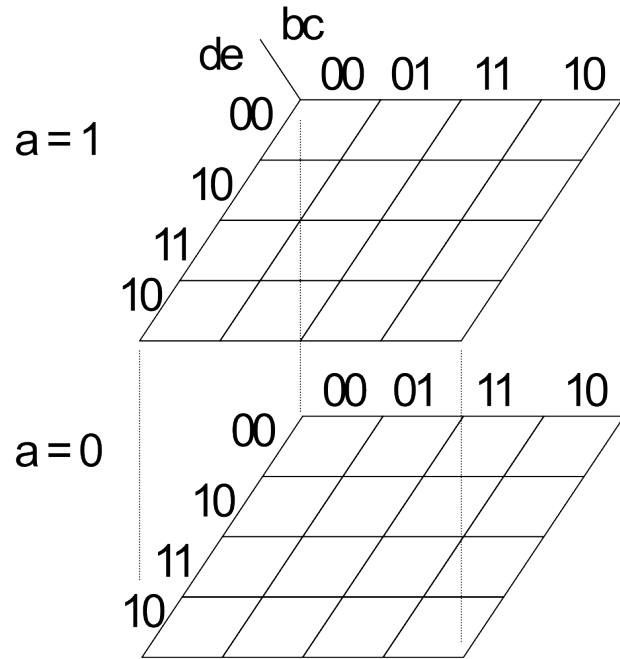




## **Boolean Simplification – Multi-level Logic**

# Multi-level Combinational Logic

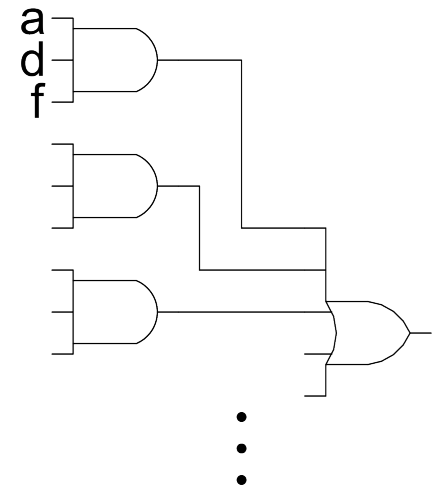- Example: reduced sum-of-products form  
 $x = adf + aef + bdf + bef + cdf + cef + g$
- Implementation in 2-levels with gates:
  - cost:** 1 7-input OR, 6 3-input AND
  - => 50 transistors
  - delay:** 3-input OR gate delay + 7-input AND gate delay



# Multi-level Combinational Logic

- Example: reduced sum-of-products form


$$x = adf + aef + bdf + bef + cdf + cef + g$$

- Implementation in 2-levels with gates:

**cost:** 1 7-input OR, 6 3-input AND

=> 50 transistors

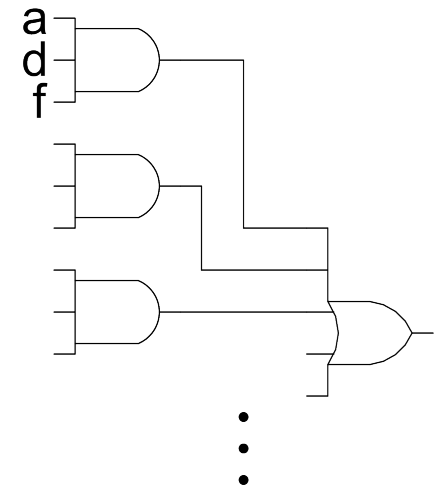**delay:** 3-input OR gate delay + 7-input AND gate delay




- Factored form:

$$x = (a + b + c)(d + e)f + g$$

**cost:** 1 3-input OR, 2 2-input OR, 1 3-input AND

=> 20 transistors

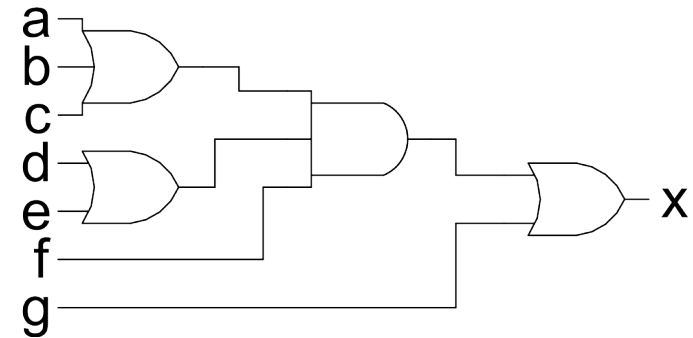
**delay:** 3-input OR + 3-input AND + 2-input OR




*Footnote: NAND would be used in place of all ANDs and ORs.*

# Multi-level Combinational Logic

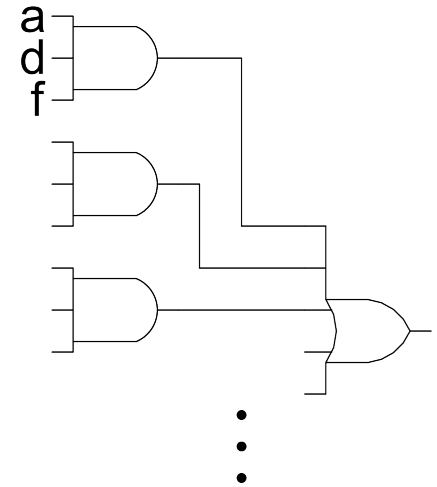- Example: reduced sum-of-products form  
 $x = adf + aef + bdf + bef + cdf + cef + g$
- Implementation in 2-levels with gates:  
**cost:** 1 7-input OR, 6 3-input AND  
=> 50 transistors  
**delay:** 3-input OR gate delay + 7-input AND gate delay



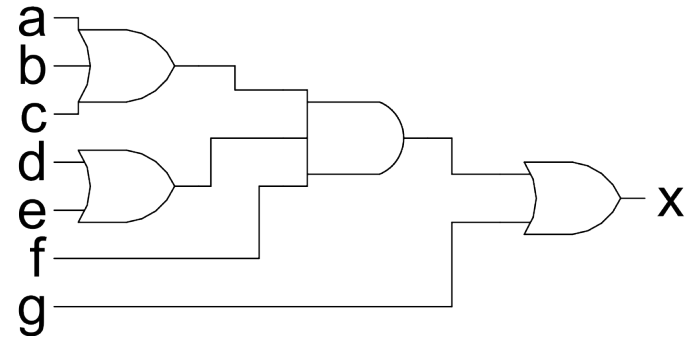- Factored form:  
 $x = (a + b + c)(d + e)f + g$   
**cost:** 1 3-input OR, 2 2-input OR, 1 3-input AND  
=> 20 transistors  
**delay:** 3-input OR + 3-input AND + 2-input OR



*Footnote: NAND would be used in place of all ANDs and ORs.*


## Which is faster?

*In general: Using multiple levels (more than 2) will reduce the cost. Sometimes also delay.*

*Sometimes a tradeoff between cost and delay.*

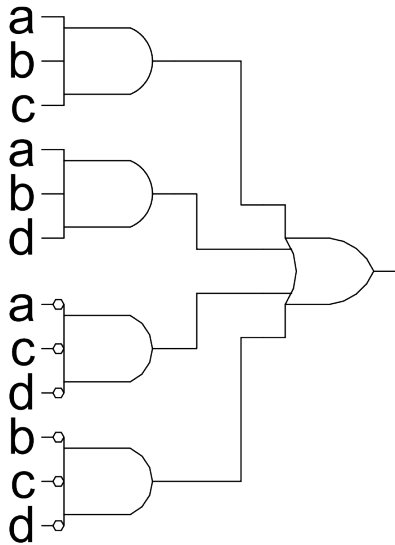
# Multi-level Combinational Logic

Another Example:  $F = abc + abd + a'c'd' + b'c'd'$



$$\text{let } x = ab \quad y = c+d$$

$$f = xy + x'y'$$

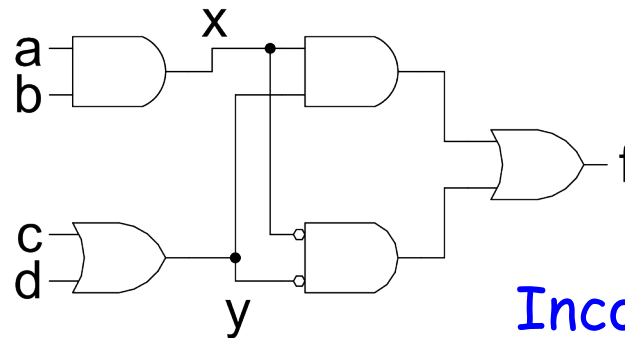

Incorporates fanout.

No convenient hand methods exist for multi-level logic simplification:

a) CAD Tools use sophisticated algorithms and heuristics

Guess what? These problems tend to be NP-complete

b) Humans and tools often exploit some special structure (example adder)



# NAND-NAND & NOR-NOR Networks





DeMorgan's Law Review:

$$(a + b)' = a' b'$$

$$a + b = (a' b')'$$

$$(a b)' = a' + b'$$

$$(a b) = (a' + b')'$$

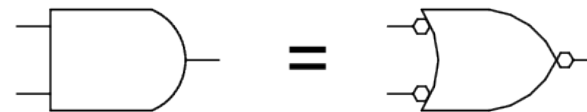
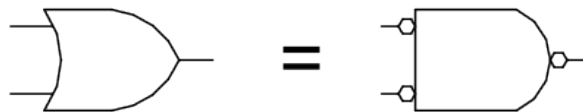
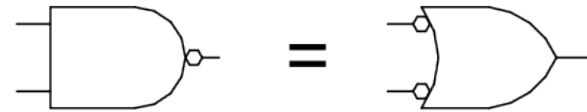
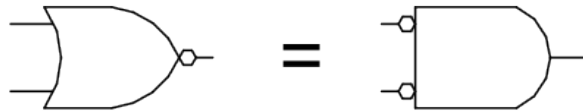


*push bubbles or introduce in pairs or remove pairs:*

$$(x')' = x.$$

# NAND-NAND & NOR-NOR Networks


- Mapping from AND/OR to NAND/NAND

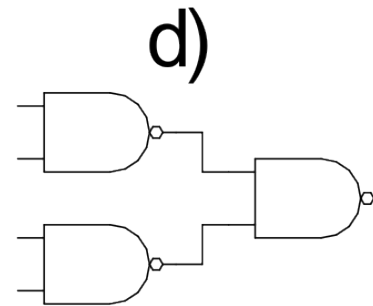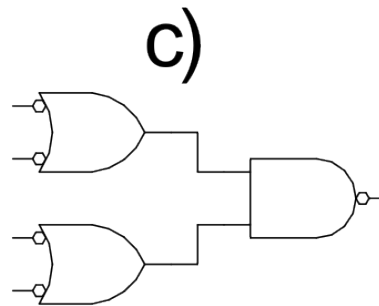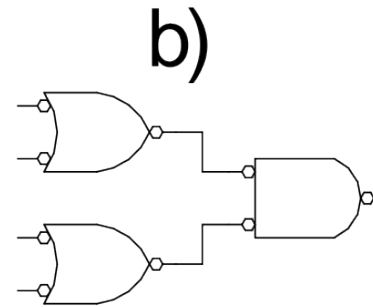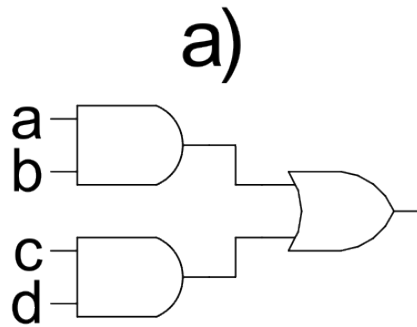

# Multi-level Networks

Convert to NANDs:

$$F = a(b + cd) + bc'$$


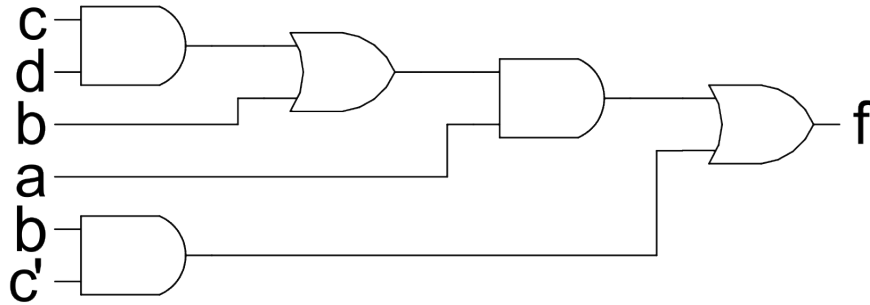


# EXOR Function Implementations



Parity, addition mod 2

$$x \oplus y = x'y + xy'$$

x	y	xor	xnor
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

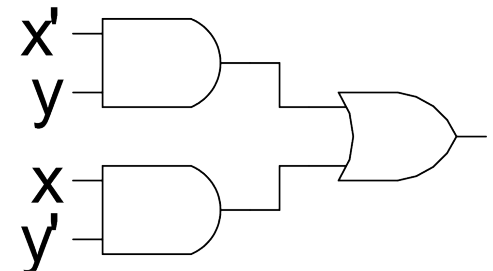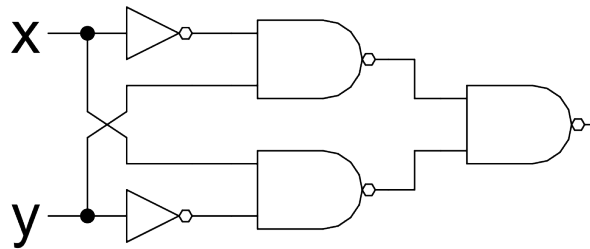

Another approach:

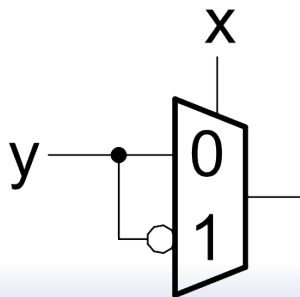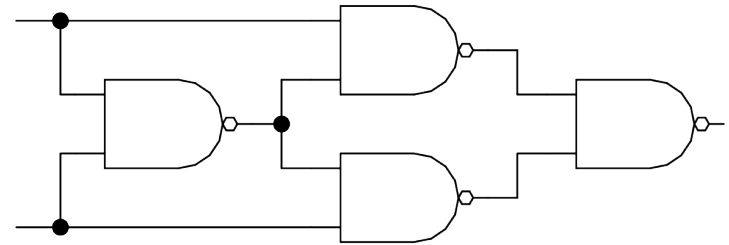

if  $x=0$  then  $y$  else  $y'$