



**EECS 151/251A**  
**Spring 2019**  
**Digital Design and**  
**Integrated Circuits**

Instructors:  
Wawrzynek


**Lecture 9**



**CMOS abstraction**


 
# CMOS Devices

- MOSFET (Metal Oxide Semiconductor Field Effect Transistor).




*The gate acts like a capacitor. A high voltage on the gate attracts charge into the channel. If a voltage exists between the source and drain a current will flow. In its simplest approximation, the device acts like a switch.*

# CMOS Transistors – State-of-the-Art

  

# Drain versus Source - Definition

 


*MOS transistors are symmetrical devices  
(Source and drain are interchangeable)*

*Source is the node w/ the lowest voltage*
 
# MOS Transistor as a Resistive Switch



MOS Transistor  $\leftrightarrow$  A Switch!



*Let's look beneath the abstraction:  
origins of  $R_{on}$  and  $V_T$*

  
# Transistor “resistance”

- Actually, nonlinear I/V characteristic:




- Linearizing makes all delay and power calculations simple (usually just 1st order ODEs):

# MOSFET Threshold Voltage

 


 Transistor “turns on” when  $V_{gs}$  is  $> V_t$ .






# ON/OFF Switch Model of MOS Transistor

 

 
# Plot on a "Log" Scale to See "Off" Current




Process engineers can:

 increase  $I_{on}$  by lowering  $V_t$  - but that raises  $I_{off}$   
decrease  $I_{off}$  by raising  $V_t$  - but that lowers  $I_{on}$ .




$I_{off} \approx 10 \text{ nA}$

# A More Realistic Switch

 


# A Logic Perspective

## NMOS Transistor

 


# A Complementary Switch

 


$Y=Z$  if  $X=0$

## PMOS Transistor

 

*Source is the node w/ the highest voltage!*



# The CMOS Inverter: A First Glance

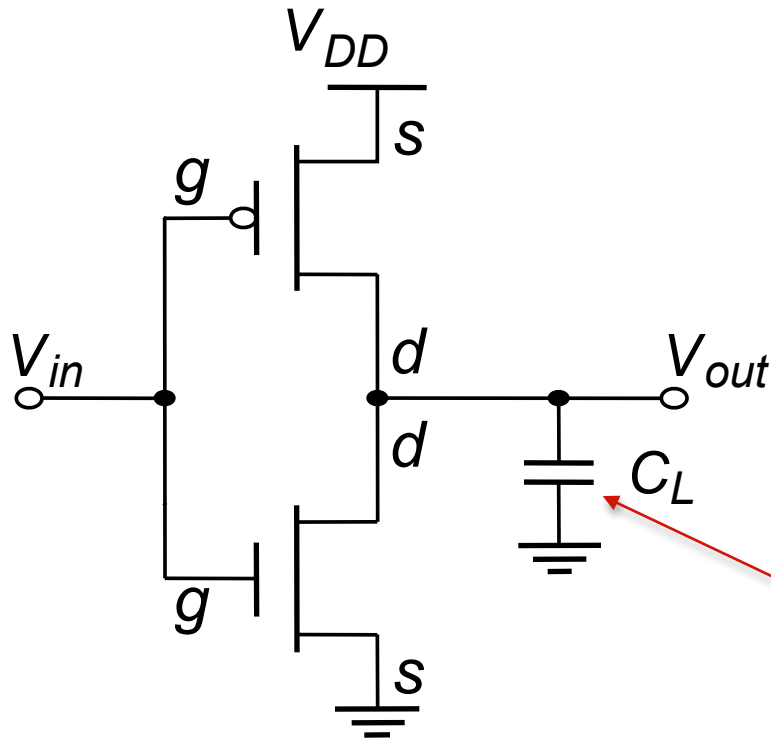

*Represents the sum of all the capacitance at the output of the inverter and everything to which it connects: (drains, interconnections gate capacitance of next gate(s))*

# The Switch Inverter

## First-Order DC Analysis\*

  

$$V_{OL} = 0$$
$$V_{OH} = V_{DD}$$

*\*First-order means we will ignore Capacitance.*




**Switch logic**



# Static Logic Gate


- At every point in time (except during the switching transients) each gate output is connected to either  $V_{DD}$  or  $V_{GND}$  via a low resistive path.
- The output of the gate assumes at all times the value of the Boolean function implemented by the circuit (ignoring, once again, the transient effects during switching periods).

Example: CMOS Inverter

 

# Building logic from switches


**Series**

 

**AND**

$Y = X$  if  $A$  AND  $B$

**Parallel**

 


**OR**

$Y = X$  if  $A$  OR  $B$

(output undefined if condition not true)

# Logic using inverting switches


**Series**

 

**NOR**

$$Y = X \text{ if } \bar{A} \text{ AND } \bar{B} \\ = \overline{A + B}$$

**Parallel**

 


**NAND**

$$Y = X \text{ if } \bar{A} \text{ OR } \bar{B} \\ = \overline{AB}$$

(output undefined if condition not true)


# Static Complementary CMOS

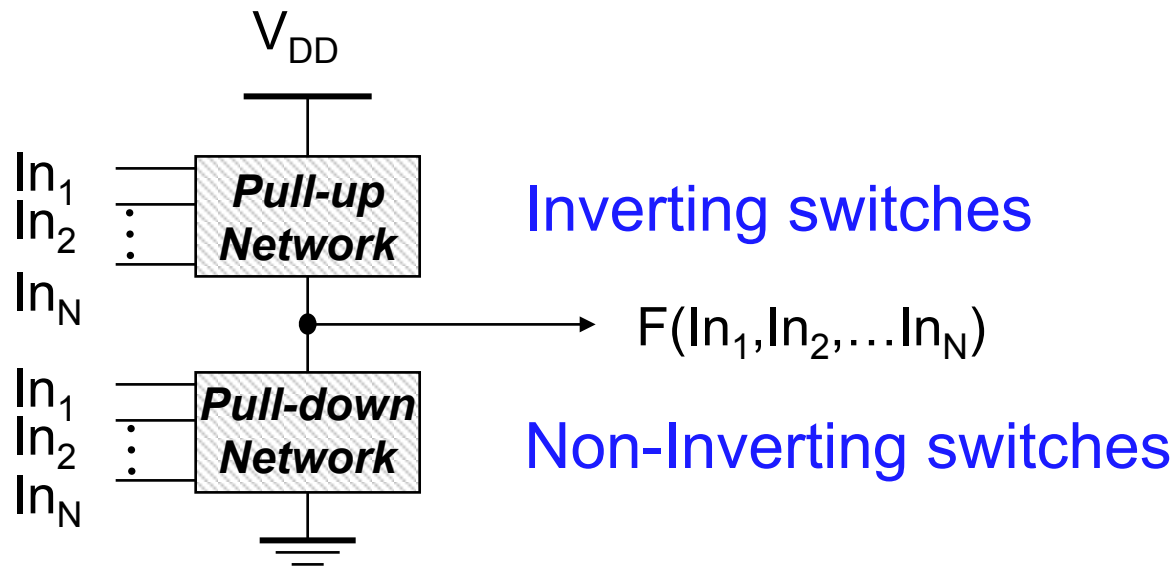

PUN and PDN are **dual** logic networks

PUN and PDN functions are **complementary**

*Dual Graphs*

 


# Complementary CMOS Logic Style

- PUN is the **dual** to PDN  
(can be shown using DeMorgan's Theorems)

$$\overline{A + B} = \overline{A} \overline{B}$$

$$\overline{A \overline{B}} = \overline{A} + B$$

- Static CMOS gates are always inverting

 


**AND = NAND + INV**

# Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


- PDN:  $G = AB \Rightarrow$  Conduction to GND
- PUN:  $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$  Conduction to  $V_{DD}$
- $\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$

# Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 
 
# Complex CMOS Gate


$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

$$\text{OUT} = \overline{D \cdot A + B \cdot C}$$






# Non-inverting logic

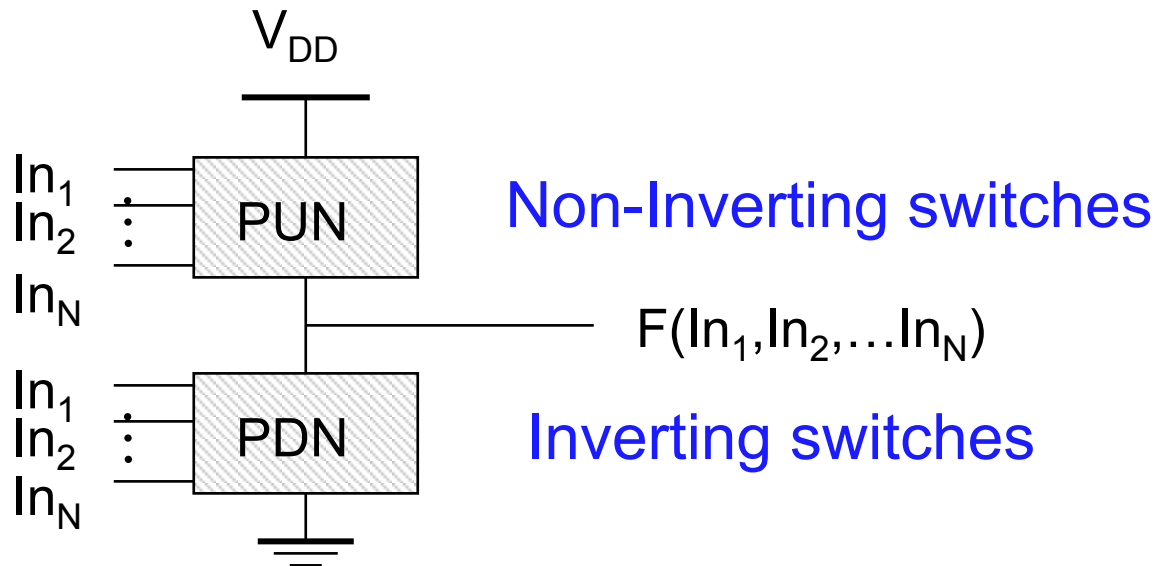

*Why is this  
a bad idea?*

PUN and PDN are **dual** logic networks  
PUN and PDN functions are **complementary**


# Switch Limitations

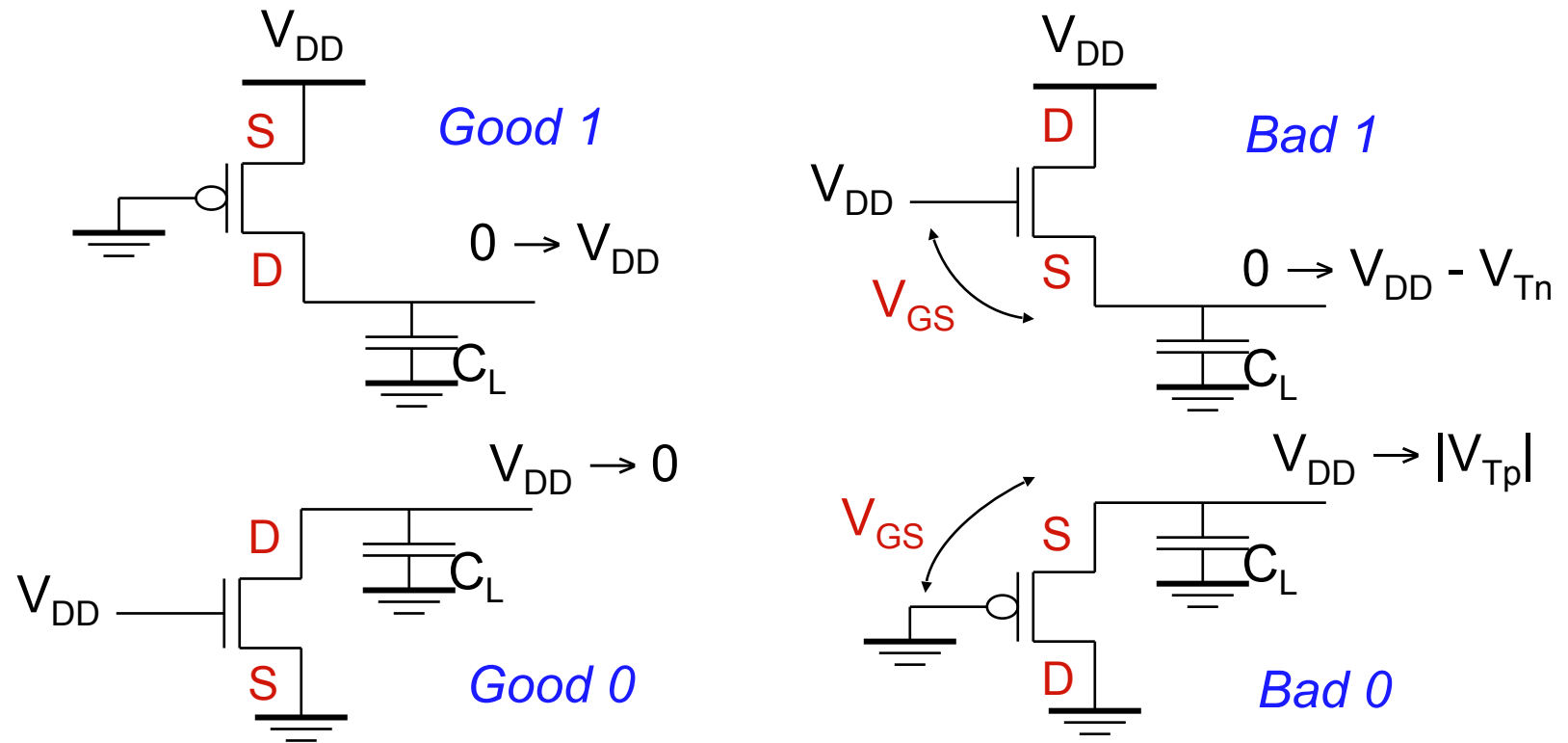

*Tough luck ...*
 
# Transmission Gate

- ❑ Transmission gates are the way to build “switches” in CMOS.
- ❑ In general, both transistor types are needed:
  - ❑ nFET to pass zeros.
  - ❑ pFET to pass ones.
- ❑ The transmission gate is bi-directional (unlike logic gates).




- ❑ Does not directly connect to V<sub>dd</sub> and GND, but can be combined with logic gates or buffers to simplify many logic structures.



# Transmission-gate Multiplexor

2-to-1 multiplexor:

$$c = sa + s'b$$

 


Switches simplify the implementation:

  

Compare the cost to logic gate implementation.

Care must be taken to not string together many pass-transistor stages. Occasionally, need to "rebuffer" with static gate.

# 4-to-1 Transmission-gate Mux

 


- The series connection of pass-transistors in each branch effectively forms the AND of  $s_1$  and  $s_0$  (or their complement).
- Compare cost to logic gate implementation

*Any better solutions?*

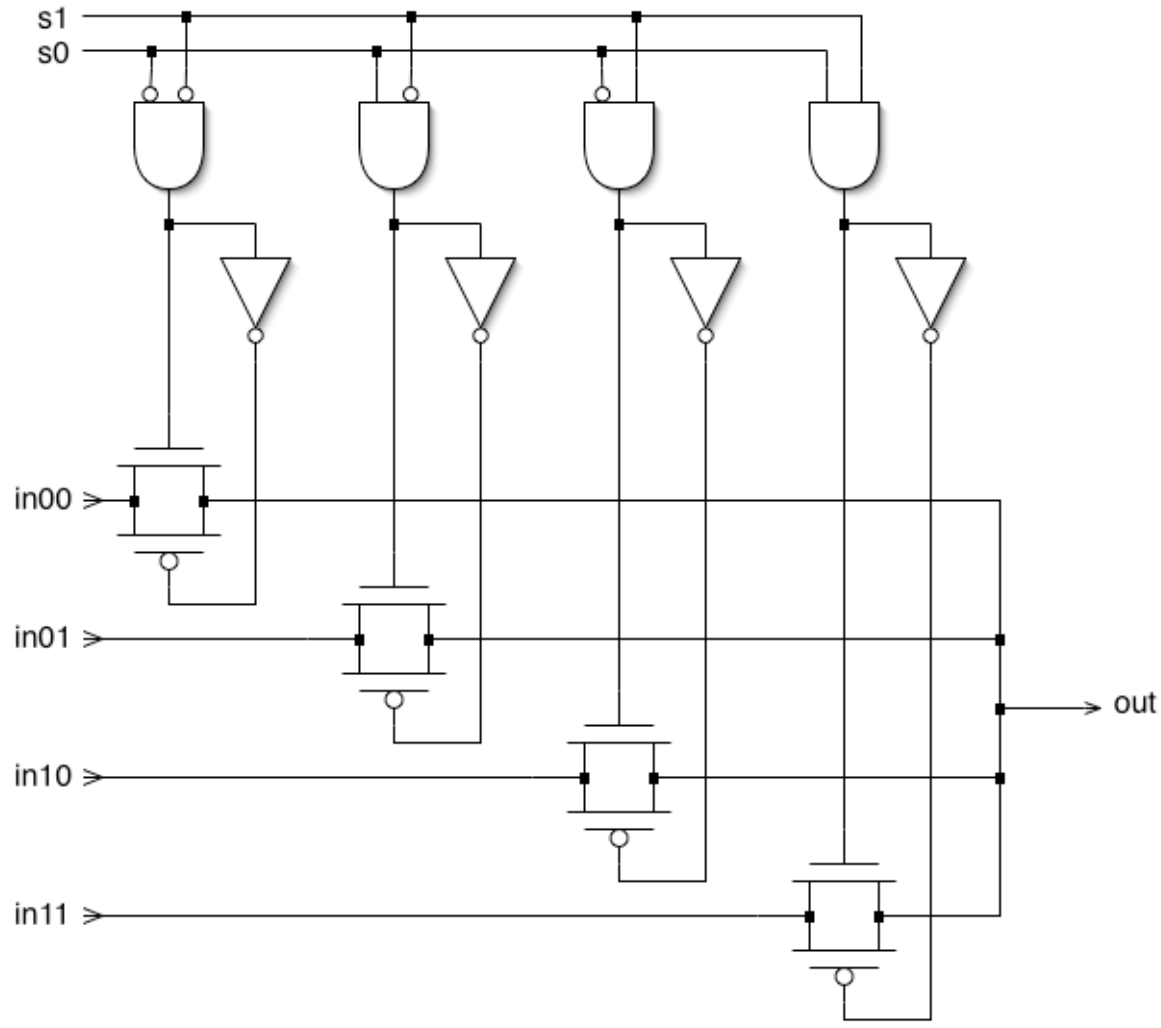
# Alternative 4-to-1 Multiplexor

- This version has less delay from in to out.
- In both versions, care must be taken to avoid turning on multiple paths simultaneously (shorting together the inputs).



# Tri-state Buffers


Tri-state Buffer:

 

OE	IN	OUT
0	0	Z
0	1	Z
1	0	0
1	1	1


“high impedance” (output disconnected)

## Variations:

 


OE	IN	OUT
0	-	Z
1	0	1
1	1	0

Inverting buffer

 


OE	IN	OUT
0	0	0
0	1	1
1	-	Z

Inverted enable

 


 transmission gate useful in implementation



 
# Tri-state Buffers

Tri-state buffers enable "bidirectional" connections.



 
Tri-state buffers are used when multiple circuits all connect to a common wire. Only one circuit at a time is allowed to drive the bus. All others "disconnect" their outputs, but can "listen".







# Tri-state Based Multiplexor


Multiplexor

 

If  $s=1$  then  $c=a$  else  $c=b$

 
 


 Transistor Circuit for inverting multiplexor:




# Latches and Flip-flops


Positive Level-sensitive *latch*:

  

 Positive Edge-triggered **flip-flop**  
built from two level-sensitive  
latches:



Latch Implementation:

 

# *Summary:*

## *Complimentary CMOS Properties*

- ❑ Full rail-to-rail swing
- ❑ Besides leakage (due to  $I_{off}$ ), no static power dissipation
- ❑ Direct path current during switching