

# EECS 151 Disc 12

Rahul Kumar (session 1)  
Yukio Miyasaka (session 2)


# Contents

- Wallace tree
- Signed multiplication
- Multiplication by a constant
- Clocks
- Packaging


# Announcement

- HW11 is not as short as we expected
  - However, each problem is quite simple (~5 min)
  - Due May 8 Monday, solution will be posted just after deadline
- 
- Unfortunately, we don't have time to do review for the final

# 7x7 Wallace Tree (Unsigned Multiplier)




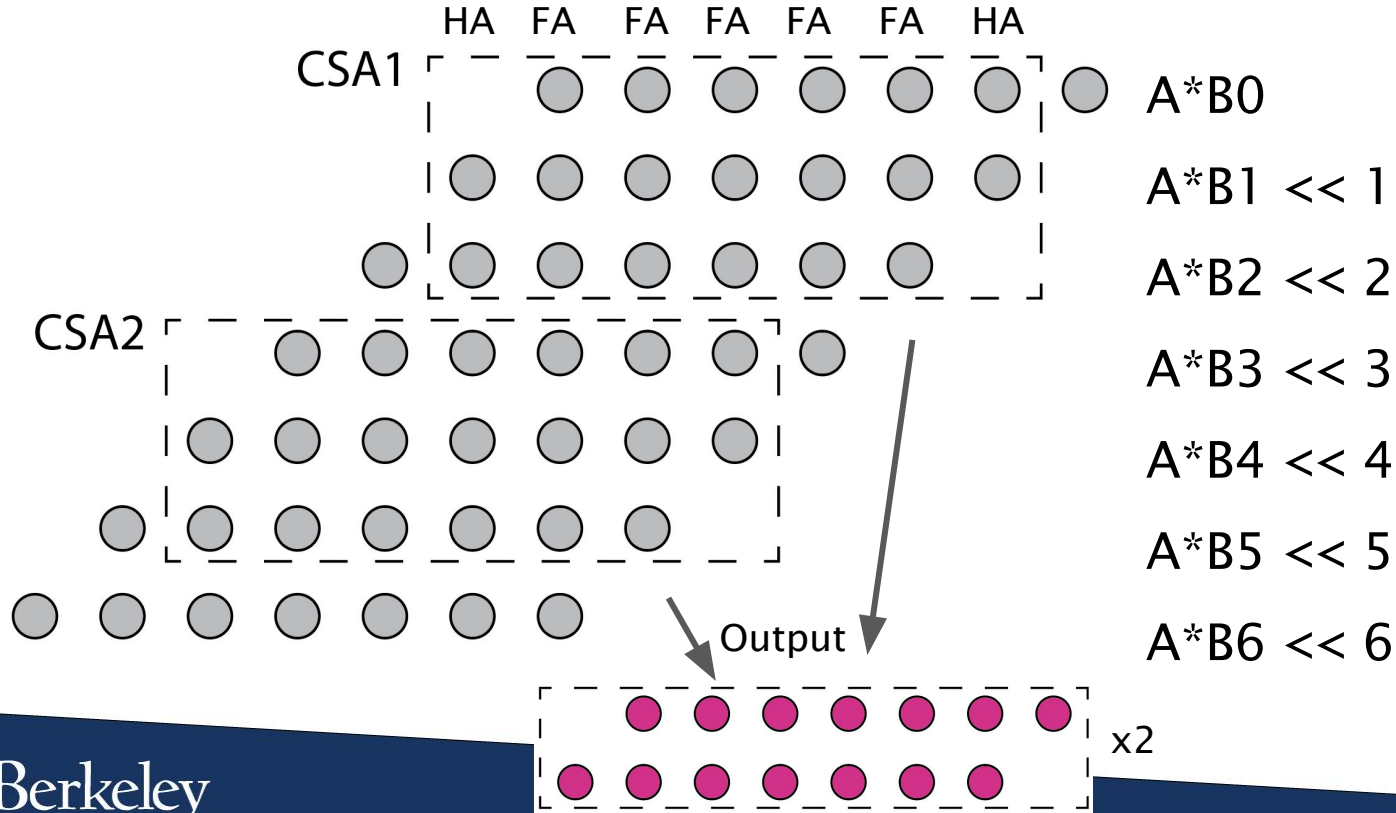


# 7x7 Wallace Tree: After 1st Stage

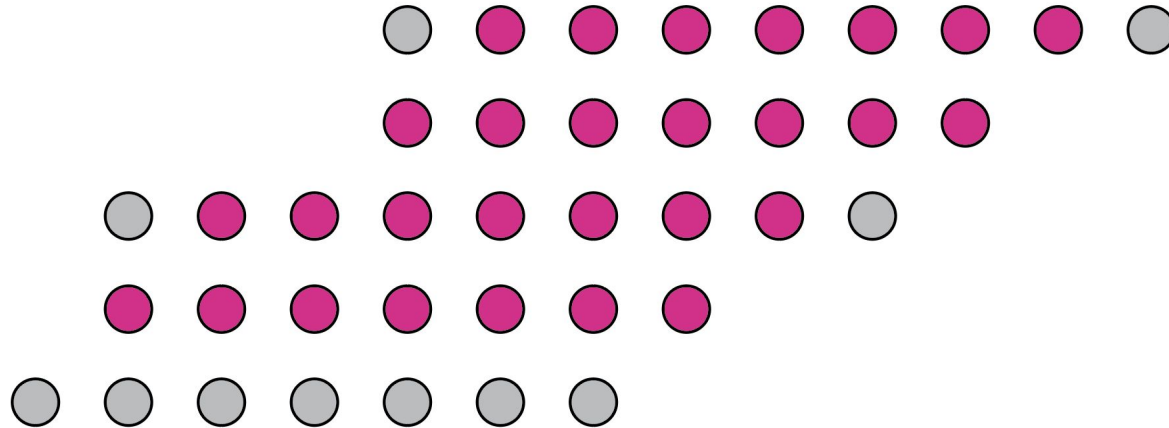
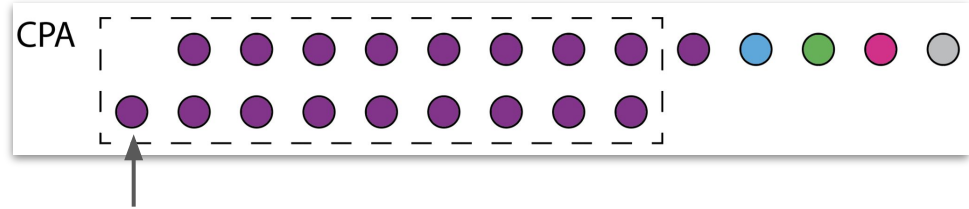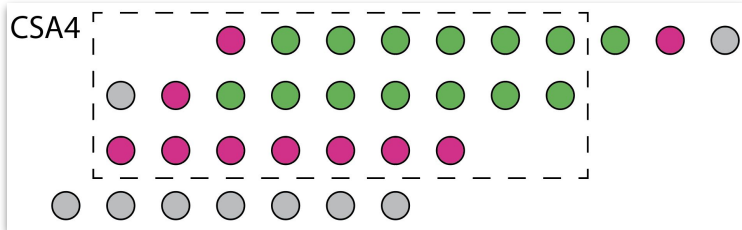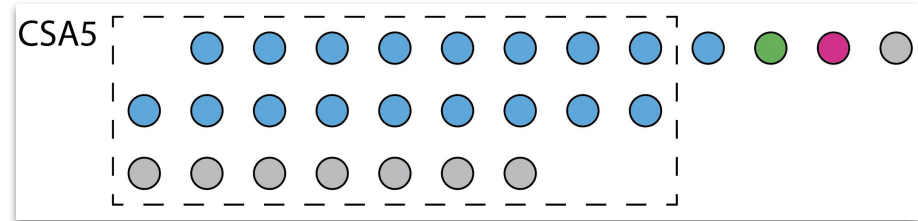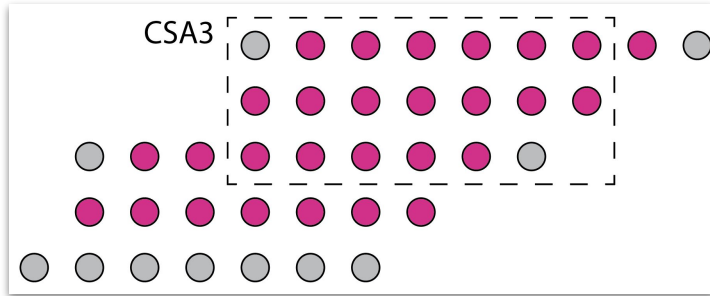
# 7x7 Wallace Tree: Following Stages

(There were some bugs in last week's slide)



The MSB adder can be just an XOR, since the result of 7x7 does not exceed 14 bits.

# Signed Multiplication

$$B = \{b_3, b_2, b_1, b_0\} = b_0 + (2*b_1) + (4*b_2) - (8*b_3)$$

$$A*B = A*b_0 + A*(2*b_1) + A*(4*b_2) - A*(8*b_3)$$

$$= A*b_0 + (A \ll 1)*b_1 + (A \ll 2)*b_2 - (A \ll 3)*b_3$$

- One more left shift each time
- Subtract the partial product for the MSB of B
- Sign extend partial products properly ( $2N$  is safe, but you can save a little by using some techniques)






# Baugh-Wooley's Algorithm

- Replace sign extension with negation and minus one at the MSB
  - $aa...axyz = a'xyz - 1000$  because
    - $00...0xyz = 1xyz - 1000$
    - $11...1xyz = 0xyz + 11...1000 = 0xyz - 1000$
- Also apply 2's complement to the last partial product
  - $-aaxyz = a'a'x'y'z' + 1 = ax'y'z' - 1000 + 1$
- Precompute constants
  - $-1000 - 10000 - 100000 - 1000000 + 1000 = -11110000 = +10010000$

# Baugh-Wooley's Signed Multiplier

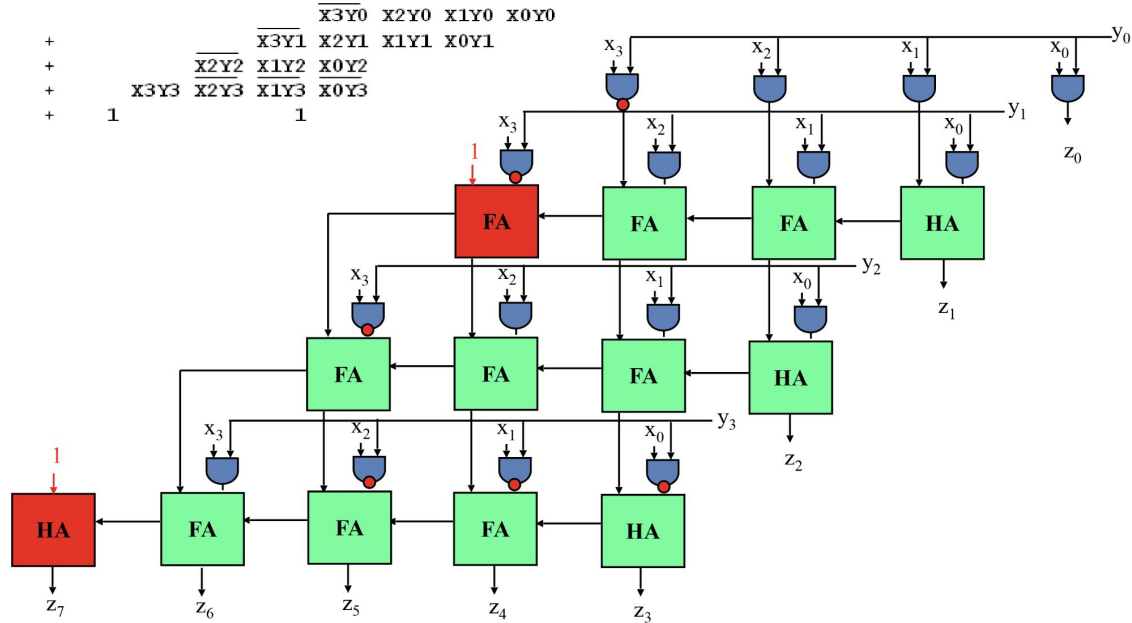

# Multiplication by a Constant


- Multiplication by a constant is just shift-and-add
  - $75X = 1001011X = (X \ll 6) + (X \ll 3) + (X \ll 1) + X$
- CSD representation utilizes subtraction
  - $01\dots11$  to  $10\dots01'$  (1' here means minus one)
  - $11'$  to  $01$ , and  $1'1$  to  $01'$ 
    - $75 = 1001011 = 1001101' = 10101'01'$
    - $75X = (X \ll 6) + (X \ll 4) - (X \ll 2) - X$
    - Doesn't help in this case

# Constant Coefficient Multiplication

- Break down the constant and cascade shift-and-add
- $75 = 3 * 5 * 5$ 
  - $(3 * 25)$ : 3 is  $(2+1)$  and 25 is  $(16+8+1)$  -> 3 adders
  - $(5 * 15)$ : 5 is  $(4+1)$  and 15 is  $(16-1)$  -> 2 adders (one used as a subtractor)
- $Y = (X \ll 2) + X$
- $Z = (Y \ll 4) - Y$
- Then,  $Z = 75X$
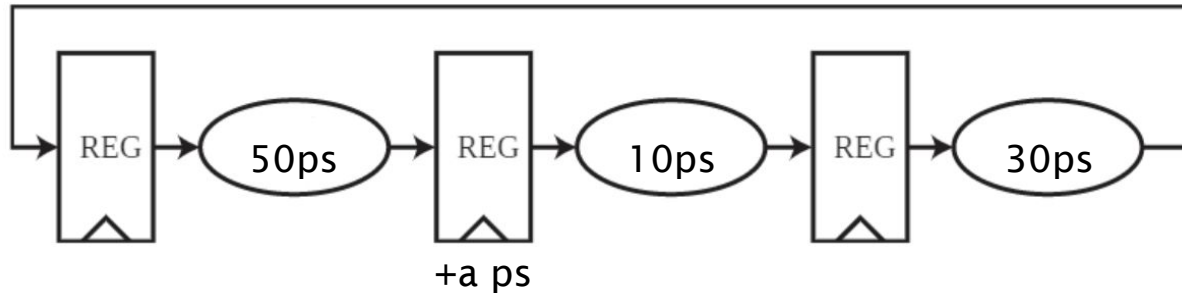
# Clock Skew

- Clock skew ... adjust delay of clock signal to reduce max delay




$(50 - a)$  ps

$(10 + a)$  ps

Each stage has 30ps delay  
when  $a = 20$ .

# Hold Time Constraint


Near the end of cycle:

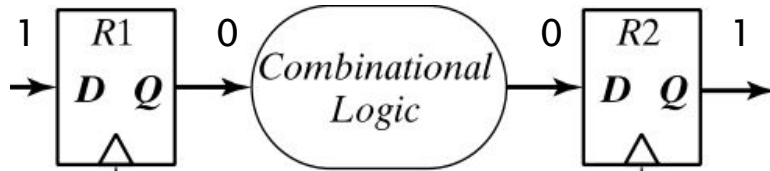

And if delay of logic is too small:



If R1 is triggered first:

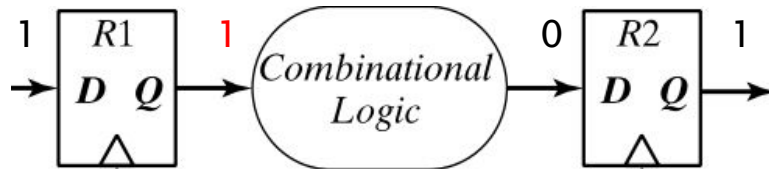

R2 cannot fetch 0 correctly:



# Clock Constraints

- Setup time constraint
  - $T > \text{clock\_to\_q} + \text{setup} + \text{max\_delay} + 2*\text{jitter}$
- Hold time constraint
  - $\text{clock\_to\_q} + \text{min\_delay} > \text{hold} + 2*\text{jitter}$

# Packaging

- C4 (solder balls) works better (smaller R) than bond wires
- Still, need to consider inductive effects
  - $V_{\text{diff}} = L * di/dt$  should be less than 0.1V
- Decoupling capacitors makes current spike smoother (low pass)
- ESD protection using diodes