

EECS 151 Disc 2

(Verilog Tutorial)

Rahul Kumar (session 1)
Yukio Miyasaka (session 2)


Contents

- Overview
- Combinational Logic
- Sequential Logic
- Generators
- Simulation

Acknowledgement: Some materials were taken from EECS 151 sp21/fa22 discussion 2 slides

Hardware Description Language (HDL)

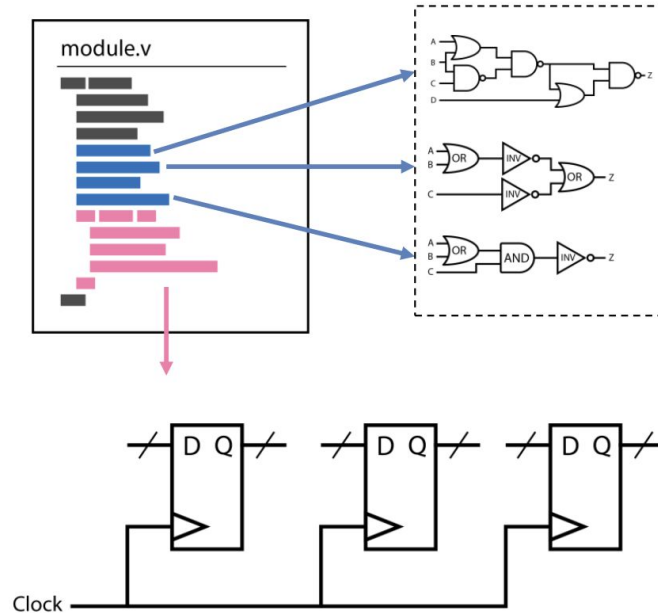- Standard for describing and representing digital systems
- Contains all information necessary to build entire digital system
- Apply RTL abstraction for combinational and state elements
- We use Verilog in this class



Verilog Basics

Not a programming language!



- C-like syntax
- However, we're writing a description of hardware
- All elements are working concurrently

Combinational Logic

Combinational logic

- Output updates (almost*) immediately with input
- Just because something is assigned at a later line doesn't mean it runs later!

 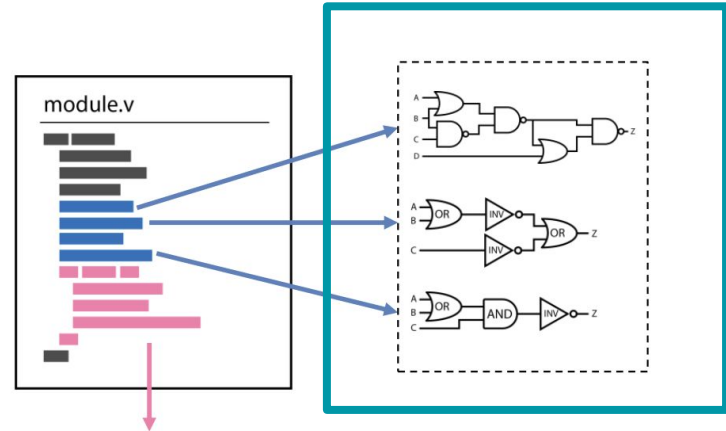(*) There are some tricky things when doing simulation



Inputs, Outputs, Wires, and Regs

Signals in Verilog are of 2 flavors

- **wire**
- **reg**

I/Os declared at beginning of module

- Followed by signal types
 - **wire** [default] / **reg**
- **input reg** doesn't make sense

Internal wires and regs declared after

- Not visible outside module

```
module Example (a, b, c, status, s);  
    input a;  
    input b;  
    input c;  
    output reg status;  
    output s;  
  
    wire internal_1;  
    reg internal_2;  
  
    ...  
endmodule
```

Inputs, Outputs, Wires, and Regs

Signals in Verilog are of 2 flavors

- **wire**
- **reg**

I/Os declared at beginning of module

- Followed by signal types
 - **wire** [default] / **reg**
- **input reg** doesn't make sense

Internal wires and regs declared after

- Not visible outside module

```
module Example (a, b, c, status, s);
```

```
    input a;  
    input b;  
    input c;  
    output reg status;  
    output s;
```

```
    wire internal_1; );
```

```
    reg internal_2;
```

```
    ...
```

```
endmodule
```

```
module Example ( Alternative
```

```
    input a,  
    input b,  
    input c,  
    output reg status,  
    output s
```

```
    wire internal_1;
```

```
    reg internal_2;
```

```
    ...
```

```
endmodule
```

Multi-Bit Signals

Width of multi-bit signals are declared between type and name

- By convention we use [Width-1:0]
- We can declare multiple signals after type and width
- We can extract a bit or a range using [i] or [i: j]

```
module Example2 (a, b, c, d, e);  
    input [3:0] a;  
    input [1:0] b, c;  
    output [1:0] d, e;  
  
    assign d[0] = a[0];  
    assign d[1] = b[1];  
    assign e = a[2:1] & c;  
  
    ...  
endmodule
```


Wire vs. Reg

wire

- Continuous assignment
`wire` internal;
`assign` internal = a & b;
- Output of instances (structural Verilog)
`wire` internal;
`and` (internal, a, b);

reg

- These are not actual registers!!!
- Signals in `always` blocks must be reg
`reg` internal;
`always` @(*)
 internal = a & b;
- Used in Behavioral Verilog except when using continuous assignment

Both can be used as input of operators/instances

The **always @(*)** Block

- Used to describe combinational logic in the behavioral Verilog
- We can use various statements inside, such as **if**, **case**, etc.
- **begin-end** is equivalent to **{-}** in C
 - Necessary to put more than one statements

```
module Example3 (a, b, s, out);  
  input a, b, s;  
  output reg out;  
  
  always @(*) begin  
    if (s) begin  
      out = a;  
    end else begin  
      out = b;  
    end  
  end  
end  
endmodule
```

Multiple Assignment

- Cannot continuously assign wire to two other wires

```
assign a = b;  
assign a = c; This is illegal!
```

- Can assign different values to reg at different points in block

```
always @(*) begin  
    a = b; This is okay.  
    a = c; a = c.  
end
```

- Compilers interpret it and use the last value to generate hardware
 - Previous values are overwritten
- Useful to handle complex conditions

```
always @(*) begin  
    out = b;  
    if (s) begin  
        out = a;  
    end  
end
```

Inferred Latches

How does this example work?

(Note: {a, b} is concatenation)

```
module Example4 (a, b, out);  
  input a, b;  
  output reg out;  
  
  always @(*) begin  
    case ({a, b})  
      2'b01: out = 1;  
      2'b10: out = 1;  
    endcase  
  end  
endmodule
```

Inferred Latches

This is not XOR!

- The output will hold a value if there is no matching cases
- Once 2'b10 or 2'b01 happen, the output will stay 1 forever

Make sure all regs are assigned a value for all cases

(Same thing happens when using **if** statements and not covering all cases)

```
module Example4 (a, b, out);
  input a, b;
  output reg out;

  always @(*) begin
    case ({a, b})
      2'b01: out = 1;
      2'b10: out = 1;
    endcase
  end
endmodule
```

Sequential Logic

In this class, we use a register library

Whenever you need a register, you have to instantiate one from the library

Specification:

- Stores an N-bit value
- Outputs the value as q
- At each positive edge of clk,
 - Resets to INIT if rst
 - Updates to d if !rst & ce
 - Hold the value otherwise

```
module REGISTER_R_CE(q, d, rst, ce, clk);
  parameter N = 1;
  parameter INIT = {N{1'b0}};
  output reg [N-1:0] q;
  input [N-1:0]      d;
  input              rst, ce, clk;
  initial q = INIT;
  always @(posedge clk)
    if (rst) q <= INIT;
    else if (ce) q <= d;
endmodule
```

Generators

Receives a parameter and creates various instances

We can use **for** loops

- Loop variables must be **genvar** when creating instances or **always** blocks inside
- (We can use **integer** in other places)


Parameters are given between module name and instance name with #()

```
wire [4:0] f;
wire g;
naryand #(.N(5)) and5(.in(f), .out(g));
```

Usage


```
module naryand (in, out);
    parameter N = 1;
    input [N-1:0] in;
    output out;
    wire [N-1:0] tmp;
    buf(tmp[0], in[0]);
    buf(out, tmp[N-1]);
    genvar i;
    generate for(i = 1; i < N; i = i + 1) begin : ands
        and(tmp[i], in[i], tmp[i-1]);
    end endgenerate
endmodule
```

Example: Shift-Register

 

```
module shift_register(clk, in, out);  
    parameter N = 1;  
    input clk, in;  
    output [N-1:0] out;  
    wire [N-1:0] tmp;  
  
    REGISTER_R_CE #(.N(N))  
        r(.q(out), .d(tmp), .rst(0), .ce(1), .clk(clk));  
  
    assign tmp = {out, in};  
endmodule
```


Example: Shift-Register

 

```
module shift_register(clk, in, out);
```

```
parameter N = 1;
```

```
input clk, in;
```

```
output [N-1:0] out;
```

```
wire [N-1:0] tmp;
```

```
REGISTER_R_CE #(
```

```
r(q(out), .d(tmp),
```

```
assign tmp = {out, in};
```

```
endmodule
```

```
module shift_register Alternative
```

```
 #(parameter N = 1)
```


```
 (clk, in, out);
```

```
input clk, in;
```

Simulation

What's a Testbench?

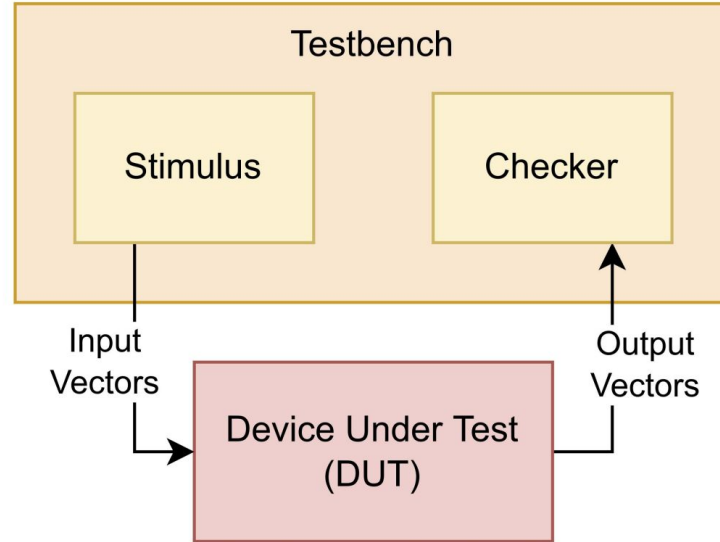- Description of tests to verify that designs behave as specified
- Generate input to drive designs
- Compare output against expected values



Testbench Structure

Testbenches are also written in Verilog

- **wire** for test output
- **reg** for test input and others

initial blocks

- Used only for the purpose of simulation
- No hardware implementation

Simulation commands

- **\$dumpfile**(dump.vcd); **\$dumpvars**;
generates a waveform
- **\$finish**(); ends simulation

```
module my_tb;
  reg in;
  wire out;
  reg expected;

  DUT dut(.in(in), .out(out));

  initial begin
    $dumpfile("dump.vcd");
    $dumpvars;
    /* Drive inputs and check here */
    $finish();
  end
endmodule
```

Printing Signals

`$display("format string", values);`

- Example: `$display("in: %b, out: %b, expected: %b", in, out, expected);`

<code>%d</code> or <code>%D</code>	Decimal format
<code>%b</code> or <code>%B</code>	Binary format
<code>%h</code> or <code>%H</code>	Hexadecimal format
<code>%o</code> or <code>%O</code>	Octal format
<code>%c</code> or <code>%C</code>	ASCII character format
<code>%v</code> or <code>%V</code>	Net signal strength
<code>%m</code> or <code>%M</code>	Hierarchical name
<code>%s</code> or <code>%S</code>	As a string
<code>%t</code> or <code>%T</code>	Current time format

Simulation Order


In simulation, DUT output may not update immediately

- Why? - Simulator may execute next line in testbench before
- The execution order is arbitrary

How can we get it updated?

- Simulation timestep advances after executing all waiting updates
- Delay testbench by `#num` after changing input
- It postpones the execution of the current sequence by `num` timesteps

Example: OAI

 

EDA Playground (<https://www.edaplayground.com/>)

- Free web-based simulator
- Built-in waveform viewer
- HIGHLY recommended for this homework!
- (Select Icarus Verilog 0.9.7 for simulator)

OAI design and testbench:

<https://www.edaplayground.com/x/Egiz>

Testing Sequential Circuits

Clock signal

- Initialized to 0
- `always #1` flips it every timestep

`task` block

- Defines a procedure
- Can be called from anywhere in testbench
- `task check` advances simulation by two timesteps, and compare output with expected values
- Why two timesteps?

```
module my_tb;
...
  reg clk;
  initial clk = 0;
  always #1 clk = ~clk;
...
  task check; begin
    #2;
    if(out !== expected) begin
      $display("FAILED");
      $finish();
    end
  end endtask
...
```


Example: Shift-Register

<https://www.edaplayground.com/x/jrmq>

*Disregard the warning about timescale for now.