


EECS 151 Disc 3

Rahul Kumar (session 1)
Yukio Miyasaka (session 2)


Contents

- Parallel to Serial Converter
- FPGA
- Boolean Algebra
- Karnaugh Maps
- DeMorgan's Law

Parallel to Serial Converter

 

 Reads input on a positive clock edge if ld is 1




```

module ParToSer (ld, x, out, clk);
  input [3:0] x;
  input ld, clk;
  output out;
  wire [3:0] q, d;

  REGISTER #(N(4))
    r(.q(q), .d(d), .clk(clk));
  assign d = ld? x: {Q[0], Q[3:1]};
  assign out = q[0];


endmodule
  
```

FPGA

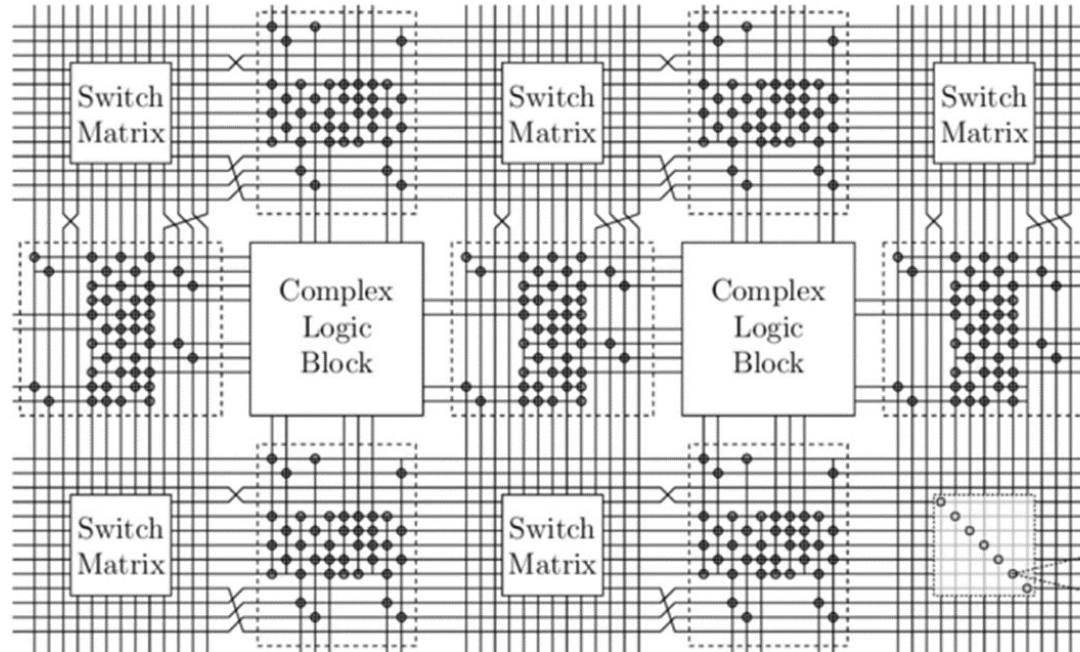


Logic Block

 - Contains LUTs and FFs
- FFs are attached at the output of LUTs
- Configuration bits are stored in shift register
- In this case, registers are chained in the ascending order of input




A6	A5	A4	A3	A2	D
0	0	0	0	0	1
0	0	0	0	1	0
0	0	0	1	0	1
		...			
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	1

 


Routing Switches

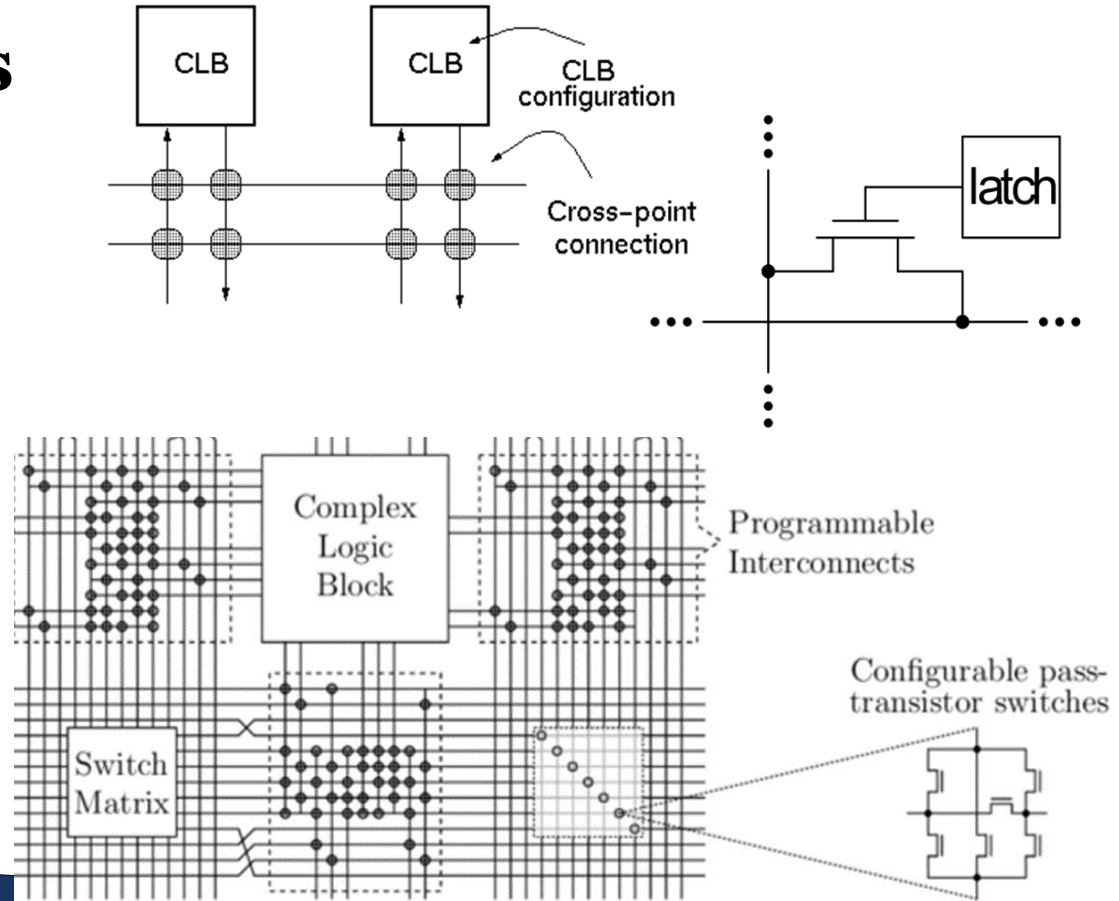- Logic block input/output is connected to wires through a single transistor
- Makes a turn in switch matrix
- No matter if it makes a turn or not, a signal passes through one transistor in switch matrix
- Some FPGAs have *double lines* which skip every other switch matrix



Critical Path Delay

 
- Assume every gate has same delay for now
- The delay of the slowest path is called *critical path delay*



What is critical path delay in this circuit?

Critical Path Delay

 - Assume every gate has same delay for now
- The delay of the slowest path is called *critical path delay*



What is critical path delay in this circuit?

Boolean Algebra

Postulates

- $a + 0 = a$ ($a * 1 = a$)
- $a + a' = 1$ ($a * a' = 0$)
- Commutative law $ab = ba$
- Distributive law $a(b + c) = ab + bc$, $a+(bc) = (a + b)(a + c)$

Theorems

- $a + a = a$ ($a * a = a$)
- $a + 1 = 1$ ($a * 0 = 0$)
- $(a')' = a$
- Associative law $a(bc) = (ab)c$

Practice

$$x + xy = ?$$

Practice

$$x + xy = x * 1 + xy$$

Practice


$$x + xy = x * 1 + xy = x(1 + y) = x * 1 = x$$

Hard to find the first step

Massage it by generating 1 (or 0) randomly

K-map

 
- Simple way to create a small SOP
- Fill cells according to the truth table
- Group as many ones as possible
- Groups can overlap
- Extract products
- Sum them up



K-map

- Simple way to create a small SOP
- Fill cells according to the truth table
- Group as many ones as possible
- Groups can overlap
- Extract products
- Sum them up

Group size must be $(2^n, 2^m)$

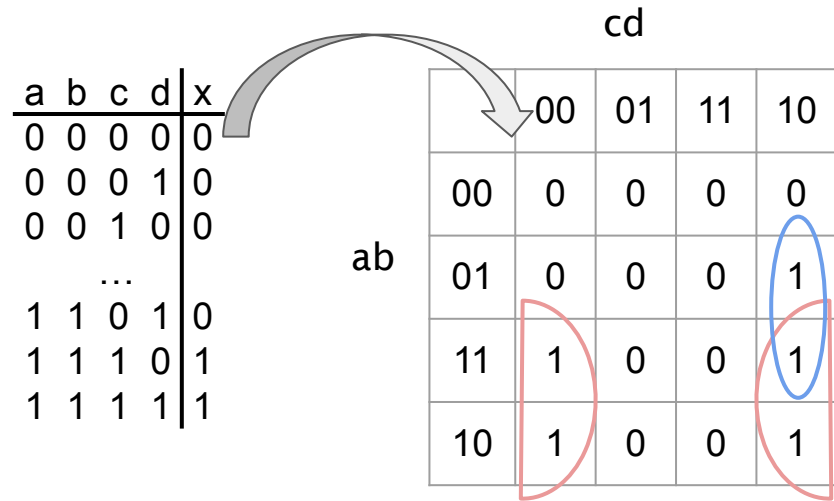


K-map

- Simple way to create a small SOP
- Fill cells according to the truth table
- Group as many ones as possible
- Groups can overlap
- Extract products
- Sum them up

a	b	c	d	x
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
		...		
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1


Group size must be $(2^n, 2^m)$

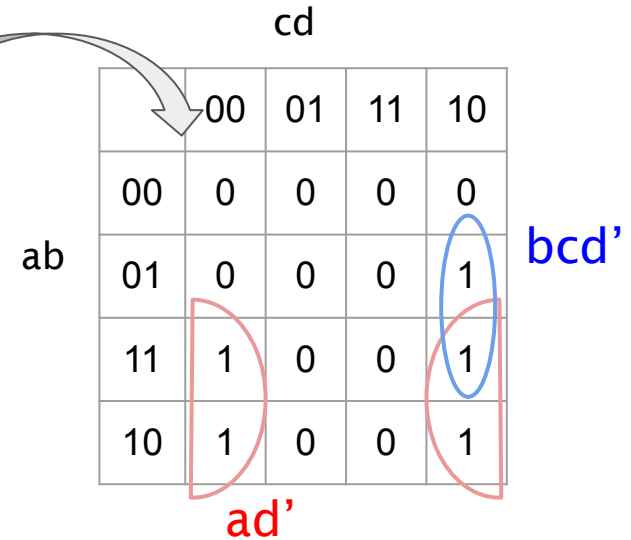

$$= ad' + bcd'$$

K-map with Don't-cares

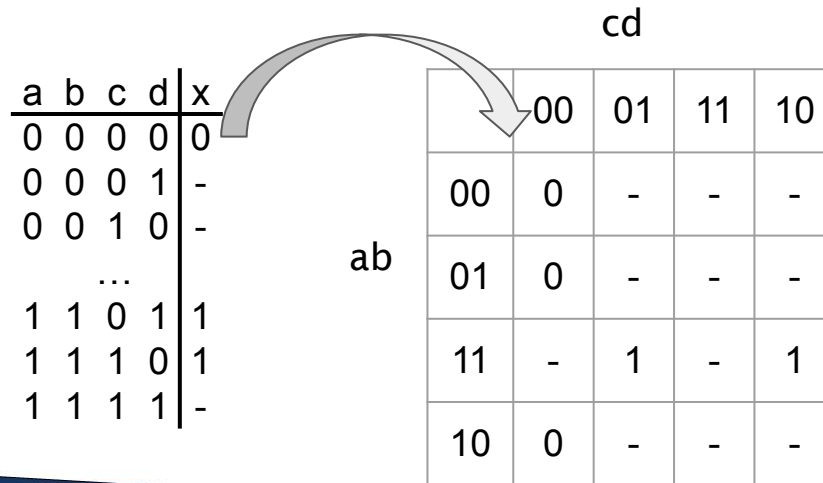- Some functions have limited input space
- They can output arbitrary values outside



K-map with Don't-cares

cd

	00	01	11	10
00	0	-	-	-
01	0	-	-	-
11	-	1	-	1
10	0	-	-	-

ab

cd

	00	01	11	10
00	0	-	-	-
01	0	-	-	-
11	-	1	-	1
10	0	-	-	-

ab

Which is better?

K-map with Don't-cares

		cd			
		00	01	11	10
ab	00	0	-	-	-
	01	0	-	-	-
	11	-	1	-	1
	10	0	-	-	-

ab

		cd			
		00	01	11	10
ab	00	0	-	-	-
	01	0	-	-	-
	11	-	1	-	1
	10	0	-	-	-



c + d

Which is better? - Depends on implementation.

DeMorgan's Law

$$(a + b)' = a'b'$$

$$(ab)' = a' + b'$$

  

“Bubble pushing”: flip the gate, propagate the bubbles.

We can freely generate two consecutive bubbles anywhere.