

# EECS 151 Disc 4

Rahul Kumar (session 1)  
Yukio Miyasaka (session 2)

# Contents

- State machines (Moore and Mealy)
- STD (State Transition Diagram)
- State assignment and encoding
- STD to Verilog
- STD to gate-level circuits

# State Machines

- A way to systematically design sequential circuits
- Moore: outputs depend only on current state
- Mealy: outputs depend on current state and input

# Example

Design a state machine to determine whether an unsigned binary integer is divisible by 3.

Inputs:


- $x$ : the input integer. Given to FSM one bit at a time.
- $rst$ : synchronous reset. At the next clock edge, clears any state associated with the FSM.

Output: one bit indicating if the value seen so far is divisible by 3.

# Example

Input is supplied one bit at a time, MSB first.

Example: 1010111

 

# Example

Draw a state transition diagram for this state machine.

# Example

- Key idea: keep track of the number modulo 3.
- If 0, the number is divisible by 3.
- Can we track  $N \% 3$  without storing  $N$ ?

# Example

What happens when we get a new bit? In pseudocode:

$$\text{next} = 2 * \text{prev} + \text{bit}$$

Same equation applies modulo 3!

$$\text{next\_residue} = (2 * \text{prev\_residue} + \text{bit}) \% 3$$



# Example


So keep 3 states,  $S_0/S_1/S_2$ , corresponding to residues mod 3.

$S_0$ : if input is 1, go to  $S_1$ . Else, stay at  $S_0$ .

$S_1$ : if input is 1, go to  $S_0$ . Else, go to  $S_2$ .


$S_2$ : if input is 1, stay at  $S_2$ . Else, go to  $S_1$ .

# Example (Moore Machine)

 
 
# Example

Implement this FSM as a Moore machine in Verilog, using a binary state encoding.




# Example


```
module div3_moore(  
    input clk,  
    input x,  
    input rst,  
    output out  
);  
    localparam S0 = 2'b00;  
    localparam S1 = 2'b01;  
    localparam S2 = 2'b10;  
    reg [1:0] next_state;  
    wire[1:0] state;  
    REGISTER_R #(.N(2), .INIT(S0)) state_reg (.q(state), .d(next_state), .rst(rst), .clk(clk));  
  
    assign out = state == S0;  
  
    always @(*) begin  
        case (state)  
            S0: begin  
                next_state = x ? S1 : S0;  
            end  
            S1: begin  
                next_state = x ? S0 : S2;  
            end  
            S2: begin  
                next_state = x ? S2 : S1;  
            end  
        endcase  
    end  
endmodule
```
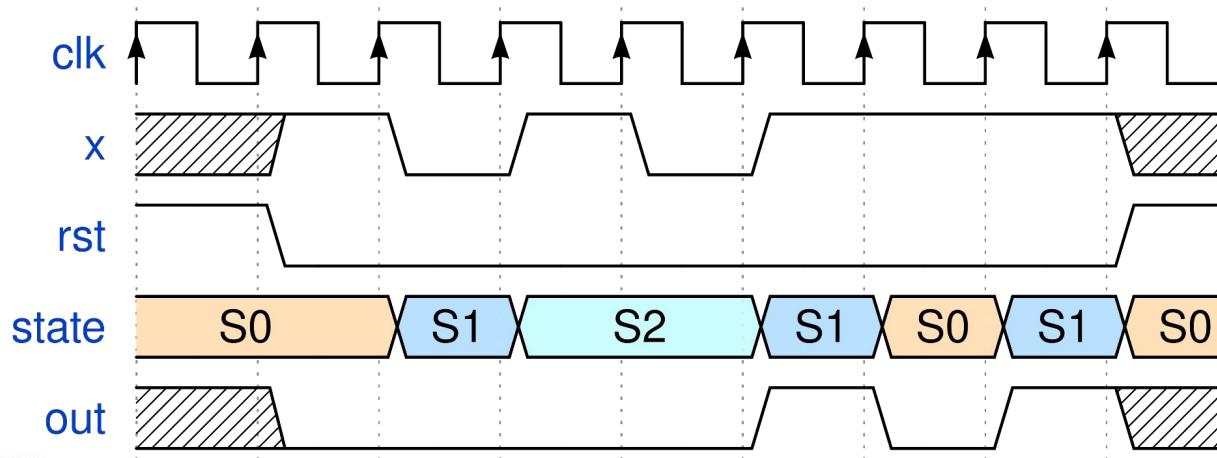
# Example

Now implement the same logic as a Mealy machine. The output should update as soon as the input updates.



# Example (Mealy Machine)

 

# Example

```
module div3_mealy(  
    input clk,  
    input x,  
    input rst,  
    output out  
);  
localparam S0 = 2'b00;  
localparam S1 = 2'b01;  
localparam S2 = 2'b10;  
reg [1:0] next_state;  
wire[1:0] state;  
REGISTER_R #(.N(2), .INIT(S0)) state_reg (.q(state), .d(next_state), .rst(rst), .clk(clk));  
  
assign out = next_state == S0;  
  
always @(*) begin  
    case (state)  
        S0: begin  
            next_state = x ? S1 : S0;  
        end  
        S1: begin  
            next_state = x ? S0 : S2;  
        end  
        S2: begin  
            next_state = x ? S2 : S1;  
        end  
    endcase  
end  
endmodule
```


# Example: Washing machine

- Takes two steps: wash and spin
- Wash twice if a double wash switch **D** is on
  - wash -> wash -> spin
- Receives a signal **T** from a timer:
  - When it should start washing
  - At the end of each step





# State Transition Diagram

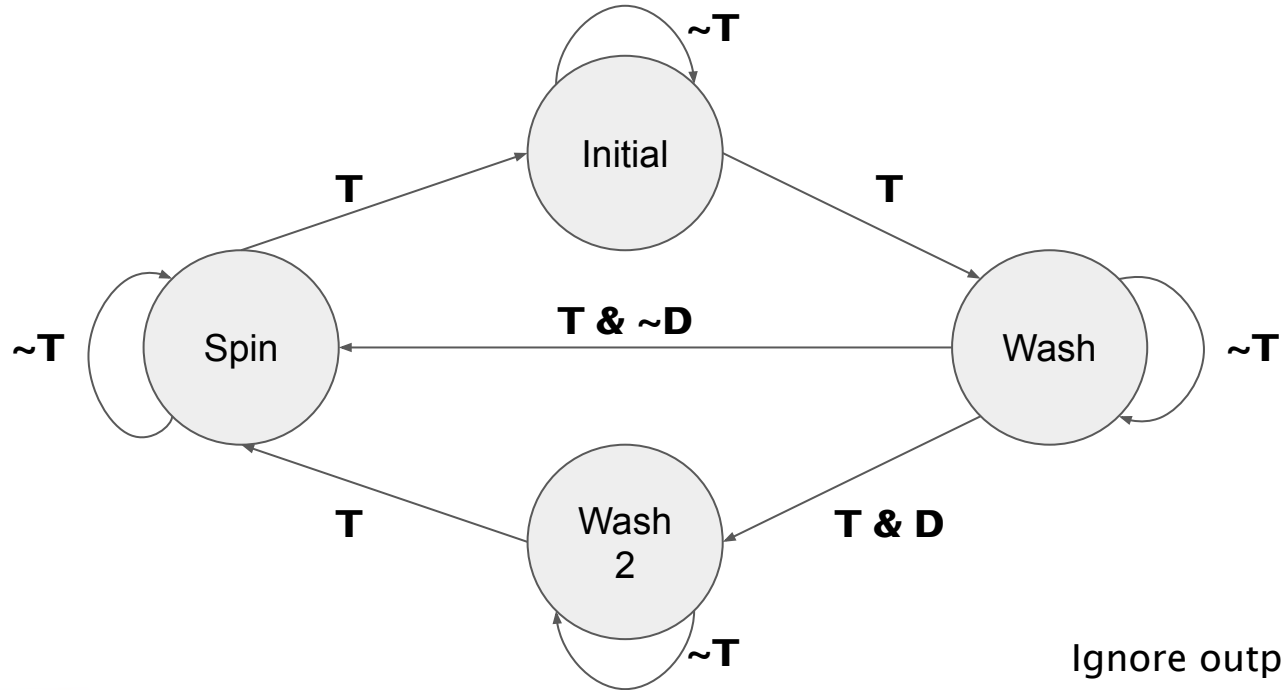

Ignore output signal for now

# State Assignment

Initial = state 0

Wash = state 1


Wash2 = state 3

Spin = state 2

s1\s0	0	1
0	Initial → Wash	↓ Wash2
1	↑ Spin ← Wash2	

Transitions in binary encoding

# Verilog with Binary Encoding

 

```
module washing_machine_binary(input clk, rst, T, D);  
  localparam Initial = 2'b00;  
  localparam Wash   = 2'b01;  
  localparam Wash2  = 2'b11;  
  localparam Spin   = 2'b10;
```

```
  reg [1:0] next_state;  
  wire[1:0] state;  
  REGISTER_R #(.N(2)) state_reg (.q(state),  
  .d(next_state), .rst(rst), .clk(clk));
```

```
  always @(*) begin  
    next_state = state;  
    case (state)  
      Initial: if(T) next_state = Wash;  
      Wash:   if(T) next_state = D? Wash2: Spin;  
      Wash2:  if(T) next_state = Spin;  
      Spin:   if(T) next_state = Initial;  
    endcase  
  end  
endmodule
```

# Gate-Level Circuit with Binary Encoding

s1	s0	T	D	n1	n0
0	0	1	-	0	1
0	1	1	0	1	0
0	1	1	1	1	1
1	0	1	-	0	0
1	1	1	-	1	0
x	y	0	-	x	y

# Gate-Level Circuit with Binary Encoding

s1	s0	T	D	n1	n0
0	0	1	-	0	1
0	1	1	0	1	0
0	1	1	1	1	1
1	0	1	-	0	0
1	1	1	-	1	0
x	y	0	-	x	y

		TD			
		00	01	11	10
s1s0	00	0	0	0	0
	01	0	0	1	1
	11	1	1	1	1
	10	1	1	0	0

**K-map for n1**

		TD			
		00	01	11	10
s1s0	00	0	0	1	1
	01	1	1	1	0
	11	1	1	0	0
	10	0	0	0	0

**K-map for n0**

# Gate-Level Circuit with Binary Encoding

s1	s0	T	D	n1	n0
0	0	1	-	0	1
0	1	1	0	1	0
0	1	1	1	1	1
1	0	1	-	0	0
1	1	1	-	1	0
x	y	0	-	x	y

TD

	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	1	1	1	1
10	1	1	0	0

s1s0

**K-map for n1**

$$n1 = s0 T + s1 T'$$

TD

	00	01	11	10
00	0	0	1	1
01	1	1	1	0
11	1	1	0	0
10	0	0	0	0


s1s0

**K-map for n0**


$$n0 = s0 T' + s1' T D + s0' s1' T$$

# Gate-Level Circuit with Binary Encoding

$$n1 = s0 T + s1 T'$$

 
 
$$\begin{aligned} n0 &= s0 T' + s1' T D + s0' s1' T \\ &= s0 T' + s1' T (D + s0') \end{aligned}$$




# One-hot Encoding

- state 0 = 0001 (Initial)
- state 1 = 0010 (Wash)
- state 2 = 0100 (Spin)
- state 3 = 1000 (Wash2)

State assignment doesn't really matter in one-hot encoding



# Verilog with One-hot Encoding

 

```
module washing_machine_onehot(input clk, rst, T, D);  
  wire [3:0] next_state, state;  
  REGISTER_R #(.N(4)) state_reg (.q(state),  
  .d(next_state), .rst(rst), .clk(clk));
```

```
  assign next_state[0] = (state[0] & ~T) |  
    (state[2] & T);  
  assign next_state[1] = (state[1] & ~T) |  
    (state[0] & T);  
  assign next_state[2] = (state[2] & ~T) |  
    (state[1] & T & ~D) |  
    (state[3] & T);  
  assign next_state[3] = (state[3] & ~T) |  
    (state[1] & T & D);
```

```
endmodule
```

Focus on incoming edges for each node

# Gate-Level Circuit with One-hot Encoding

```
assign next_state[0] = (state[0] & ~T) |  
                      (state[2] & T);  
assign next_state[1] = (state[1] & ~T) |  
                      (state[0] & T);  
assign next_state[2] = (state[2] & ~T) |  
                      (state[1] & T & ~D) |  
                      (state[3] & T);  
assign next_state[3] = (state[3] & ~T) |  
                      (state[1] & T & D);
```

